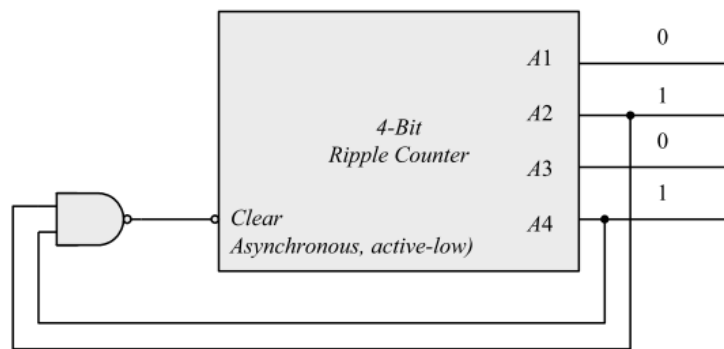


ITI1100C
Assignment #6
Solutions

- 6.11** **(a)** A count down counter.
(b) A count up counter.

6.13



- 6.19** **(b)** From the state table in Table 6.5: /a partir de la table 6.5

$$D_{Q1} = Q'_1$$

$$D_{Q2} = \sum (1, 2, 5, 6)$$

$$D_{Q4} = \sum (3, 4, 5, 6)$$

$$D_{Q8} = \sum (7, 8)$$

$$\text{Don't care: } d = \sum (10, 11, 12, 13, 14, 15)$$

Simplifying with maps:

$$D_{Q2} = Q_2Q'_1 + Q'_8Q'_2Q_1$$

$$D_{Q4} = Q_4Q'_1 + Q_4Q'_2 + Q'_4Q_2Q_1$$

$$D_{Q8} = Q_8Q'_1 + Q_4Q_2Q_1$$

(a)

Present state	Next state	Flip-flop inputs			
		$A_8 A_4 A_2 A_1$	$A_8 A_4 A_2 A_1$	$J_{A8} K_{A8}$	$J_{A4} K_{A4}$
0000	0001	0 x	0 x	0 x	1 x
0001	0010	0 x	0 x	1 x	x 1
0010	0011	0 x	0 x	x 0	1 x
0011	0100	0 x	1 x	x 1	x 1
0100	0101	0 x	x 0	0 x	1 x
0101	0110	0 x	x 0	1 x	x 1
0110	0111	0 x	x 0	x 0	1 x
0111	1000	1 x	x 1	x 1	x 1
1000	1001	x 0	0 x	0 x	1 x
1001	0000	x 1	0 x	0 x	x 1

$$\begin{aligned}
 J_{A1} &= 1 \\
 K_{A1} &= 1 \\
 J_{A2} &= A_1 A_8' \\
 K_{A2} &= A_1 \\
 J_{A4} &= A_1 A_2 \\
 K_{A4} &= A_1 A_2' \\
 J_{A8} &= A_1 A_2' A_4 \\
 K_{A8} &= A_1
 \end{aligned}$$

$$d(A_8, A_4, A_2, A_1) = \Sigma (10, 11, 12, 13, 14, 15)$$

	T – Flip Flop	D – Flip Flop	J K – Flip Flop
AND Gates#	5	7	4
OR Gates#	4	4	0
Total	9	11	4

When compared between the above three designs, BCD counter that uses JK Flip Flop needs less number of combinational gates. so, it is most efficient.

Present state <i>ABC</i>	Next state <i>ABC</i>	Flip-flop inputs					
		J_A	K_A	J_B	K_B	J_C	K_C
000	001	0	x	0	x	1	x
001	010	0	x	1	x	x	1
010	011	0	x	x	0	1	x
011	100	1	x	x	1	x	1
100	101	x	0	0	x	1	x
101	110	x	0	1	x	x	1
110	000	x	1	x	1	0	x
111	xxx	x	x	x	x	x	x

