

Solution

ELEC 2607

Assignment 1

20 Marks

1. Using the method of exhaustive proof show whether $\overline{a+b+c}$ is equal to $\overline{(a+b)} \cdot \bar{c}$.

2 marks

	ab			
c	00	01	11	10
0	1	0	0	0
1	0	0	0	0

$\overline{a+b+c}$

	ab			
c	00	01	11	10
0	1	0	0	0
1	0	0	0	0

$\overline{(a+b)} \cdot \bar{c}$

①

Same compact truth table \Rightarrow equal

①

2. Draw the simplest logic gate or circuit for the following descriptions. The inputs are a, b, c .

The output is z .

4 marks

① (a) $z = 1$ only if $abc = 110$




① (b) $z = 0$ unless $abc = 010$



② (c) $z = 0$ only if " $abc = 110$ or $abc = 011$ "
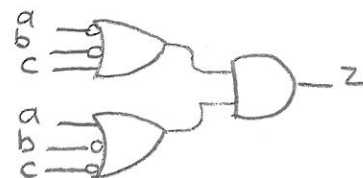
$$\bar{z} = abc + \bar{a}bc \Rightarrow z = (\bar{a} + \bar{b} + c)(a + \bar{b} + \bar{c})$$



3. Simplify the following

4 marks

① (a) $(X + Y + \bar{Y}Z)(Y + X)(Y + \bar{X})$ to 1 literal

$$\begin{aligned} &= (X + Y + \bar{Y}Z)(YY + Y\bar{X} + XY + X\bar{X}) = (X + Y + \bar{Y}Z)(Y + Y\bar{X} + YX + 0) \\ &= (X + Y + \bar{Y}Z)[Y + Y(X + \bar{X}) + 0] = (X + Y + \bar{Y}Z)Y = Y \end{aligned}$$

① (b) $(BCD + C)CD$ to 2 literals

$$= BCDCD + CCD = BCD + CD = CD(B + 1) = CD$$

② (c) $A\bar{B} + AC + \bar{C}B$ to 3 literals

according to consensus: $AC + \bar{C}B = AC + AB + \bar{C}B$

$$\begin{aligned} \Rightarrow A\bar{B} + AC + \bar{C}B &= A\bar{B} + AB + AC + \bar{C}B = A + AC + \bar{C}B \\ &= A + \bar{C}B \end{aligned}$$

one may also simplify by expressing as $A\bar{B}(C + \bar{C}) + AC + \bar{C}B$

4. Prove algebraically that $(a+b)(b+c)(c+a) = ab+bc+ca$

2 mark

$$\begin{aligned} LHS &= (ab + ac + bb + bc)(c+a) = (ab + ac + b + bc)(c+a) \\ &= [b(a+1+c) + ac](c+a) = (b+ac)(c+a) \\ &= bc + ab + acc + aac = bc + ab + ca = RHS \end{aligned}$$

5. Use duality on $\bar{a}\bar{b} + ab = (a + \bar{b})(\bar{a} + b)$ to find an alternate expression for $\bar{a}\bar{b} + ab$.

$$(\bar{a} + \bar{b})(a + b) = \bar{a}\bar{b} + ab$$

by applying duality on

1 mark

$\Rightarrow (\bar{a} + \bar{b})(a + b)$ is another

1 both sides.

expression for $\bar{a}\bar{b} + ab = a \oplus b$

6. Convert the following expressions to a form where the bar is over single variables only.

4 marks

(a) $a(\overline{bc+de}) + \overline{(d+a)cg} = a(\overline{bc+de}) + (\overline{d+a} \cdot cg)$

$$= \{a(\{b\bar{c}\} + \{d\bar{e}\}) + \{\bar{a}\bar{d}cg\}$$

$$= \{\bar{a} + (\{\bar{b}+c\} \cdot \{\bar{d}+\bar{e}\})\} + \{a+d+\bar{c}+\bar{g}\} = [\bar{a} + (\bar{b}+c)(\bar{d}+\bar{e})] + (a+d+\bar{c}+\bar{g})$$

(b) $a(\overline{bc+\bar{e}d}) + \overline{(d+ab)(cg)} + \overline{adcg}$

$$= a[\overline{bc+(e+\bar{d})}] + \overline{[(d+ab)+(cg)]} + [a(\bar{d}+\bar{c}+\bar{g})]$$

$$= \{a[(\bar{b}\bar{c})+e+\bar{d}]\} + [d+(ab)+(cg)] + [a(\bar{d}+\bar{c}+\bar{g})]$$

$$= \{\bar{a} + [(\bar{b}+c) \cdot \bar{e} \cdot d]\} \cdot [\bar{d} \cdot (\bar{a}+\bar{b}) \cdot (\bar{c}+\bar{g})] \cdot [\bar{a} + (d+cg)]$$

7. Derive the equations for y and z from the following table and simplify the answer as much as possible. Then implement y and z using a minimum number of 2-input and 3-input gates (note: inverters (bubbles) don't count). Also identify the function obtained by y and z (eg. is the function an 'and', 'xor', 'or', 'majority gate' etc.?)

3 marks

$$y = \bar{a}\bar{b}\bar{c} + a\bar{b}\bar{c} + a\bar{b}c + \bar{a}bc$$

$$= \bar{c}(\bar{a}\bar{b} + ab) + c(a\bar{b} + \bar{a}b)$$

$$= \bar{c}(a \oplus b) + c(a \oplus b)$$

$$= \overline{c \oplus (a \oplus b)}$$

$$= a \oplus b \oplus c \quad \text{XNOR}$$

c	b	a	y	z
0	0	0	1	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	0

$$z = \bar{a}\bar{b}\bar{c} + a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}bc$$

$$= \bar{a}\bar{b}(c+\bar{c}) + a\bar{b}\bar{c} + \bar{a}b\bar{c}$$

$$= \bar{a}\bar{b} + a\bar{b}\bar{c} + \bar{a}b\bar{c}$$

$$= \bar{a}\bar{b} + \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c} + a\bar{b}\bar{c} + \bar{a}b\bar{c}$$

$$= \bar{a}\bar{b} + \bar{b}\bar{c} + \bar{a}\bar{c}$$

$$= \overline{ab + bc + ac}$$

$$= \text{Majority}(a, b, c)$$

