

# ITI1100Z

Professor: Qi Hao

## Assignment # 5


**Submission Deadline July 8, 2018 midnight (11h59 PM), Brightspace**

From the textbook Chapter five pages from 315 to 317 in the 6<sup>th</sup> edition, solve the following problems:

**5.2, 5.6, 5.9, 5.10, 5.12, 5.16(a)**


5.2

Total  
5 points

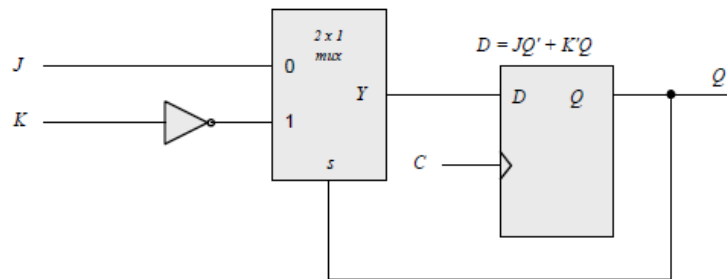

5.6

Total  
8 points

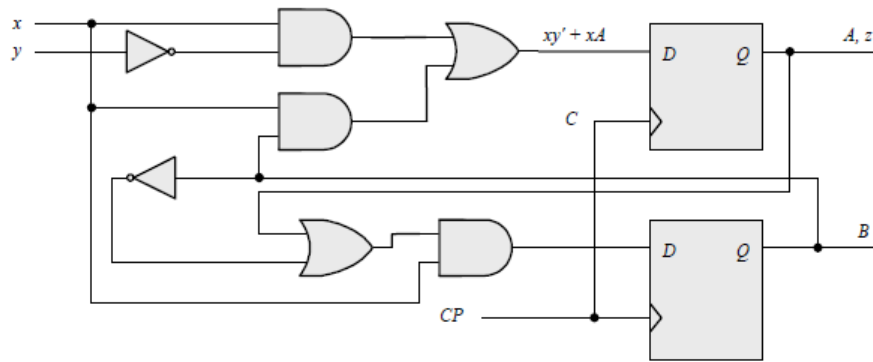


2 points

(b)  $A(t+1) = xy' + xB$   
 $B(t+1) = xA + xB'$   
 $z = A$

3 points

Present state		Inputs		Next state		Output
A	B	x	y	A	B	z
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

(c)

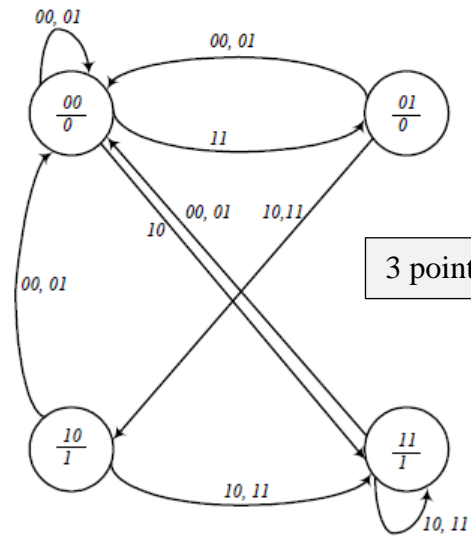


3 points

Note: 5.6 (b) and (c) are wrong. Correct answers are:

b)

<u>Present state</u>		Inputs		<u>Next state</u>		Output
A	B	X	Y	A	B	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	1	1
1	0	1	1	0	1	1
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

c)

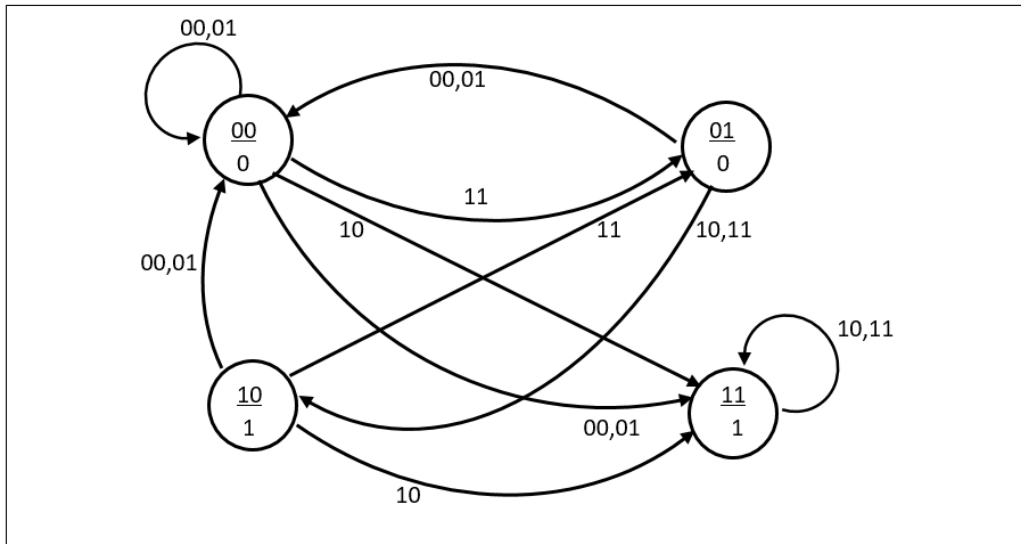

5.9

Total  
6 points

$$J_A = x \quad K_A = B$$


$$J_B = x \quad K_B = A'$$

3 points

$$A(t+1) = J_A A' + K_A' A = xA' + B'A$$

$$B(t+1) = J_B B' + K_B' B = xB' + AB$$

$x$	$A$	$B$	$xA' + B'A$	$xB' + AB$
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

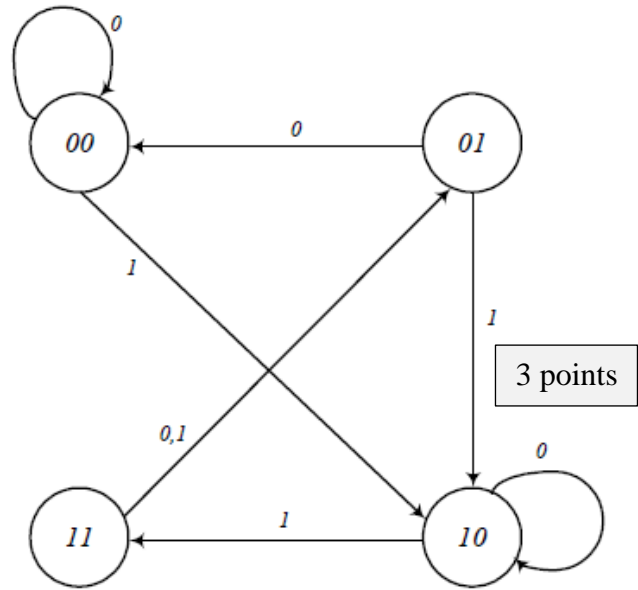

3 points

Note: 5.9 error correction


$$J_A = x \quad K_A = B$$


$$J_B = x \quad K_B = A'$$

$$A(t+1) = J_A A' + K_A' A = xA' + B'A$$

$$B(t+1) = J_B B' + K_B' B = xB' + AB$$

$x$	$A$	$B$	$xA' + B'A$	$xB' + AB$
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

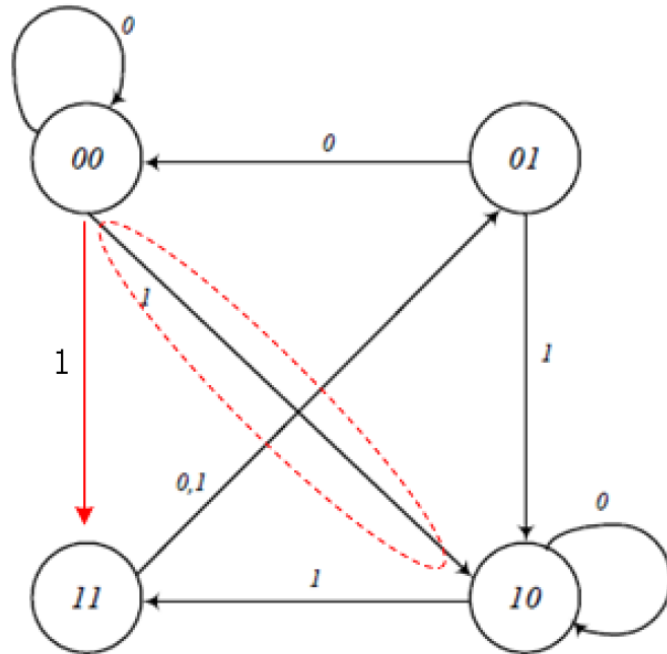

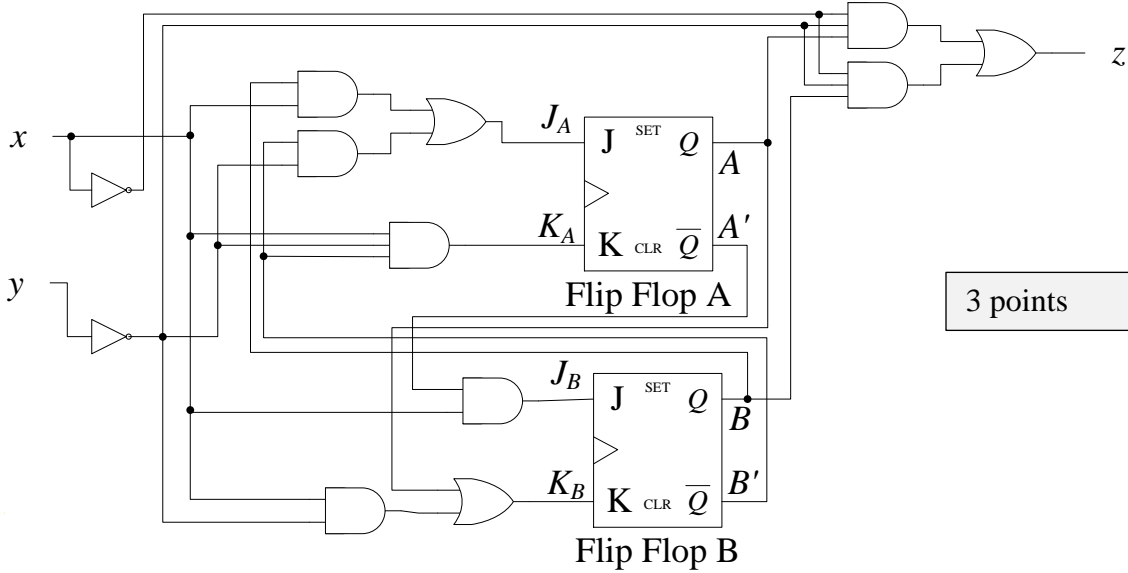

5.10 (a)

3 points


Total 10 points

(b)

Present state		Inputs		Next state		Output	FF Inputs			
A	B	x	y	A	B	z	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	1	0	1	1	1	1
0	0	1	1	0	1	0	0	0	1	0
0	1	0	0	0	1	1	0	0	0	0
0	1	0	1	0	1	0	0	0	0	0
0	1	1	0	1	0	0	1	0	1	0
0	1	1	1	1	1	0	1	0	1	0
1	0	0	0	1	0	0	1	0	0	1
1	0	0	1	1	0	0	0	0	0	1
1	0	1	0	0	0	0	1	1	0	1
1	0	1	1	1	0	0	0	0	0	1
1	1	0	0	1	0	1	0	0	0	1
1	1	0	1	1	0	0	0	0	0	1
1	1	1	0	1	0	0	1	0	0	1
1	1	1	1	1	0	1	1	0	0	1


3 points  
(1.5 points for next state/output)  
(1.5 points for FF inputs)

(c)

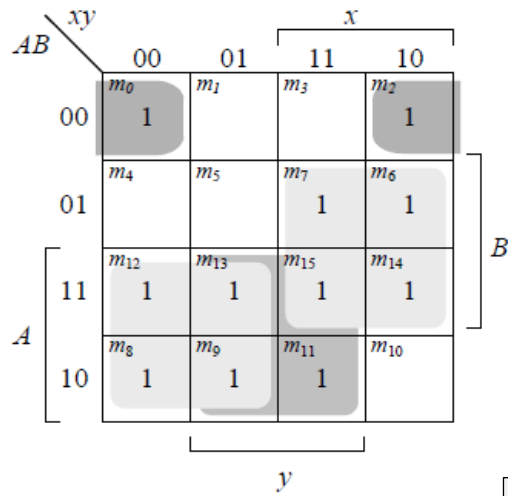

$$A(t+1) = Ax' + Bx + Ay + A'B'y'$$

2 points

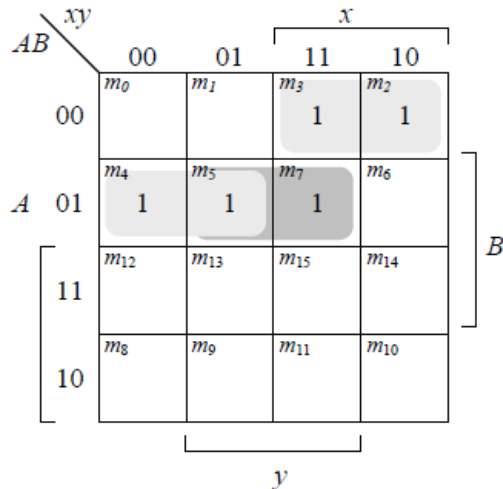

$$B(t+1) = A'B'x + A'B'(x' + y)$$

2 points

**Note: 5.10 (c) Error Correction:**  $B(t + 1) = A'xy + A'B'x + A'Bx'$  , or  $B(t + 1) = A'B'x + A'B(x' + y)$


5.12

Present state	Next state		Output	
	0	1	0	1
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>a</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>d</i>	0	1

Total  
7 points

Note: 5.12 correct answers are:

a)

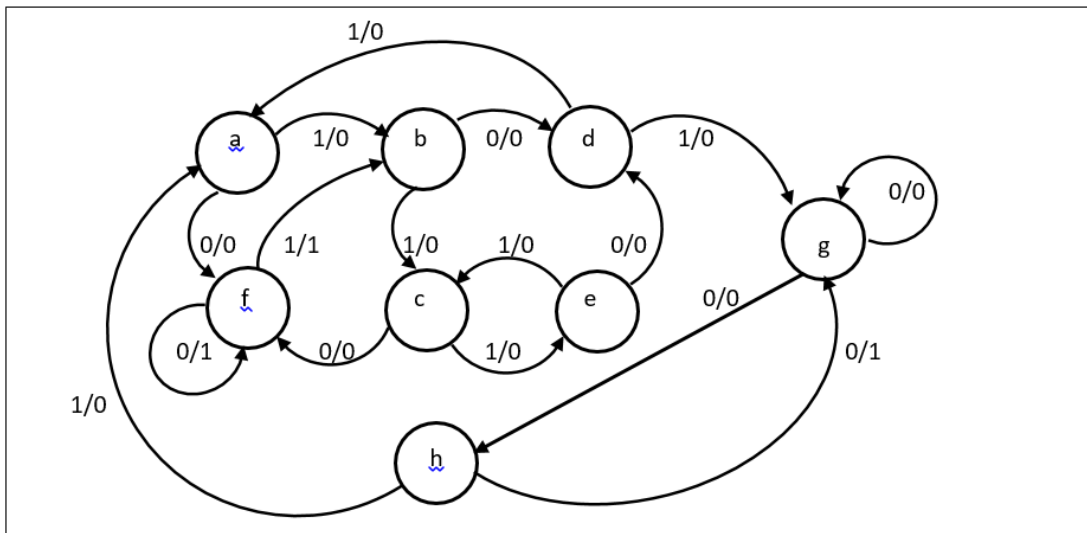

Total  
2 points

b)

Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
a	f	b	0	0
*b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
*e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0



Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
*a	f	b	0	0
b	d	c	0	0
c	f	b	0	0
d	g	a	1	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0


Total  
3 points

Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
a	f	b	0	0
b	d	a	0	0
*d	g	a	1	0
f	f	b	1	1
g	g	h	0	1
*h	g	a	1	0



Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
a	f	b	0	0
b	d	a	0	0
d	g	a	1	0
f	f	b	1	1
g	g	d	0	1

c)

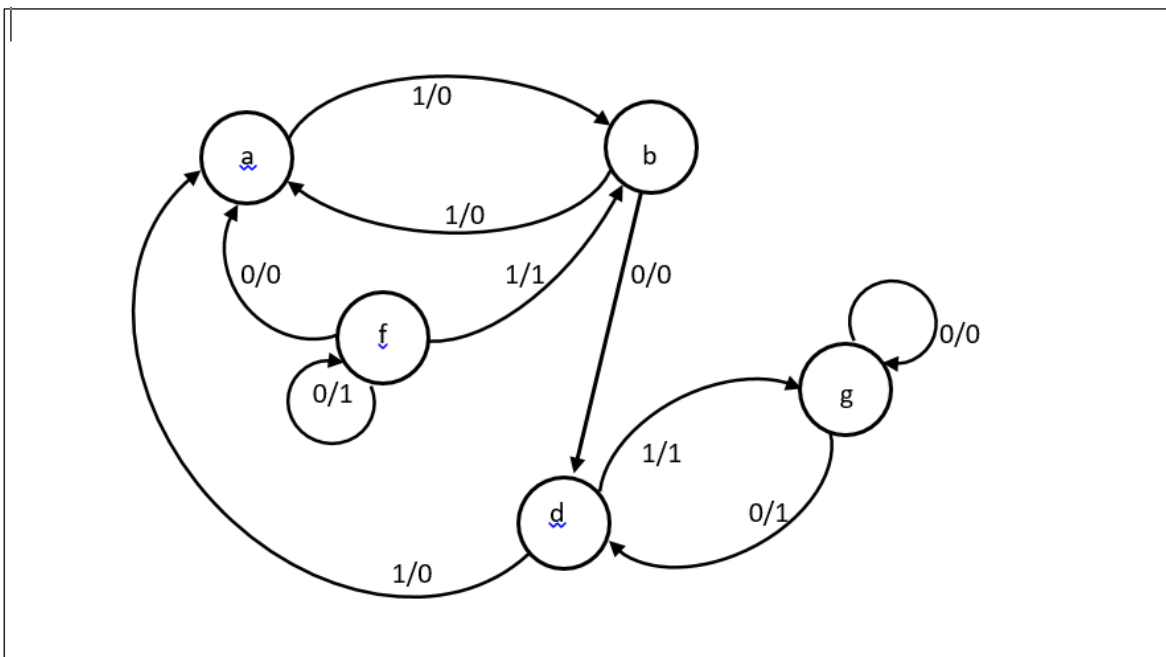

Total  
2 points

5.16


Total  
4 points

(a)  $D_A = Ax' + Bx$


$D_B = A'x + Bx'$

Present state		Input	Next state	
A	B	x	A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

1 point

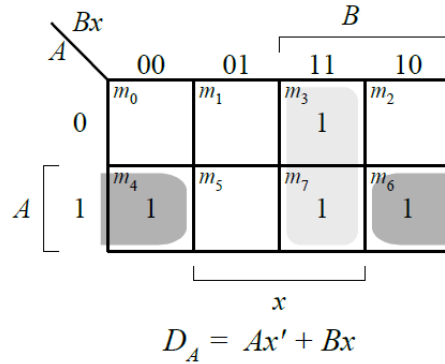

1 point

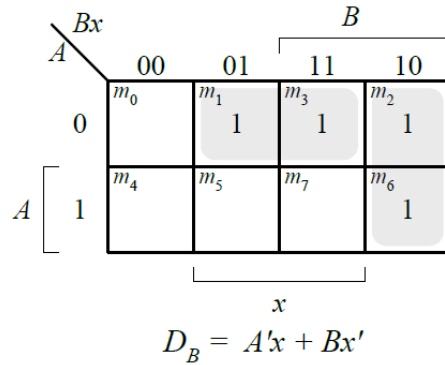

1 point

This work is protected  
and is provided so  
their courses ar  
or sale of an  
will destr

1 point for circuit diagram