

ELG3136A

Fall 2018

Assignment 7

Posting Date: Monday, November 12, 2018

General instructions

- 1. Your equations and solutions may be hand-written, scanned into a PDF format.**
- 2. A typed solution, with all relevant circuit diagrams drawn with VISIO (or other software), will be given a bonus mark of up to 10% the full mark**
- 3. Once you have a PDF file for your entire assignment you can upload it to your account on the Brightspace.**
- 4. Only one PDF file will be accepted.**

ELG3136 - Fall 2018

Assignment 7

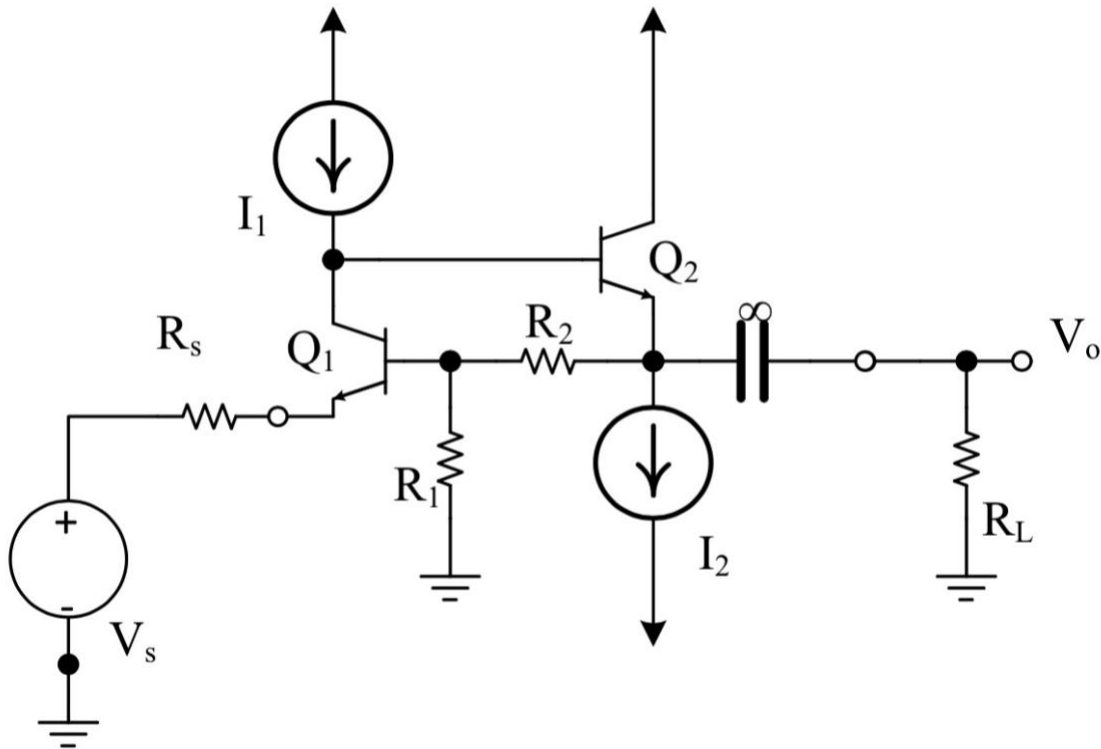


Figure 1

Consider the circuit shown above, where it is given that this circuit is a feedback circuit of Type I, i.e. Voltage-Voltage amplifier.

1. Using DC analysis for the circuit, calculate the DC emitter current for both transistors, and the DC voltage at the emitter of the transistor Q_2 .
 - Assume that the transistors are biased in the active mode and that
 - $R_1 = 1\text{k}\Omega$
 - $R_2 = 10\text{k}\Omega$
 - $R_L = 1\text{k}\Omega$
 - $R_s = 100\Omega$
 - $\beta_1 = \beta_2 = 100$
 - $I_1 = 0.1\text{ mA}$
 - $I_2 = 1\text{ mA}$
2. Redraw the circuit in the small-signal domain, while highlighting its feedforward and feedback components.
As a hint, the circuit must fit in the block diagram shown in Figure 2.

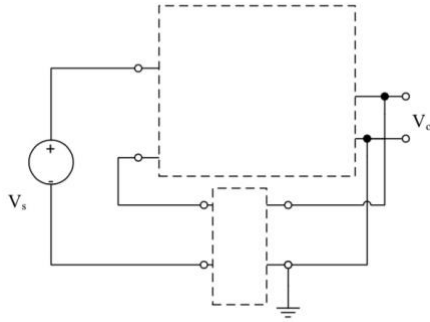


Figure 2

3. Assuming that R_2 is very large, derive an expression for the open-loop voltage gain. You must show clearly how you disconnect the feedback component from the system.
4. Derive an expression for the Feedback gain, K .
5. Using the results from the DC analysis above, and using AC small-signal analysis calculate the value of the small-signal open-loop voltage gain.
6. Calculate the overall (closed-loop) voltage gain.