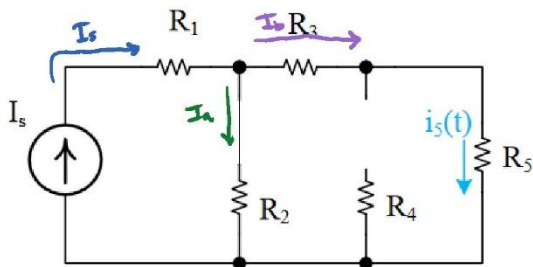


- $I_s = 8 \text{ A}$
- $R_1 = 4 \Omega$
- $R_2 = 6 \Omega$
- $R_3 = 12 \Omega$
- $R_4 = 4 \Omega$
- $R_5 = 2 \Omega$
- $C = 0.1 \text{ F}$

At $t < 0$ the switch is closed and the capacitor acts as an open circuit (dc steady state)





$$I_5(0) = \frac{I_s \times R_2}{(R_2 + R_3 + R_5)}$$

$$I_5(0) = \frac{8 \times 6 \Omega}{20 \Omega}$$

$$I_5(0) = 2.4 \text{ A}$$

After $t > 0$

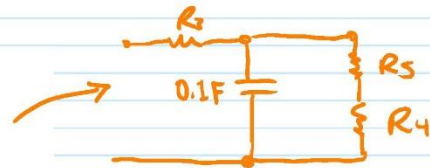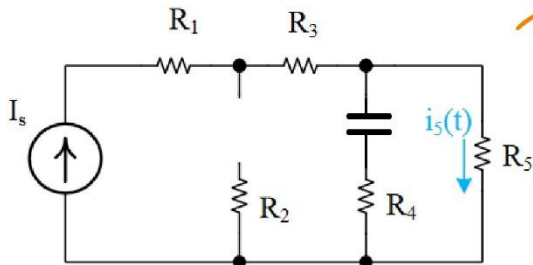

$$R_{eq} = R_5 + R_4 = 2 \Omega + 4 \Omega$$


$$R_{eq} = 6 \Omega$$

$$\tau = RC$$

$$\tau = (6 \Omega)(0.1 \text{ F})$$

$$\tau = 0.6 \text{ sec}$$

At $t = \infty$

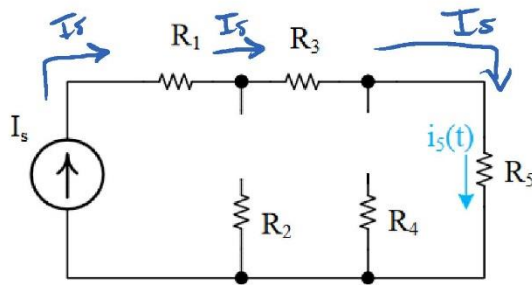

$$I_s(\infty) = I_s = 8A$$

Current as a function of time :

$$I_s(t) = I_s(\infty) + (I_s(0) - I_s(\infty))e^{-\frac{t}{\tau}}$$

$$I_s(t) = 8A + (2.4A - 8A)e^{-t/0.6}$$

$$I_s(t) = 8 - 5.6e^{-\frac{t}{0.6}}$$