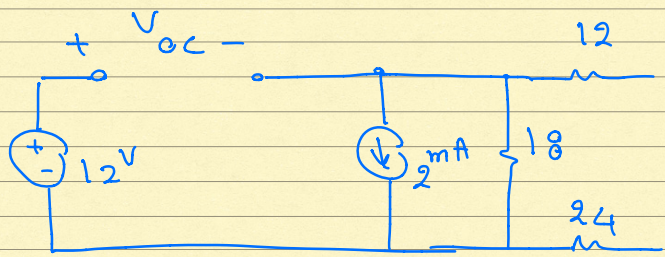


Solution of Assignment 4 by Emad Gad


Part 1) Thevenin Equivalent circuit

V_{oc}, R_z

To find V_{oc} , we remove R , and leave an open circuit



we can simplify the circuit

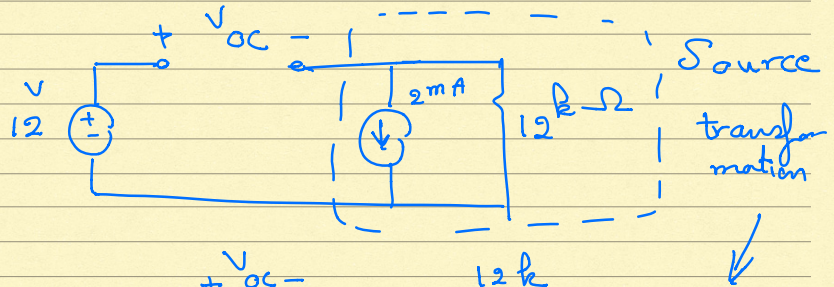



KVL @ the only loop gives

$$-12 + V_{oc} + 12 \times 0 - 24 = 0$$

$$V_{oc} = 36V$$

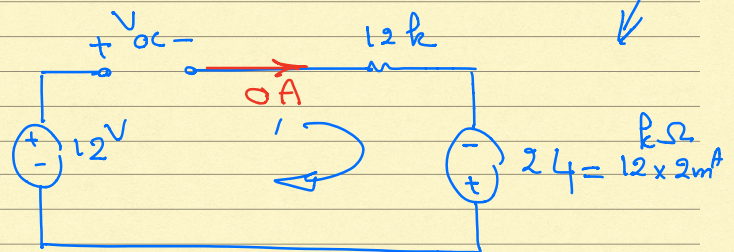To find R_z , we deactivate independent sources




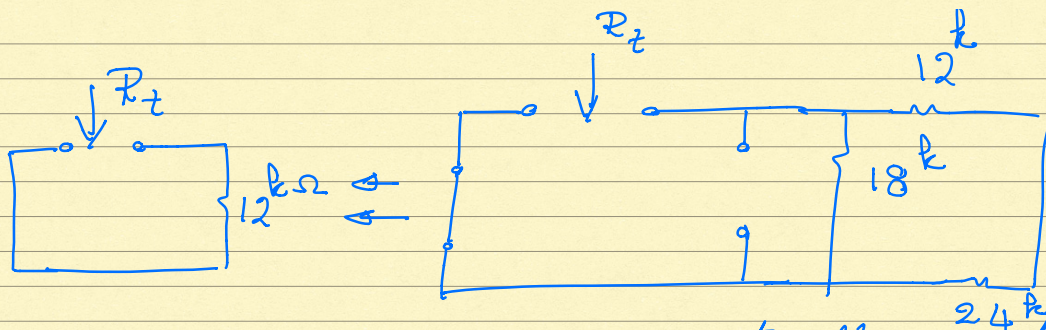


The circuit after deactivating independent sources

$$R_T = 12 \text{ k}\Omega$$

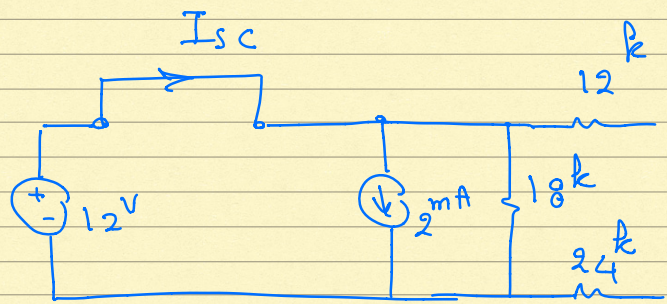Part 2) To find the Norton Equivalent circuit we need to find I_{sc} and R_T



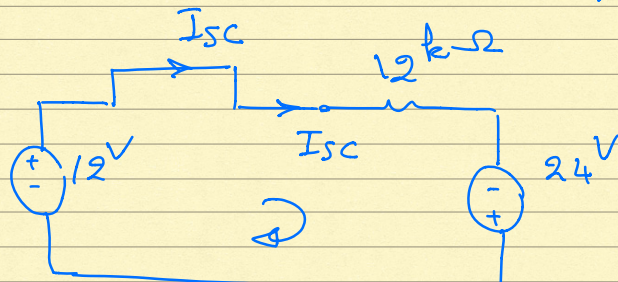We can simplify the circuit as we did in part 1)



writing a KVL a loop

$$-12 \text{ V} + 12 \text{ k}\Omega \times I_{sc} - 24 = 0$$

$$I_{sc} = \frac{36V}{12k} = \frac{36}{12000} = 3 \text{ mA}$$

R_t has already been computed and found to be


$$R_t = 12 \text{ k} \Omega$$

Notice also that R_t can be obtained alternatively from V_{oc} and I_{sc} , using

$$R_t = \frac{V_{oc}}{I_{sc}} = \frac{36}{3 \text{ mA}} = \frac{36}{0.003} = 12000 \Omega = 12 \text{ k} \Omega$$

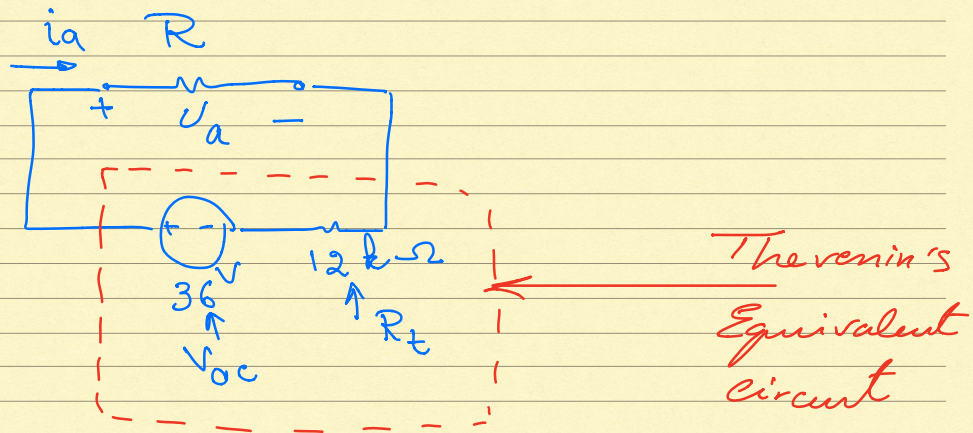Part 3)

Using the Thevenin equivalent, we can replace the circuit between the terminals with its Thevenin as shown here



$$i_a = \frac{V_{oc}}{R_t + R} \quad 0 \leq R \leq 100 \text{ k} \Omega$$

a) maximum current i_a is at min R ,

$$i_{a \text{ max}} = \frac{V_{oc}}{0 + R_t} = \frac{36}{12000} = 3 \text{ mA}$$

b) maximum voltage for V_a

$$V_a = i_a \times R = \frac{V_{oc}}{R + R_t} \times R = \frac{V_{oc}}{1 + \frac{R_t}{R}}$$

maximum value for V_a is at the value, where R is maximum, i.e. at $R = 200000 \Omega$

$$V_{a_{max}} = \frac{36}{1 + \frac{12000}{200000}} = 32.14 V$$

c) maximum power delivered to R is

$$P_{max} = \frac{V_{oc}^2}{4 R_t} = \frac{36^2}{4 \times 12000} = 0.027 W = 27 mW$$

This power is delivered to R when

$$R = R_t = 12000 \Omega$$