

### Problem (1)

The period of the sinusoid is half the period of  $i(t)$ . Let  $T$  be the period of  $i(t)$  and  $T/2$  be the period of the sinusoid. Then


$$i(t) = \begin{cases} 10 \sin \frac{4\pi}{T} t & 0 < t < \frac{T}{4} \\ -10 \sin \frac{4\pi}{T} t & \frac{T}{2} < t < \frac{3T}{4} \\ 0 & \text{otherwise} \end{cases}$$

$$\begin{aligned} I_{RMS} &= \frac{100}{T} \left[ \int_0^{T/4} \sin^2 \frac{4\pi}{T} t dt + \int_{T/4}^{3T/4} \sin^2 \frac{4\pi}{T} t dt \right] \\ &= \frac{100}{T} \left[ \left( \frac{t}{2} - \frac{\sin \frac{8\pi}{T} t}{18\pi} \right) \Big|_0^{T/4} + \left( \frac{t}{2} - \frac{\sin \frac{8\pi}{T} t}{18\pi} \right) \Big|_{T/2}^{3T/4} \right] = 25 \end{aligned}$$


$$I_{rms} = \sqrt{25} \Rightarrow I_{rms} = 5 \text{ mA}$$
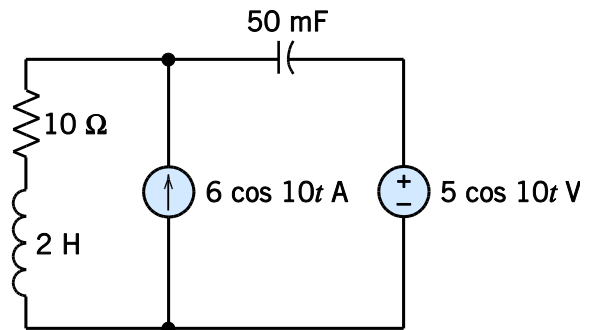
## Problem (2)

For the circuit shown, determine the complex power of the  $R$ ,  $L$ , and  $C$  elements and show that the complex power delivered by the sources is equal to the complex power absorbed by the  $R$ ,  $L$ , and  $C$  elements.



**Solution:**

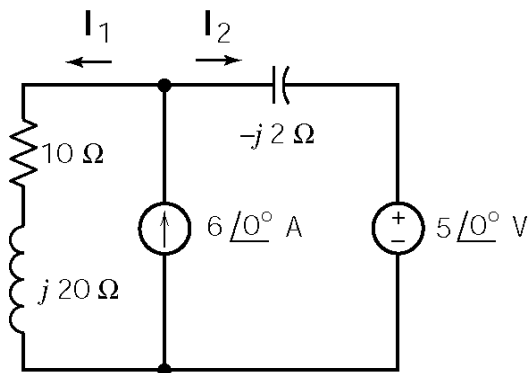

KVL:

$$(10 + j20)\mathbf{I}_1 = 5\angle 0^\circ - j2\mathbf{I}_2$$

$$\Rightarrow (10 + j20)\mathbf{I}_1 + j2\mathbf{I}_2 = 5\angle 0^\circ$$

KCL:

$$\mathbf{I}_1 + \mathbf{I}_2 = 6\angle 0^\circ$$

Solving these equations using Cramer's rule:

$$\Delta = \begin{vmatrix} 10 + j20 & j2 \\ 1 & 1 \end{vmatrix} = 10 + j18$$

$$\mathbf{I}_1 = \frac{1}{\Delta} \begin{vmatrix} 5 & j2 \\ 6 & 1 \end{vmatrix} = \frac{5 - j12}{10 + j18} = 0.63\angle 232^\circ \text{ A} = -0.39 - j0.5 \text{ A}$$

$$\mathbf{I}_2 = 6 - \mathbf{I}_1 = 6 + 0.39 + j.5 = 6.39 + j.5 = 6.41\angle 4.47^\circ \text{ A}$$

Now we are ready to calculate the powers. First, the powers delivered:

$$\mathbf{S}_{5\angle 0^\circ} = \frac{1}{2}(5\angle 0^\circ)(-\mathbf{I}_2^*) = 2.5(6.41\angle(180-4.47)) = -16.0 + j1.25 \text{ VA}$$

$$\mathbf{S}_{6\angle 0^\circ} = \frac{1}{2}[5 - j2\mathbf{I}_2](6\angle 0^\circ) = [5 - j2(6.39 + j.5)]3 = 18.0 - j38.3 \text{ VA}$$

$$\mathbf{S}_{\text{Total delivered}} = \mathbf{S}_{5\angle 0^\circ} + \mathbf{S}_{6\angle 0^\circ} = \underline{2.0 - j37.2 \text{ VA}}$$

Next, the powers absorbed:

$$\mathbf{S}_{10\Omega} = \frac{1}{2}10|\mathbf{I}_1|^2 = \frac{10}{2}(.63)^2 = 2.0 \text{ VA}$$

$$\mathbf{S}_{j20\Omega} = \frac{j20}{2}|\mathbf{I}_1|^2 = j4.0 \text{ VA}$$

$$\mathbf{S}_{-j2\Omega} = \frac{1}{2}(-j2)|\mathbf{I}_2|^2 = -j(6.41)^2 = -j41.1 \text{ VA}$$

$$\mathbf{S}_{\text{Total absorbed}} = \underline{2.0 - j37.1 \text{ VA}}$$

To our numerical accuracy, the total complex power delivered is equal to the total complex power absorbed.