

Op - amps

IDEAL: $R_i \rightarrow \infty$, $I_i \rightarrow 0$, $V_2 = V_1$, $A \rightarrow \infty$, $R_o \rightarrow 0$

$V_o = A(V_2 - V_1)$, $A = \frac{V_o}{V_s}$

INVERTING:

$A = \frac{V_o}{V_s} = -\frac{R_2}{R_1}$

$R_{in} = R_1$

SUMMING (-ive):

$I_a = \frac{V_a - V_1}{R_A} = \frac{V_a}{R_A}$


$I = \frac{V_1 - V_o}{R} = \frac{-V_o}{R}$

$\Rightarrow V_o = -R \left[\frac{V_a}{R_A} \dots \right]$

NON-INVERTING:

$A = \frac{V_o}{V_s} = 1 + \frac{R_2}{R_1}$

INTEGRATOR:

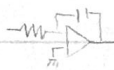


$\omega_o = \frac{1}{RC}$

$H(j\omega) = \frac{-Z_2}{Z_1} = -\frac{1}{j\omega C \cdot R}$

$|H(j\omega)| = \frac{\omega_o}{\omega}$

$\angle H(j\omega) = -90^\circ$

(poor) Low PASS FILTER

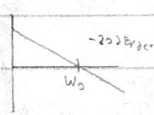

MODIFIED INTEGRATOR:




$\omega_o = \frac{1}{CR_2}$

$H(j\omega) = \frac{-R_2/R_1}{1 + j\omega CR_2}$

$|H(j\omega)| = \left| \frac{K}{1 + j\omega/\omega_o} \right|$

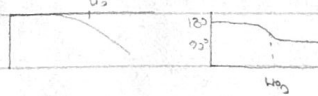$\angle H(j\omega) = 180^\circ - \angle \left[1 + j\omega/\omega_o \right]$



DIFFERENTIATOR:




$\omega_o = \frac{1}{RC}$

$H(j\omega) = -j\omega RC$

$|H(j\omega)| = \omega/\omega_o$

$\angle H(j\omega) = -90^\circ$

(poor) HPF

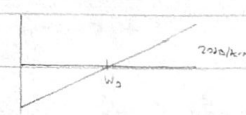

MODIFIED DIFFERENTIATOR:




$\omega_o = \frac{1}{CR_1}$

$H(j\omega) = -\frac{1}{1 - j\omega/\omega_o}$

$|H(j\omega)| = \left| \frac{1}{1 - j\omega/\omega_o} \right|$

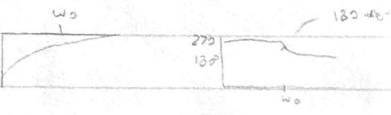$\angle H(j\omega) = 180^\circ - \angle \left[1 - j\omega/\omega_o \right]$



DIODES

FB \rightarrow Depletion Region Shrinks

Break down occurs due to - Kinetic energy of minority carrier

RB \rightarrow Depletion Region Grows

- Zener/Field effect

$V_D = V_{D0} + I_D r_D$

$I_D = I_S (e^{V_D/nV_T} - 1)$ $r_D = \frac{nV_T}{I_D}$

$V_T = 25 \text{ mV @ room temp}$

$V_Z = V_{Z0} + I_Z r_Z$

(for physical model)

$V_{rms} = \frac{V_{pk}}{\sqrt{2}}$


$I_{D2} = e^{(V_{D2} - V_{D1})/nV_T}$

SMALL SIGNAL ANALYSIS:

DC ANALYSIS: FIND I_D (using specific model)

AC ANALYSIS: $r_D = \frac{nV_T}{I_D}$

CLIPPER:

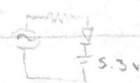

RECTIFICATION:

HWR: $V_{DC} = \frac{V_m}{\pi}$, PIV = V_m

FWR: $V_{DC} = \frac{2V_m}{\pi}$, PIV = $2V_m$ (center tapped), V_m (Bridge)

CLAMPER:



-ive: $V_o = 0V$, $V_C = 2V$
+ive: $V_o = -V_C = -2V$
 $V_C = 6V$




$r_D = \frac{1}{g_D}$

→ KVL for BE circ
to obtain current

BJT's

EBJ: FB
CBJ: FB

EBJ: FB
CBJ: RB

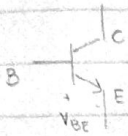

SAURATION

$$V_{BE} > 0.7V$$

$$V_{CE} < V_{BE}$$

ACTIVE

$$V_{BE} > 0.7V$$

$$V_{CE} > V_{BE}$$

$$(V_C > V_B > V_E)$$

$$I_E = I_B + I_C = (\beta + 1)I_B$$

$$I_C = \beta I_B = \alpha I_E$$

$$I_B = (1 - \alpha)I_E$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$g_m = \frac{I_C}{V_t} = \frac{\beta}{r_{\pi}} = \frac{\alpha}{r_e}$$

$$r_D = \frac{|V_A|}{I_C}$$

$$r_{\pi} = \frac{V_t}{I_B} = (\beta + 1)r_e$$

$$r_e = \frac{V_t}{I_E} = \frac{r_{\pi}}{\beta + 1}$$

$$G = \frac{V_o}{V_i} \cdot \frac{V_o}{V_i} = A_v$$

CNF: G

R_i

R_o

A_{v1}

A_{v2}

Phase inv

AMP

CE BYPASSED


$$R_1 || R_2 || r_{\pi}$$

$$r_D || R_C$$

$$\frac{R_i}{R_i + R_S}$$

$$-g_m R_C'$$

✓

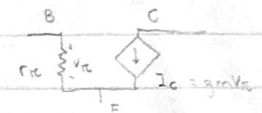

AMP

CE UN-

$$R_1 || R_2 || (r_{\pi} + R_i(\beta + 1))$$

$$R_C$$

$$\frac{R_i}{R_i + R_S}$$

$$-\alpha \frac{R_C'}{r_e + R_E} \approx -\frac{R_C'}{R_E}$$

✓

AMP

CB


$$R_E || r_e$$

$$R_C$$

$$\frac{R_i}{R_i + R_S}$$

$$\frac{\alpha R_C' R_L}{r_e} = g_m R_C'$$

✗

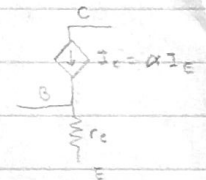

BUFFER

CC

$$(R_1 || R_2) || [r_e + (\beta + 1)(R_E || R_L)]$$

$$R_E || (r_e + \frac{R_C || R_L}{\beta + 1})$$


$$\frac{R_i}{R_i + R_S}$$

$$\frac{R_E || R_C}{r_e + (R_E || R_C)}$$

✗

"emitter follower"

MOSFET'S

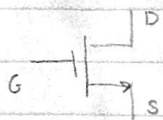

TRIODE

$$V_{GS} > V_t$$

$$V_{DS} < V_{GS} - V_t$$

SAURATION

$$V_{GS} > V_t$$

$$V_{DS} \geq V_{GS} - V_t$$

$$I_{D(sat)} = \frac{1}{2} \frac{K_n'}{K_n} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$I_{D(tr)} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t) V_{DS}$$

phase inv

R_i

R_o

A_v

$$I_{D(tr)} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t) V_{DS}$$

AMP

✓

CS

$$\infty$$

$$r_{D1} || r_{D2}$$

$$-g_m R_C' = -g_m (r_{D1} || r_{D2} || R_L)$$

$$g_m = \sqrt{2 \cdot I_{D(sat)} \cdot K_n} \quad g_{m0} = g_m \cdot f$$

AMP

✗

CG

$$\left(\frac{1}{g_{m1} + g_{m01}} \right) \left(\frac{1 + r_{D2}}{1 + r_{D1}} \right)$$

$$r_{D1} || r_{D2}$$

$$\frac{r_{D1} r_{D2} [\frac{1}{r_{D1}} + g_{m1} + g_{m01}]}{r_{D1} + r_{D2}} = \frac{1}{1 + (g_{m1} + g_{m01}) r_{D1}}$$

$$r_D = \frac{|V_A|}{I_{D(sat)}}$$

BUFFER

✗

CD


$$\infty$$

$$r_{D1} || r_{D2} || \frac{1}{g_m} || \frac{1}{g_{m0}}$$

$$\frac{g_{m1} R_C'}{1 + g_{m1} R_C'}$$

→ KVL across source and drain to achieve V_{GS} in terms of I_{D(sat)}

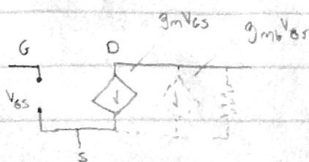→ plug into I_D eqn, solve quadratic → solve V_{GS}, pick answer that isn't too small



$$CG: V_{GS} = V_G - V_S = 0 - V_S = -V_S$$

$$(g_{m1} + g_{m01})V_S + \frac{V_i - V_o}{r_{D1}} = \frac{V_o}{r_{D2}}$$

$$\Rightarrow v_i[\cdot] = v_o[\cdot]$$

$$\Rightarrow A_v = \frac{v_o}{v_i} = \dots$$

$$CD: V_{GS1} = V_i - V_S$$

$$\diamond g_{m01}(-V_S)$$

$$\diamond g_{m1}(V_S)$$