



uOttawa

L'Université canadienne
Canada's university

CEG2136

Computer Architecture I

Basic Computer Organization

Voicu Groza

SITE Hall, Room 5017

562 5800 ext. 2159

Groza@SITE.uOttawa.ca

Université d'Ottawa | University of Ottawa



www.uOttawa.ca


CEG 2136 Computer Architecture I



Outline

- Instruction Codes
- Addressing Modes
- The Datapath of the Basic Computer
- Basic Computer Instructions
 - Register - Reference Instructions
 - Memory-Reference Instructions
 - Input-Output and Interrupt
- The Control Unit of the Basic Computer

Basic Operation of a Computer

 

1. The computer *accepts* information in the form of programs and data through an input unit and *stores* it in memory
2. The information stored in memory is *fetches*, under program control, and *processed* in an ALU
3. The processed information *leaves* the computer through an output unit
4. All activities inside the computer are *directed* by the control unit

3

Instruction Codes

- An **instruction code** is a group of bits (binary code) that instruct the computer to perform a sequence of micro-operations.
- Instruction codes together with data (operands) are stored in the computer memory.
- The control unit then interprets the binary code of the instruction and proceeds to execute it by deploying a sequence of micro-operations.
- An instruction code is usually divided in two parts: an **operation code (opcode)** and an **address code**.
- The operation code defines the operation to be performed: addition, subtraction, logic AND, etc.
- The address code usually (but not always) specifies the address of the operand.

4


Instruction Codes

- The control unit receives the instruction code from the memory, interprets the operation code, and then issues a sequence of control signals to initiate the necessary sequence of micro-operations to be performed on the specified operands.
- An instruction code must specify not only the operation (defined by the operation code), but also the registers or memory words where the operands are to be found, as well as the register or memory word where the result is to be stored.
- A memory word can be specified within the instruction code by specifying its address in memory.
- A processor register can be specified within the instruction code by assigning k bits that identify one of the 2^k possible processor registers available in the system.
- In this chapter, we will discuss the basic organization, functionality, and design of a small-scale computer system.


5

Stored Program Organization

 - A 4096×16 memory unit is used \Rightarrow 16-bit words.
- The memory is divided into two parts:
 - A program part, storing the program (set of instructions) to be executed,
 - A data part, storing the data (operands) to be used for the instructions of the program.




- Each **instruction** in the program part of the memory is divided in two parts:
 - The first part is composed of 4 bits (bits 12 to 15) and it specifies the operation code (**opcode**) of one of a maximum of $2^4 = 16$ possible operations that can be performed.
 - The second part is composed of 12 bits (bits 0 to 11) and it specifies the address of the operand in memory.
- The 12 bits in the address part of the instruction code can specify a maximum of $2^{12} = 4096$ different word addresses in the memory, which is the size of the memory used in our case.

 


Stored Program Operation


- Each word in the data part of the memory holds a 16-bit operand.
 - The accumulator AC is a processor register that is usually used to store one operand of the operation to be performed.
-
- A program instruction is executed in the following sequential order:
 1. The control unit reads the 16-bit instruction code from the program portion of the memory.
 2. The 12-bit address part of the instruction code is then used to read the 16-bit operand from the data portion of the memory.
 3. The 4-bit operation code is then used to perform the desired operation on the operand just read.

 

Basic Computer Registers & Memory

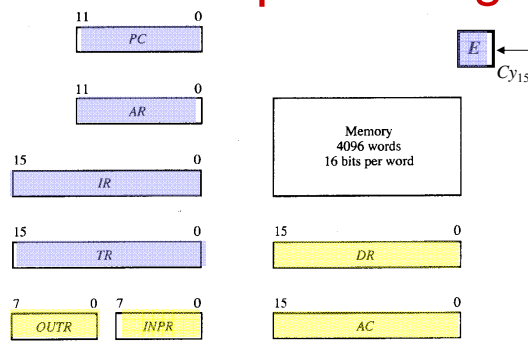


Memory 4096 words of 16 bits

 

Register symbol	Number of bits	Register name	Function
DR	16	Data register	Holds memory operand
AC	16	Accumulator	Processor register
IR	16	Instruction register	Holds instruction code
TR	16	Temporary register	Holds temporary data
AR	12	Address register	Holds address for memory
PC	12	Program counter	Holds address of instruction
INPR	8	Input register	Holds input character
OUTR	8	Output register	Holds output character

Basic Computer Instruction List (Hex)

 

Symbol	Hexadecimal code		Description
	I = 0	I = 1	
AND	0xxx	8xxx	AND memory word to AC
ADD	1xxx	9xxx	Add memory word to AC
LDA	2xxx	Axxx	Load memory word to AC
STA	3xxx	Bxxx	Store content of AC in memory
BUN	4xxx	Cxxx	Branch unconditionally
BSA	5xxx	Dxxx	Branch and save return address
ISZ	6xxx	Exxx	Increment and skip if zero
CLA	7800		Clear AC
CLE	7400		Clear E
CMA	7200		Complement AC
CME	7100		Complement E
CIR	7080		Circulate right AC and E
CIL	7040		Circulate left AC and E
INC	7020		Increment AC
SPA	7010		Skip next instruction if AC positive
SNA	7008		Skip next instruction if AC negative
SZA	7004		Skip next instruction if AC zero
SZE	7002		Skip next instruction if E is 0
HLT	7001		Halt computer
INP	F800		Input character to AC
OUT	F400		Output character from AC
SKI	F200		Skip on input flag
SKO	F100		Skip on output flag
ION	F080		Interrupt on
IOF	F040		Interrupt off

Addressing Modes

- Register Addressing
 - Operands reference internal registers
 - Also called *inherent addressing* (Motorola)
 - Immediate Addressing
 - Operand is constant and is contained in the instruction word *immediately* following the opcode
 - Direct Addressing
 - The Operand is to be fetched from the memory location whose address is given by the 12 bits following the opcode in the instruction word
 - Indirect Addressing
 - Instruction specifies where the **address of the operand** is located
- NOT IMPLEMENTED HERE:**
- Indexed addressing
 - Finds the data address using an index (an offset)
 - Relative Addressing
 - Add offset to current value of the PC

Notation used in Comments

- Register Name: Indicates a register and its contents
 - Example: AC refers to the contents of accumulator AC
- → (->) Right arrow indicates data transfer operation (<-> indicates an exchange of data)
 - Example: AC -> DR indicates the contents of AC are transferred (copied) to DR
- M[...] Contents of a memory location
 - Example: M[1234H] -> AC indicates that the contents of memory location HEX1234 are transferred to AC
- M[M[...]] Indirect addressing – inner parentheses specifies a memory address that contains the data address
 - Example: AC -> M[M[1234H]] indicates that the contents of AC are transferred to a memory location whose address is found in memory location with address 1234H (STA @1234H)

11


Inherent Addressing (Register Addressing)

- All data for instructions are in the CPU
- Instructions with inherent addressing
 - Are among the fastest to execute
 - Coded with the least amount of bits
- Also called Register Addressing or Implied Addressing

CLA		; 0 -> AC															
		15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
		Opcode				Register Address											
CLA = 7800 _H		0	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0
INC		; AC <- AC+1															
		15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
		Opcode				Register Address											
INC = 7020 _H		0	1	1	1	0	0	0	0	0	0	1	0	0	0	0	0

12

Immediate Addressing

 

An argument is contained in the bits immediately following the opcode.

It is not implemented in this BASIC COMPUTER !!!

The lsb 12-bit contents of the instruction word (i.e., the operand) are moved to accumulator AC



Immediate Addressing Examples


LDA #64 ; Decimal 64 -> AC
 LDA #64H ; Hexadecimal 64 -> A

- The # symbol indicates immediate addressing
- It is easy to forget the #

Direct Addressing


- Instruction contains the data address
 - Single-level addressing
 - **Operand's address** is given by the low-order 12 bits following the opcode.
 - Instructions encoded with opcodes 0 - 6 (msb IR₁₅=0) access addresses \$000-\$FFF directly

Example: LDA 4 ; A ← M[4]

 

The 16-bit contents of the selected memory location are copied, as specified by the instruction, to the accumulator AC.

 The lsb 12-bit of the instruction word (004) represent the address of the memory location where the operand is stored




Memory

Indirect Addressing


- Also called *pointer addressing*
- Instruction contains address of memory location holding the data address (*pointer*)
- Two level addressing mechanism
 - First level provided by instruction gives *address of memory containing an address*
 - Second level is the *address* that specifies where the *data* is located
 - Instructions encoded with opcodes 8 - E (msb $IR_{15}=1$) access addresses \$000-\$FFF indirectly. Actually the memory space they can address is 64kW (kilo words)
 
```
Example:
LDA @9BAH
;AC <- M[M[9BAH]]
```




1. The lsb 12 bits of the instruction word (\$9BA) represent the *address* of the memory location where *data address* (9B5) is stored; *data address* points to the memory location where *data* is stored

 2. The 16-bit contents of memory location \$9B5 are moved to the accumulator AC




Direct VS Indirect Address

 The instruction code is composed of a 3-bit opcode, a 12-bit address, and an indirect address mode bit I ($I = 0$ for a direct address, and $I = 1$ for an indirect one).



(a) Instruction format


Fig. (b) shows a direct address mode ($I = 0$) with an opcode of an ADD operation. The 12-bit address code holds the binary equivalent of 457. \Rightarrow The operand is found in address 457 of the memory.

 

(b) Direct address

The operand is fetched and added to the number stored in the accumulator AC.


Fig. (c) shows an indirect address mode ($I = 1$) with an opcode of an ADD operation. The 12-bit address code holds the binary equivalent of 300. \Rightarrow The address of the operand is fetched from address 300, which contains the binary equivalent of 1350. The operand is then fetched from address 1350 and added to the number stored in the accumulator AC.

 

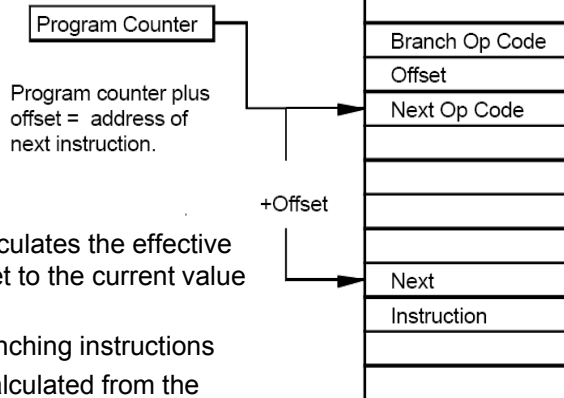(c) Indirect address


Relative Addressing

- The address of the operand is called the **effective address**.
- For instance, the effective address in the previous Fig. (b) is 457, whereas it is 1350 in Fig. (c).
- Relative addressing calculates the effective address by adding offset to the current value of the PC
 - Used mostly for branching instructions
 - Normally offset is calculated from the address of the next op-code
- Not implemented in our BASIC Computer



17


Basic Computer

 

18


Computer Registers

- The memory unit has a capacity of 4096 words with 16 bits each.
- As shown in Figure 29(a), each 16-bit instruction code is composed of 12 address bits, a 3-bit opcode, and one bit to specify a direct or indirect address.
- The data register (*DR*) holds the operar read from the memory.
- The accumulator (*AC*) is a general purpose processing register.
- The instruction register (*IR*) holds the instruction read from the memory.
- The temporary register (*TR*) holds temporary data during processing
- The address register (*AR*) is a 12-bit register that holds the address of the word to be accessed in the memory.
- The program counter (*PC*) is a 12-bit register that holds the address of the next instruction to be fetched from the memory after the current instruction is executed.
- *INPR* is an input register that holds an 8-bit code of a character read from an input device. *OUTR* is an output register that holds an 8-bit code of a character to be transferred to an output device.

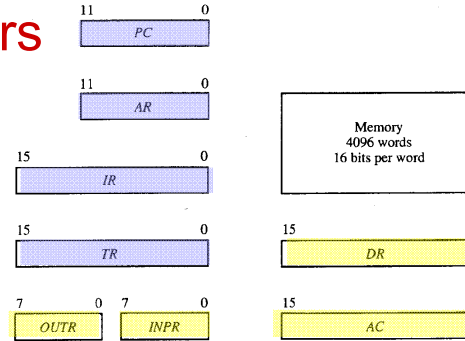



BASIC COMPUTER

Data Path

 

- The common bus lines are connected to the data input lines of each register as well as the data inputs of the memory.
- The particular register whose *LD* (load) input bit is enabled, receives the data from the bus during the next clock pulse.
- The content of the bus is loaded into the memory when its *Write* control bit is activated.
- The memory places one of its 16-bit words on the bus when its *Read* control bit is activated and $S_2S_1S_0 = 111$.
- Two of the registers connected to the bus have 12 bits only (*AR* and *PC*).
- When the content of *AR* or *PC* is applied to the 16-bit bus, the bus' 4 msb's are reset to '0'.
- When *AR* or *PC* loads the content of the bus, only the 12 lsb's are transferred to the register.

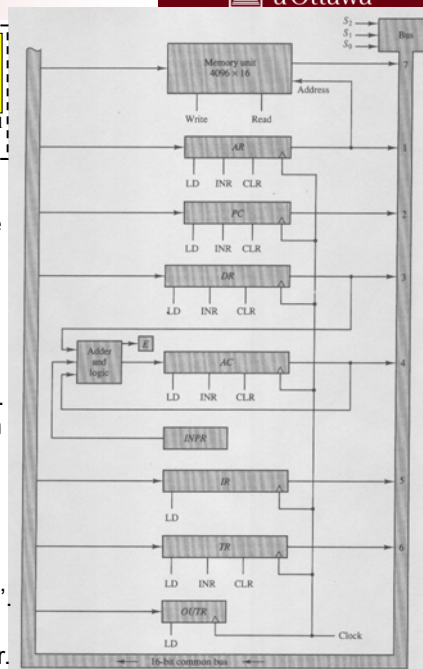

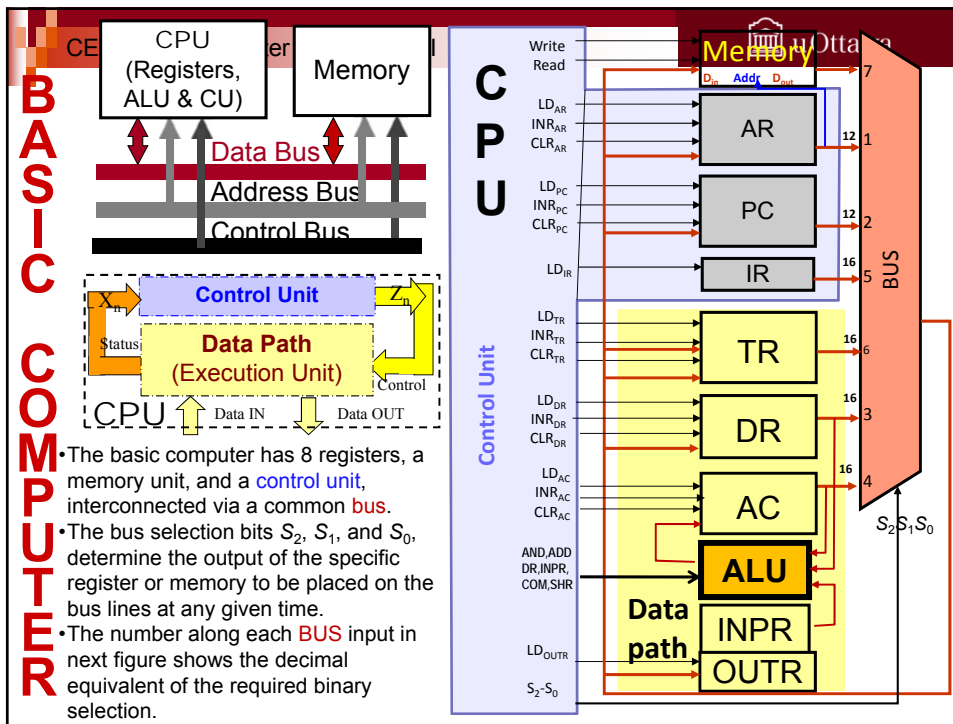

CEG 2136 Computer Architecture I uOttawa

Basic Computer Instructions

(a) Memory - reference instruction

15	14	12	11	0
1	Opcode		Address	

(Opcode = 000 through 110)

(b) Register - reference instruction

15	12	11	0
0	1	1	1
Register operation			

(Opcode = 111, $I = 0$)

(c) Input - output instruction

15	12	11	0
1	1	1	1
I/O operation			

(Opcode = 111, $I = 1$)

Symbol	$I=0$	$I=1$	Description
MRI			
AND	0xxx	8xxx	AND memory word to AC
ADD	1xxx	9xxx	Add memory word to AC
LDA	2xxx	Axxx	Load memory word to AC
STA	3xxx	Bxxx	Store content of AC in memory
BUN	4xxx	Cxxx	Branch unconditionally
BSA	5xxx	Dxxx	Branch and save return address
ISZ	6xxx	Exxx	Increment and skip if zero
RRI			
CLA	7800		Clear AC
CLE	7400		Clear E
CMA	7200		Complement AC
CME	7100		Complement E
CIR	7080		Circulate right AC and E
CIL	7040		Circulate left AC and E
INC	7020		Increment AC
SPA	7010		Skip next instruction if AC positive
SNA	7008		Skip next instruction if AC negative
SZA	7004		Skip next instruction if AC zero
SZE	7002		Skip next instruction if E is 0
HLT	7001		Halt computer
IOI			
INP		F800	Input character to AC
UT		F400	Output character from AC
SKI		F200	Skip on input flag
SKO		F100	Skip on output flag
ION		F080	Interrupt on
IOP		F040	Interrupt off


There are 3 instruction formats.

The opcode is composed of 3 bits ($I_{14}I_{13}I_{12}$)

000-110 = operations to be performed on AC


- the rest of the 12-bit ($I_{11} - I_0$) specify an address in memory:
- $I_{15} = 0$ => instruction with direct address
- $I_{15} = 1$ => instruction with indirect address
- 111 & $I_{15} = 0$** => a register reference instr.
- 111 & $I_{15} = 1$** => an input-output instruction.

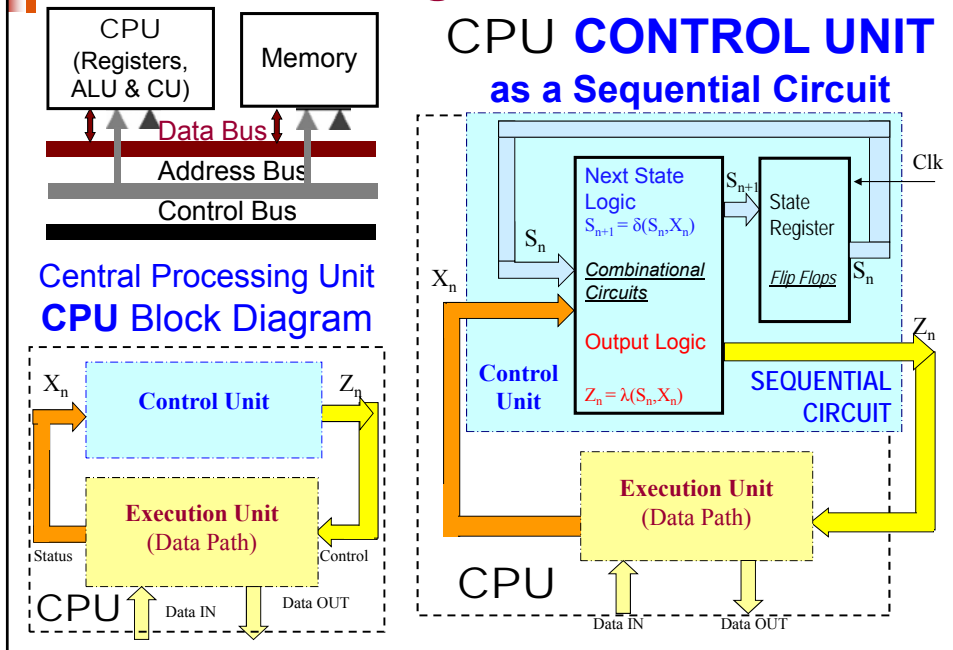the other 12 bits ($I_{11} - I_0$) are used to specify the type of operation to be performed



Algorithmic State Machine (ASM)

 - The ASM method is utilized to solve a given problem, assuming that the target is a digital electronic **device**, consisting in a **datapath** and a **control unit**.



- The following are the five major steps in the ASM methodology:

- ASM # 1. Using *pseudocode* describe the algorithm to be executed by the device
- ASM # 2. Convert the pseudocode into an *ASM flowchart* (with *RTL*)
- ASM # 3. Design the *datapath* based on the ASM flowchart
- ASM # 4. Create a *detailed ASM chart* (equivalent to FSM) with *control signals* that have to be generated by the *control unit* to direct the *datapath*
- ASM # 5. Design the *control logic* based on the detailed ASM chart

- If followed correctly, the ASM method produces a hardware design in a systematic and logical manner
 - Very robust and easily modified
 - Refined through pseudocode iterations

ASM Flowchart Rules (ASM#2)


- There are some rules that have to be abided by during ASM design
 1. State boxes should contain only RTL statements, control signals in parentheses, and state-transfer statements in parentheses
 2. All operations within a state box should be concurrently executable in one clock cycle
 3. If the operations in two consecutive state boxes can be executed in the same clock cycle, then the two state boxes can be combined into one state box
 4. Condition boxes should contain only simple queries that can be evaluated using purely combinational logic
 5. A new register must be assigned for each unique name in the set of RTN statements
 6. For each register-transfer statement, there must be a path between the source and the destination registers (if a transformation takes place during the transfer, then a combinational device, such as an adder or ALU, must be inserted into the path between the source and destination registers)
 7. If there are several paths leading into a combinational device or register, a multiplexer or tri-state buffer must be used
 8. For each simple binary query in a condition box, a combinational device or status signal must be used
 9. Finally, control signal inputs must be attached to each register and multiplexer so that register transfers can be precisely controlled

27

ASM Design Example

- The datapath of a dedicated coprocessor has three 16-bit registers *AR*, *BR*, and *CR*.
- When the coprocessor is triggered by a signal *start*, it will perform the following operations:
 - Transfer two 16-bit signed numbers (provided by the microcontroller over two data buses *DB-A* and *DB-B* in 2's-complement representation) to *AR* and *BR*.
 - If the number in *AR* is negative, divide the number in *AR* by 2 and transfer the result to register *CR*.
 - If the number in *AR* is positive but nonzero, multiply the number in *BR* by 2 and transfer the result to register *CR*.
 - If the number in *AR* is zero, clear register *CR* to 0.
 - Signalize the end of the processing by setting a flag *done*.


#1 Block Diagram

 


28
 
#1 Block Diagram

- Transfer two 16-bit signed numbers (provided by the microcontroller over two data buses *DB-A* and *DB-B* in 2's-complement representation) to *AR* & *BR*.
- If the number in *AR* is negative, divide the number in *AR* by 2 and transfer the result to register *CR*.
- If the number in *AR* is positive but nonzero, multiply the number in *BR* by 2 and transfer the result to register *CR*.
- If the number in *AR* is zero, clear register *CR* to 0.
- Signalize the end of the processing by setting a flag *done*.




#2 ASM Flowchart (High Level RTL)

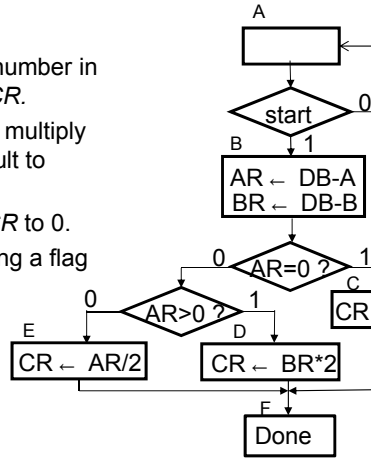

29


#2 ASM Flowchart (High Level RTL)

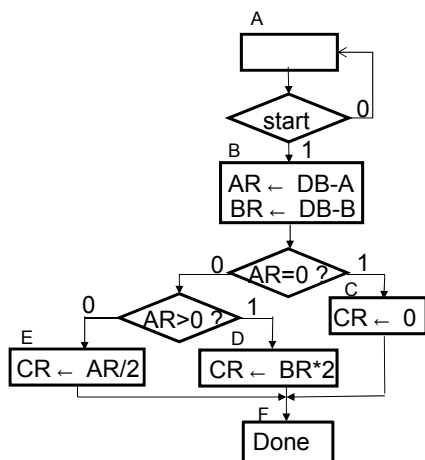


	$Z_n = \lambda(S_n)$	$S_{n+1} = \delta(S_n, X_n)$
A Start:		SC ← B
B:	AR ← DB-A, BR ← DB-B	
B ARZ:		SC ← C
B ARZ' ARG:		SC ← D
B ARZ' ARG':		SC ← E
C:	CR ← 0	SC ← F
D:	CR ← BR*2	SC ← F
E:	CR ← AR/2	SC ← F
F:		SC ← A

30

#3 ASM Datapath

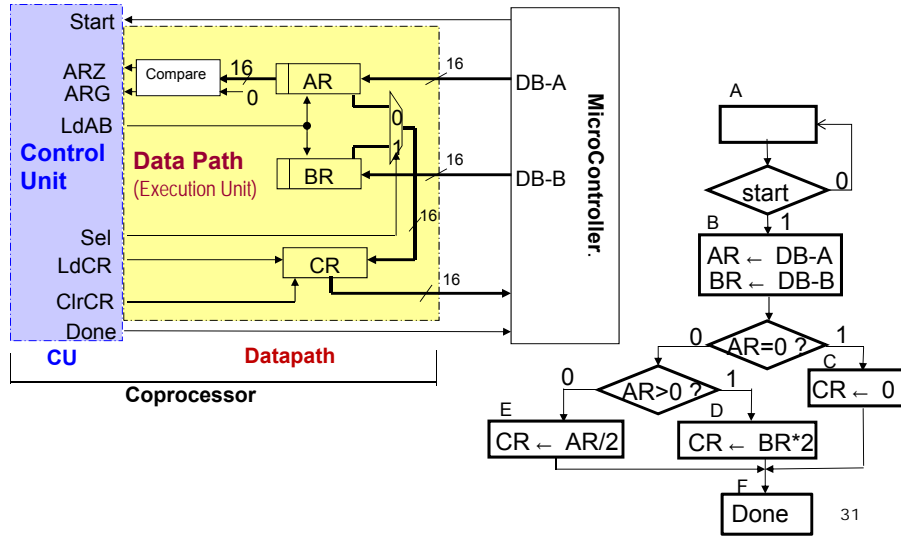


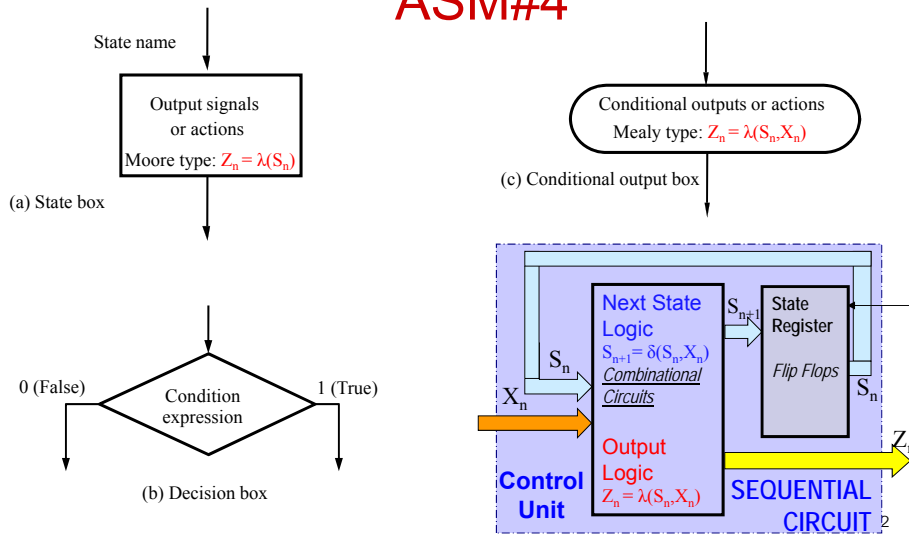Symbols used in ASM detailed charts ASM#4




ASM Flowcharts Constructs (ASM#2)

- Original ASM constructs consisted of **state** boxes, **condition** boxes and **conditional output** boxes
 - Conditional output boxes (Mealy FSM's) are difficult to represent in text or table ASM chart format, and allow conditional data transfers (RTL) ... can be avoided
- ASM textual or tabular charts have replaced flowcharts because of their ease of modeling complexity and representing large synchronous sequential circuits

 


ASM Flowcharts (ASM#2)

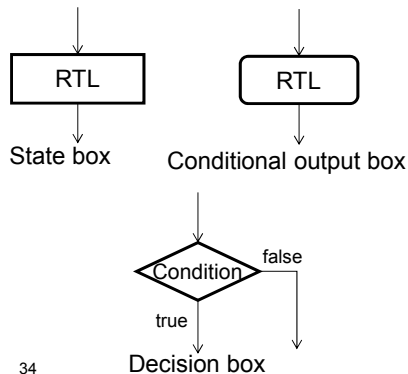ASM textual or tabular charts replace flowcharts because of their ease of modeling complexity and representing large synchronous sequential circuits.



ASM Detailed Chart (ASM#4)

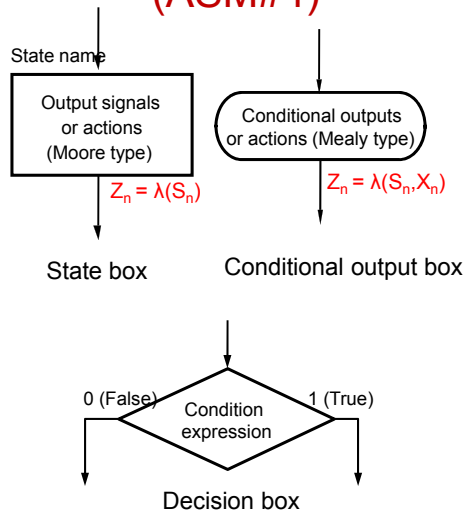


Algorithmic State Machine (ASM)


The following are the major steps in the ASM methodology:

- Create an algorithm, using *pseudocode*, to describe the desired operation of the device
- Convert the pseudocode into an *ASM chart* (the basic brick = **ASM block**)
- Design the *datapath* based on the ASM chart
- Create a *detailed ASM chart* based on the datapath
- Design the *control logic* based on the detailed ASM chart

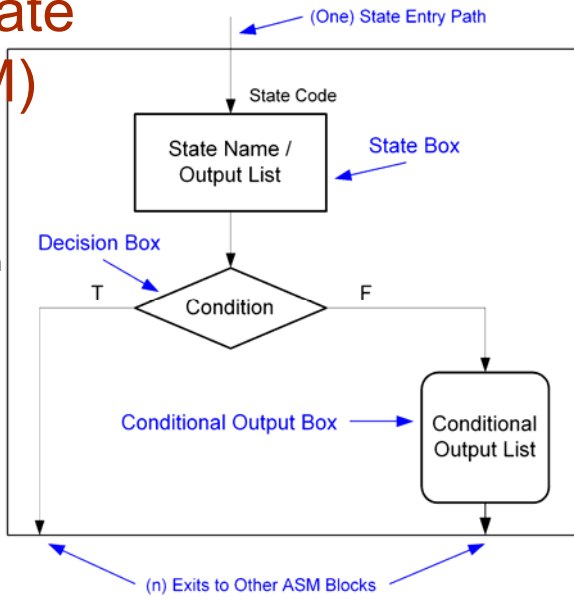Combination of **datapath** and **control logic** makes up the actual logic system that will solve the original problem.




ASM Detailed Chart (ASM#4)

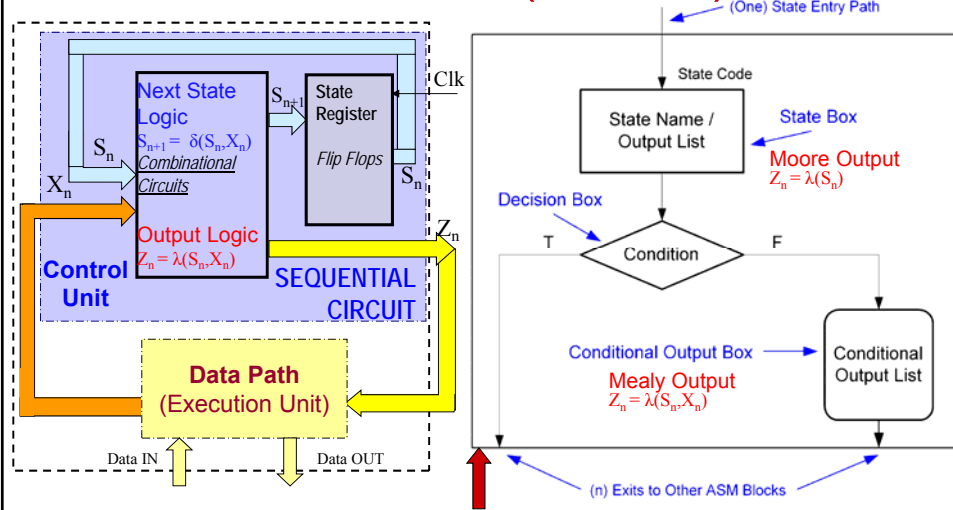

The basic brick = **ASM block**
 Combination of **datapath** and **control unit** makes up the actual logic system that will solve the original problem.

ASM Detailed Chart Rules (ASM#4)


- There are some rules that have to be abided by during detailed ASM chart design
 1. For each box in the ASM chart, there should be a corresponding box in the *detailed ASM chart*
 2. A state box should contain a comma-delimited list of entries of the form *csig* or *cond*: (*csig*,...,*csig*) where *csig* is a control signal or state transfer statement in parentheses and *cond* is a logical combination of status signals.
 3. For each RTL operation in a state box of an ASM chart, there should be a list of control signals that accomplishes the RTL operation in the corresponding state box of the detailed ASM chart. These control signals are generated by the *control unit* through its output function $Z = \lambda(S,X)$ - as CU is a sequential circuit.
 4. All control signals are assumed to have the value '1' if specified and the value '0' if left unspecified
 5. For each condition box in the ASM chart, there should be a corresponding condition box in the detailed ASM chart
 6. Each condition box in the detailed ASM chart must contain a logical combination of status signals that implements the combinational logic query in the corresponding ASM chart condition box
- Rules 1-6 provide the mapping between the ASM chart and the detailed ASM chart
- Pay special attention to the state box and conditional box mappings!
- Control logic is the heart of the digital circuit, and is often the most complex and detailed block of the entire system, and thus must be designed **very carefully!**
- The detailed ASM chart should easily be converted to a control path, as long as the aforementioned rules are followed

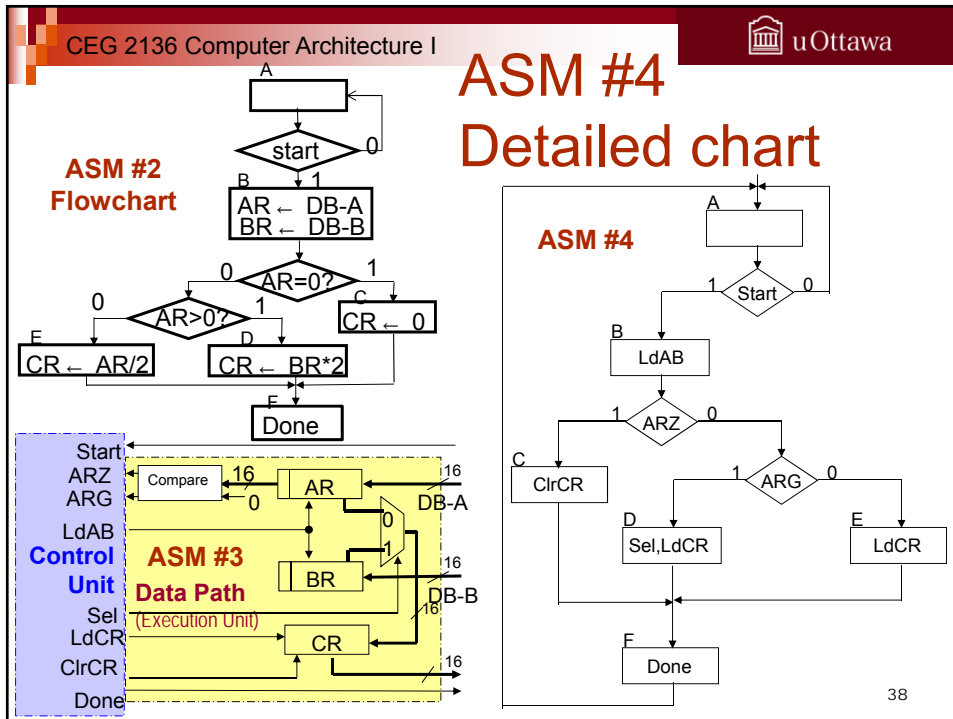


Control Unit Design (ASM#5)

There are three major methods for implementing the State Register of sequential circuits which are used as control logic ASM-based circuits:

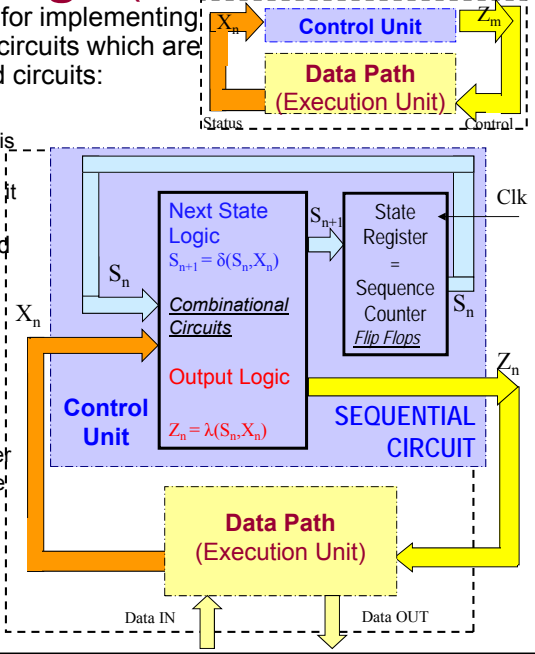1. The **one-FF-per-state** method
 - Also called One-hot, we will see this method during this lecture
 - Most popular design technique, as it is simple and easy to model
 2. The **Binary Encoded State** method
 - Uses state encoding to reduce the number of D flip-flops required in the state register
 - Control logic is spread out over several different digital devices
 3. The **sequence-counter** method
 - Matches the cyclical nature of instruction execution on a computer
 - Control is simplified because of the cyclical state transition pattern
- The **PLD-based** method
- Amalgamates all logic devices into one single VLSI chip
 - Could contain both the datapath and the control logic!




ASM #5.3

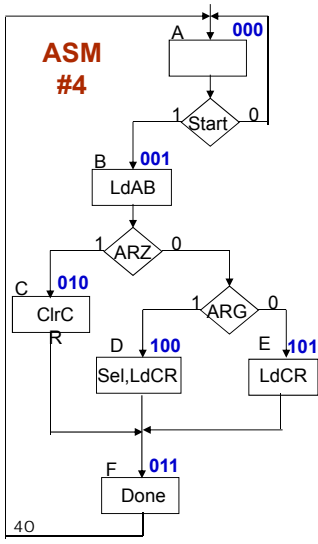

RTL	delta		lambda								
	Z_n = A	S_{n+1} = delta	SC++	ClrSC	LdSC	SC_{n+1} D_2, D_1, D_0	LdAB	LdCR	ClrCR	Sel	Done
A Start:		SC ← B	1								
B:	AR ← DB-A, BR ← DB-B						1				
B ARZ:		SC ← C	1								
B · ARZ' · ARG:		SC ← D		1	100						
B · ARZ' · ARG':		SC ← E		1	101						
C:	CR ← 0	SC ← F	1						1		
D:	CR ← BR * 2	SC ← F		1	011		1			1	
E:	CR ← AR / 2	SC ← F		1	011		1				
F:		SC ← A	1								1

Next State Logic $S_{n+1} = \delta(S_n, X_n)$
 $SC++ = A \cdot start + B \cdot ARZ + C$
 $ClrSC = F$
 $LdSC = B \cdot ARZ' \cdot ARG + B \cdot ARZ' \cdot ARG' + D + E$
 $D_0 = B \cdot ARZ' \cdot ARG' + D + E$
 $D_1 = D + E$
 $D_2 = B \cdot ARZ' \cdot ARG + B \cdot ARZ' \cdot ARG'$

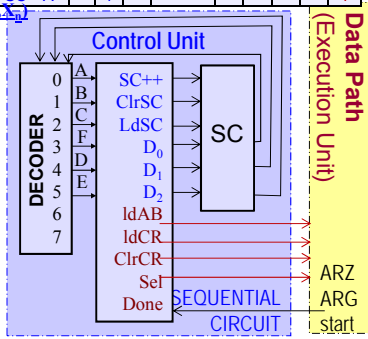Output Logic $Z_n = \lambda(S_n)$
 $LdAB = B$
 $LdCR = D + E$
 $ClrCR = C$
 $Sel = D$
 $Done = F$




Rules for a Safe Design

1. Keep the design simple and modular
 - Use an iterative procedure, if necessary, to build through refinement
 - Implement one module at a time, while unit testing each one
2. Develop good documentation during the design
3. Beware of clock skew
 - Use similar path lengths to all flip-flops
 - Do not use gated clocks!
 - Use all positive-edge-triggered or all negative-edge-triggered flip-flops
4. Be wary of asynchronous inputs to the circuit
 - Avoid them whenever possible!
 - Synchronize any ones that cannot be avoided
 - Use debounced switches to provide clean input signals
5. Beware of noise on power and signal lines
6. Avoid dependencies on minimum logic gate delays
7. Initialize all flip-flops to known values at the beginning

41

Basic Instruction Cycle

 

- Computer performs the instruction cycle forever! (or at least until it is turned off, faces an error or is instructed to do so)

42


Instruction Cycle

- A program residing in the memory of the computer consists of a sequence of instructions.
- Each instruction is executed in several steps:
 1. Fetch an instruction from memory.
 2. Decode the instruction.
 3. Read the effective address from memory if the instruction has an indirect address.
 4. Execute the instruction.
- Upon the completion of step 4, the control goes back to step 1 to start over the cycle for the next instruction.
- The process is repeated indefinitely unless a HALT instruction is encountered.



43

ASM#1

Detailed Instruction Cycle



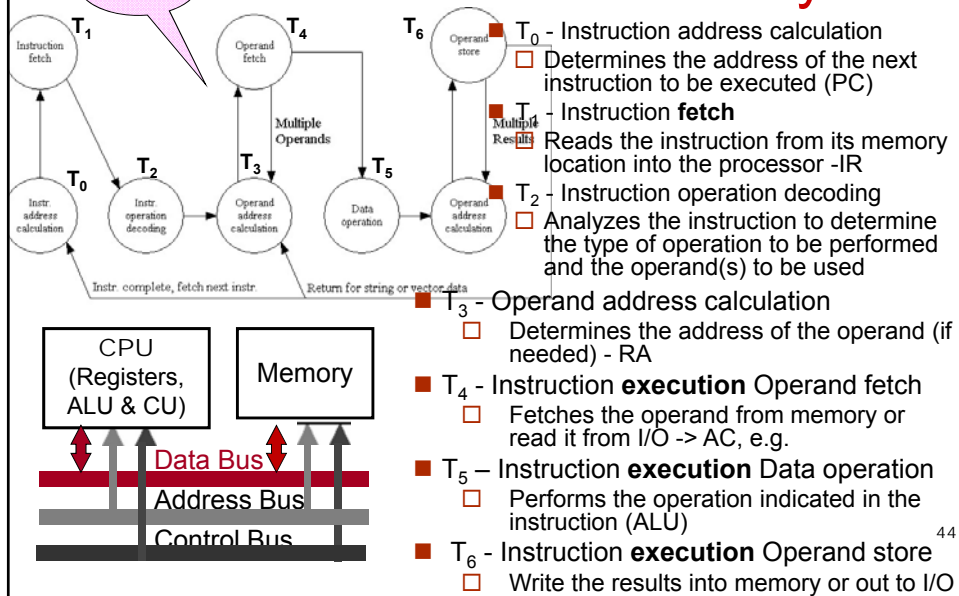




44

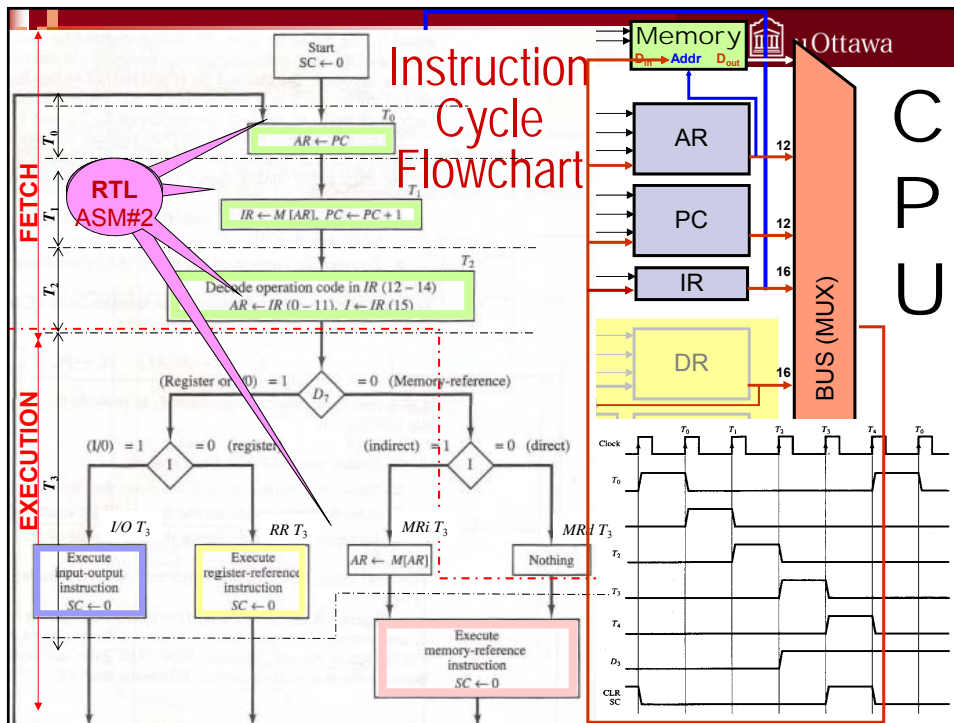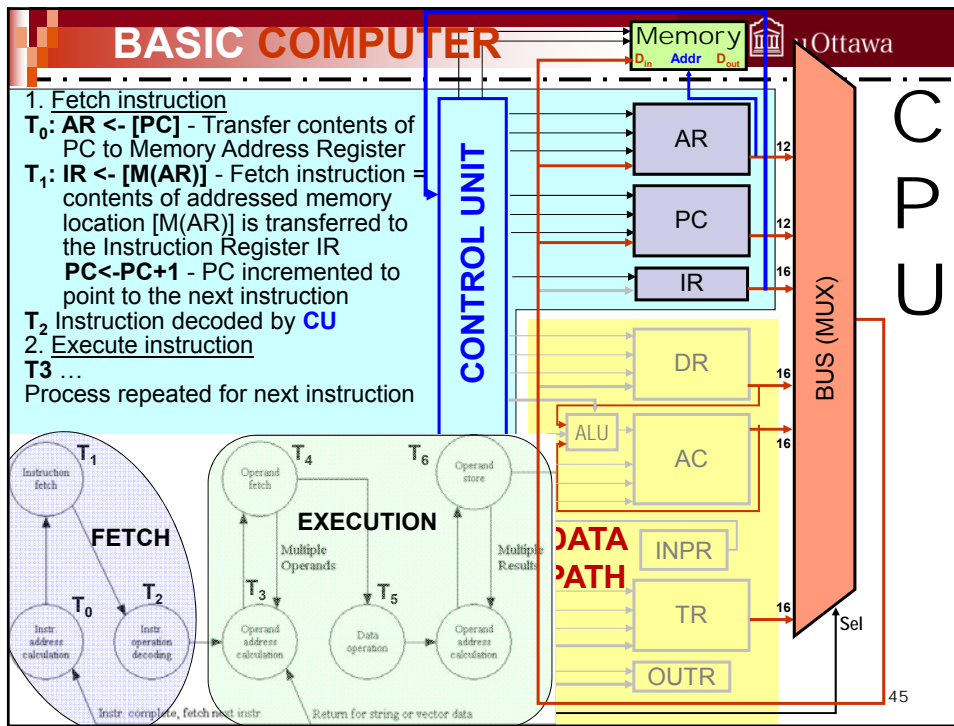


Fetch & Decode

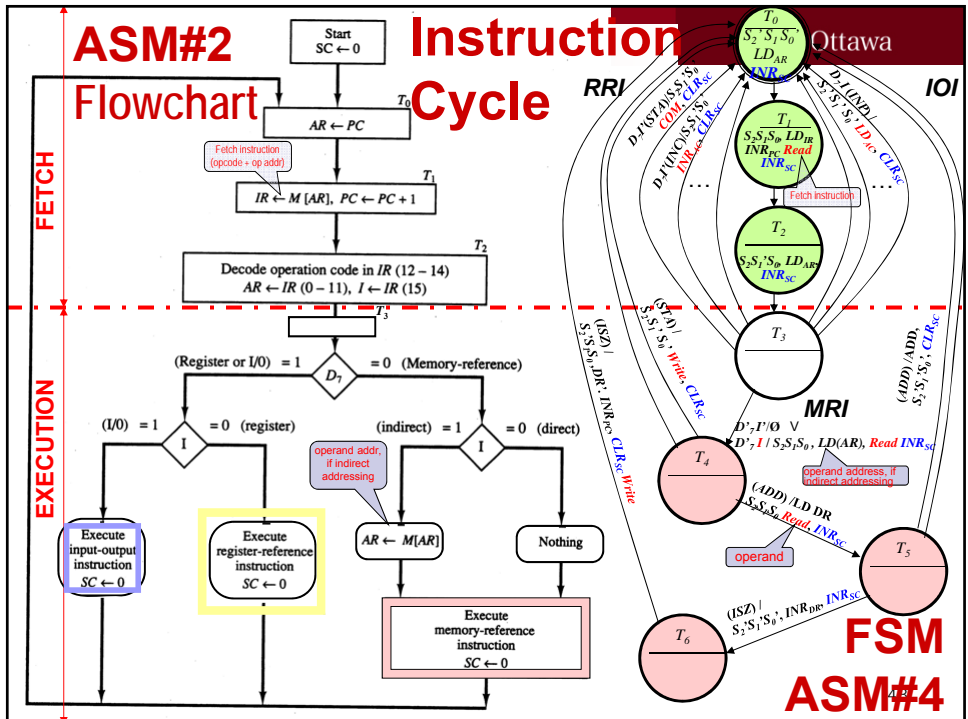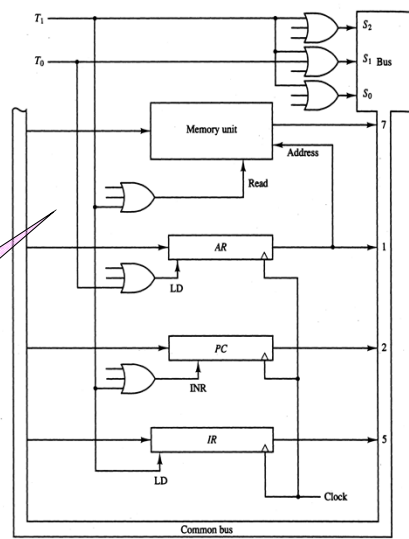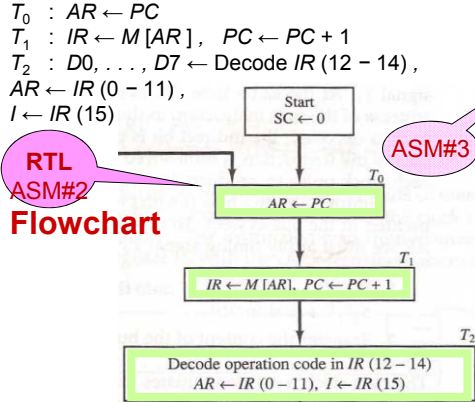- When a program is executed, the program counter gets initially loaded with the address of the first instruction of the program, and SC is cleared making $T_0=1$
- After each clock pulse, SC is automatically incremented, so that the timing signals go through T_0, T_1, T_2, \dots
- The micro-operations of the fetch and decode phases can be specified by the following RTL statements:



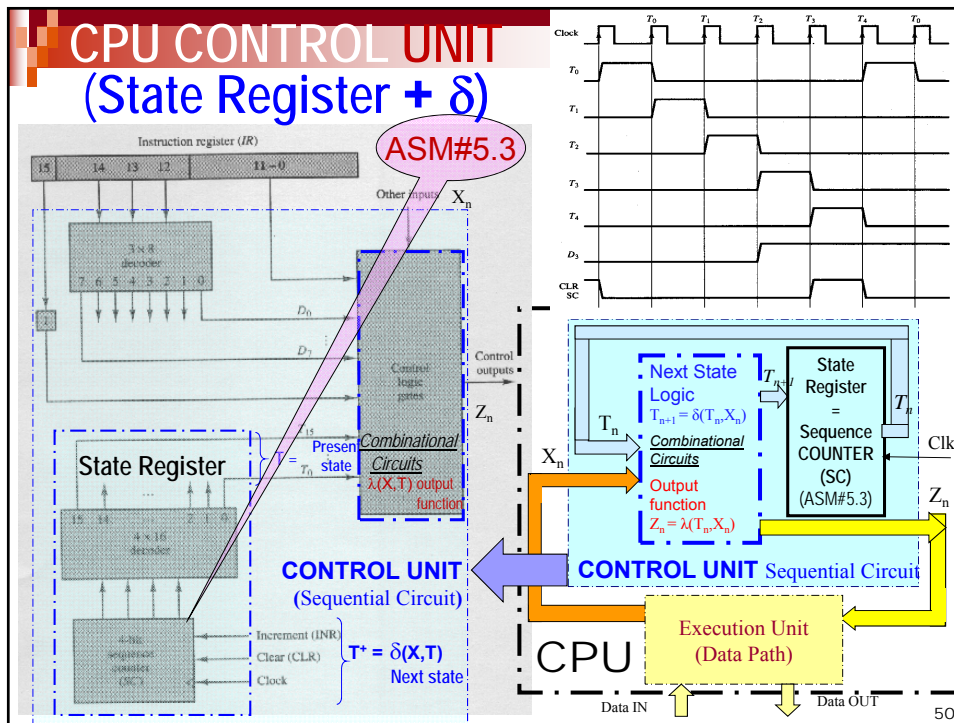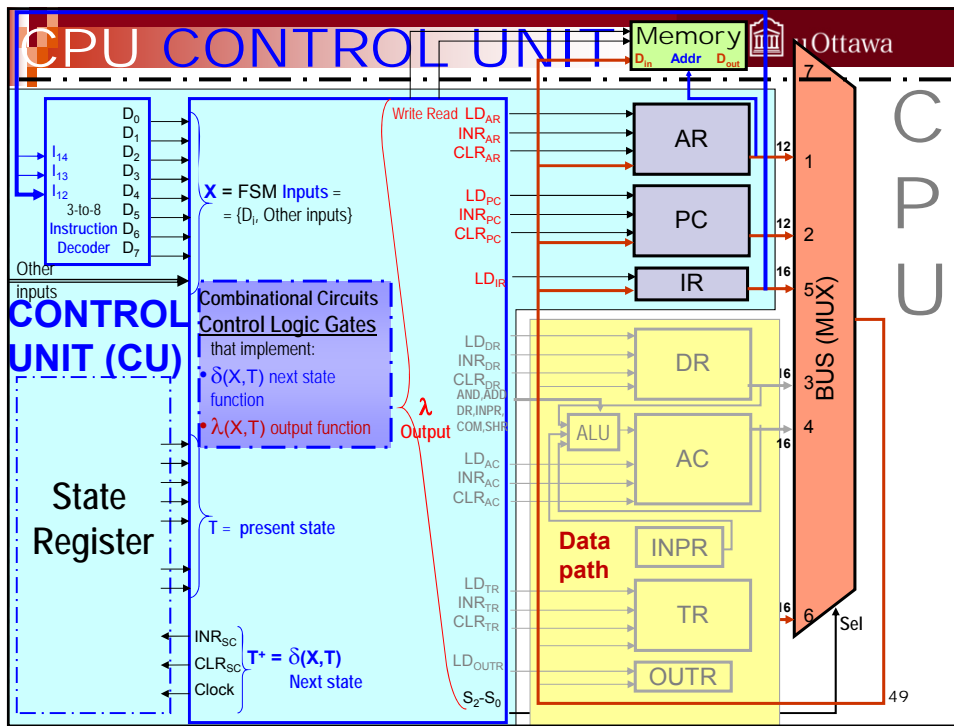




CPU CONTROL UNIT (State Register + δ)

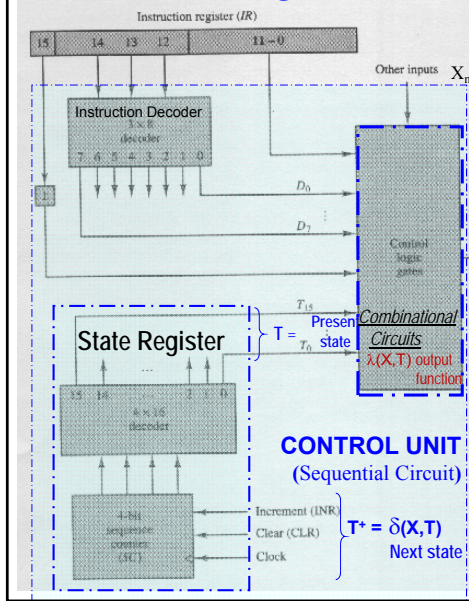


- The control unit (CU) is a *programmable sequential circuit*, whose transition (δ) and output (λ) functions changes in accord with the current instruction $I_{14}I_{13}I_{12}$.
- CU consists of a State Register (sequence counter SC + 4x16 decoder) & Combinational Circuits that compute the *output function* (λ - control signals for the multiplexers and registers in the system) & the *transition function* (δ - CLR clears SC at the end of the execution of every instruction to return SC to the initial state T_0 , for the next instruction).
- The current instruction is read from memory and it is stored in the instruction register IR during its execution.
- The 3-bit opcode $IR_{14}IR_{13}IR_{12}$ is decoded using a 3 x 8 decoder (*Instruction Decoder*);
- the outputs of the *Instruction Decoder* are $D_0 - D_7$, each corresponding to one operation.
- IR_{15} is transferred to a flip-flop.
- SC can count in binary from 0 to 15. The outputs of SC are decoded into 16 timing signals $T_0 - T_{15}$
- The 12 least significant bits of IR, $I_{11} - I_0$, and $T_0 - T_{15}$, are all passed as inputs to the Control Logic Gates.

51

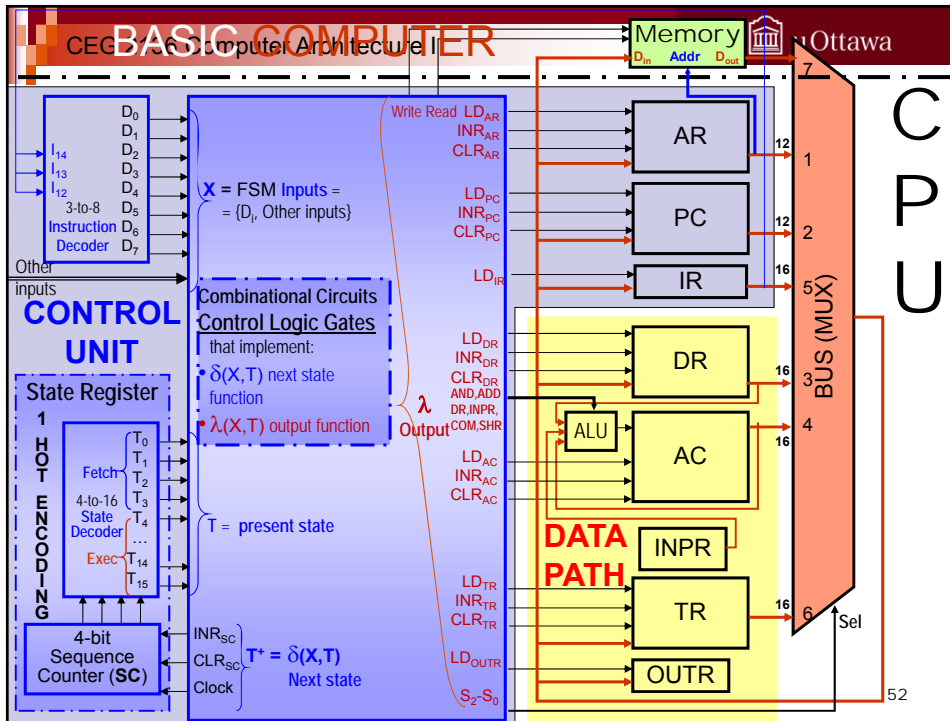

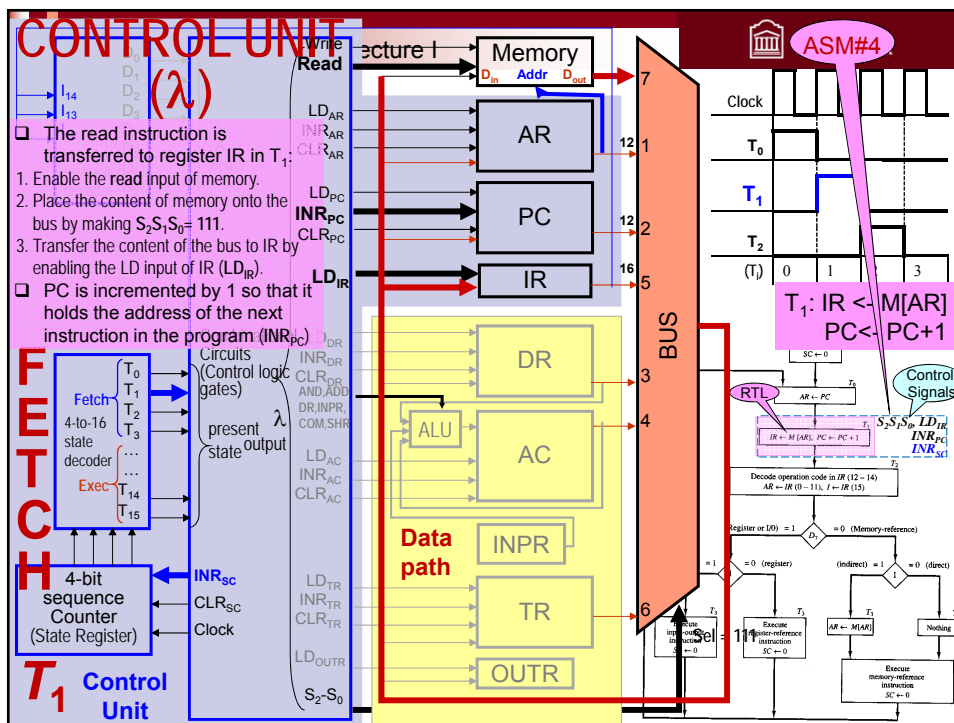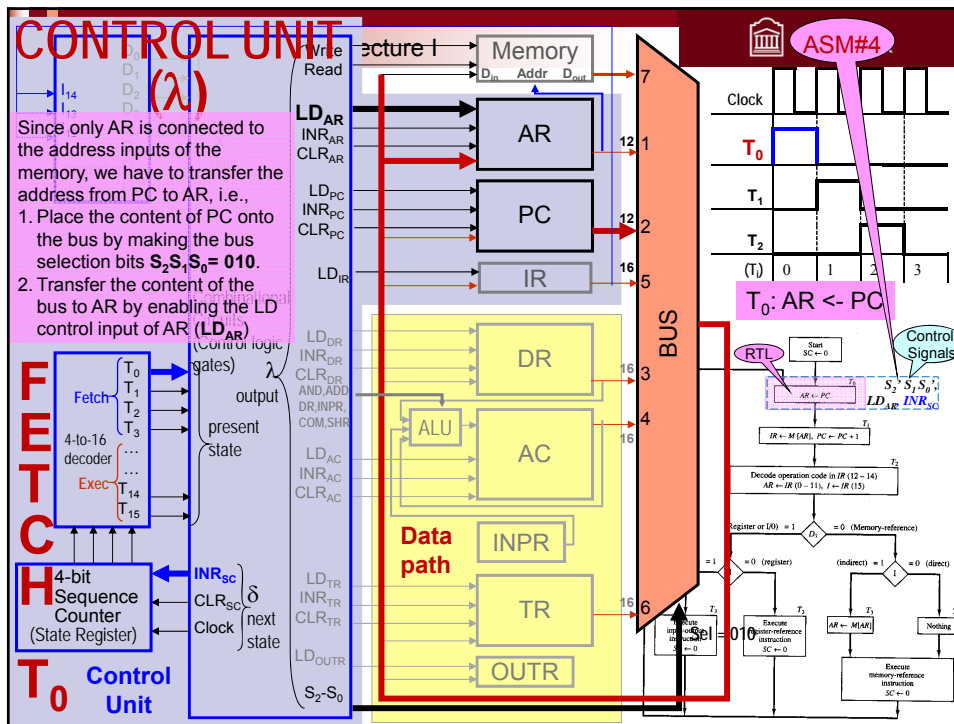

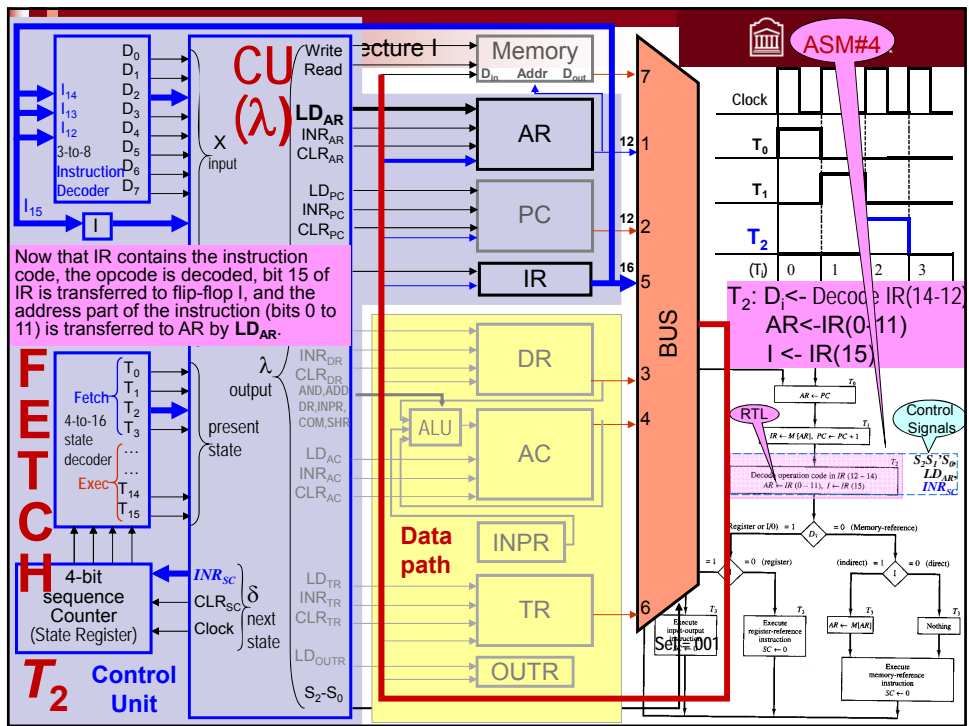

CEG 2136 Computer Architecture I uOttawa

Determine the Type of Instruction

- The instruction fetching and decoding take place at times T_0 to T_2 .
- During T_3 , CU determines the type of instruction just read from the memory.
- The following segment of the ASM flowchart for instruction cycle presents an initial configuration of the instruction cycle.
- $D_7 = 0$ (opcode is 000 to 110) refers to a **memory-reference** instruction.

□ If $I = 1$, then the instruction carries an indirect address and the operand's effective address is read by transferring it to AR.

■ All four operations taking place at time T_3 can be symbolized by:

- $D_7 / I T_3 : AR \leftarrow M[AR]$
- $D_7 / I' T_3 : \text{Nothing}$
- $D_7 / I' T_3 : \text{Execute a **register-reference** instruction}$
- $D_7 / I T_3 : \text{Execute an **input-output** instruction}$

RTL

ASM#2

56

Recall: Basic Computer Instruction List (Binary)

D ₇	Instr.	I ₁₄	I ₁₃	I ₁₂	I ₁₁	I ₁₀	I ₉	I ₈	I ₇	I ₆	I ₅	I ₄	I ₃	I ₂	I ₁	I ₀	I ₁₅ =0 MRI Direct Addr.	I ₁₅ =1 MRI Indirect Addr.
D ₇ =0 mem	D ₀	0	0	0	AR ₁₁	AR ₁₀	AR ₉	AR ₈	AR ₇	AR ₆	AR ₅	AR ₄	AR ₃	AR ₂	AR ₁	AR ₀	AND=\$0adr	AND,=\$8(addr)
	D ₁	0	0	1	AR ₁₁	AR ₁₀	AR ₉	AR ₈	AR ₇	AR ₆	AR ₅	AR ₄	AR ₃	AR ₂	AR ₁	AR ₀	ADD=\$1adr	ADD,=\$9(addr)
	D ₂	0	1	0	AR ₁₁	AR ₁₀	AR ₉	AR ₈	AR ₇	AR ₆	AR ₅	AR ₄	AR ₃	AR ₂	AR ₁	AR ₀	LDA=\$2adr	LDA,=\$A(addr)
	D ₃	0	1	1	AR ₁₁	AR ₁₀	AR ₉	AR ₈	AR ₇	AR ₆	AR ₅	AR ₄	AR ₃	AR ₂	AR ₁	AR ₀	STA=\$3adr	STA,=\$B(addr)
	D ₄	1	0	0	AR ₁₁	AR ₁₀	AR ₉	AR ₈	AR ₇	AR ₆	AR ₅	AR ₄	AR ₃	AR ₂	AR ₁	AR ₀	BUN=\$4adr	BUN,=\$C(addr)
	D ₅	1	0	1	AR ₁₁	AR ₁₀	AR ₉	AR ₈	AR ₇	AR ₆	AR ₅	AR ₄	AR ₃	AR ₂	AR ₁	AR ₀	BSA=\$5adr	BSA,=\$D(addr)
D ₆	1	1	0	AR ₁₁	AR ₁₀	AR ₉	AR ₈	AR ₇	AR ₆	AR ₅	AR ₄	AR ₃	AR ₂	AR ₁	AR ₀	ISZ=\$6adr	ISZ,=\$E(addr)	
RRI																		
IOI																		
D ₇ =1 reg	D ₇	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	CLA=\$7800	INP=\$F800
	D ₇	1	1	1	0	1	0	0	0	0	0	0	0	0	0	0	CLE=\$7400	OUT=\$F400
	D ₇	1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	CMA=\$7200	SKI=\$F200
	D ₇	1	1	1	0	0	0	1	0	0	0	0	0	0	0	0	CME=\$7100	SKO=\$F100
	D ₇	1	1	1	0	0	0	0	1	0	0	0	0	0	0	0	CIR=\$7080	ION=\$F080
	D ₇	1	1	1	0	0	0	0	0	1	0	0	0	0	0	0	CIL=\$7040	IOF=\$F040
	D ₇	1	1	1	0	0	0	0	0	0	1	0	0	0	0	0	INC=\$7020	n/a
	D ₇	1	1	1	0	0	0	0	0	0	0	1	0	0	0	0	SPA=\$7010	n/a
	D ₇	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0	SNA=\$7008	n/a
	D ₇	1	1	1	0	0	0	0	0	0	0	0	0	1	0	0	SZA=\$7004	n/a
	D ₇	1	1	1	0	0	0	0	0	0	0	0	0	0	1	0	SZE=\$7002	n/a
	D ₇	1	1	1	0	0	0	0	0	0	0	0	0	0	0	1	HLT=\$7001	n/a

Binary encoding One-hot (bit-per-state) encoding adr = 12 bit address 57
(adr) = address of the op address

Instruction Cycle (EXEC) Register-Reference Instructions (RRI)


From the Instruction List: $I_{14}I_{13}I_{12} = 111 \Rightarrow D_7 = 1$
 • $I_{15} = 1 = 0$

RTL
ASM#2

$D_7, I_{15} = r$ (common to all register-reference instructions)
 $IR(i) = B_i$ [bit in $IR(0-11)$ that specifies the operation]

- | | | | |
|------------|-------------|---|------------------|
| CLA | rB_{11} : | $AC \leftarrow 0$ | Clear AC |
| CLE | rB_{10} : | $E \leftarrow 0$ | Clear E |
| CMA | rB_9 : | $AC \leftarrow \overline{AC}$ | Complement AC |
| CME | rB_8 : | $E \leftarrow \overline{E}$ | Complement E |
| CIR | rB_7 : | $AC \leftarrow shr AC, AC(15) \leftarrow E, E \leftarrow AC(0)$ | Circulate right |
| CIL | rB_6 : | $AC \leftarrow shl AC, AC(0) \leftarrow E, E \leftarrow AC(15)$ | Circulate left |
| INC | rB_5 : | $AC \leftarrow AC + 1$ | Increment AC |
| SPA | rB_4 : | If $(AC(15) = 0)$ then $(PC \leftarrow PC + 1)$ | Skip if positive |
| SNA | rB_3 : | If $(AC(15) = 1)$ then $(PC \leftarrow PC + 1)$ | Skip if negative |
| SZA | rB_2 : | If $(AC = 0)$ then $PC \leftarrow PC + 1$ | Skip if AC zero |
| SZE | rB_1 : | If $(E = 0)$ then $(PC \leftarrow PC + 1)$ | Skip if E zero |
| HLT | rB_0 : | $S \leftarrow 0$ (S is a start-stop flip-flop) | Halt computer |

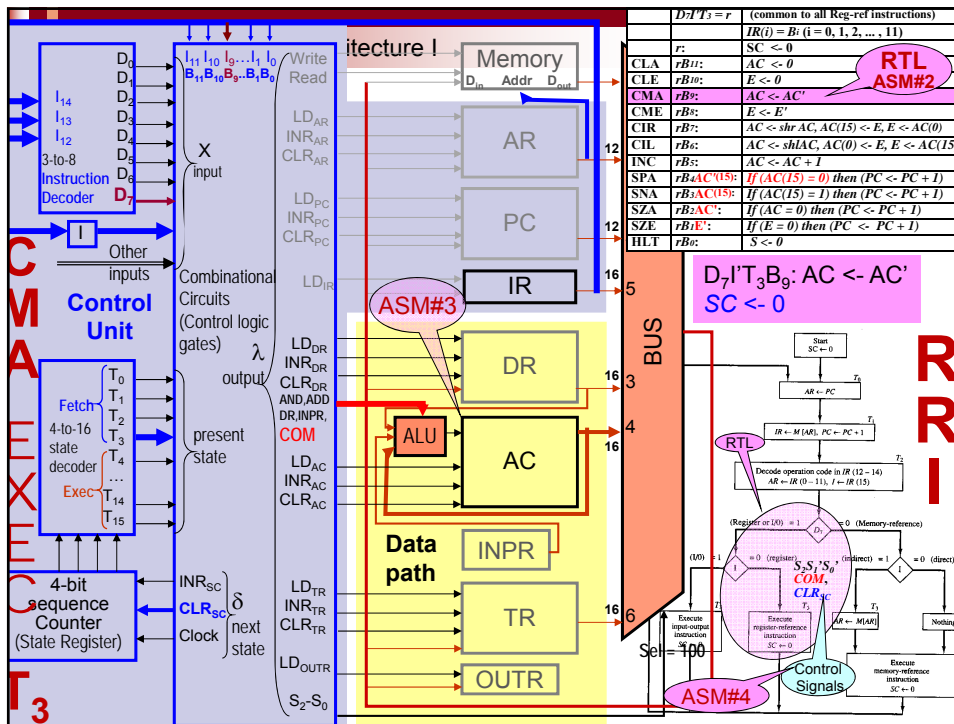Every Register-Reference Instruction is executed during T₃



CEG 2136 Computer Architecture I uOttawa

Instruction Cycle (EXEC)

Memory-Reference Instructions (MRI)

From the Instruction List:



$I_{14}I_{13}I_{12} = [000 - 110] \Rightarrow D_i = 1, i = \{0 \dots 6\}$

- $I_{15} = I = 0 \Rightarrow$ direct addressing
- $I_{15} = I = 1 \Rightarrow$ indirect addressing

Symbol	Operation decoder	Symbolic description
AND	D ₀	AC ← AC ∧ M[AR]
ADD	D ₁	AC ← AC + M[AR], E ← C _{out}
LDA	D ₂	AC ← M[AR]
STA	D ₃	M[AR] ← AC
BUN	D ₄	PC ← AR
BSA	D ₅	M[AR] ← PC, PC ← AR + 1
ISZ	D ₆	M[AR] ← M[AR] + 1, If M[AR] + 1 = 0 then PC ← PC + 1

RTL ASM#2

60

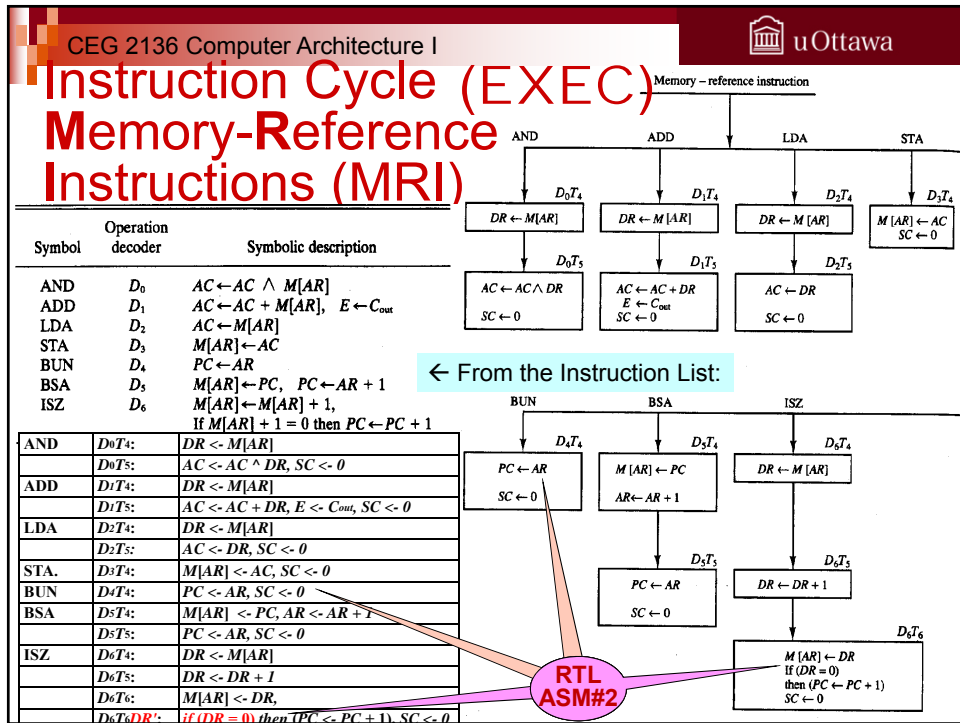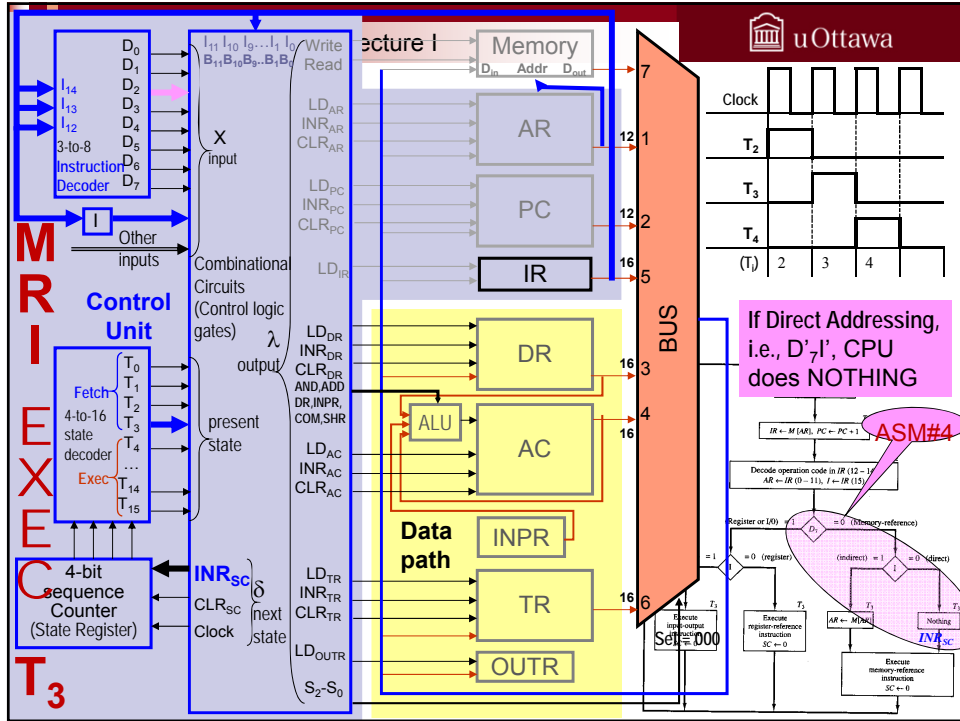

Note on RTL


- The RTL statements should be read as having the present values on the right side of "=", while the left side refers to the next state of that register; the transfer (register load) takes place on the rising edge of the clock.

- For example:


$$D_1T_5: DR \leftarrow AC, AC \leftarrow AC + DR$$

reads:

 
$$D_1T_5: DR(n+1) \leftarrow AC(n) \\ AC(n+1) \leftarrow AC(n) + DR(n)$$



Even the second RTL makes sense since $AC(n) + DR(n)$ is the ALU's output which is to be loaded into AC on the rising edge of the clock. After loading the newer value into AC, there will be a delay until the ALU output will change, since ALU needs some time to "figure out" what is the newer result. As such, by the time ALU output will change, the rising edge will be gone and nothing will be allowed into AC until the next rising edge!

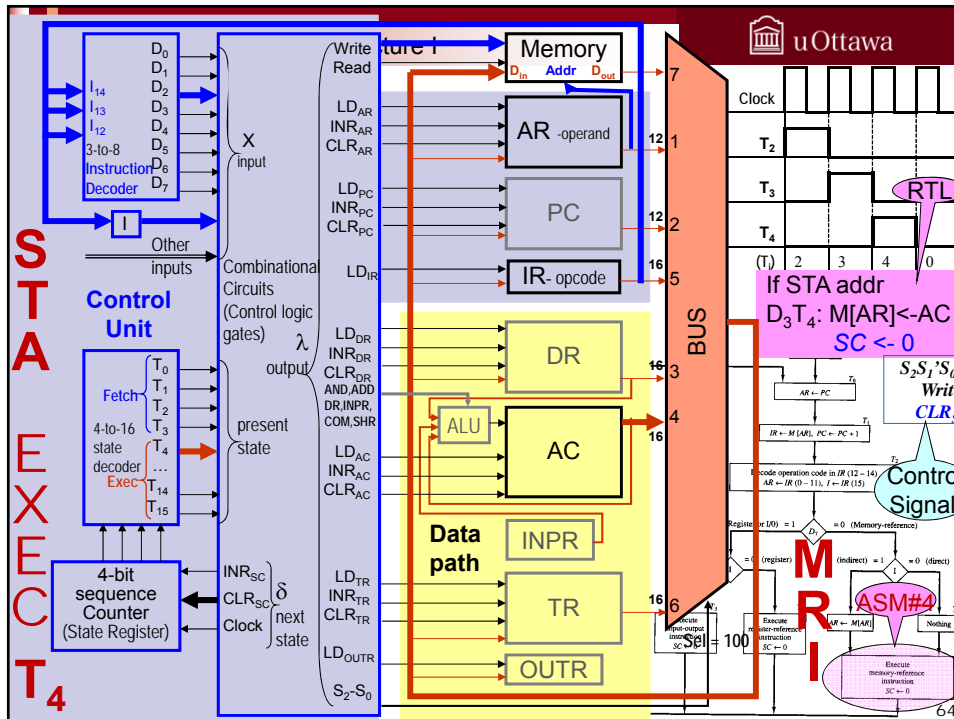


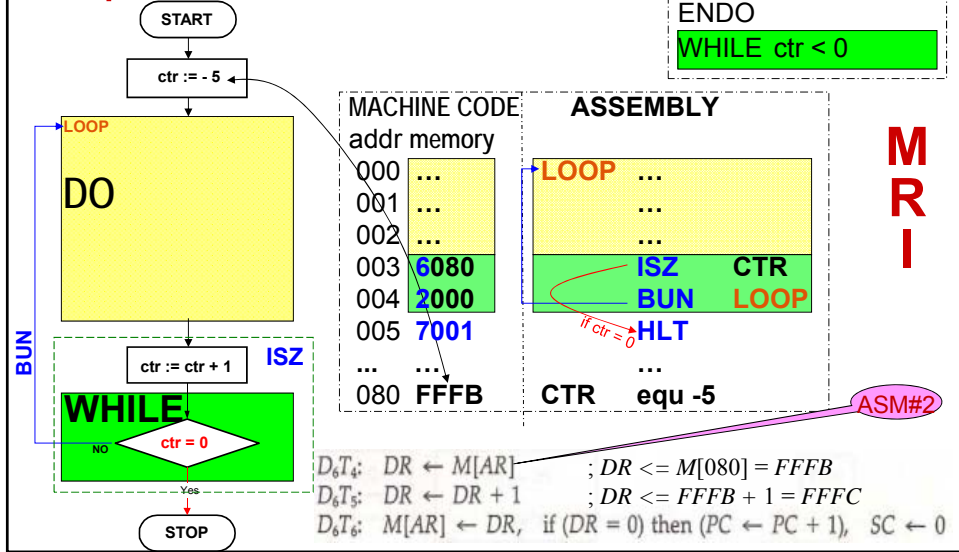ISZ – Increment & Skip if Zero implements DO-WHILE




How ...

 1. ... DOES A SUBROUTINE WORK?
2. ... TO DEFINE IT?
3. ... TO USE IT?




HOW DOES IT WORK?

 - A subroutine is a program module that is independent of the main program
- To use it, the main program transfers control to the subroutine
- The subroutine performs its function and then returns control to the main program




MAIN CALLS SUBROUTINE

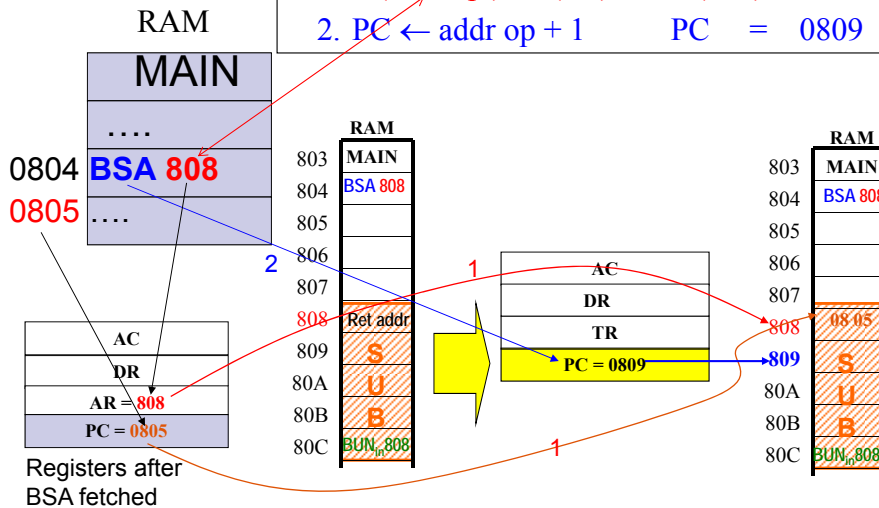1. $m(addr\ op) \leftarrow (PC)$ $m(808) = 0805$
2. $PC \leftarrow addr\ op + 1$ $PC = 0809$



SUBROUTINE RETURNS TO MAIN

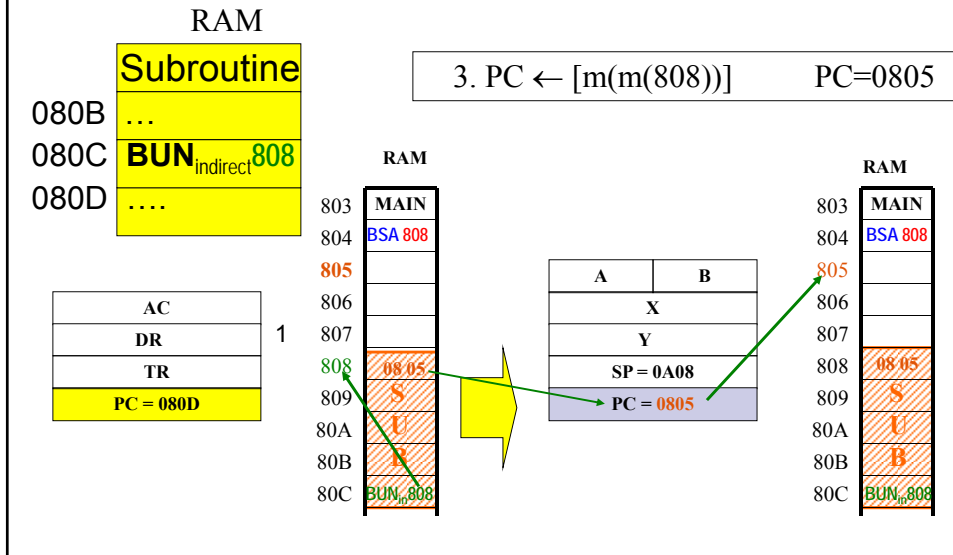

BSA: Branch and Save Return Address

The BSA instruction


1. **stores the return address** (i.e., the address of the instruction to be run after the subroutine is executed, 21 in our example; this address is already prepared in PC) into the memory location specified by its effective address (135).
2. **branches to the first instruction of the subroutine** which is stored in the memory at the next address (136) after the stored return address.
3. The subroutine has to end with an indirect BUN to the return addr.

20 BSA 135
 21 next instruction
 22

 135 stored ret. addr (21)
 136 Subroutine 1st instr
 137


 159 Subroutine last instr
 160 BUN_{indirect} 135

 $D_5 T_4 : M[AR] \leftarrow PC, AR \leftarrow AR + 1$
 $D_5 T_5 : PC \leftarrow AR, SC \leftarrow 0$




CPU & I/O Interface

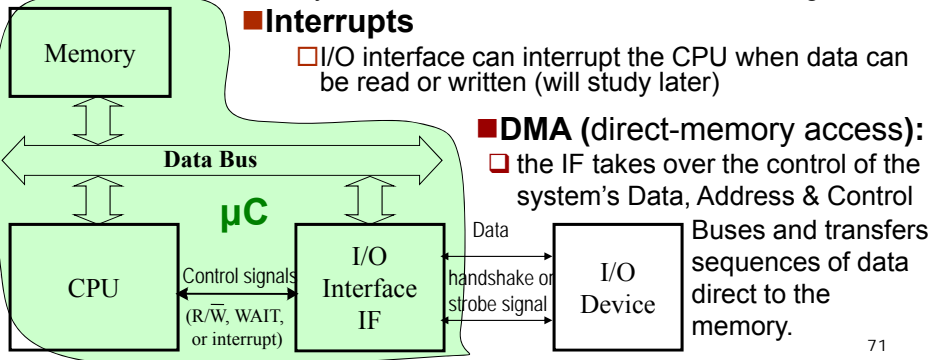- Hardware provides an **interface** to the I/O device. Contains:
 - data register (for data transfer, here: INPR and OUTR)
 - status register (flags=peripheral ready, here: FGI & FGO)
 - control register (here: R, IEN)
- **SW Polling (Programmed Control)**
 - CPU monitors the status register
 - When data is ready, CPU reads or writes from/to the data register




Software Polling

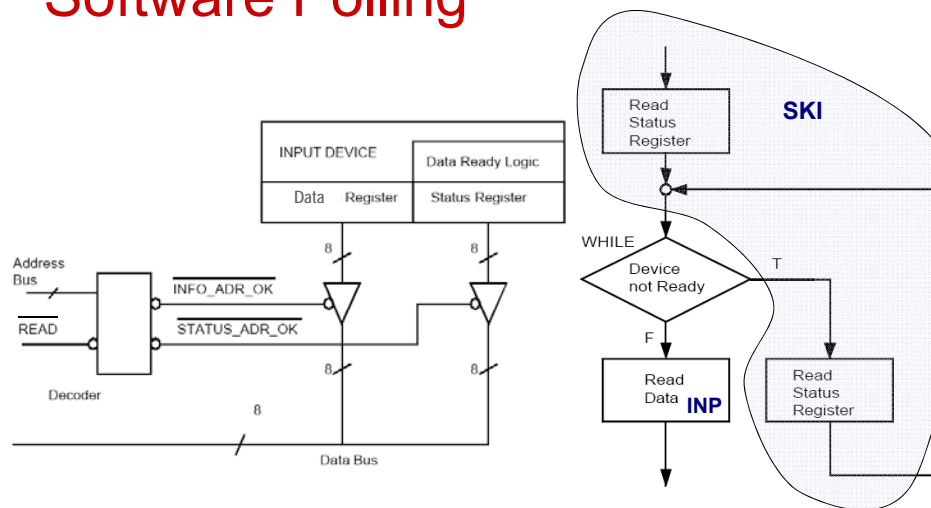


Basic Computer I/O Instructions (IOI)

$D_7IT_3 = p$ (common to all input-output instructions)
 $IR(i) = B_i$ [bit in $IR(6-11)$ that specifies the instruction]

	p :	$SC \leftarrow 0$	Clear SC
INP	pB_{11} :	$AC(0-7) \leftarrow INPR, FGI \leftarrow 0$	Input character
OUT	pB_{10} :	$OUTR \leftarrow AC(0-7), FGO \leftarrow 0$	Output character
SKI	pB_9 :	If $(FGI = 1)$ then $(PC \leftarrow PC + 1)$	Skip on input flag
SKO	pB_8 :	If $(FGO = 1)$ then $(PC \leftarrow PC + 1)$	Skip on output flag
ION	pB_7 :	$IEN \leftarrow 1$	Interrupt enable on
IOF	pB_6 :	$IEN \leftarrow 0$	Interrupt enable off

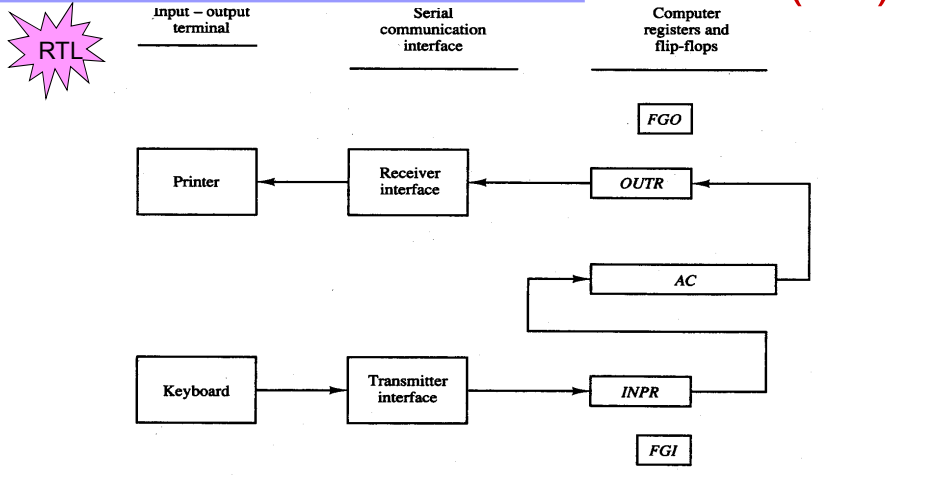


Interrupt Fundamental Concepts

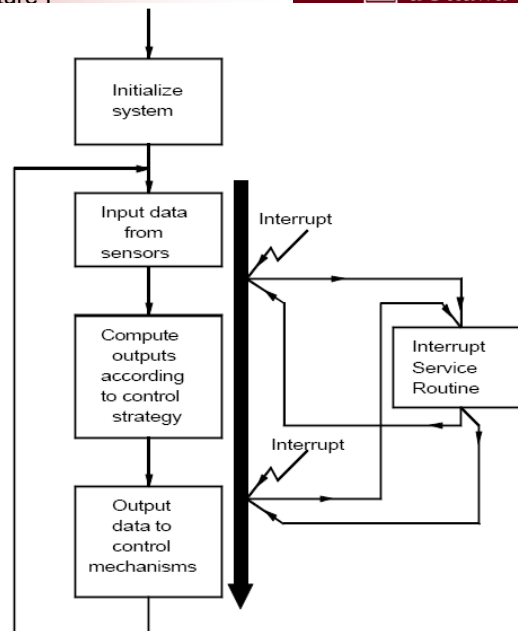

Internal Asynchronous CPU Timing

 - Interrupts can occur at any time during an instruction cycle



75

Internal CPU Interrupt Hardware

- Use a flip-flop (**R**) to catch IRQ
 - Multiple device interrupt lines can be wire-ORed together
 - CPU must wait until CPU can interrupt the process
- Can enable/disable interrupt using enable-disable flip-flop (**IEN**)
 - When interrupt is acknowledged, interrupts are disabled
- The source of interrupt is signaled by **FGI** (input flag) or by **FGO** (output flag)
 - > the Interrupt Service Routine (ISR) has to check which I/O device generated the IRQ
- At the end of ISR, **BUN_{ind}0** is executed to return to the interrupted program

76


Interrupt System Specification

- Allow for asynchronous events to occur and be recognized.
- Wait for the current instruction to finish before servicing an interrupt.
- Service interrupt with a sub-routine and return to interrupted code.
- Enabling and disabling interrupts
- Multiple (here 2) sources of interrupts
 - Simultaneous interrupts.

77



Interrupt Service Cycle (INT)


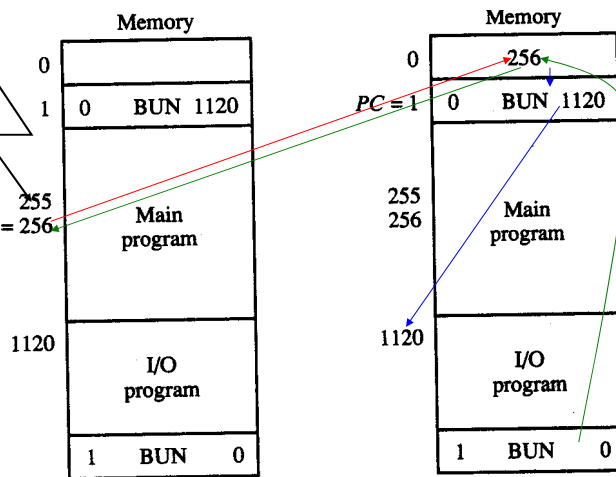
1. Save the PC (address of the next instruction) at the address 0
2. BUN directly to the ISR address 1120 corresponding to the interrupt
3. Disable interrupts (IEN<-0, R<-0)
4. Execute the Interrupt Service Routine (ISR)
5. Resume the interrupted program with BUN indirectly to address 0





(a) Before interrupt

(b) After interrupt cycle

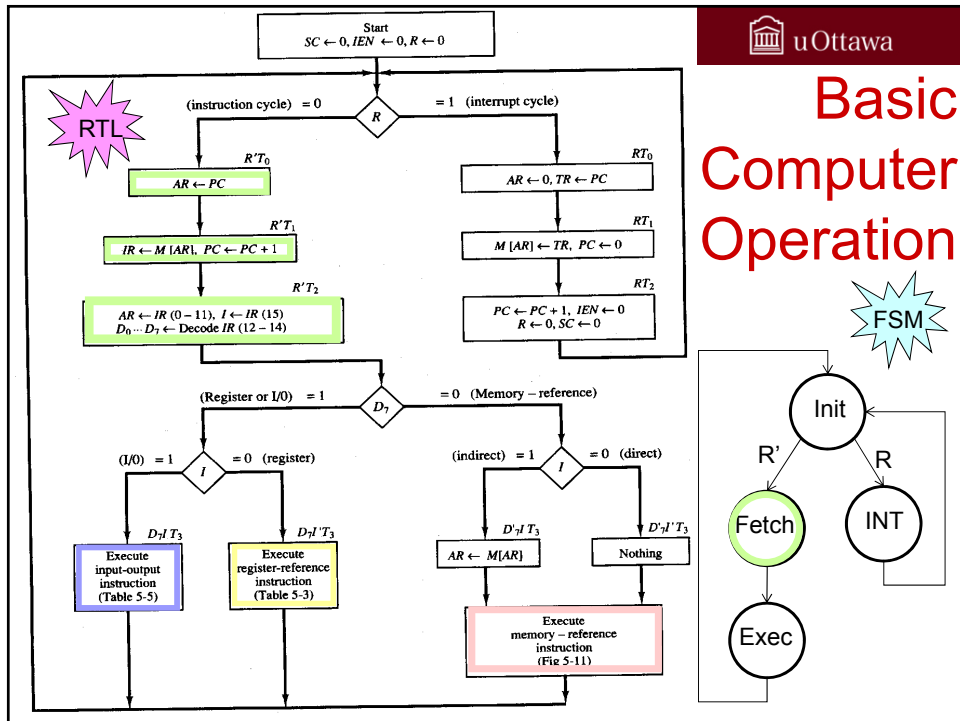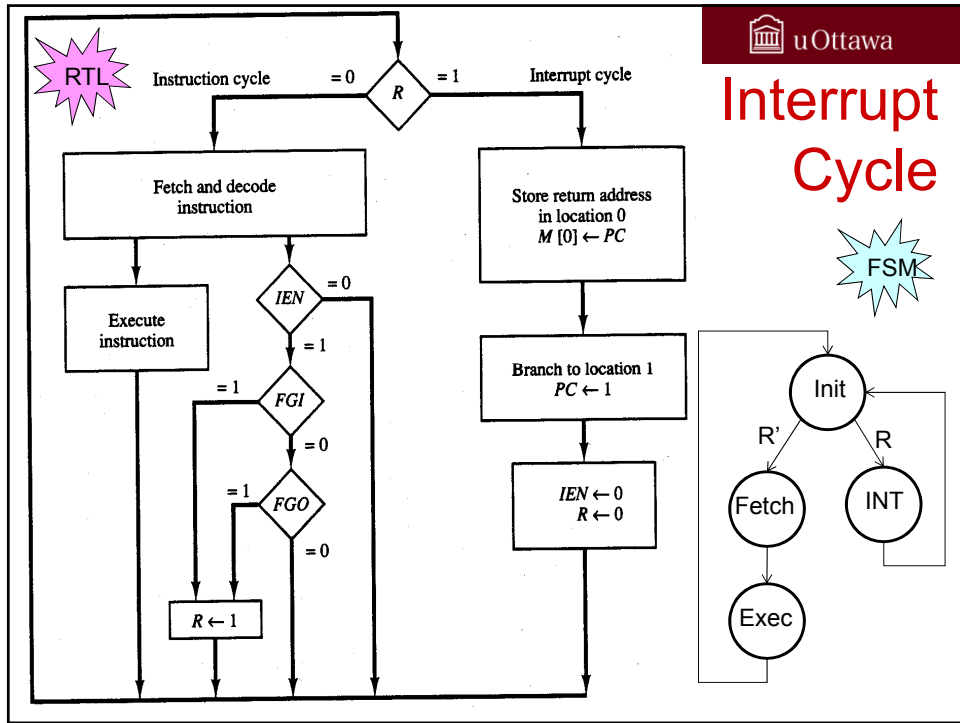

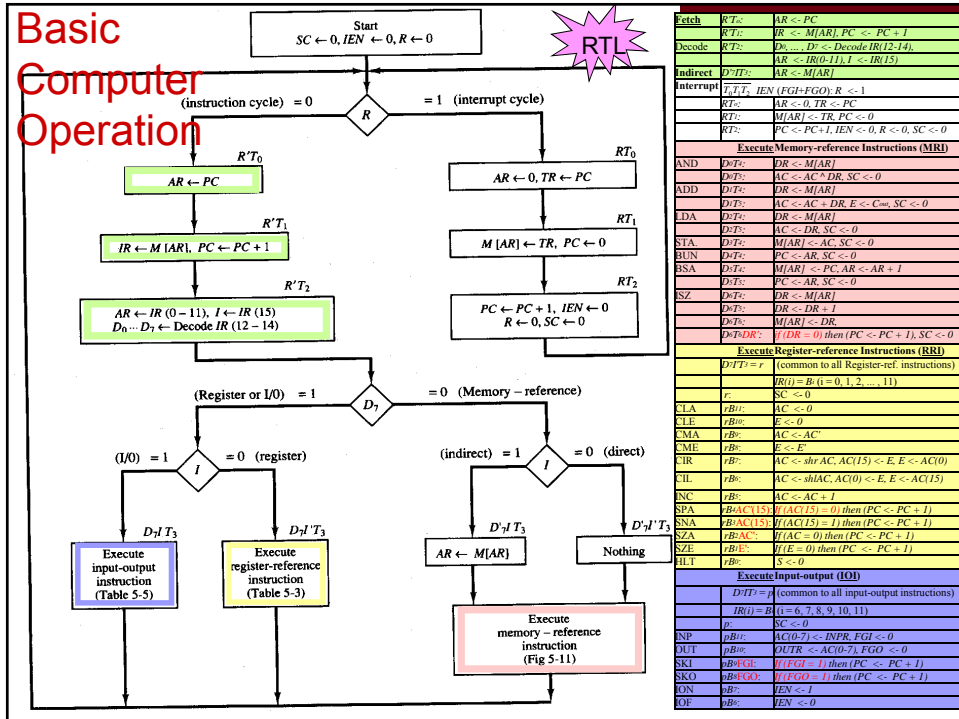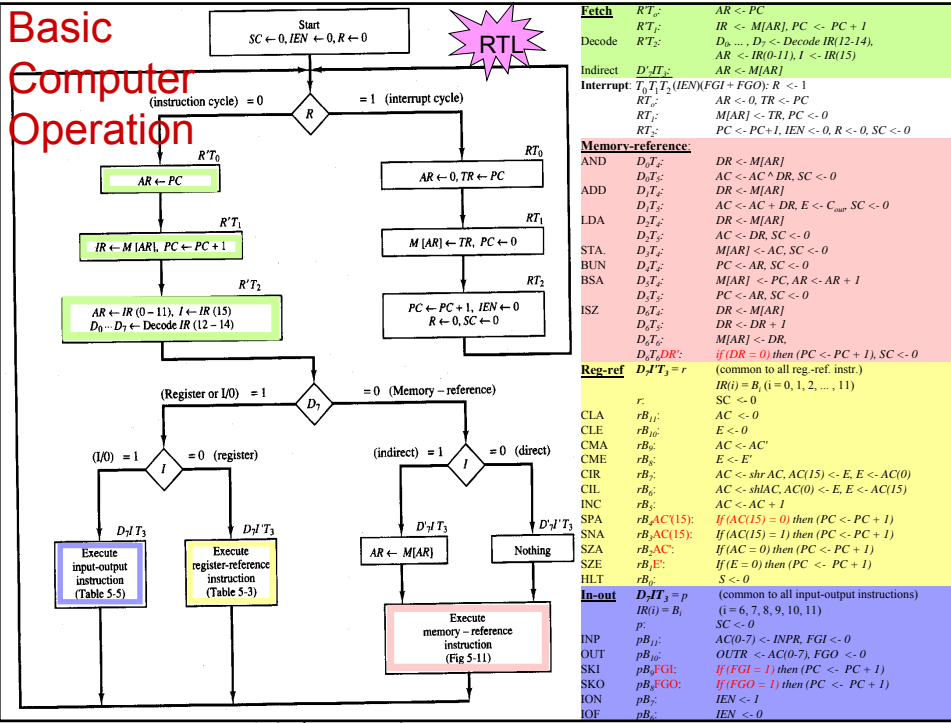

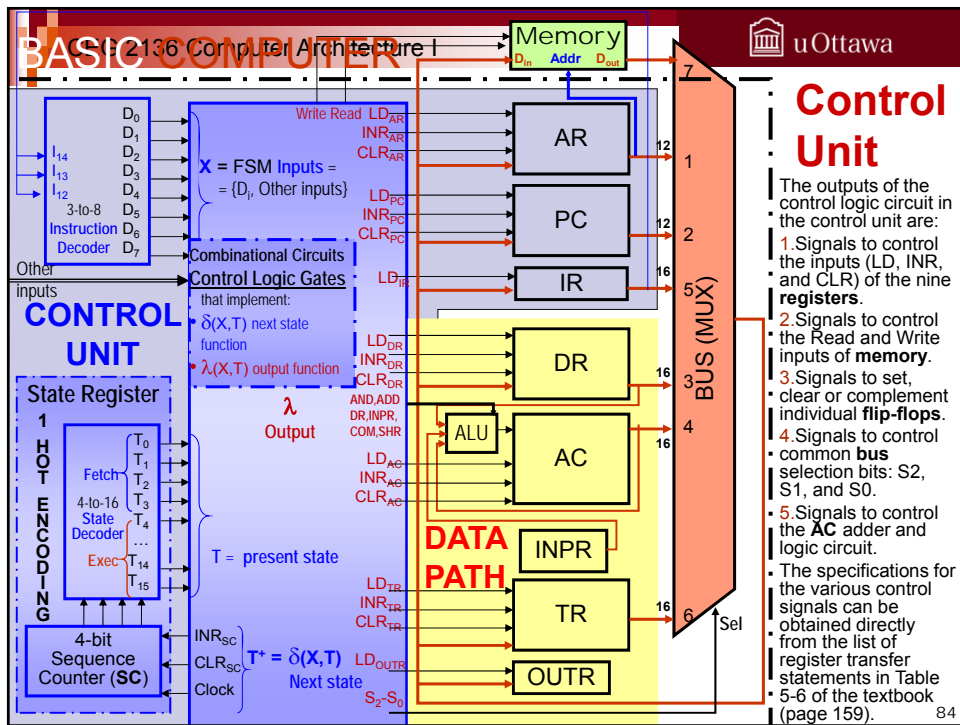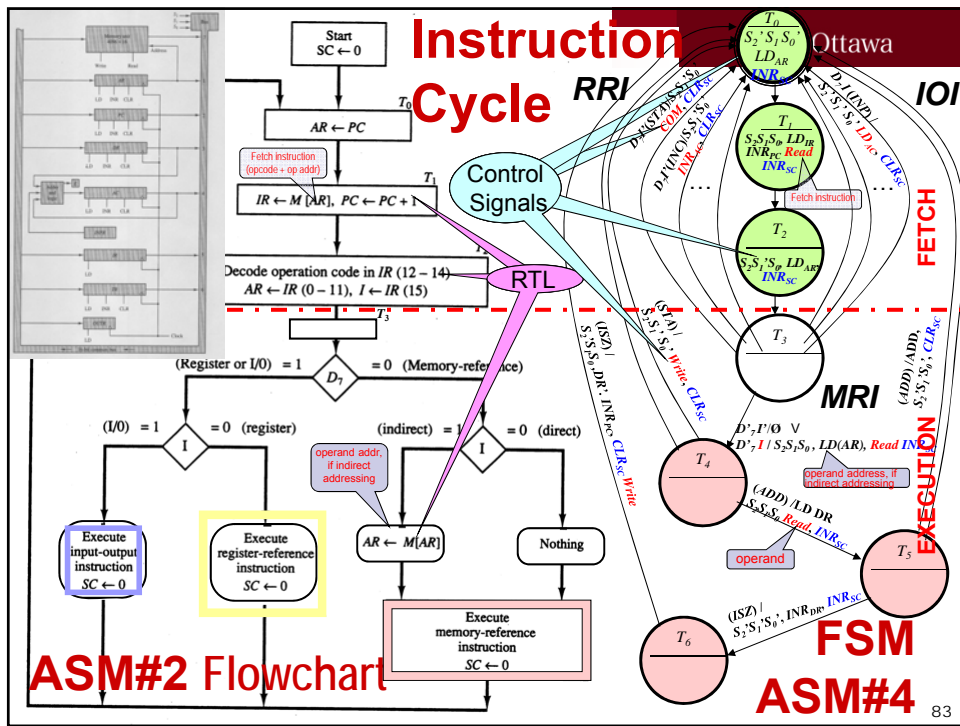

Control Unit Design

Inputs: $X = \{D_i, \text{Other inputs}\}$


IR => D_i Instruction Decoder -
AND, ADD, LDA, STA, BUN,
BSA, ISZ, {RRI, IOI}

Outputs: $Z = \{LD_{AR}, INR_{AR},$
 $CLR_{AR}, LD_{PC}, INR_{PC},$
 $CLR_{PC}, \text{Write, Read,}$
 $LD_{IR}, LD_{DR}, INR_{DR},$
 $CLR_{DR}, LD_{TR}, INR_{TR},$
 $CLR_{TR}, LD_{AC}, INR_{AC},$
 $\dots\}$

States : $\{T_0, T_1, T_2, T_3, \dots, T_{15}\}$

$T^{n+1} = \delta(X^n, T^n)$ next state function

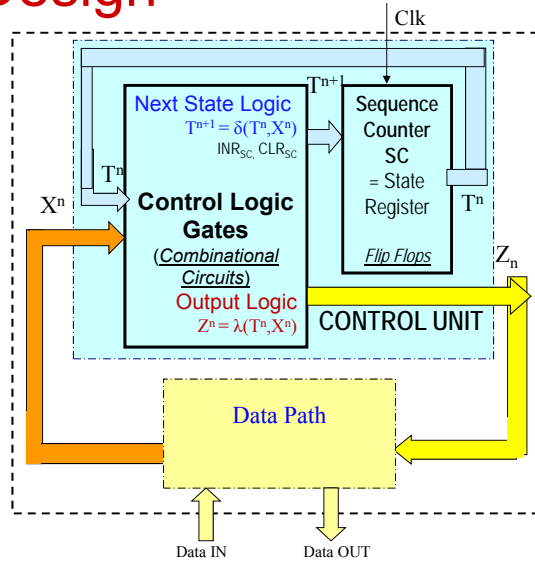$Z^n = \lambda(X^n, T^n)$ output function




RTL ASM#2

			S_2, S_1, S_0	
Fetch	$R T_0:$	$AR \leftarrow PC$	010	LD_AR
	$R T_1:$	$IR \leftarrow M[AR], PC \leftarrow PC + 1$	111	Read, LD_IR, INC_PC
Decode	$R T_2:$	$D_0 \dots D_7 \leftarrow \text{Decode IR}(12-14),$ $AR \leftarrow IR(0-11), I \leftarrow IR(15)$	101	LD_AR, LD_I & IR(15)
	Indirect	$D_7 T_3:$	111	Read, LD_AR
Interrupt:				
$T_0, T_1, T_2, IEN(FGI + FGO):$	$R \leftarrow 1$			S_R
$R T_0:$	$AR \leftarrow 0, TR \leftarrow PC$	010		CL_AR, LD_TR,
$R T_1:$	$M[AR] \leftarrow TR, PC \leftarrow 0$	110		Write, CL_PC
$R T_2:$	$PC \leftarrow PC + 1, IEN \leftarrow 0, R \leftarrow 0, SC \leftarrow 0$			INC_PC, R_SC, R_R, R_IEN,
Memory-reference:				
AND	$D_0 T_0:$	$DR \leftarrow M[AR]$		
	$D_0 T_3:$	$AC \leftarrow AC \wedge DR, SC \leftarrow 0$		
ADD	$D_0 T_0:$	$DR \leftarrow M[AR]$		
	$D_0 T_3:$	$AC \leftarrow AC + DR, E \leftarrow C_{out}, SC \leftarrow 0$		
LDA	$D_0 T_0:$	$DR \leftarrow M[AR]$		
	$D_0 T_3:$	$AC \leftarrow DR, SC \leftarrow 0$		
STA	$D_0 T_0:$	$M[AR] \leftarrow AC, SC \leftarrow 0$		
BUN	$D_0 T_0:$	$PC \leftarrow AR, SC \leftarrow 0$		
BSA	$D_0 T_0:$	$M[AR] \leftarrow PC, AR \leftarrow AR + 1$		
	$D_0 T_3:$	$PC \leftarrow AR, SC \leftarrow 0$		
ISZ	$D_0 T_0:$	$DR \leftarrow M[AR]$		
	$D_0 T_3:$	$DR \leftarrow DR + 1$		
	$D_0 T_3:$	$M[AR] \leftarrow DR$		
	$D_0 T_3, DR:$	$(DR = 0) \text{ then } (PC \leftarrow PC + 1), SC \leftarrow 0$		

$LD_AR = R T_0 + R T_2 + D_7 T_3$; $CLR_AR = R T_0$; $INR_AR = D_5 T_4$

ASM#5

ASM#3

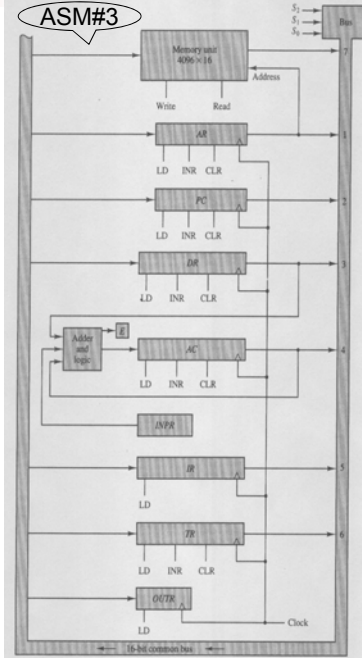

CEG 2136 Computer Archi Control Signals ASM#4 uOttawa

RTL ASM#2

			S_2, S_1, S_0	LD_{AR}	LD_{DR}	$INCR_{PC}$	LD_{PC}	CLR_{PC}	LD_{DR}
Fetch	RT_1 :	$AR \leftarrow PC$							
	RT_2 :	$IR \leftarrow M[AR], PC \leftarrow PC + 1$							
Decode	RT_2 :	$D_0, \dots, D_7 \leftarrow \text{Decode IR}(12-14)$							
		$AR \leftarrow IR(0-11), I \leftarrow IR(15)$							
Indirect	D_7, T_3 :	$AR \leftarrow M[AR]$							
Interrupt:									
	$T_0, T_1, IEN(FGI + FGO)$:	$R \leftarrow 1$							
	RT_0 :	$AR \leftarrow 0, TR \leftarrow PC$							
	RT_1 :	$M[AR] \leftarrow TR, PC \leftarrow 0$							
	RT_2 :	$PC \leftarrow PC + 1, IEN \leftarrow 0, R \leftarrow 0, SC \leftarrow 0$							
Memory-reference:									
AND	D_0, T_4 :	$DR \leftarrow M[AR]$							
	D_0, T_5 :	$AC \leftarrow AC \wedge DR, SC \leftarrow 0$							
ADD	D_0, T_4 :	$DR \leftarrow M[AR]$							
	D_0, T_5 :	$AC \leftarrow AC + DR, E \leftarrow C_{out}, SC \leftarrow 0$							
LDA	D_0, T_4 :	$DR \leftarrow M[AR]$							
	D_0, T_5 :	$AC \leftarrow DR, SC \leftarrow 0$							
STA	D_0, T_4 :	$M[AR] \leftarrow AC, SC \leftarrow 0$							
BUN	D_0, T_4 :	$PC \leftarrow AR, SC \leftarrow 0$							
BSA	D_0, T_4 :	$M[AR] \leftarrow PC, AR \leftarrow AR + 1$							
	D_0, T_5 :	$PC \leftarrow AR, SC \leftarrow 0$							
ISZ	D_0, T_4 :	$DR \leftarrow M[AR]$							
	D_0, T_5 :	$DR \leftarrow DR + 1$							
	D_0, T_6 :	$M[AR] \leftarrow DR$							
	D_0, T_7, DR :	if $(DR = 0)$ then $(PC \leftarrow PC + 1), SC \leftarrow 0$							

ASM#3

CEG 2136 Computer Archi Control Signals ASM#4 uOttawa

RTL ASM#2

		To	From S_2, S_1, S_0	LD_{AR}	LD_{DR}	$INCR_{PC}$	LD_{PC}	CLR_{PC}	LD_{DR}	INR_{DR}	CLR_{DR}	LD_{AC}	INR_{AC}	CLR_{AC}
Fetch	RT_1 :	$AR \leftarrow PC$	010	1										
	RT_2 :	$IR \leftarrow M[AR], PC \leftarrow PC + 1$	111	Read		INR_{PC}			1	1				
Decode	RT_2 :	$D_0, \dots, D_7 \leftarrow \text{Decode IR}(12-14)$												
		$AR \leftarrow IR(0-11), I \leftarrow IR(15)$	101	LD_I	1									
Indirect	D_7, T_3 :	$AR \leftarrow M[AR]$	111	Read					1					
Interrupt:														
	$T_0, T_1, IEN(FGI + FGO)$:	$R \leftarrow 1$	S_R											
	RT_0 :	$AR \leftarrow 0, TR \leftarrow PC$	010	CLR_{AR}				1						
	RT_1 :	$M[AR] \leftarrow TR, PC \leftarrow 0$	110	Write										1
	RT_2 :	$PC \leftarrow PC + 1, IEN \leftarrow 0, R \leftarrow 0, SC \leftarrow 0$	R_{IN}	R_R		CLR_{PC}			1					
Memory-reference:														
AND	D_0, T_4 :	$DR \leftarrow M[AR]$	111	Read							1	1		
	D_0, T_5 :	$AC \leftarrow AC \wedge DR, SC \leftarrow 0$	AND	CLR_{SC}										1
ADD	D_0, T_4 :	$DR \leftarrow M[AR]$	111	Read							1	1		
	D_0, T_5 :	$AC \leftarrow AC + DR, E \leftarrow C_{out}, SC \leftarrow 0$	ADD	CLR_{SC}										1
LDA	D_0, T_4 :	$DR \leftarrow M[AR]$	111	Read							1	1		
	D_0, T_5 :	$AC \leftarrow DR, SC \leftarrow 0$	DR	CLR_{SC}										1
STA	D_0, T_4 :	$M[AR] \leftarrow AC, SC \leftarrow 0$	100	CLR_{SC}										
BUN	D_0, T_4 :	$PC \leftarrow AR, SC \leftarrow 0$	001	CLR_{SC}										
BSA	D_0, T_4 :	$M[AR] \leftarrow PC, AR \leftarrow AR + 1$	010	INR_{AR}					1					
	D_0, T_5 :	$PC \leftarrow AR, SC \leftarrow 0$	001	CLR_{SC}										
ISZ	D_0, T_4 :	$DR \leftarrow M[AR]$	111	Read							1	1		
	D_0, T_5 :	$DR \leftarrow DR + 1$		INR_{DR}										
	D_0, T_6 :	$M[AR] \leftarrow DR$		Write										
	D_0, T_7, DR :	if $(DR = 0)$ then $(PC \leftarrow PC + 1), SC \leftarrow 0$		INR_{PC}										1


AR Control Logic

RTL ASM#2

- Scan Table 5-6 & find all the RTL statements in which AR is modified.
- $R'T_0 : AR \leftarrow PC$
- $R'T_2 : AR \leftarrow IR(0-11)$
- $D_7IT_3 : AR \leftarrow M[AR]$
- $RT_0 : AR \leftarrow 0$
- $D_5T_4 : AR \leftarrow AR + 1$
- The first three statements are performed by enabling the LD bit of AR (i.e., LD(AR)).
- The 4-th is done by activating the CLR
- The 5-fth statement is performed by enabling the INR bit of AR (i.e., INR(AR)).

ASM#5

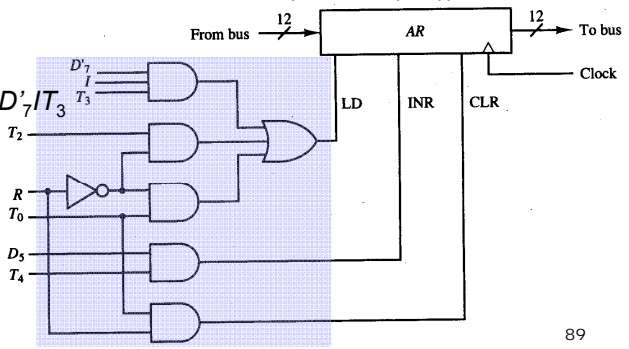
$LD(AR) = R'T_0 \vee R'T_2 \vee D_7IT_3$
 $CLR(AR) = RT_0$
 $INR(AR) = D_5T_4$



Control Signals ASM#4

		Register-reference:	R_{REG}	S_{SEN}
	$D_7IT_3 = r$	(common to all RRI)		
	$IR(i) = B_i$	($i = 0, 1, 2, \dots, 11$)		
	r :	$SC \leftarrow 0$		
CLA	rB_{ij} :	$AC \leftarrow 0$		
CLE	rB_{ij} :	$E \leftarrow 0$		
CMA	rB_{ij} :	$AC \leftarrow AC'$		
CME	rB_{ij} :	$E \leftarrow E'$		
CIR	rB_{ij} :	$AC \leftarrow shr AC, AC(15) \leftarrow E, E \leftarrow AC(0)$		
CIL	rB_{ij} :	$AC \leftarrow shl AC, AC(0) \leftarrow E, E \leftarrow AC(15)$		
INC	rB_{ij} :	$AC \leftarrow AC + 1$		
SPA	$rB_{AC}(15)$:	If $(AC(15) = 0)$ then $(PC \leftarrow PC + 1)$		
SNA	$rB_{AC}(15)$:	If $(AC(15) = 1)$ then $(PC \leftarrow PC + 1)$		
SZA	rB_{AC} :	If $(AC = 0)$ then $(PC \leftarrow PC + 1)$		
SZE	rB_E :	If $(E = 0)$ then $(PC \leftarrow PC + 1)$		
HLT	rB_{ij} :	$S \leftarrow 0$		
Input-output:				
	$D_7IT_3 = p$	(common to all IO instructions)		
	$IR(i) = B_i$	($i = 6, 7, 8, 9, 10, 11$)		
	p :	$SC \leftarrow 0$		
INP	pB_{ij} :	$AC(0-7) \leftarrow INPR, FGI \leftarrow 0$		
OUT	pB_{ij} :	$OUTR \leftarrow AC(0-7), FGO \leftarrow 0$		
SKI	pB_{FGI} :	If $(FGI = 1)$ then $(PC \leftarrow PC + 1)$		
SKO	pB_{FGO} :	If $(FGO = 1)$ then $(PC \leftarrow PC + 1)$		
ION	pB_{ij} :	$IEN \leftarrow 1$	1	1
IOF	pB_{ij} :	$IEN \leftarrow 0$	1	1

RTL ASM#2

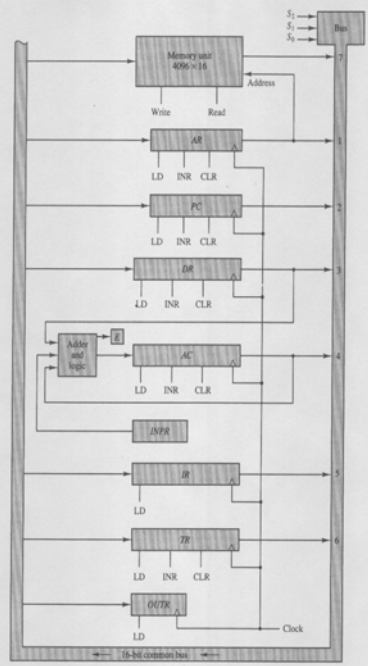

IEN FF Control Logic

- The control logic circuit for the individual flip-flops of the control unit can be determined in a similar manner.
- For example, Table 5-6 (of the textbook) shows that flip-flop IEN is loaded in the following statements:

RTL
ASM#2

$pB_7 : IEN \leftarrow 1 \quad S_{IEN} = 1$
 $pB_6 : IEN \leftarrow 0 \quad R_{IEN1} = 1$
 $RT_2 : IEN \leftarrow 0 \quad R_{IEN2} = 1$

Control Signals ASM#4


when $p = D_7IT_3$, $B_7 = IR(7)$, and $B_6 = IR(6)$

ASM#5

Should a JK flip-flop being used:


$$J_{IEN} = \Sigma(S_{IEN}) = pB_7 = D_7IT_3B_7$$
 
$$K_{IEN} = \Sigma(R_{IEN}) = pB_6 + RT_2$$



Bus Control

	x_1	x_2	x_3	x_4	x_5	x_6	x_7	S_2	S_1	S_0
AR	1	0	0	0	0	0	0	0	0	1
PC	0	1	0	0	0	0	0	0	1	0
DR	0	0	1	0	0	0	0	0	1	1
AC	0	0	0	1	0	0	0	1	0	0
IR	0	0	0	0	1	0	0	1	0	1
TR	0	0	0	0	0	1	0	1	1	0
M	0	0	0	0	0	0	1	1	1	1

 

Source Register (from Table 5-6):

AR: $x_{AR} = x_1 = D_4T_4 \vee D_5T_5$

PC: $x_{PC} = x_2 =$

DR: $x_{DR} = x_3 =$

AC: $x_{AC} = x_4 =$

IR: $x_{IR} = x_5 =$

TR: $x_{TR} = x_6 =$


M : $x_M = x_7 = R'T_1 \vee D_7'I_3 \vee (D_0 \vee D_1 \vee D_2 \vee D_6)T_4$

$$S_2 = x_1 + x_3 + x_5 + x_7$$

$$S_1 = x_2 + x_3 + x_6 + x_7$$


$$S_0 = x_4 + x_5 + x_6 + x_7$$

ALU Block Diagram

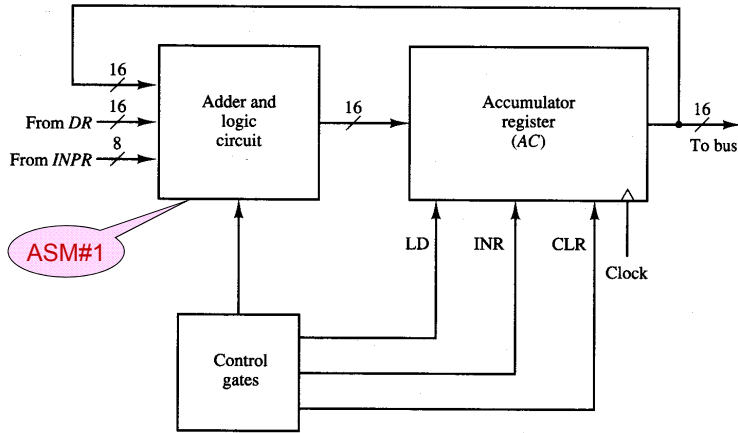

ASM#1

AC+ALU

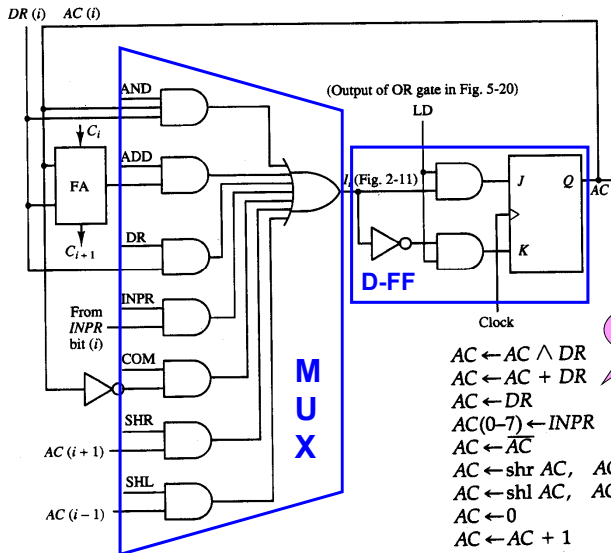


ASM#3

RTL
ASM#2

- $AC \leftarrow AC \wedge DR$
 - $AC \leftarrow AC + DR$
 - $AC \leftarrow DR$
 - $AC(0-7) \leftarrow INPR$
 - $AC \leftarrow \overline{AC}$
 - $AC \leftarrow shr\ AC, AC(15) \leftarrow E$
 - $AC \leftarrow shl\ AC, AC(0) \leftarrow E$
 - $AC \leftarrow 0$
 - $AC \leftarrow AC + 1$
- AND with DR
Add with DR
Transfer from DR
Transfer from INPR
Complement
Shift right
Shift left
Clear
Increment

AC Control Logic (ASM#5)

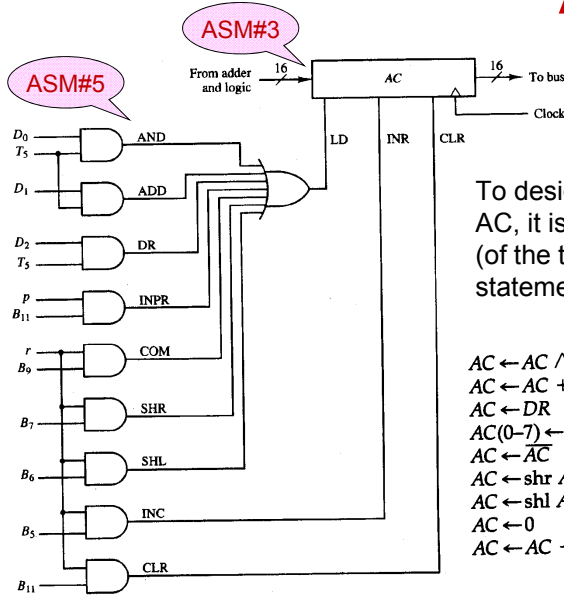


To design the logic associated with AC, it is necessary to scan Table 5-6 (of the textbook) and extract all the statements in which AC is loaded:

- | | |
|---|---|
| <p>RTL
ASM#2</p> <ul style="list-style-type: none"> $AC \leftarrow AC \wedge DR$ $AC \leftarrow AC + DR$ $AC \leftarrow DR$ $AC(0-7) \leftarrow INPR$ $AC \leftarrow \overline{AC}$ $AC \leftarrow shr\ AC, AC(15) \leftarrow E$ $AC \leftarrow shl\ AC, AC(0) \leftarrow E$ $AC \leftarrow 0$ $AC \leftarrow AC + 1$ | <ul style="list-style-type: none"> AND with DR Add with DR Transfer from DR Transfer from INPR Complement Shift right Shift left Clear Increment |
|---|---|

Data Exchange with ISRs

- Use global data
- May need to disable interrupts for critical regions of code using this data

Input-Output and Interrupt

 

ASM Example

