

$$1) \overline{AC + B(A+\bar{C})} \equiv \sum \text{minterms } F = f(a,b,c) = f(\bar{a}, \bar{b}, \bar{c})$$

$$= \overline{AC} \cdot \overline{B(A+\bar{C})}$$

$$= (\bar{A} + \bar{C}) \cdot (\bar{B} + \overline{A+\bar{C}})$$

$$= (\bar{A} + \bar{C}) \cdot (\bar{B} + (A \cdot C))$$

$$\triangleright \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}C + \bar{C}AC$$


$$= \bar{B}(\bar{A} + \bar{C}) + \bar{A}C$$

$\therefore f(a,b,c) \neq f(\bar{a}, \bar{b}, \bar{c})$ $\therefore Z$ is not a self dual

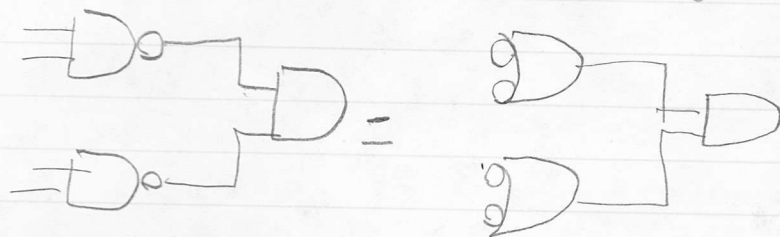
2) Step 1) Convert NAND with invert to AND



Step 2) convert NAND to OR with Demorgan's law









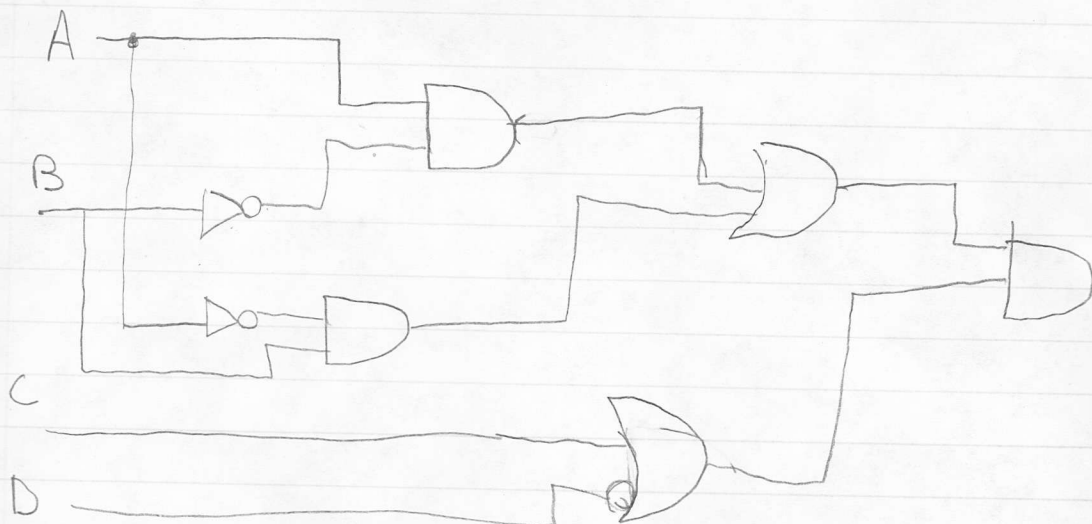
Step 3) Take inverters and cancel each other finally we have:



3.

$A_1 A_0 A_3 A_2$
 $A_2 A_3 A_0 A_1$

a) Karnaugh maps

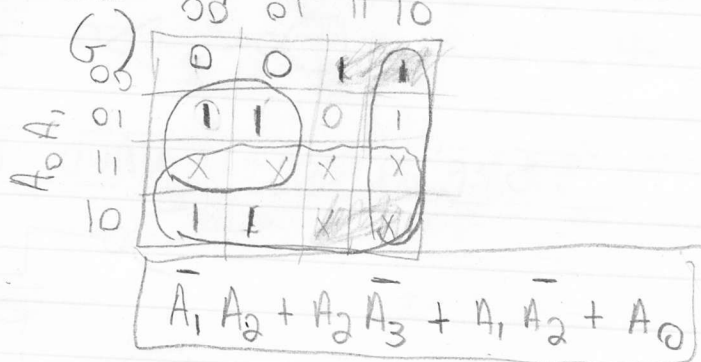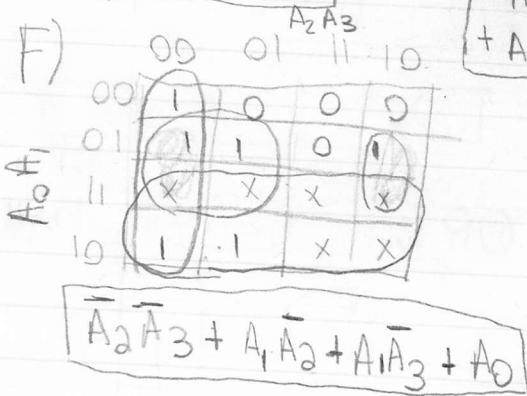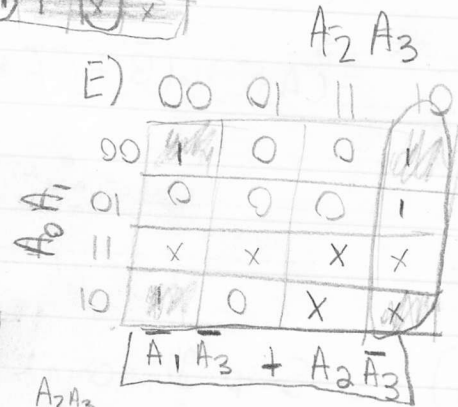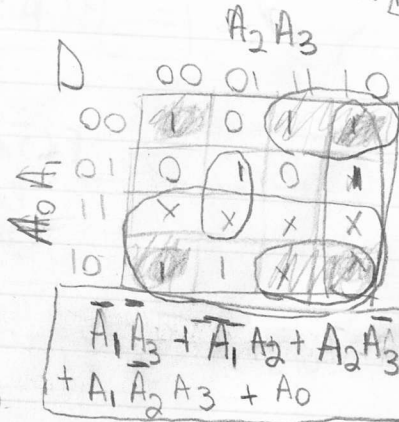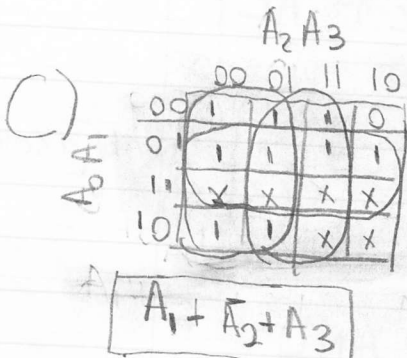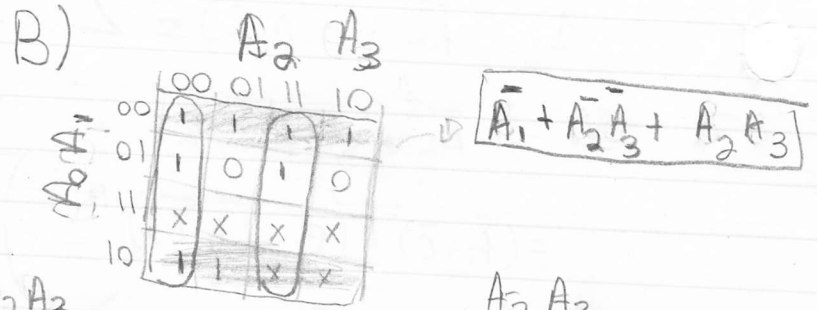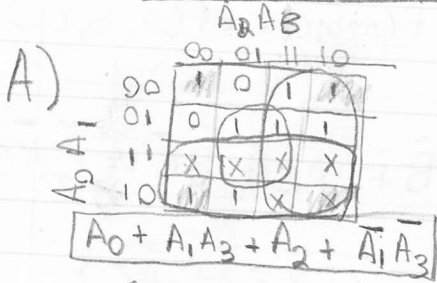

Sum of Products

where u input $A_0 A_1 A_2 A_3$

$A = A_0 + A_1 A_3 + A_2 + \bar{A}_1 \bar{A}_3$

$E = \bar{A}_1 \bar{A}_3 + A_2 \bar{A}_3$

$B = \bar{A}_1 + \bar{A}_2 \bar{A}_3 + A_2 A_3$

$F = \bar{A}_2 \bar{A}_3 + A_1 \bar{A}_2 + A_1 \bar{A}_3 + A_0$

$C = A_1 + \bar{A}_2 + A_3$

$G = \bar{A}_1 A_2 + A_2 \bar{A}_3 + A_1 \bar{A}_2 + A_0$

$D = \bar{A}_1 \bar{A}_3 + \bar{A}_1 A_2 + A_2 \bar{A}_3 + A_1 \bar{A}_2 A_3 + A_0$

4)

a) $-2^{(n-1)}$ to $2^{(n-1)} - 1$

So: -128 to 127

b) $A = 111100100$ $B = 001000110$
 $-A = 000011100$ $-B = 110111010$] With sign extension

b) $A+B$

$$\begin{array}{r} 111100100 \\ + 001000110 \\ \hline 000101010 \end{array}$$

c) $B-A$

$$\begin{array}{r} 001000110 \\ B+(-A) + 000011100 \\ \hline 001100000 \end{array}$$

∴ because first 2 digits are the same no overflow.

∴ no overflow

d) $-A-B$

$$\begin{array}{r} 000011100 \\ 110111010 \\ \hline 111010110 \end{array}$$

∴ no overflow.

5)

		cd			
		00	01	11	10
ab	00	1	0	1	1
	01	0	0	0	0
	11	0	0	1	1
	10	1	0	0	1

		cd			
		00	01	11	10
ab	00	0	0	x	0
	01	1	1	1	1
	11	0	x	0	x
	10	x	0	0	1

$= \bar{a}b + a\bar{b}\bar{c}$