

- P1. The next figure shows the state diagram of a logic circuit which has a unique one-bit external input x .
- Start off by deriving the state table of the circuit. Then, assuming that JK flip-flops are to be used in the implementation, extend the state table with the excitation table of the circuit.
 - Find simplified expressions for each flip-flop inputs.

SOLUTION:


1. **13 points** Map the FSM logic diagram to State table.
To find the excitation table, fill the J and K columns using:
A) the "copy & paste recipe:"

- J = next state** if present state is 0
- J = don't care (x) if **present state is 1**
- K = don't care (x)** if present state is 0
- K = complement of the next state** if present state is 1

... or B) The JK FF Excitation Table, i.e.:

	if $Q^n = 0$	if $Q^n = 1$
J =	[1] Q^{n+1}	[2] x
K =	[3] x	[4] $(Q^{n+1})'$

1 point for correct labeling the table


 


	A^n or Q_1^n	B^n or Q_0^n	X	A^{n+1} or Q_1^{n+1}	B^{n+1} or Q_0^{n+1}	J_A or J_1	K_A or K_1	J_B or J_2	K_B or K_0
				0.5 x 8 = 4	0.5 x 8 = 4	0.5 x 8 = 4			
(0)	0	0	0	0	0	0	x	0	x
(1)	0	0	1	1	0	1	x	0	x
(2)	0	1	0	x	x	x	x	x	x
(3)	0	1	1	x	x	x	x	x	x
(4)	1	0	0	0	0	x	1	0	x
(5)	1	0	1	1	1	x	0	1	x
(6)	1	1	0	1	0	x	0	x	1
(7)	1	1	1	1	1	x	0	x	0

  2. **12 points** Find simplified expressions for each flip-flop inputs
If the state is represented by logic variables A and B

$J_A = X$ $K_A = B'X'$ $J_B = AX$ $K_B = X'$

OR, if the state is represented by logic variables Q_1 and Q_0



- P2. **25 points** Design a 3-bit shift **right left** register which has a data input *Serial In* and a control input “*Sh*” (shift). The operation of the sequential circuit is described in the functional Table 1. Design the sequential circuit using three D flip-flops.
- (P2.1.) **6 pts** Provide the *equations for the next state variables* of the D flip-flops $\{Q_i^{n+1}, i = [0, 1, 2]\}$, by firstly filling out the *next state* columns of Table 1.
- (P2.2.) **13 pts** Draw the logic diagram of the circuit that you designed; explain your work.
- (P2.3.) **6 pts** Design a D flip-flop using a T flip-flop; draw the logic diagram of your designed D flip-flop.

Because of the typo in the first line of question (written “right” instead of “left”, do accept any implementation: left or right)

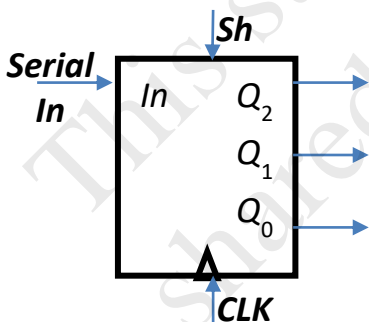


Table 1.


Sh	Function	Q_2^{n+1}	Q_1^{n+1}	Q_0^{n+1}
0	Shift Left	Q_1^n	Q_0^n	Serial In
1	Preserve present state	Q_2^n	Q_1^n	Q_0^n

$Q_2^{n+1} = Sh Q_2^n + Sh' \cdot Q_1^n$

$Q_1^{n+1} = Sh Q_1^n + Sh' \cdot Q_0^n$

$Q_0^{n+1} = Sh Q_0^n + Sh' \cdot \text{Serial In}$

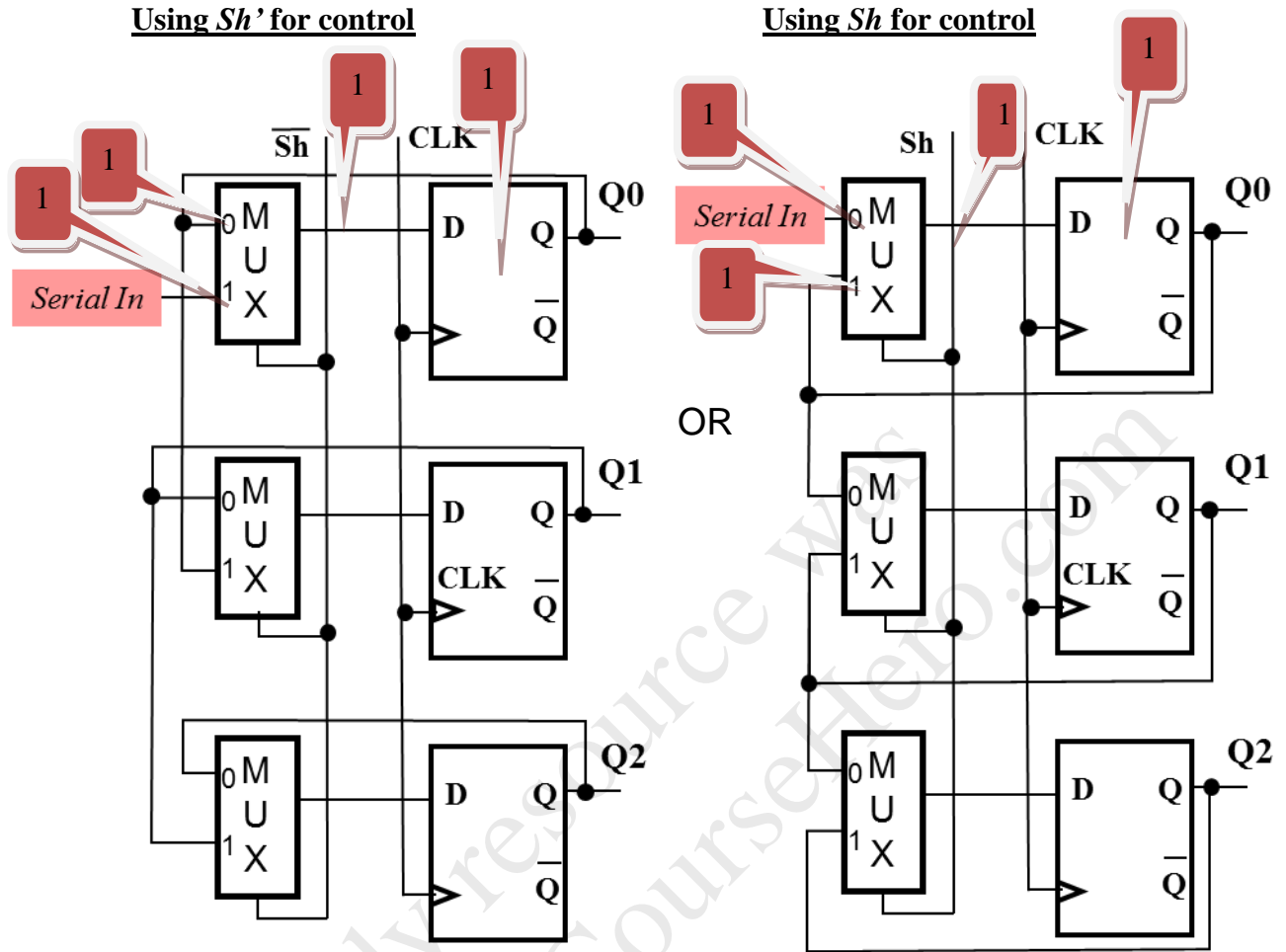
(P2.2.) Draw the logic diagram of the circuit that you designed. **13 pts = 3 x 4 pts + 1 point (for clock & Sh)**



... also accept implementation with gates!

(P2.3) **6 pts** Design a D flip-flop using a T flip-flop; draw the logic diagram of your designed D FF

1pt	Q^n	D	Q^{n+1}	1pt	T	1pt
0.25	0	0	0	0.25	0	0.25
0.25	0	1	1	0.25	1	0.25
0.25	1	0	0	0.25	1	0.25
0.25	1	1	1	0.25	0	0.25

 

$T = Q'D + QD'$ or $T = Q \oplus D$ **1pt**