

ELG 2138 Fall 2008 Midterm Exam

Student Name: _____


Student ID# : _____

Student Signature: _____

Only basic scientific calculators allowed


P.1 (25%)

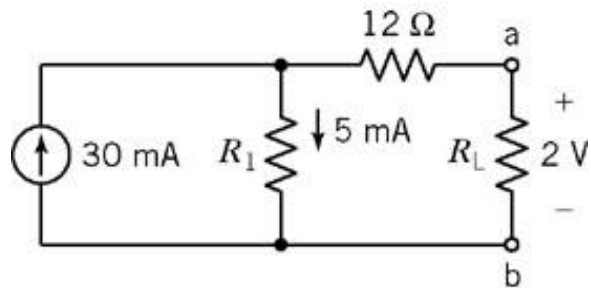Determine the values of R_I and R_L in the following circuit:




P.2 (25%)

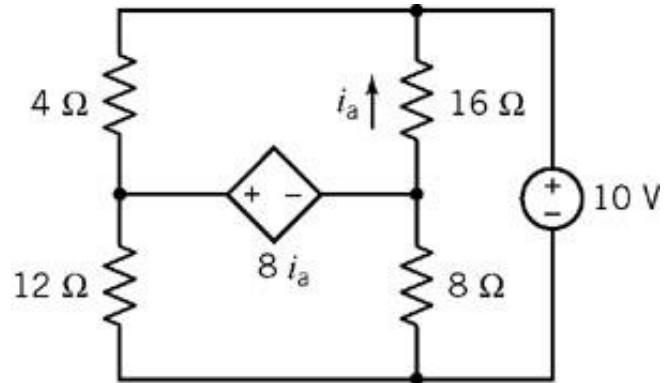Using Node Voltage Analysis, determine the value of the power supplied by the dependent source in the following circuit:




P.3 (25%)

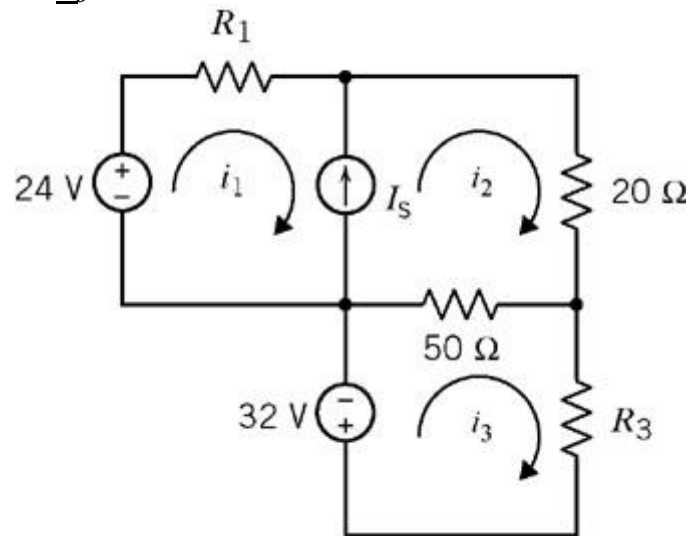The values of the mesh currents in the circuit below are $i_1 = -2.2213\text{A}$, $i_2 = 0.7787\text{A}$, and $i_3 = 0.077\text{A}$. Using *Mesh Current Analysis*, determine the values of the resistances R_1 and R_3 .



P.4 (25%)

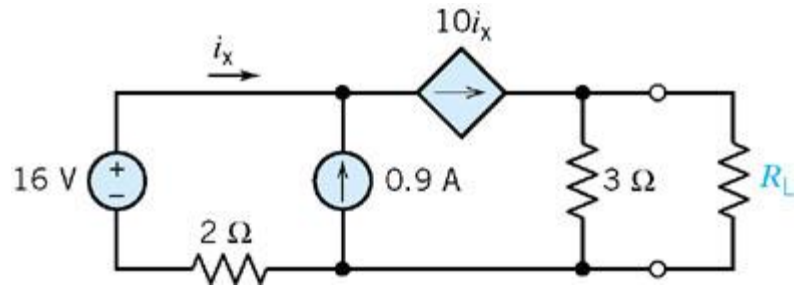In the following circuit, find the maximum power to the load R_L , if the maximum power transfer condition is met:



P.5 (5%)

What is a typical value for the internal resistance of a laboratory voltmeter? Why is it designed with this value of internal resistance? (Explain your answer in one or two sentences)