

CEG2136: Computer Architecture I / CEG2536: Architecture des Ordinateurs I
MIDTERM EXAMINATION


Professors: Voicu Groza, Fadi Malek and Mohamed Ali Ibrahim

Question 1 (20 points)

a) (5 points) You have a SRAM memory chip with a capacity of 64k x 8




- 1) How many data lines does it have? *Answer 1)*8.....
- 2) How many address lines does it have? *Answer 2)*16.....
- 3) What is its capacity expressed in "bits"? *Answer 3)* $2^{16} \times 2^3$ bits = 2^{19} bits = 2^9 kbits = 512 kbits = 0.5 M bits

 b) **15 points** Using D-type flip-flops, design a 3-bit Gray code counter which has the following counting sequence:



Draw the transition table of the counter and derive the excitation equations of the D flip flops' inputs.


$Q_2(n)$	$Q_1(n)$	$Q_0(n)$	$Q_2(n+1)$	$Q_1(n+1)$	$Q_0(n+1)$	D_2	D_1	D_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	1
0	1	0	1	1	0	1	1	0
0	1	1	0	1	0	0	1	0
1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	1	0	0
1	1	0	1	1	1	1	1	1
1	1	1	1	0	1	1	0	1

   

Question 2 (20 points) Design a 3-bit register whose function is described in the following table, where M and N are two control bits. Using the proper digital components (encoders, decoders, multiplexers, etc.) logic gates, and D flip-flops, draw a detailed diagram of the logic circuit of the register.

f^{MN}	MN	Operation	With counters	Next state	D_i
f^0	0 0	No change		$Q_2 Q_1 Q_0$	Q_i
f^1	0 1	Loading external inputs $I_2 I_1 I_0$	$I_2 I_1 I_0$	I_i	I_i
f^2	1 0	Decrement by 1 (count down)		$Q_2 Q_1 Q_0 - 1$?
f^3	1 1	Increment by 3 (count up)		$Q_2 Q_1 Q_0 + 3$?

 Using the D FF Excitation equation $D_i = Q_i^{n+1}$ for $i=0,1,2$



$f^2: MN=10: Q-1$

Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+
0	0	0	1	1	1
0	0	1	0	0	0
0	1	0	0	0	1
0	1	1	0	1	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

$f_0^2: D_0 = Q_0'$

$D_2 = Q_2 Q_1 + Q_2 Q_0 + Q_2' Q_1' Q_0'$


$f_2^2: D_2 = (Q_2 \oplus (Q_0 + Q_1))'$

D_1

Q_1	Q_0	00	01	11	10
0	0	1	0	0	0
0	1	0	1	1	1
1	0	1	0	1	0
1	1	0	0	1	0

$D_1 = Q_1' Q_0' + Q_1 Q_0 = Q_1 \odot Q_0$

$f_1^2: D_1 = (Q_1 \oplus Q_0)'$

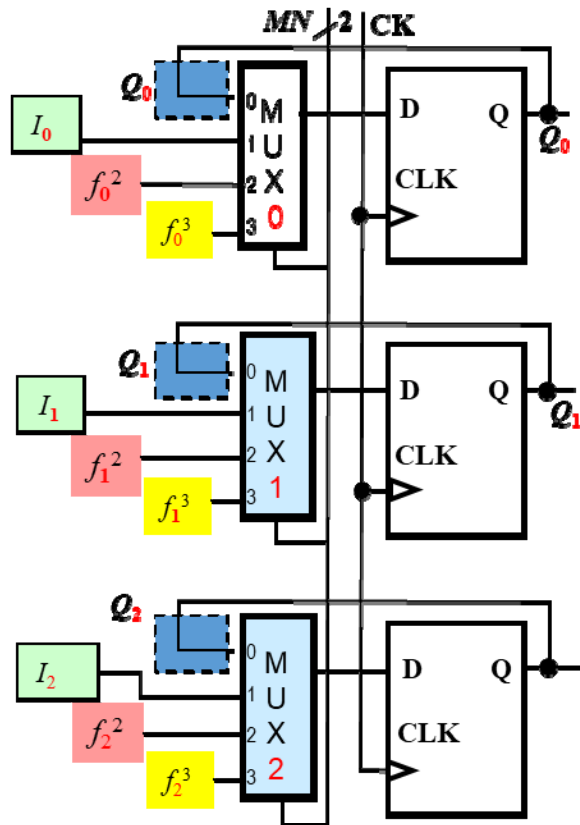

$f^3: MN=11: Q+3$

Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+
0	0	0	0	1	1
0	0	1	1	0	0
0	1	0	1	0	1
0	1	1	1	1	0
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	0	0	1
1	1	1	0	1	0

$f_0^3: D_0 = Q_0'$

$D_2 = Q_2' Q_1 + Q_2' Q_0 + Q_2 Q_1' Q_0'$


$f_2^3: D_2 = Q_2 \oplus (Q_0 + Q_1)$

D_1

Q_1	Q_0	00	01	11	10
0	0	1	0	1	0
0	1	0	1	1	0
1	0	1	0	1	0
1	1	0	0	1	0

$D_1 = Q_1' Q_0' + Q_1 Q_0 = Q_1 \odot Q_0$

$f_1^3: D_1 = (Q_1 \oplus Q_0)'$

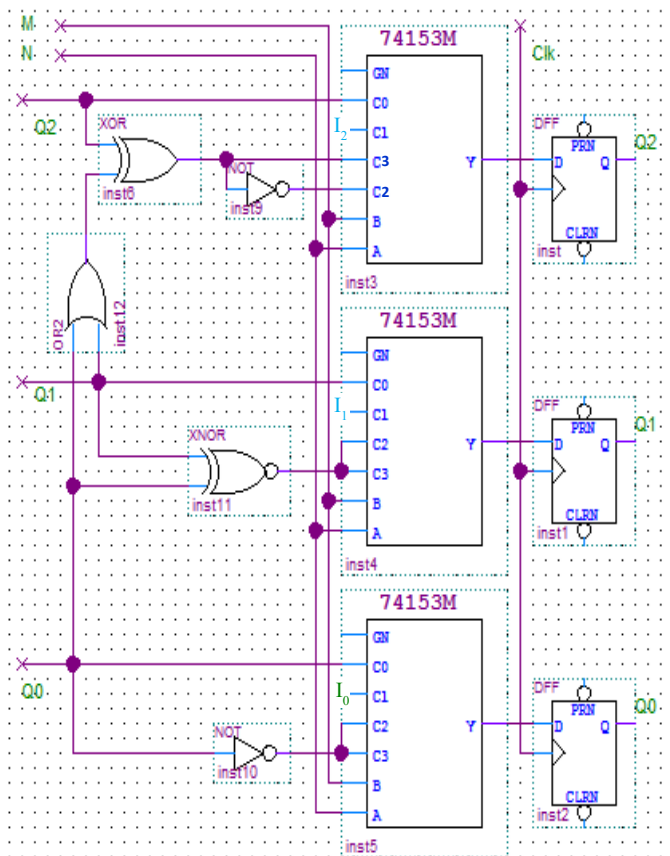

OR Comprehensive solution:

Control	Present State			Next State			Excitation Equations
MN	$Q_2(n)$	$Q_1(n)$	$Q_0(n)$	$Q_2(n+1)$	$Q_1(n+1)$	$Q_0(n+1)$	
00	x	x	x	$Q_2(n)$	$Q_1(n)$	$Q_0(n)$	$D_i = Q_i, i = 0,1,2$
01	x	x	x	I_2	I_1	I_0	$D_i = I_i, i = 0,1,2$
10	0	0	0	1	1	1	
	0	0	1	0	0	0	$D_2 = Q_2(Q_0+Q_1) + Q_2'Q_1'Q_0'$
	0	1	0	0	0	1	$= Q_2 \odot (Q_1+Q_0)$
	0	1	1	0	1	0	$D_1 = Q_1'Q_0'+Q_1Q_0$
	1	0	0	0	1	1	
	1	0	1	1	0	0	$D_0 = Q_0'$
	1	1	0	1	0	1	
	1	1	1	1	1	0	
11	0	0	0	0	1	1	
	0	0	1	1	0	0	$D_2 = Q_2'(Q_0+Q_1) + Q_2Q_1'Q_0'$
	0	1	0	1	0	1	$= Q_2 \oplus (Q_1+Q_0)$
	0	1	1	1	1	0	$D_1 = Q_1'Q_0'+Q_1Q_0$
	1	0	0	1	1	1	
	1	0	1	0	0	0	$D_0 = Q_0'$
	1	1	0	0	0	1	
	1	1	1	0	1	0	

$$D_2 = M'N'Q_2 + M'NI_2 + MN'Q_2 \odot (Q_1+Q_0) + MNQ_2 \oplus (Q_1+Q_0)$$


$$D_1 = M'N'Q_1 + M'NI_1 + MN'(Q_1 \odot Q_0) + MN(Q_1 \odot Q_0) = M'N'Q_1 + M'NI_1 + M(Q_1 \odot Q_0)$$

$$D_0 = M'N'Q_0 + M'NI_0 + MQ_0'$$

Implementation with MUX's and gates (as above) or with gates, exclusively.


... or with MUX's & adders

MN	Operation	$D_2D_1D_0$
00	No change	$Q_2 Q_1 Q_0$
01	Loading $I_2 I_1 I_0$	$I_2 I_1 I_0$
10	Decrement by 1	$Q_2 Q_1 Q_0 + 1 1 1$
11	Increment by 3	$Q_2 Q_1 Q_0 + 0 1 1$

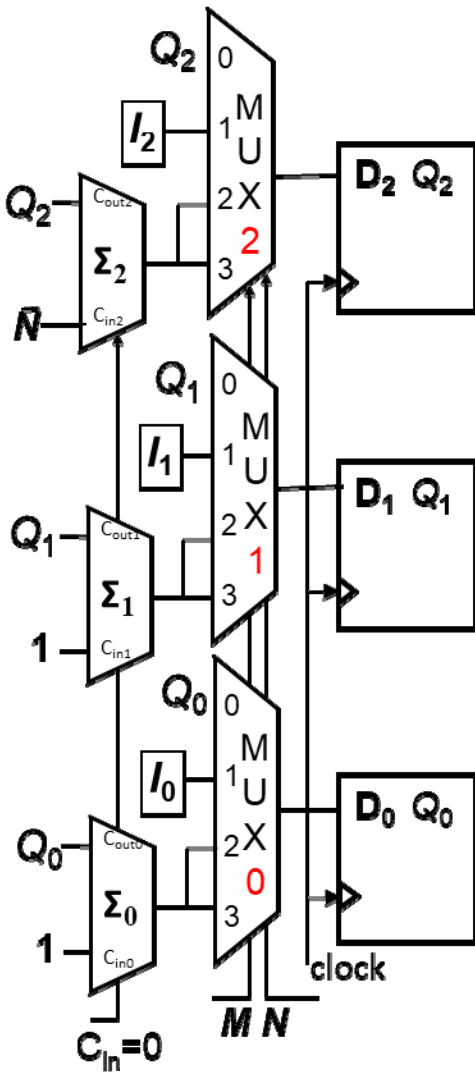

... or with adders

MN	$D_2D_1D_0 =$	1 st term +	2 nd term +	cy
00	$Q_2Q_1Q_0 =$	$Q_2 Q_1 Q_0 +$	$0 0 0 +$	0
01	$I_2 I_1 I_0 =$	$I_2 I_1 I_0 +$	$0 0 0 +$	0
10	$Q_2Q_1Q_0 - 1 =$	$Q_2 Q_1 Q_0 +$	$1 1 1 +$	0
11	$Q_2Q_1Q_0 + 3 =$	$Q_2 Q_1 Q_0 +$	$0 1 1 +$	0

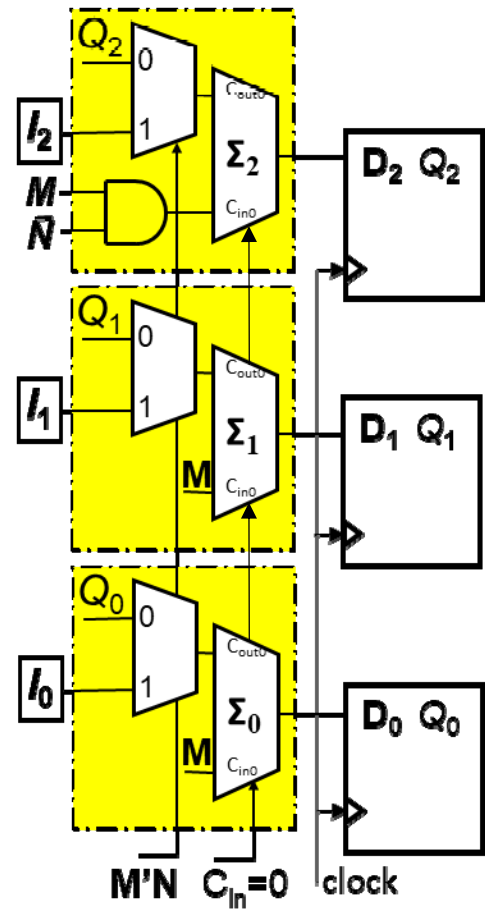

Question 3 (30 points)

The 2's complement representation is used in an 8-bit register which contains the binary value 11011000.

- a. What is the decimal value of the number stored initially in the register?

R	2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0
	1	1	0	1	1	0	0	0

Conversion to decimal

$$1101\ 1000 = -x \Rightarrow x = 2\text{'s complement of } 1101\ 1000 = 0010\ 1000 = 40 \Rightarrow 1101\ 1000 = -40$$

or

$$1101\ 1000 = -2^7 + 2^6 + 2^4 + 2^3 = -128 + 64 + 16 + 8 = -128 + 88 = -40$$

- b. What is the register value after an arithmetic shift right? Give your result both in binary and decimal.

2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0
1	1	0	1	1	0	0	0
1	1	1	0	1	1	0	0

Conversion to decimal

$$1110\ 1100 = -y \Rightarrow y = 2\text{'s complement of } 1110\ 1100 = 0001\ 0100 = 20 \Rightarrow 1110\ 1100 = -20$$

or

$$1110\ 1100 = -2^7 + 2^6 + 2^5 + 2^3 + 2^2 = -128 + 64 + 32 + 8 + 4 = -128 + 108 = -20$$

- c. Starting again from the initial number 11011000, determine the register value after an arithmetic shift left, both in binary and decimal.

2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0
1	1	0	1	1	0	0	0
1	0	1	1	0	0	0	0

Conversion to decimal:

$$1011\ 0000 = -z \Rightarrow z = 2\text{'s complement of } 1011\ 0000 = 0101\ 0000 = 64+16 = 80 \Rightarrow 1011\ 0000 = -80$$

or

$$1011\ 0000 = -2^7 + 2^5 + 2^4 = -128 + 32 + 16 = -128 + 48 = -80$$

- d. What arithmetic operations are performed by these shifts?

Division by 2 in b.

Multiplication by 2 in c.

- e. Is there any overflow?

NO

Justify your answer.

Both results (-20 and -80) can be represented with 8 bits 2's complement representation, i.e., are included in the range of the numbers that can be represented with 8 bits 2's complement representation $[-128, 127]$: $-128 < -20 < 127$ and $-128 < -80 < 127$

Overflow can be signaled by a circuit that detects if the 2 m.s.b. are not identical, but not carry, since there are no adders to generate carries.

Question 4 (30 points)

A 3-bit arithmetic circuit takes three control bits, x , y and z , and two 3-bit data inputs, A and B . The operations supported by the arithmetic unit are described in the following table. Draw a detailed logic diagram of the circuit using 1-bit full adders and the digital components of your choice (encoders, decoders, multiplexers, etc.) (Note: A' is the 1's complement of A)

z	0	1
$x y$		
0 0	$F = A + B$ (add)	$F = A + B + 1$
0 1	$F = A + B'$	$F = A - B$ (subtract)
1 0	$F = A$ (transfer)	$F = A + 1$ (increment)
1 1	$F = A - 1$ (decrement)	$F = A' + 1$ (2's complement of A)

The result F will be calculated with 3 adders:

$$F = R + S + cy = F_2F_1F_0 = R_2R_1R_0 + S_2S_1S_0 + cy$$

z	0	1
$x y$	$R_2R_1R_0 + S_2S_1S_0 + cy$	$F = R_2R_1R_0 + S_2S_1S_0 + cy$
0 0	$A_2A_1A_0 + B_2B_1B_0 + 0$	$A_2A_1A_0 + B_2B_1B_0 + 1$
0 1	$A_2A_1A_0 + B_2'B_1'B_0 + 0$	$A_2A_1A_0 + B_2'B_1'B_0 + 1$
1 0	$A_2A_1A_0 + 000 + 0$	$A_2A_1A_0 + 000 + 1$
1 1	$A_2A_1A_0 + 111 + 0$	$A_2'A_1'A_0 + 000 + 1$

NOTE: MUX's inputs might be numbered in a weird order below!!!

