

Basic Quantities.

Let us focus on some terms we will regularly use when analysing electrical circuits.

Current.


Rate of change of charge

$$i(t) = \frac{dq(t)}{dt} \quad \text{or} \quad q(t) = \int_{-\infty}^t i(x) dx$$


i - current (ampere)

q - charge (coulomb)

t - time

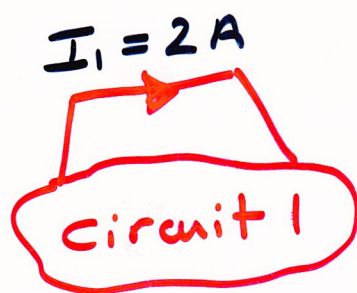

2C flowing L to R
in 1s.

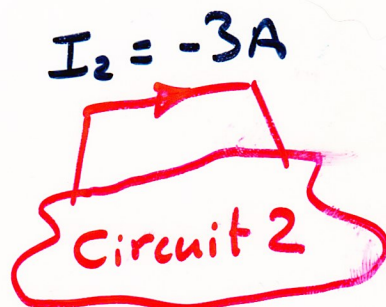

3C flowing R to L
in 1s.


Voltage, electromotive force (EMF) or potential difference.

Charges in motion yield an energy transfer. Voltage between two points is defined as the difference in energy level of a unit charge located at each of the two points.


$$V = \frac{W}{q}$$

V - potential difference (V)
 W - energy change or work done (J)
 q - charge (C).

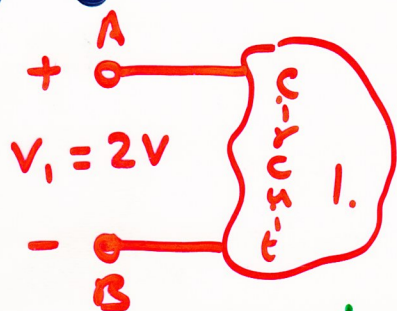By implication from this definition one point has a higher potential w.r.t. the other. Represented by sign convention.




A has higher potential

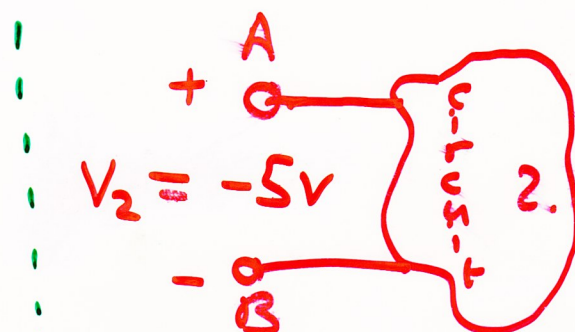


B has higher potential

Voltage - Current relationships.

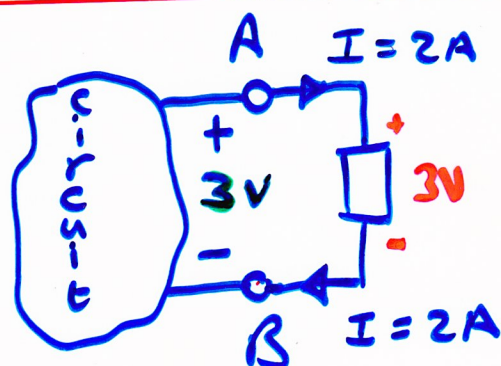


Energy absorbed.

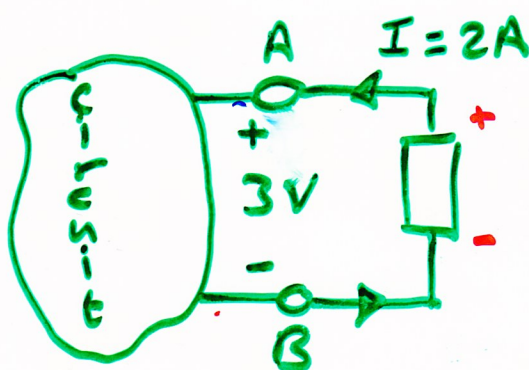

Energy supplied

Note the current flow convention

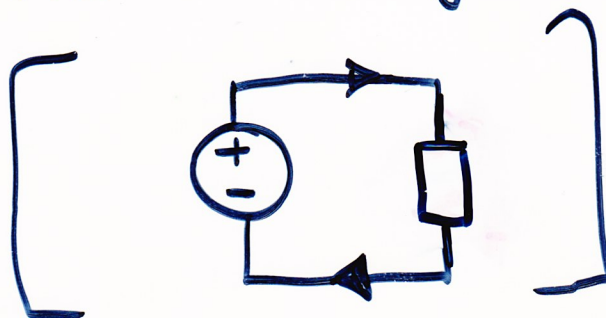

Current direction
is $+$ \rightarrow $-$.
Opposite of actual
electron flow.

4
Considering the potential difference in terms of energy and charge changes.

$$V = \frac{dW}{dq}$$

V - potential diff.

dW - energy change with charge change, dq .

But $i = dq/dt$

$$\text{So } \underbrace{V i}_{\text{green wavy}} = \frac{dW}{dq} \frac{dq}{dt} = \frac{dW}{dt} = \underbrace{P}_{\text{green wavy}}$$


P is power.

$$\text{Alternatively } \Delta W = \int_{t_1}^{t_2} V i dt$$

$$\underline{P = iV}$$

Examples

(1)
(Irwin El. 1 a)

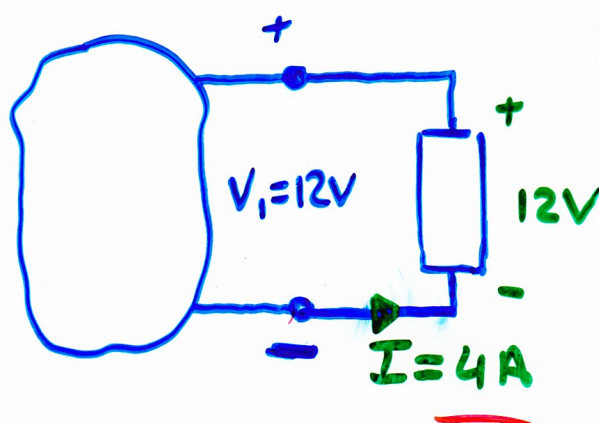

Determine the amount of power absorbed or supplied by the element.


$$V = 12V$$

$$I = -4A$$

$$\therefore P = -48W$$

48W supplied.

(2)
(Irwin 1.36)

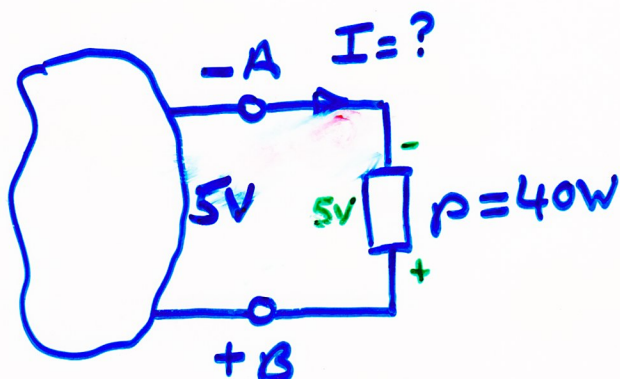

Determine the current

$$P = 40W \text{ (absorbing)}$$

$$V_{AB} = -5V$$

$$\text{Now } P = IV$$

$$I = \frac{P}{V}$$

$$I = \frac{40}{-5} = -8A$$

Circuit Elements

Circuit elements classified by the current through it and the voltage (or p.d.) across it.

Two types: **active** and **passive**

ACTIVE - generates energy e.g. batteries, transistor devices.



PASSIVE - no energy generation e.g. resistors, capacitors & inductors.

Deal with passive components later.
Consider **ACTIVE** elements now.

4 active sources

1. Independent voltage source
- 2 " current "
- 3 Dependent voltage source
- 4 " current "


Independent Sources.

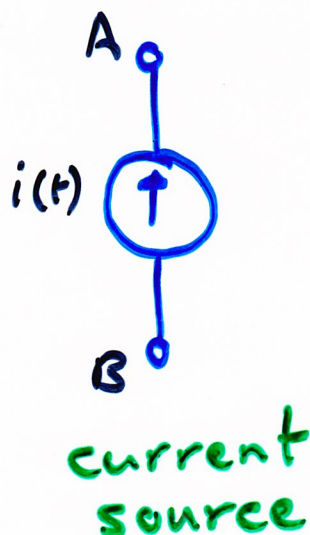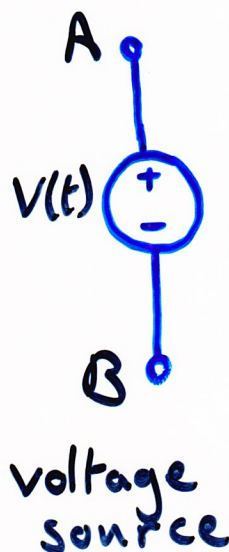


voltage source - voltage maintained independent of current through it.

current source - current maintained independent of voltage across it.


Dependent Sources.

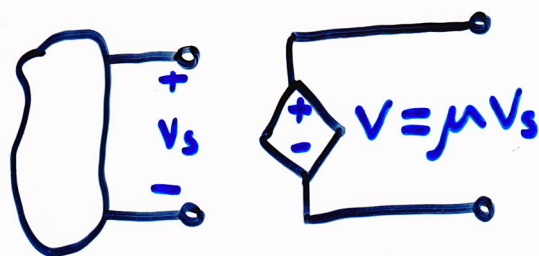


voltage dependent voltage source

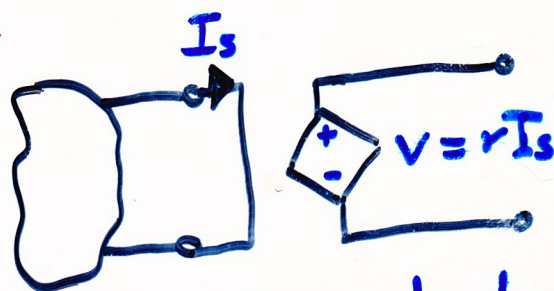

current dependent voltage source

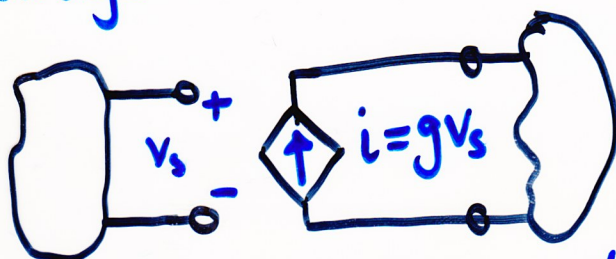

voltage dependent current source

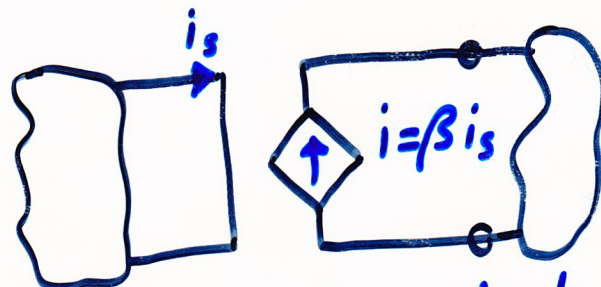


current dependent current source.

Examples

8

(1)

(Irwin
Ext. 1.4b)

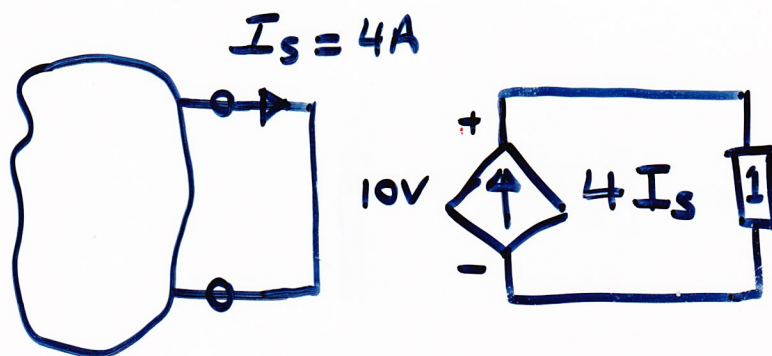

Power supplied to element 1?


$$I_s = 4A$$

$$\begin{aligned}\therefore \text{Current source produces, } I &= 4I_s \\ &= 4 \times 4 \\ &= \underline{16A}\end{aligned}$$

Potential across the element is 10V.

$$\begin{aligned}\text{So, power} &= I \times V \\ &= 16 \times 10 \\ &= \underline{160W}\end{aligned}$$

(2)
(Irwin
#1.3)

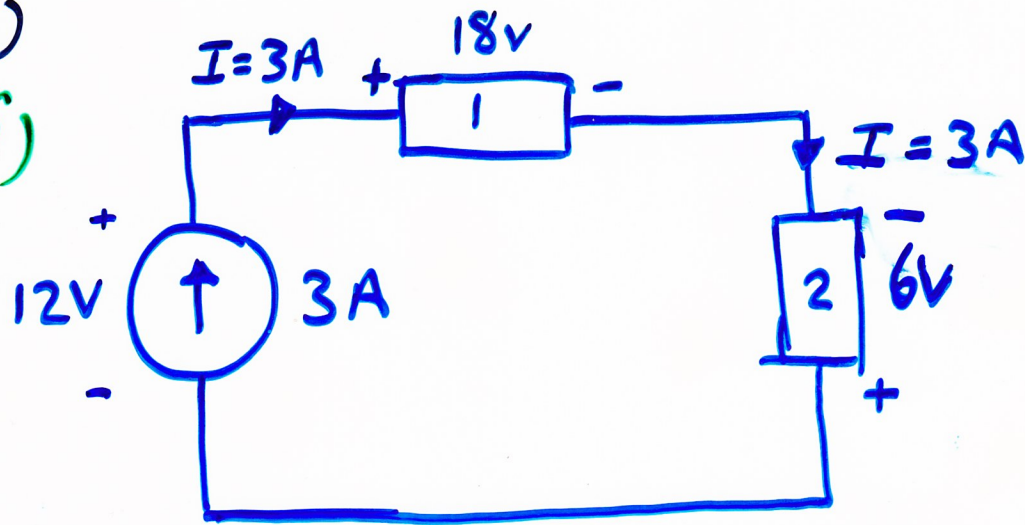


What are the power levels absorbed or supplied by elements 1 & 2?

Current source, $P_{\text{source}} = 12 \times 3 = -36 \text{ W}$
SUPPLIED!

Element 1, $P_1 = 3 \times 18 = 54 \text{ W}$
ABSORBED

Element 2, $P_2 = 3 \times -6 = -18 \text{ W}$
18W SUPPLIED.

(3) Problem 1.39 from Irwin.

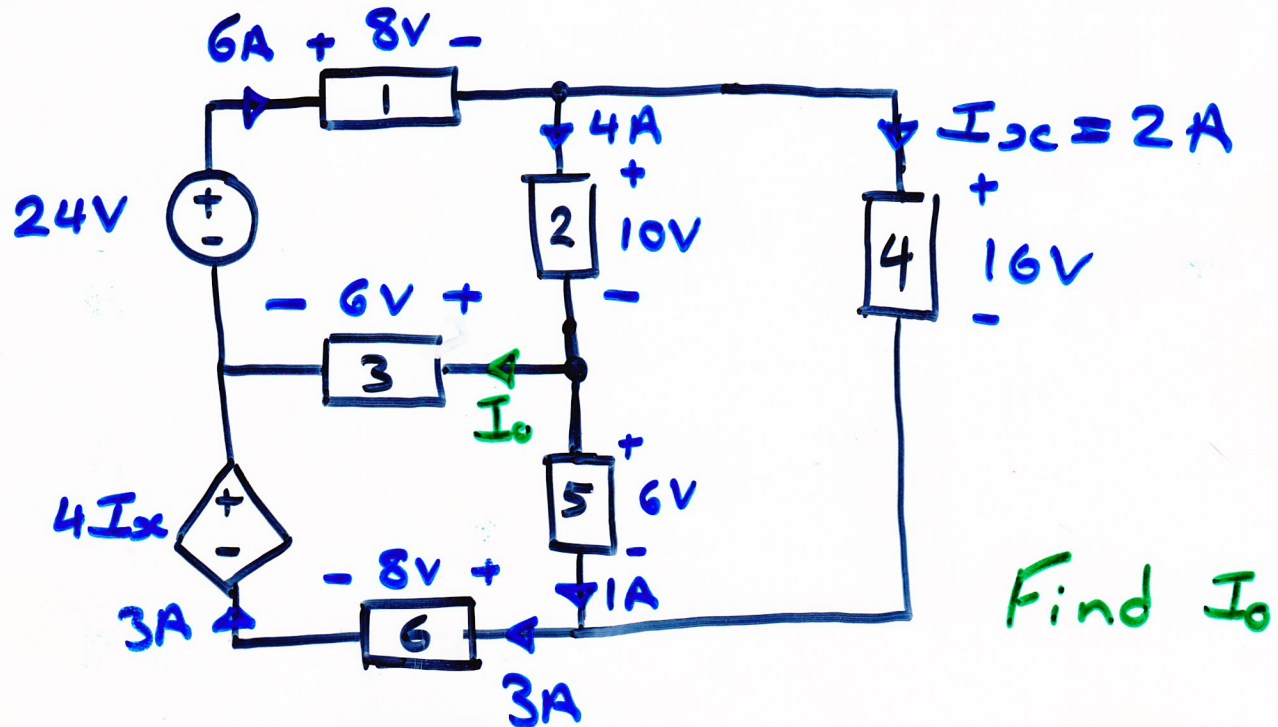

Voltage of dependent source, $V_{os} = 4 \times 2 = 8V$.

$$P_{os} = 8 \times -3 = -24W$$

$$P_{24V} = 24 \times -6 = -144W$$

$$P_1 = 8 \times (6) = 48W$$

$$P_2 = 10 \times (4) = 40W$$

$$P_4 = 16 \times (2) = 32W$$

$$P_5 = 6 \times (1) = 6W$$

$$P_6 = 8 \times (3) = 24W$$

$$\text{Total} = 18W$$

So element 3 must absorb 18W. Potential diff across is 6V so current is $18/6 = 3A$