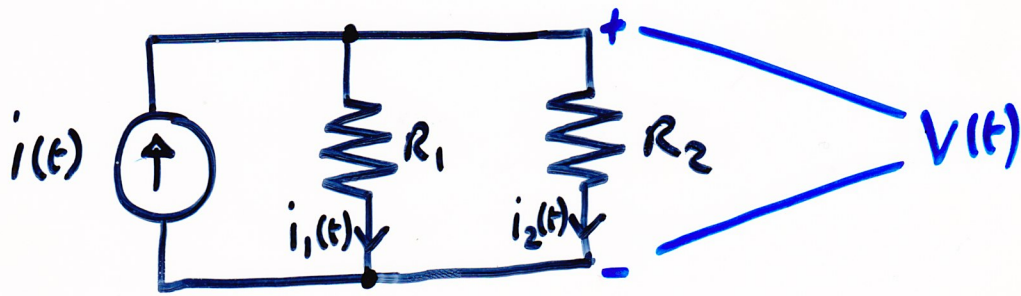


## Single-Node Pair Circuit.



Apply KCL  $i(t) = i_1(t) + i_2(t)$

Using Ohm's law

$$i(t) = \frac{V(t)}{R_1} + \frac{V(t)}{R_2}$$
$$= \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V(t)$$

$$\therefore \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$



What about size of  $R_p$  compared to  $R_1$  &  $R_2$   
Let  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$  so  $R_p =$   
 $\frac{R_1 R_2}{R_1 + R_2}$   
c.f.  $R_1$  &  $R_2$

What about currents?

$$i_1(t) = \frac{V(t)}{R_1}$$


$$\text{But } V(t) = R_p i(t) = \frac{R_1 R_2}{R_1 + R_2} i(t)$$

$$\underline{i_1(t) = \frac{R_2}{R_1 + R_2} i(t)}$$

Similarly

$$\underline{i_2(t) = \frac{R_1}{R_1 + R_2} i(t)}$$

# Multiple Source Networks

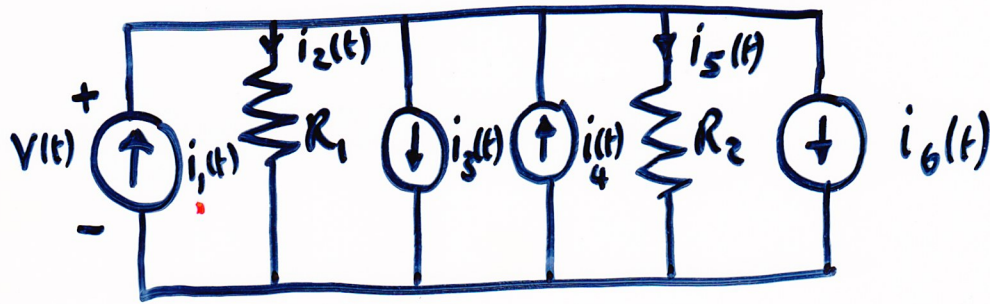


Apply KCL

$$i_1(t) - i_2(t) - i_3(t) + i_4(t) - i_5(t) - i_6(t) = 0$$

$$i_1(t) - i_3(t) + i_4(t) - i_6(t) = i_2(t) + i_5(t) = \underline{i_0(t)}$$


Above circuit is equivalent to

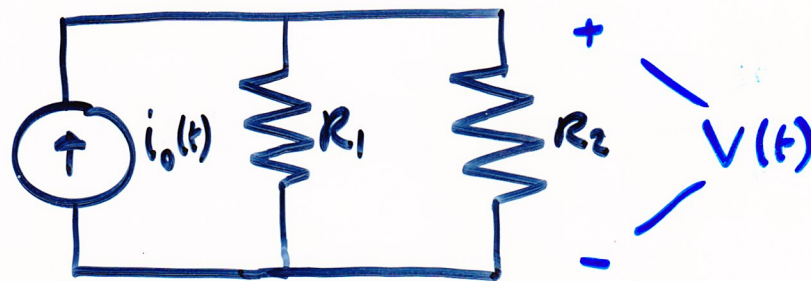

$$\therefore i_0(t) = \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V(t)$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

## Multiple Resistors

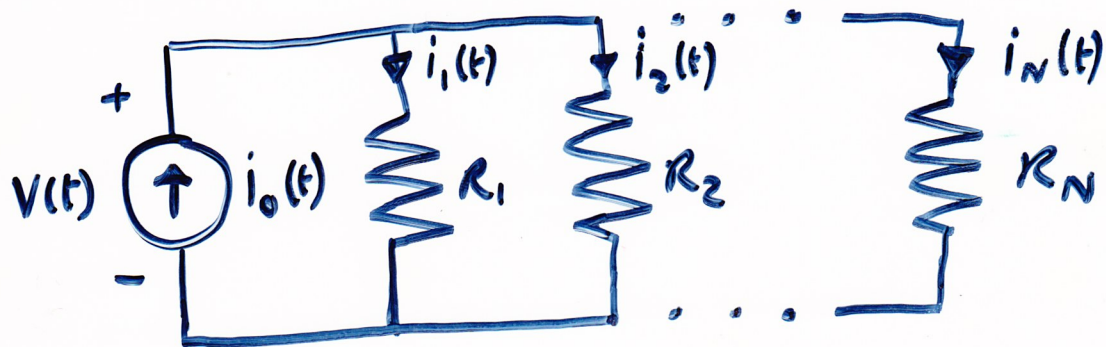

Applying KCL

$$\begin{aligned} i_0(t) &= i_1(t) + i_2(t) + \dots + i_N(t) \\ &= \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right) V(t) \end{aligned}$$

$$\therefore i_0(t) = \frac{V(t)}{R_p}$$


$$\text{Where } \frac{1}{R_p} = \sum_{i=1}^N \frac{1}{R_i}$$

$$i_j(t) = \frac{V(t)}{R_j}$$

$$i_j(t) = \frac{R_p}{R_j} i_0(t)$$




# Series & Parallel Resistor Combination

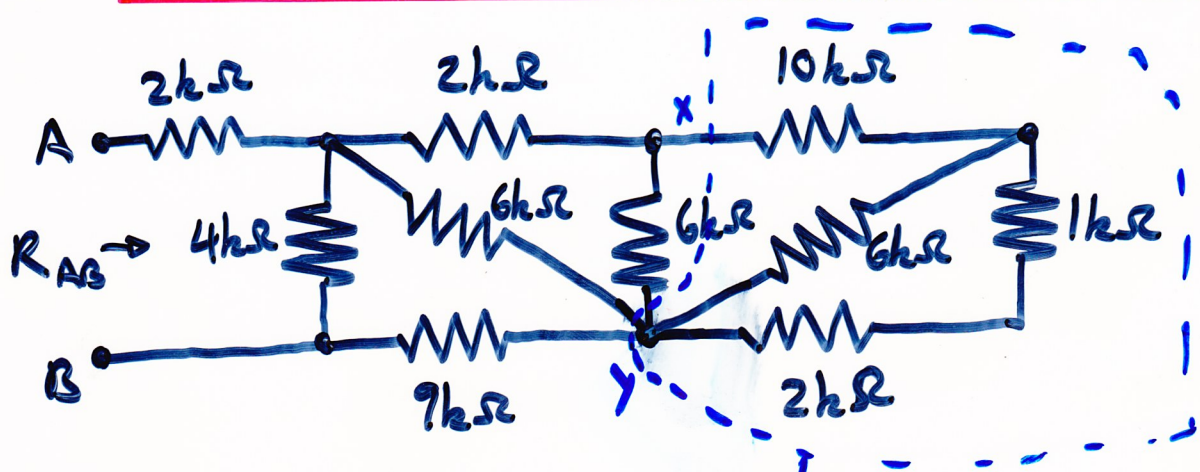


Circuit A

Simplify

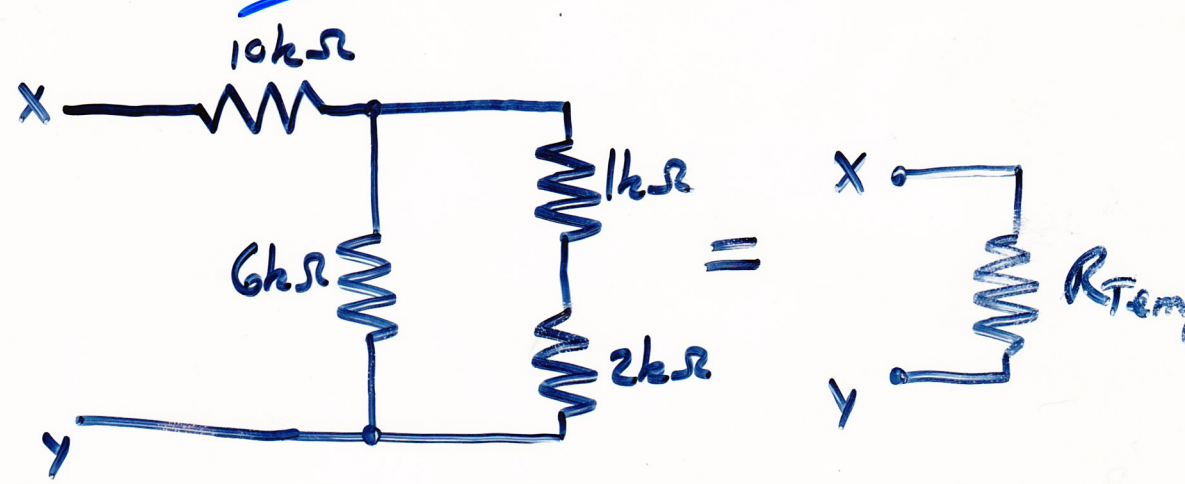


$$\begin{aligned}
 R_{Temp} &= 10k\Omega + \frac{3 \times 6}{3 + 6} k\Omega \\
 &= 10k\Omega + 2k\Omega \\
 &= \underline{\underline{12k\Omega}}
 \end{aligned}$$

Circuit A can be drawn as:

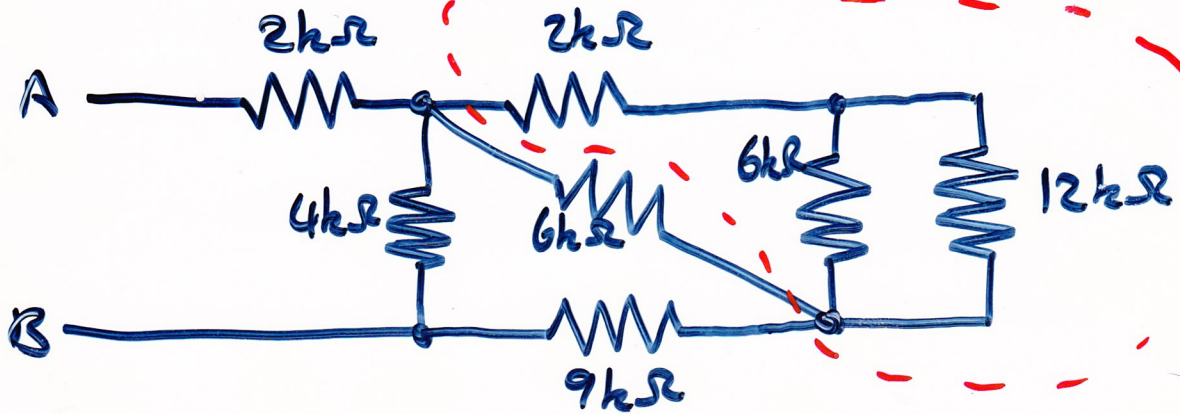


$$\begin{aligned}
 R_{\text{Temp}} &= 2\text{k}\Omega + \frac{6 \times 12}{6 + 12} \text{k}\Omega \\
 &= 2\text{k}\Omega + \frac{72}{18} \text{k}\Omega = 2\text{k}\Omega + 4\text{k}\Omega \\
 &= 6\text{k}\Omega
 \end{aligned}$$

Now we have:

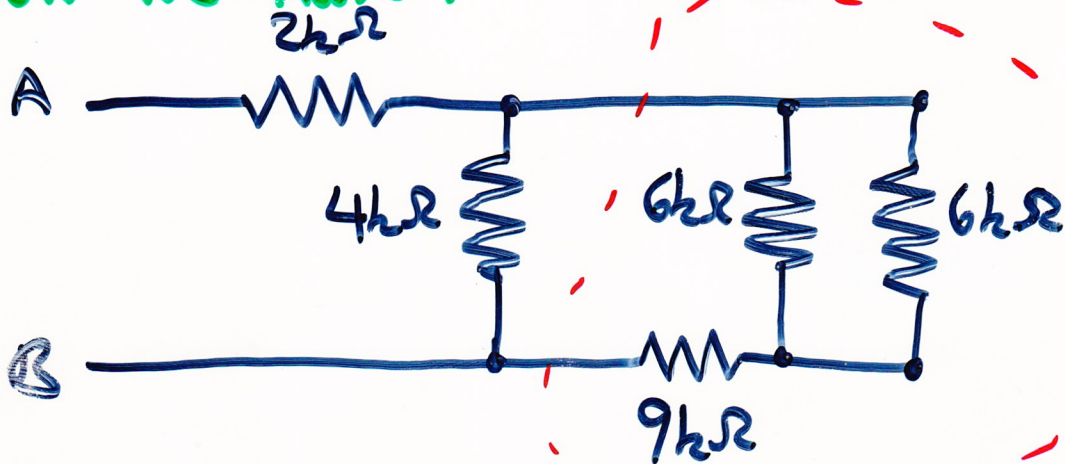

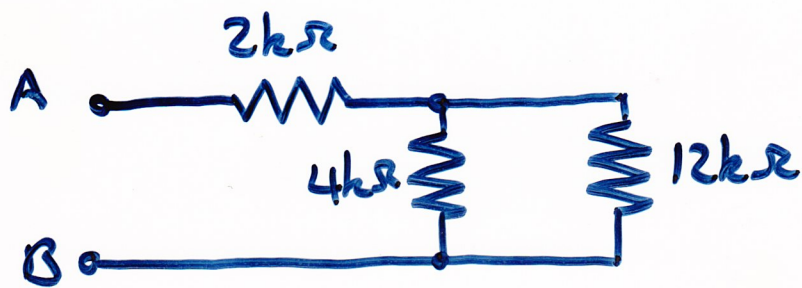
$$\begin{aligned}
 R_{\text{Temp}} &= 9\text{k}\Omega + \frac{6 \times 6}{6 + 6} \text{k}\Omega = 9\text{k}\Omega + 3\text{k}\Omega \\
 &= 12\text{k}\Omega
 \end{aligned}$$




$$R = 2k\Omega + \frac{4 \times 12}{4 + 12} k\Omega$$

$$= 2k\Omega + 3k\Omega$$

$$= 5k\Omega$$

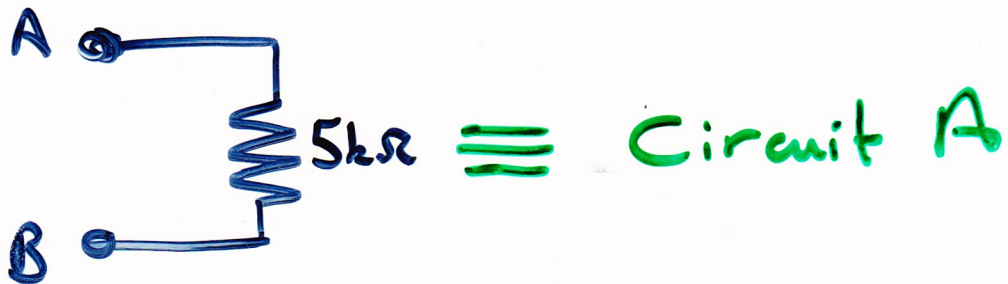




You try

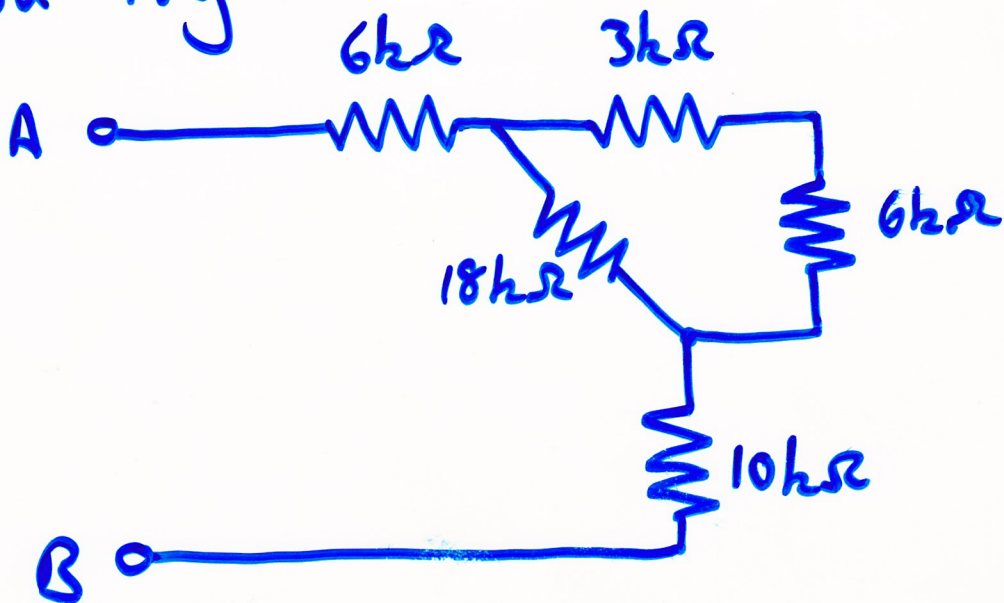

Ans?


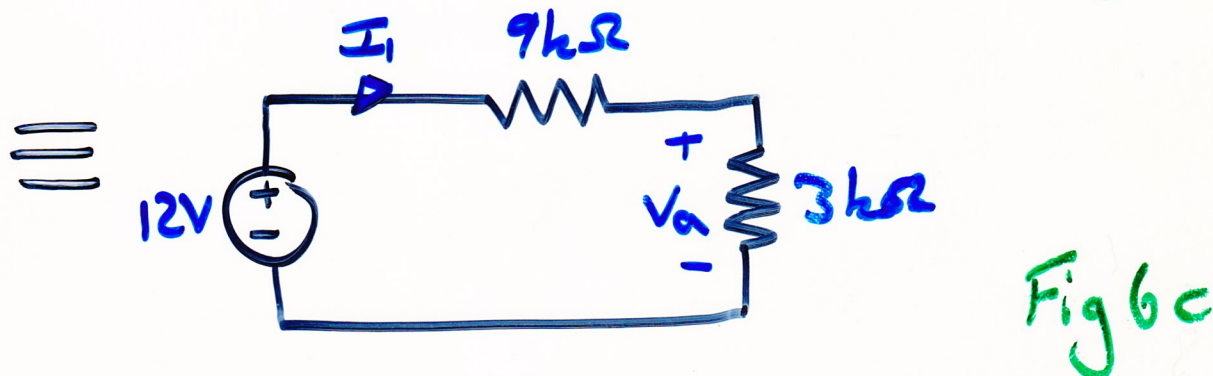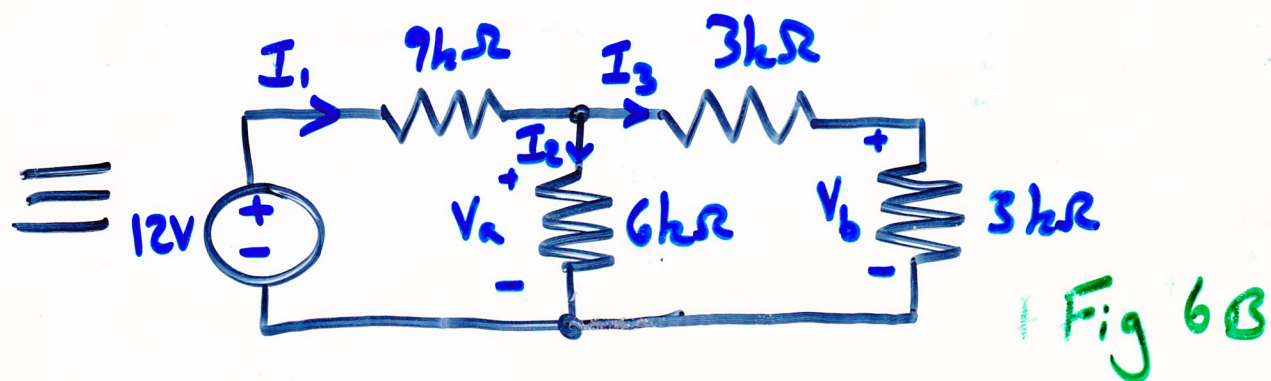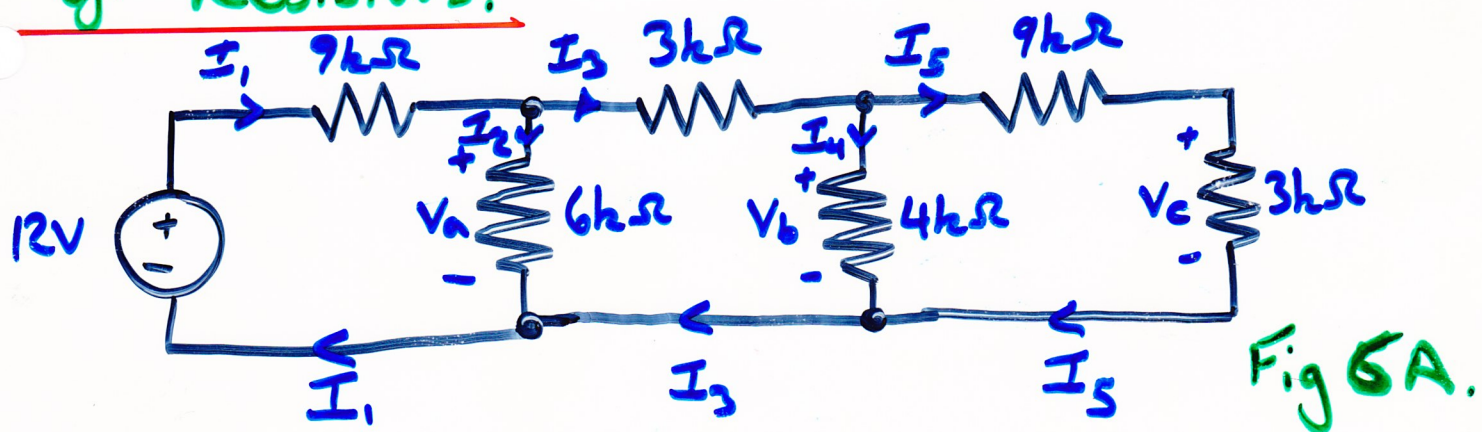
## Circuits with Series-Parallel Combination of Resistors.



Using Fig. 6C

$$I_1 = 12 / (9 + 3)k = \underline{1mA}$$

$$V_a = 1 \times 10^{-3} \times 3 \times 10^3 = \underline{3V}$$

$$I_2 = 3 / 6k = \underline{0.5mA}$$



Using Fig 6B and KCL

$$I_3 = 1\text{mA} - 0.5\text{mA} = 0.5\text{mA}$$

$$V_b = 0.5 \times 10^{-3} \times 3 \times 10^3 = 1.5\text{V}$$

Using fig 6A and Ohm's Law

$$\begin{aligned} I_4 &= 1.5 / 4\text{k} \\ &= 3/8\text{mA} \end{aligned}$$

Using KCL



$$\begin{aligned} I_5 &= \frac{1}{2} - \frac{3}{8}\text{mA} \\ &= \frac{1}{8}\text{mA} \end{aligned}$$

$$\begin{aligned} \therefore V_c &= \frac{1}{8}\text{mA} \times 3\text{k}\Omega \\ &= 3/8\text{V} \end{aligned}$$

---
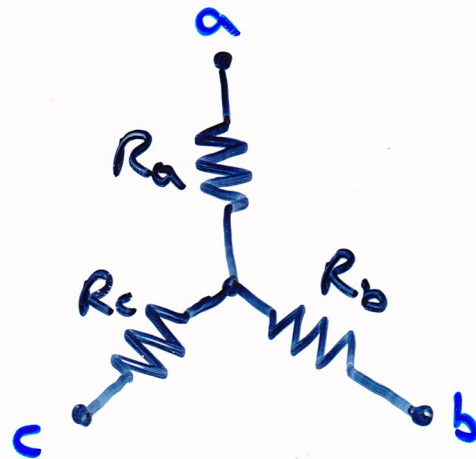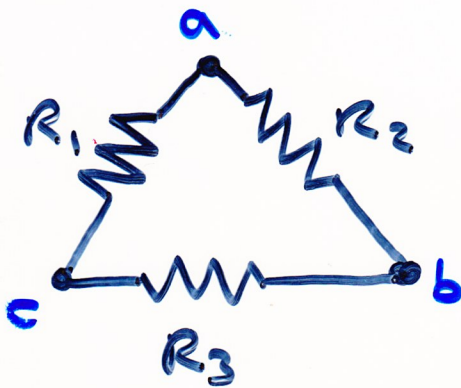
# $\gamma \rightleftharpoons \Delta$ Transformations

Here exploring relationships/equivalency between circuits of the form.



$$R_{ab} = R_a + R_b = \frac{R_2 (R_1 + R_3)}{R_2 + R_1 + R_3}$$

$$R_{bc} = R_b + R_c = \frac{R_3 (R_1 + R_2)}{R_3 + R_1 + R_2}$$

$$R_{ca} = R_c + R_a = \frac{R_1 (R_2 + R_3)}{R_1 + R_2 + R_3}$$

Solving the simultaneous equations

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

Similarly

$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b}$$



$$R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a}$$



## Example

(Irwin e.g. 2.22) [2.26]

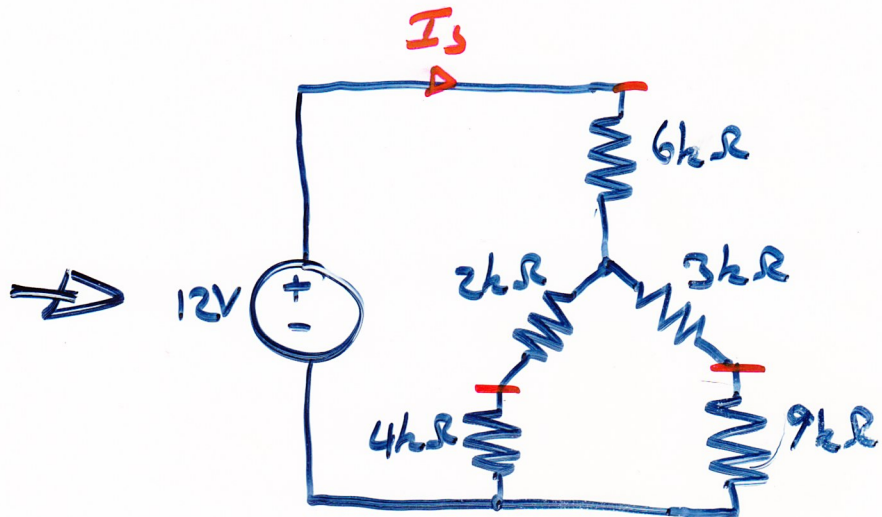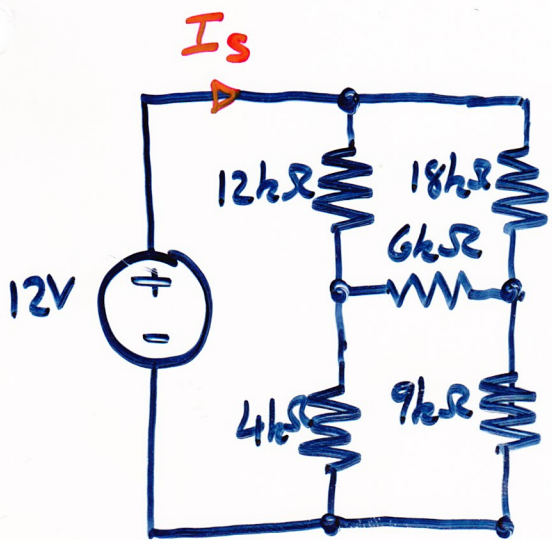

Have  $6\text{k}\Omega$  and  $12\text{k}\Omega$  in parallel.

$$R_{\text{para}} = \frac{12 \times 6 \text{ k}\Omega}{6 + 12} = \frac{12 \text{ k}\Omega}{3} = \underline{4\text{k}\Omega}$$

$$\begin{aligned} \therefore I_s &= 12 / (6 + 4) \text{ k} \\ &= 1.2 \text{ mA.} \end{aligned}$$