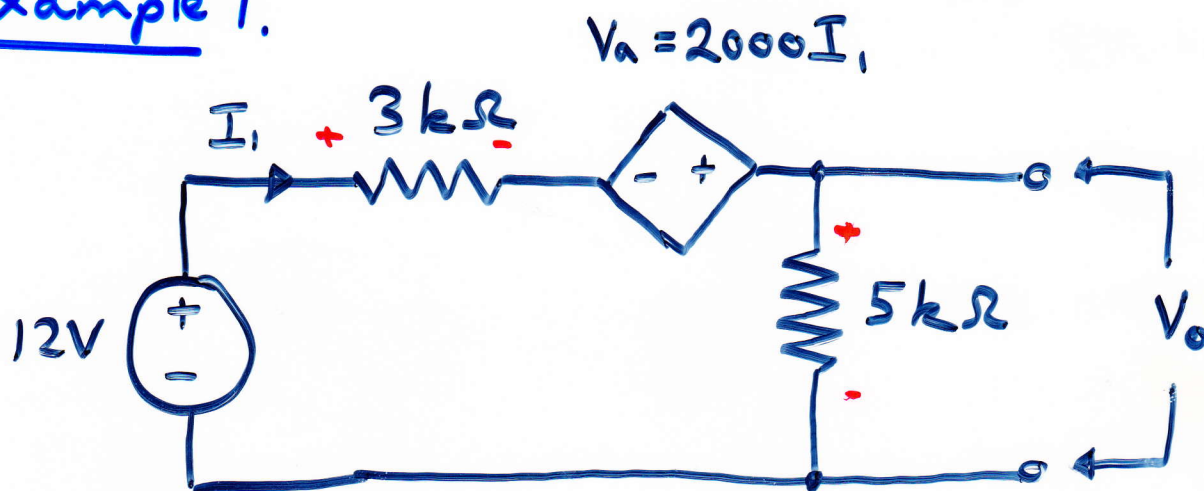


# Circuits with Dependent Sources.

## Example 1.



Determine  $V_0$ .

Apply KVL

$$-12 + I_1 3 \times 10^3 - V_a + 5 \times 10^3 I_1 = 0$$

$$-12 + I_1 3 \times 10^3 - 2000 I_1 + 5 \times 10^3 I_1 = 0$$

$$\therefore I_1 (3 \times 10^3 - 2 \times 10^3 + 5 \times 10^3) = 12$$


$$I_1 = \frac{12}{6 \times 10^3} = \underline{2 \text{ mA}}$$

$$\begin{aligned} \therefore V_0 &= 2 \times 10^{-3} \times 5 \times 10^3 \\ &= \underline{10 \text{ V}} \end{aligned}$$

# Strategy to Problem Solving:

1. Write KVL and/or KCL equations, treating dependent sources as independent sources.
2. Write equation that specifies the relationship of the dependent source to the controlling parameter.
3. Solve equations for unknown.


## Example 2

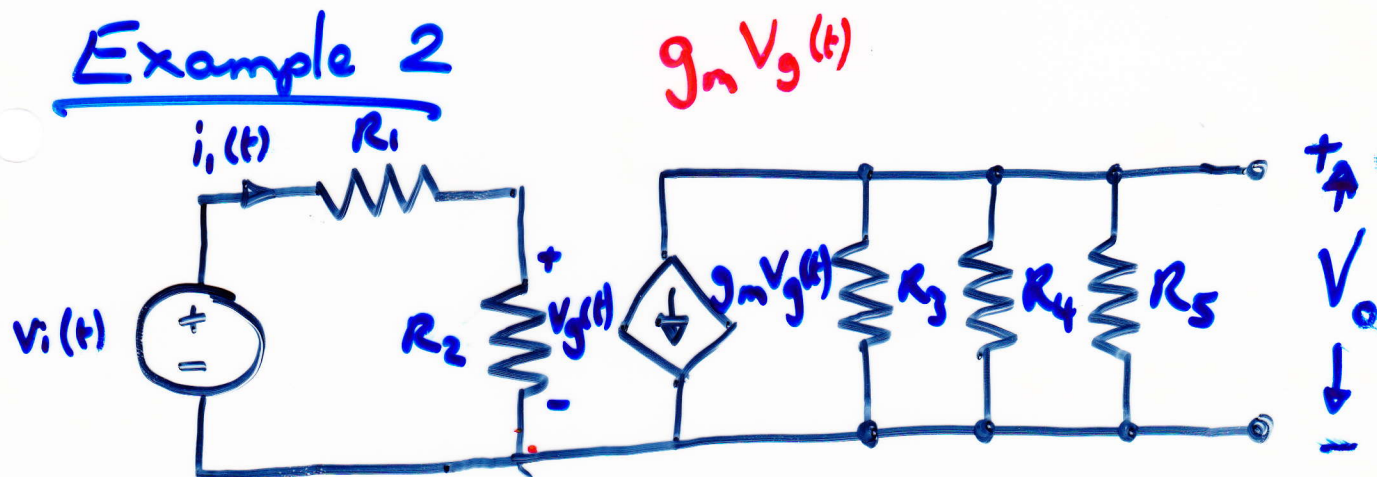

Equivalent circuit for FET common-source amp or BJT common-emitter amp.

Determine an expression for the gain of the amp (i.e.  $V_{out}/V_{in}$ ).

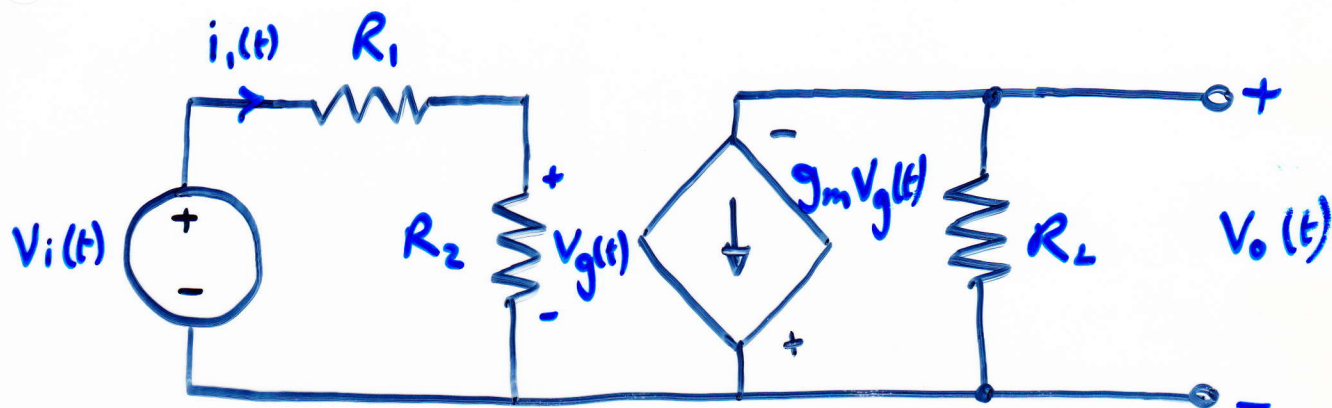Combine  $R_3$ ,  $R_4$  &  $R_5$  into an equivalent resistance, often called a load resistance.



$$\text{So } \frac{1}{R_L} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}$$

Apply KVL to input section of the circuit

$$\begin{aligned} V_i(t) &= i_1(t) R_1 + i_1(t) R_2 = i_1(t) (R_1 + R_2) \\ &= i_1(t) R_1 + V_g(t) \end{aligned}$$

$$\text{But } i_1(t) = V_i(t) / (R_1 + R_2)$$

$$\therefore V_g(t) = \frac{R_2}{(R_1 + R_2)} V_i(t) \quad \left\{ - (7.1) \right.$$

At the output side

$$V_o = -g_m V_g(t) R_L$$

*i/p* ~~~~~  
*o/p* ~~~~~



Substituting in (7.1) gives

$$V_o = -g_m R_2 \frac{V_i(t) R_L}{(R_1 + R_2)}$$

$$\therefore \frac{V_o(t)}{V_i(t)} = -\frac{g_m R_L R_2}{(R_1 + R_2)}$$

Considering some values

$$R_1 = 100 \Omega, R_2 = 1 k\Omega, g_m = 0.045 S$$

$$R_3 = 50 k\Omega, R_4 = R_5 = 10 k\Omega$$


$$\frac{1}{R_L} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} = \frac{1}{50k} + \frac{1}{10k} + \frac{1}{10k}$$

$$= \frac{1+5+5}{50k}$$

$$R_L = \frac{50k}{11} = 4.55 k\Omega$$

$$\begin{aligned} \text{So } \frac{V_o(t)}{V_i(t)} &= \frac{-0.045 \times 4.55 \times 10^3 \times 1 \times 10^3}{(100 + 1000)} = \frac{-0.045 \times 4.55 \times 10^3}{1.1} \\ &= \underline{\underline{-165.45}} \quad \checkmark \checkmark \end{aligned}$$

Example (Irwin extension) E 2.18

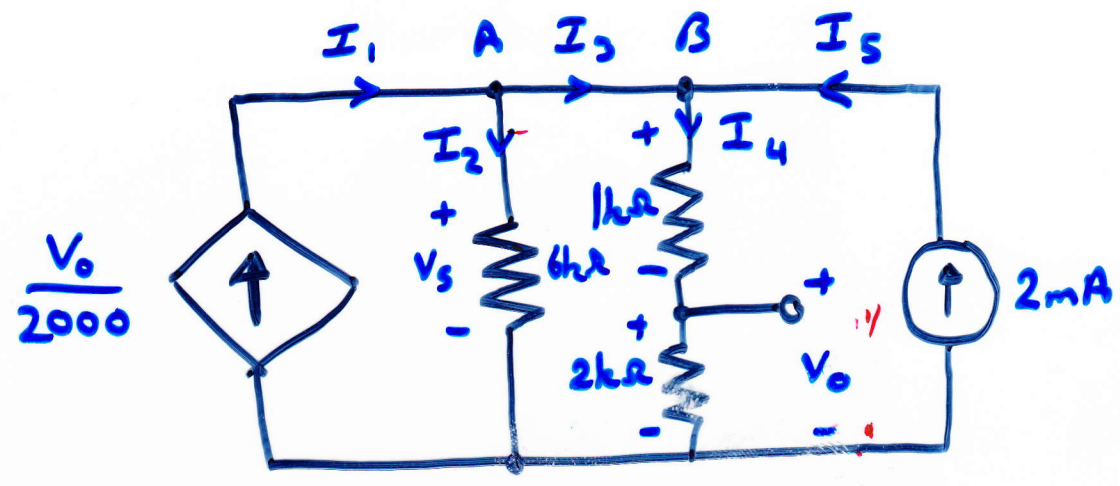

$$I_1 = V_0 / 2000 \text{ A}$$

$$I_5 = 2 \text{ mA}$$

Apply KCL at node A.

$$V_0 / 2000 = I_2 + I_3 \quad -(1)$$

KCL at node B

$$2 \text{ mA} + I_3 = I_4 \quad -(2)$$

Also

$$I_4 = V_0 / 2000 \quad -(3)$$

$$V_5 = I_2 \times 6 \text{ k}\Omega$$

$$V_0 = \frac{2}{3} V_5$$

Sub (3) into (2)

$$2 \times 10^{-3} + I_3 = V_0 / 2000$$

Compare this with (i)

Can see

$$I_2 = 2 \times 10^{-3} \text{ A}$$

$$\therefore V_s = 6 \text{ k}\Omega \times 2 \text{ mA} \\ = 12 \text{ V}$$


$$\text{So } V_o = \frac{2}{3} V_s = \frac{2}{3} \times 12$$

$$\therefore \underline{V_o = 8 \text{ V}}$$

# Nodal Analysis.

In this type of analysis the variables are the node voltages, with one node being selected as a reference node. The other nodes in the circuit are defined with respect to this node.

## Example 1.

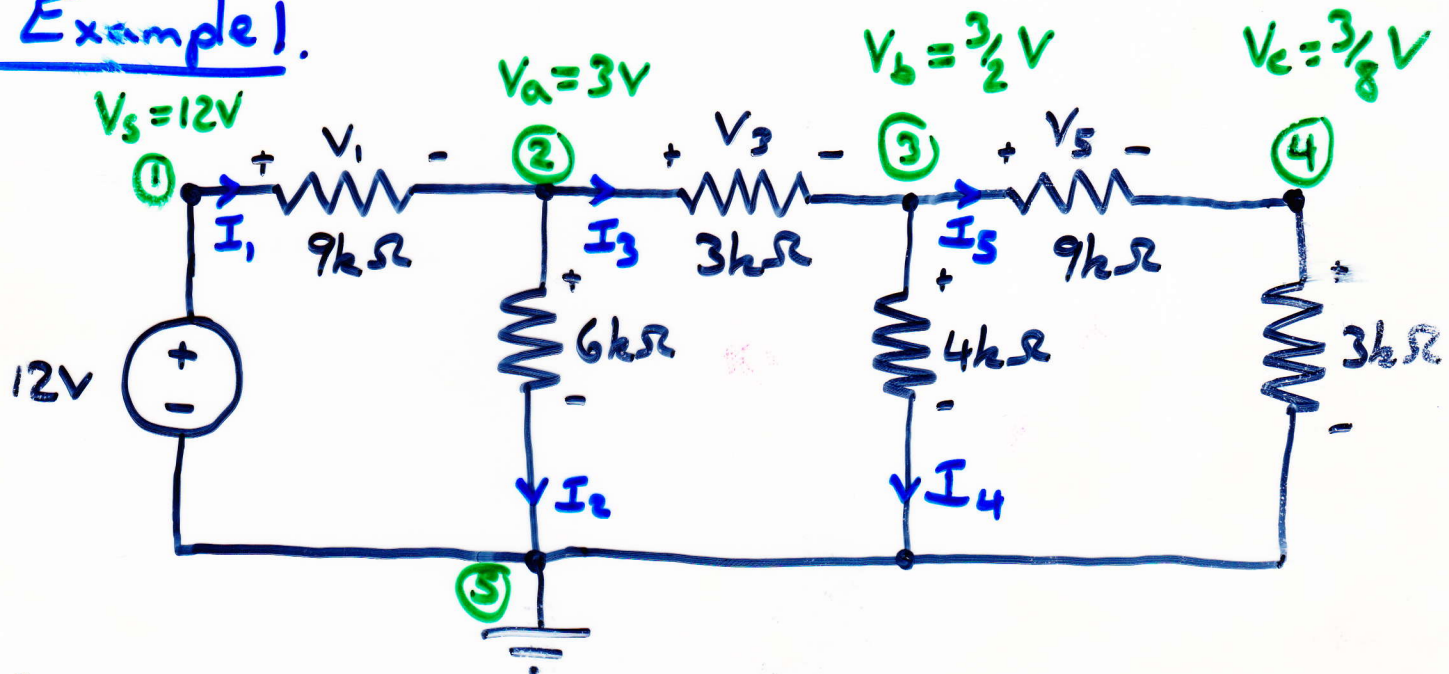

(Circuit was examined previously in lecture 4 - series and parallel resistors).

$V_s, V_a, V_b$  and  $V_c$  are measured w.r.t. node 5, which is labeled the ground.



Knowing the nodal voltages we can determine the branch currents and hence the power in each element.

For example consider the left most  $9k\Omega$  resistor

$$\begin{aligned} V_1 &= V_s - V_a \\ &= 12V - 3V \\ &= 9V \end{aligned}$$

$$\begin{aligned} \therefore I_1 &= \frac{V_s - V_a}{9k\Omega} = \frac{9}{9k} \\ &= \underline{1mA}. \end{aligned}$$

Similarly,

$$I_2 = \frac{V_a - 0}{6k} = \frac{3}{6k} = \underline{\frac{1}{2}mA}$$

$$I_3 = \frac{V_a - V_b}{3k\Omega} = \frac{3 - 3/2}{3k} = \frac{3/2}{3k} = \underline{\frac{1}{2}mA}$$




$$I_4 = \frac{V_b - 0}{4k} = \frac{\frac{3}{2} - 0}{4k} = \underline{\underline{\frac{3}{8} \text{ mA}}}$$

$$I_5 = \frac{V_b - V_c}{9k} = \frac{\frac{3}{2} - \frac{3}{8}}{9k} = \frac{\frac{9}{8}}{9k} = \underline{\underline{\frac{1}{8} \text{ mA}}}$$

## Example 2.

Example 3-1.

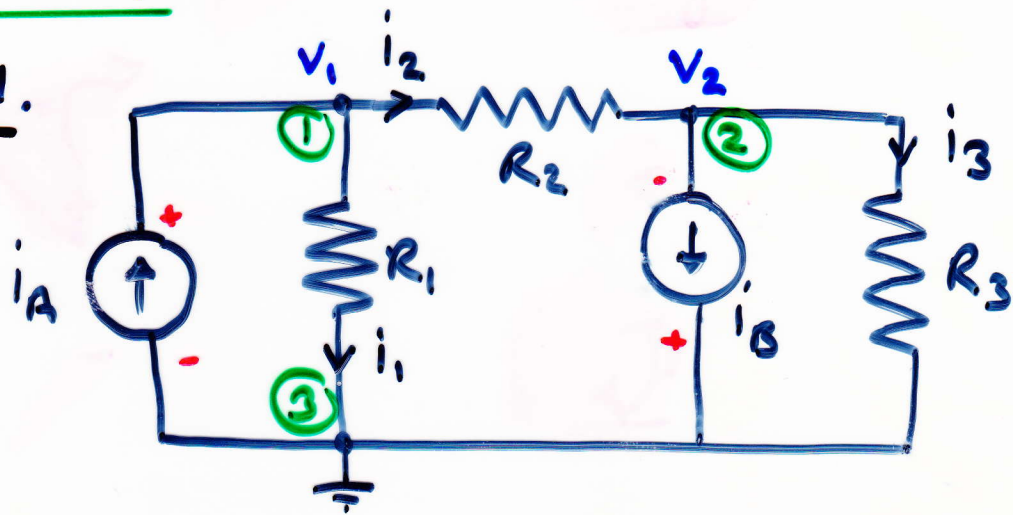

Applying KCL at node ①

$$-i_A + i_1 + i_2 = 0$$

Using Ohm's law,  $i = Gv$

$$-i_A + G_1(v_1 - 0) + G_2(v_1 - v_2) = 0$$

$$V_1(G_1 + G_2) - G_2 V_2 = i_A \quad *$$

KCL at node 2 gives

$$-i_2 + i_B + i_3 = 0$$

Again using Ohm's Law

$$-G_2(V_1 - V_2) + i_B + G_3(V_2 - 0) = 0$$

$$-G_2 V_1 + (G_2 + G_3) V_2 = -i_B \quad *$$

So we have 2 equations for two unknown voltages.

$$V_1(G_1 + G_2) - G_2 V_2 = i_A$$

$$-V_1 G_2 + (G_2 + G_3) V_2 = -i_B$$

Solution of the simultaneous equations can be done by Gaussian elimination or matrix methods. By way of example let us consider the following values.

$$I_A = 1\text{mA}, R_1 = 12\text{k}\Omega, R_2 = \underline{6\text{k}\Omega}, I_B = 4\text{mA} \text{ \& } R_3 = 6\text{k}\Omega$$

## Gaussian elimination

$$V_1 \left( \frac{1}{12k} + \frac{1}{6k} \right) - V_2 \left( \frac{1}{6k} \right) = 1 \times 10^{-3}$$

$$-V_1 \left( \frac{1}{6k} \right) + V_2 \left( \frac{1}{6k} + \frac{1}{6k} \right) = -4 \times 10^{-3}$$

So have:

$$\frac{V_1}{4k} - \frac{V_2}{6k} = 1 \times 10^{-3}$$

$$-\frac{V_1}{6k} + \frac{V_2}{3k} = -4 \times 10^{-3}$$

Now

$$V_1 = V_2 \left( \frac{2}{3} \right) + 4 \quad \text{--- (8.1)}$$

$$\therefore -\frac{1}{6k} \left( \frac{2}{3} V_2 + 4 \right) + \frac{V_2}{3k} = -4 \times 10^{-3}$$

$$\text{Or } \underline{V_2 = -15V}$$

Sub. back into (8.1) gives

$$V_1 = -15 \left( \frac{2}{3} \right) + 4$$

$$\underline{V_1 = -6V}$$

Using matrix equations

$$GV = I$$

$$G = \begin{bmatrix} \frac{1}{4k} & -\frac{1}{6k} \\ -\frac{1}{6k} & \frac{1}{3k} \end{bmatrix}, V = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \& I = \begin{bmatrix} 1 \times 10^{-3} \\ -4 \times 10^{-3} \end{bmatrix}$$

Matrix solution

$$V = G^{-1} I$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{4k} & -\frac{1}{6k} \\ -\frac{1}{6k} & \frac{1}{3k} \end{bmatrix}^{-1} \begin{bmatrix} 1 \times 10^{-3} \\ -4 \times 10^{-3} \end{bmatrix}$$

$$A = \begin{bmatrix} a & b \\ c & d \end{bmatrix}$$

Need  $G^{-1}$ .

$$\text{Adj } G = \begin{bmatrix} \frac{1}{3k} & \frac{1}{6k} \\ \frac{1}{6k} & \frac{1}{4k} \end{bmatrix}$$

$$\text{Adj } A = \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

and determinant,

$$\begin{aligned} |G| &= \left(\frac{1}{3k}\right)\left(\frac{1}{4k}\right) - \left(-\frac{1}{6k}\right)\left(-\frac{1}{6k}\right) \\ &= \frac{1}{18k^2} \end{aligned}$$



8.7

$$\therefore \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = 18k^2 \begin{bmatrix} \frac{1}{3k} & \frac{1}{6k} \\ \frac{1}{6k} & \frac{1}{4k} \end{bmatrix} \begin{bmatrix} 1 \times 10^{-3} \\ -4 \times 10^{-3} \end{bmatrix}$$


Adj(G)  
151

$$= 18k^2 \begin{bmatrix} \frac{1}{3k^2} & -\frac{4}{6k^2} \\ \frac{1}{6k^2} & -\frac{1}{k^2} \end{bmatrix}$$

$$= \begin{bmatrix} -6 \\ -15 \end{bmatrix}$$

Could use Matlab, see Irwin p ~~70~~<sup>101</sup>

Example

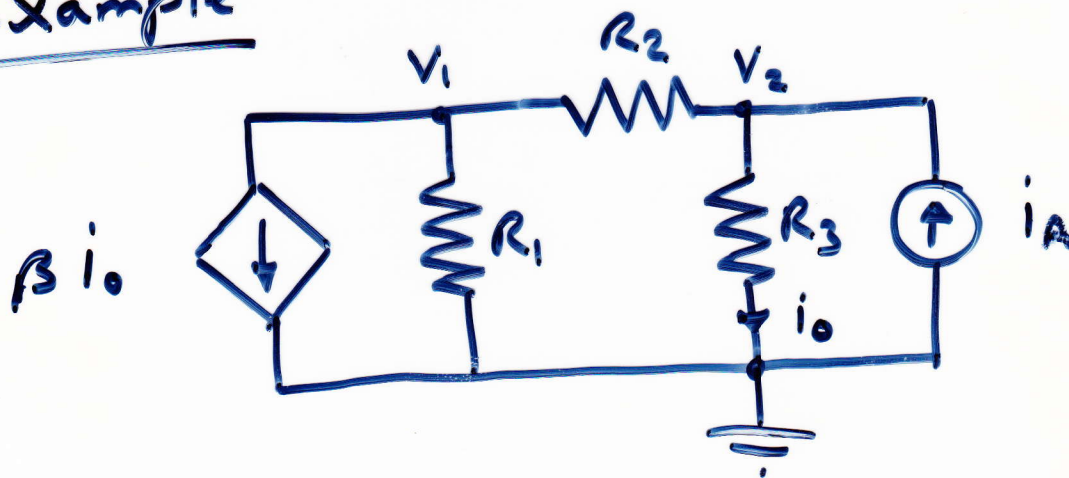

Equations for non-reference nodes:

$$\beta i_o + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_2 - V_1}{R_2} + i_o - i_A = 0$$

Where  $i_o = V_2 / R_3$

Simplifying  $(G_1 + G_2)V_1 - (G_2 - \beta G_3)V_2 = 0$  (8.2)

$$-G_2 V_1 + (G_2 + G_3)V_2 = i_A$$
 (8.3)

If  $\beta = 2$ ,  $R_2 = 6k\Omega$ ,  $i_A = 2mA$ ,  $R_1 = 12k\Omega$   
and  $R_3 = 3k\Omega$

Then 8.2 becomes

$$\left(\frac{1}{12k} + \frac{1}{6k}\right)V_1 - \left(\frac{1}{6k} - \frac{2 \times 1}{3k}\right)V_2 = 0$$

$$\frac{1}{4k} V_1 + \frac{1}{2k} V_2 = 0$$
 (8.4)

And 8.3 becomes

$$-\frac{1}{6h}V_1 + \left(\frac{1}{6h} + \frac{1}{3h}\right)V_2 = 2 \times 10^{-3}$$

$$-\frac{1}{6h}V_1 + \frac{1}{2h}V_2 = 2 \times 10^{-3} \quad (8.5)$$

Subtract (8.5) from (8.4)

$$V_1 \left( \frac{1}{4h} + \frac{1}{6h} \right) = -2 \times 10^{-3}$$

$$V_1 \left( \frac{5}{12h} \right) = -2 \times 10^{-3}$$

$$V_1 = -\frac{24}{5}V$$

Sub. for  $V_1$  into (8.4)

$$-\frac{1}{4h} \times \frac{24}{5} + \frac{1}{2h}V_2 = 0$$

$$V_2 = \frac{12}{5}V$$


---