

# Thévenin & Norton's Theorems.



## Introduction to the theorems.

Two powerful and useful techniques for circuit analysis.


Principles are:

**Thévenin's theorem:-** can replace an entire network, exclusive of the load, by an equivalent circuit containing only an independent voltage source in series with a resistor in such a way that the current-voltage relationship at the load is unchanged.

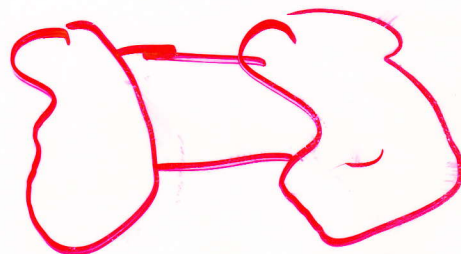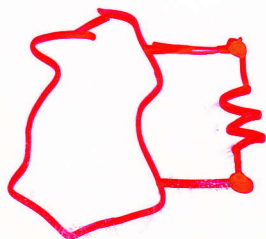
**Norton's theorem:-** identical to above but the equivalent circuit is an independent current source in parallel with a resistor.



Consider ...

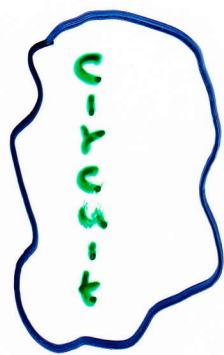


(a)

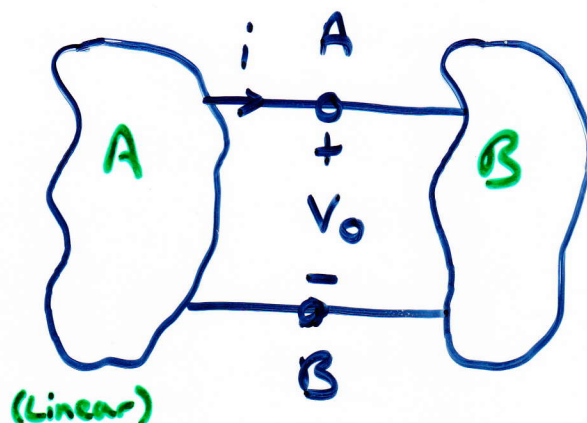

(Linear)

(b)

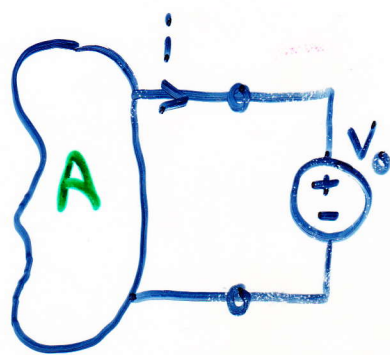


(c)

Applying principle of superposition with (c)

$$i = i_0 + i_{sc}$$

$i_0$  = current due to  $V_0$

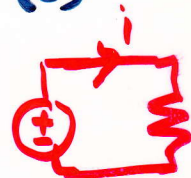$i_{sc}$  = short-circuited current due to all sources in circuit A. ( $V_0$  replaced by short-circuit)



Also 
$$i_0 = \frac{-V_0}{R_{Th}}$$

$R_{Th}$  = equivalent resistance looking back in circuit A from terminals A-B (all independent sources in A made zero).

$$\therefore i = \frac{-V_0}{R_{Th}} + i_{sc} \quad (11.1)$$

Consider specific case of  $i=0$  and so  $V_o$  is the open-circuit voltage.

$$i = 0 = -\frac{V_{oc}}{R_{Th}} + i_{sc}$$




$$\therefore V_{oc} = R_{Th} i_{sc}$$

So can now write

$$i = \frac{-V_o}{R_{Th}} + \frac{V_{oc}}{R_{Th}}$$

$$\therefore \underline{V_o = V_{oc} - R_{Th} i}$$


This equation equates to

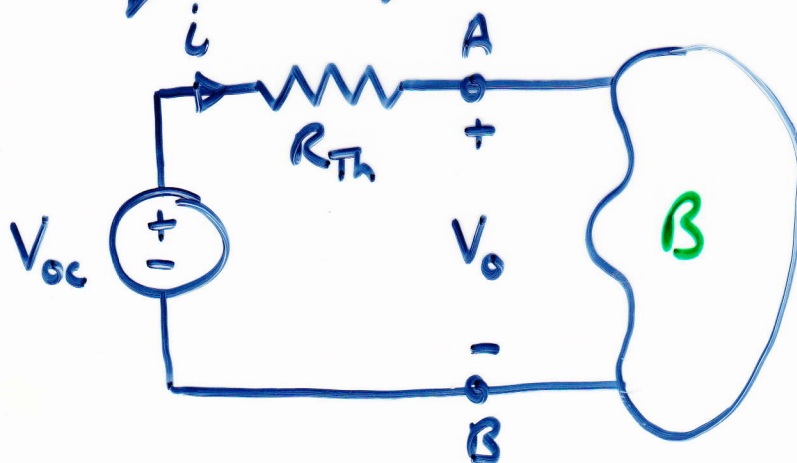





Look at (11.1) can see we have
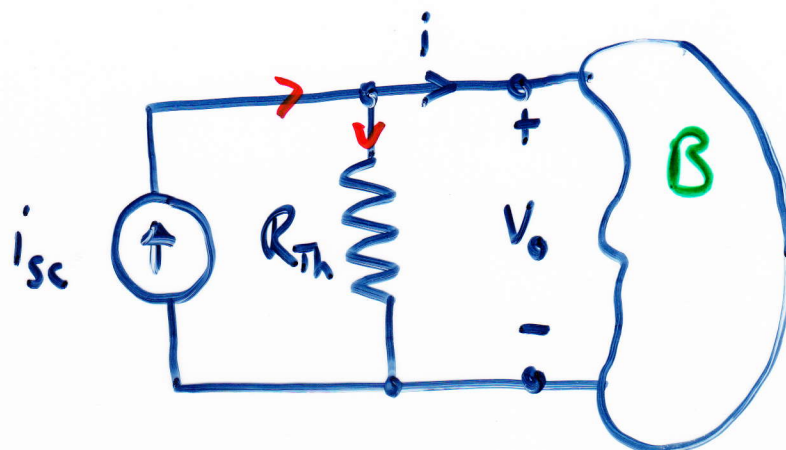
$$\left\{ i = \frac{-V_o}{R_{Th}} + i_{sc} \quad (11.1) \right\}$$




Note the interchangeability ...

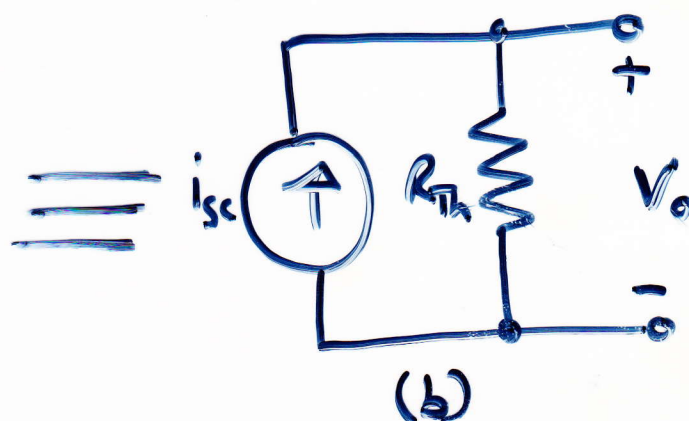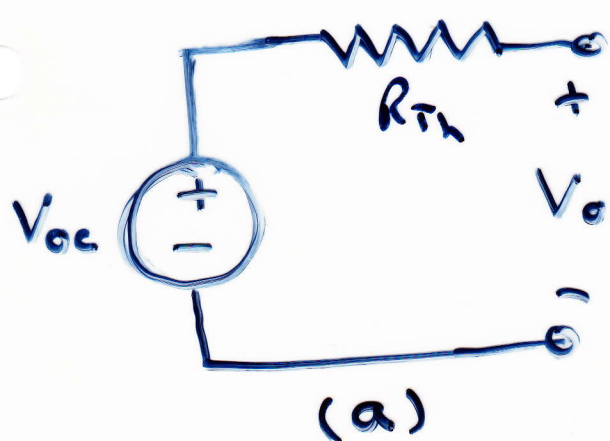

This equivalence is ONLY at the external nodes, e.g. (b) dissipate power, (a) does not.


# Examples

①

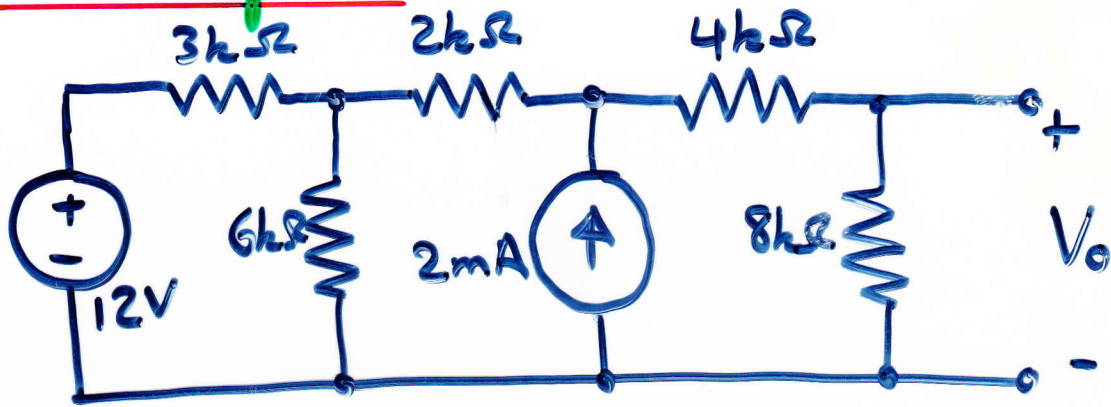


Simplify L.H.S.

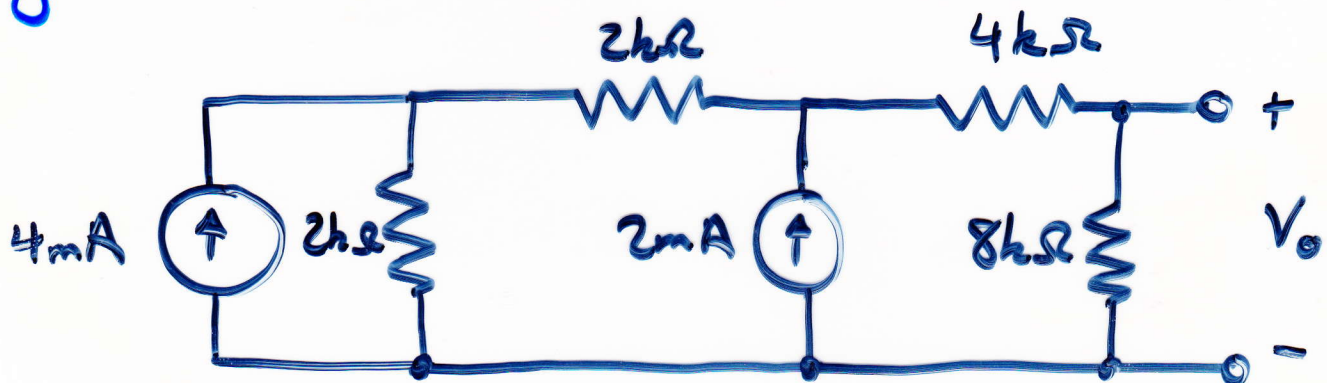
$3k\Omega$  resistor and 12V supply give 4mA current source and  $3k\Omega$  resistor in parallel. Combining  $3k\Omega$  and  $6k\Omega$  in parallel we get...



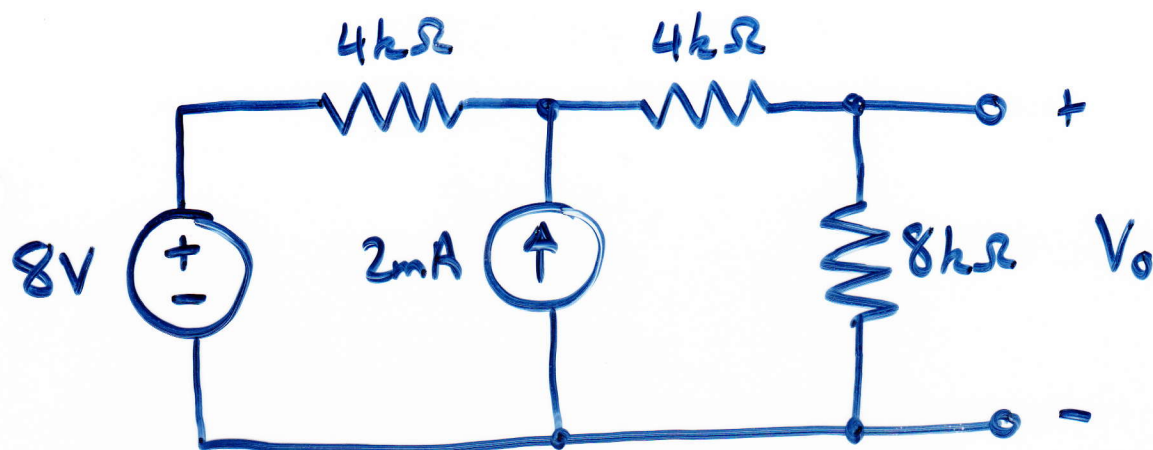Convert current source to voltage source.  
Combine the resulting series resistors.



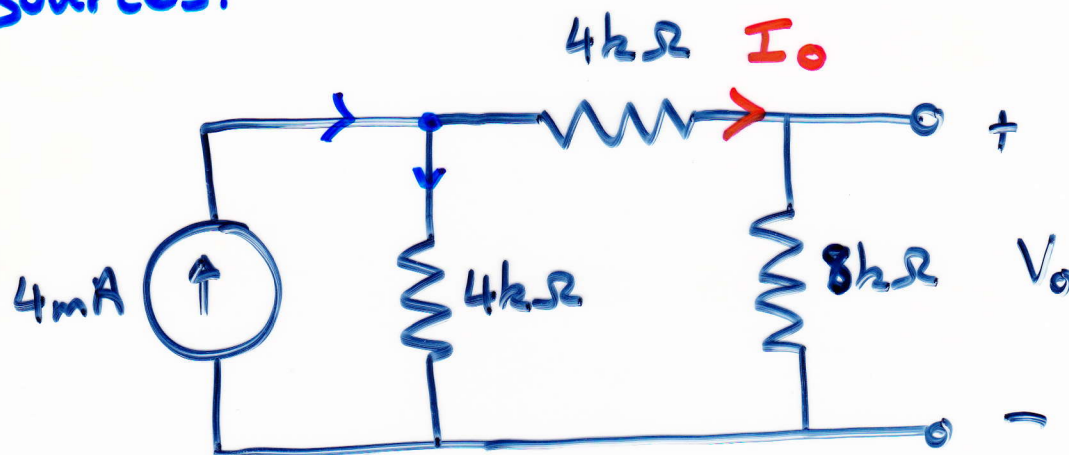Converting again AND combining current sources.




To find  $I_o$  use current division

$$I_o = 4 \text{ mA} \times \left( \frac{4 \text{ k}}{4 \text{ k} + (4 \text{ k} + 8 \text{ k})} \right)$$


$$\underline{I_o = 1 \text{ mA}}$$

$$\therefore V_o = 1 \times 10^{-3} \times 8 \text{ k} = \underline{\underline{8 \text{ V}}}$$

②

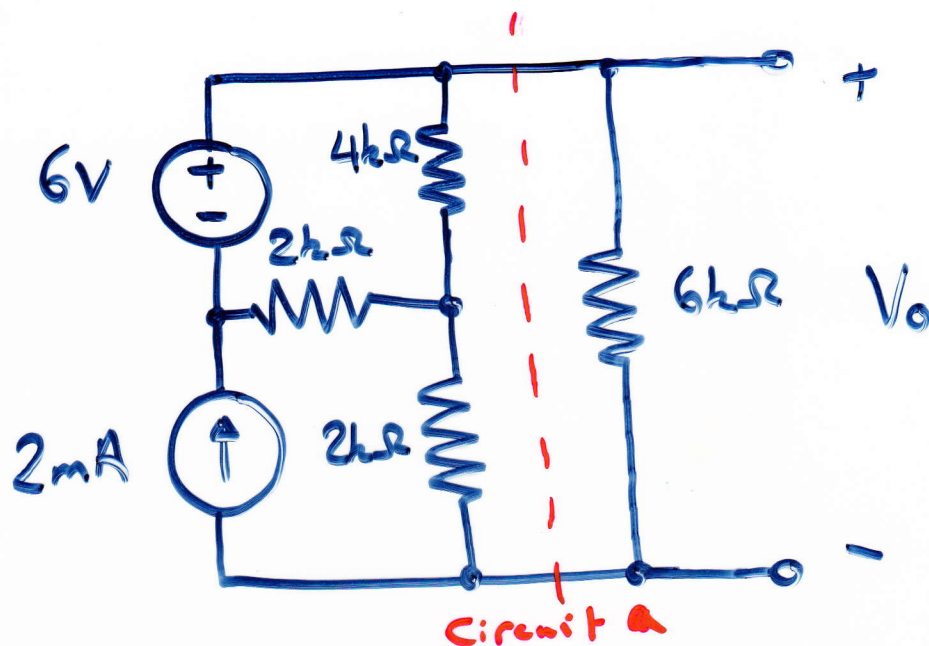

Consider L.H.S of dashed line.

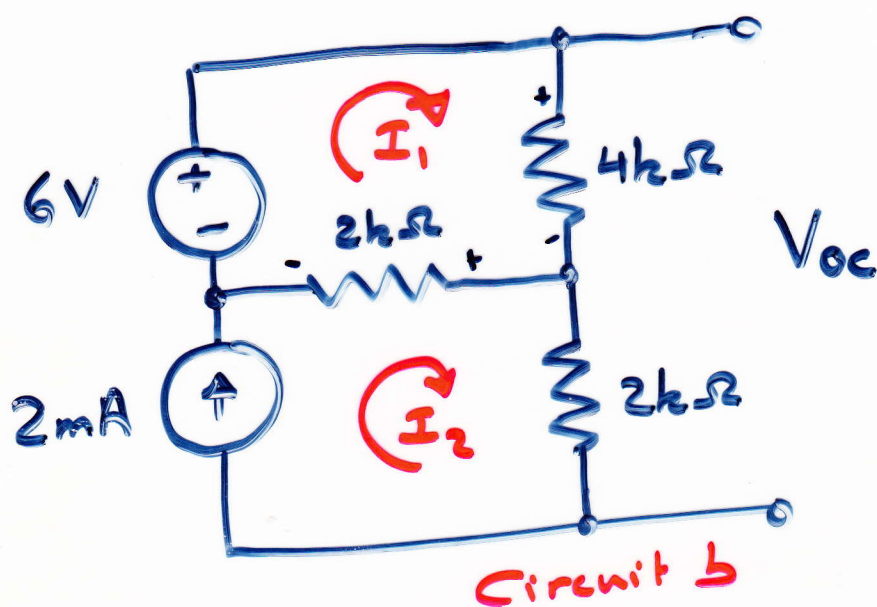

$$I_2 = 2\text{mA}$$

$$-6 + 4kI_1 + 2k(I_1 - I_2) = 0$$


$$\therefore 6kI_1 = 6 + 4$$

$$I_1 = \frac{5}{3} \text{ mA}$$



$$\begin{aligned}
 V_{oc} &= 4k \times \frac{5}{3} \times 10^{-3} + 2k \times 2 \times 10^{-3} \\
 &= \frac{20}{3} + 4 = \underline{\underline{\frac{32}{3} \text{ V}}}
 \end{aligned}$$


The Thévenin resistance of circuit b is

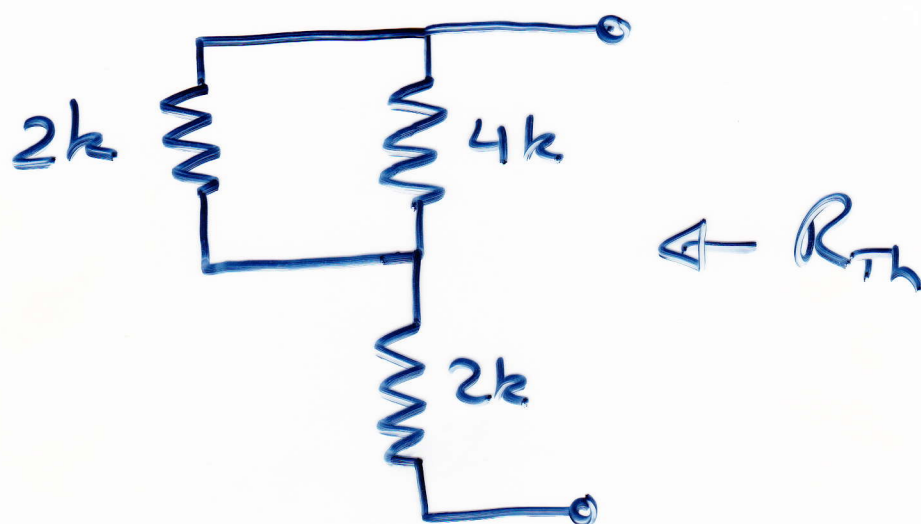


$$\begin{aligned}
 R_{Th} &= \frac{2 \times 4}{4 + 2} k + 2k = \frac{8k}{6} + 2k \\
 &= \underline{\underline{\frac{10}{3} k\Omega}}
 \end{aligned}$$



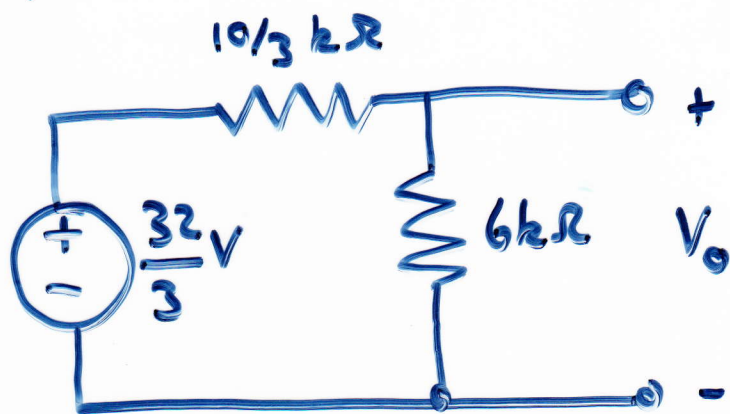Know voltage and  $R_{Th}$ , so redrawing original circuit (circuit a)



Alternatively

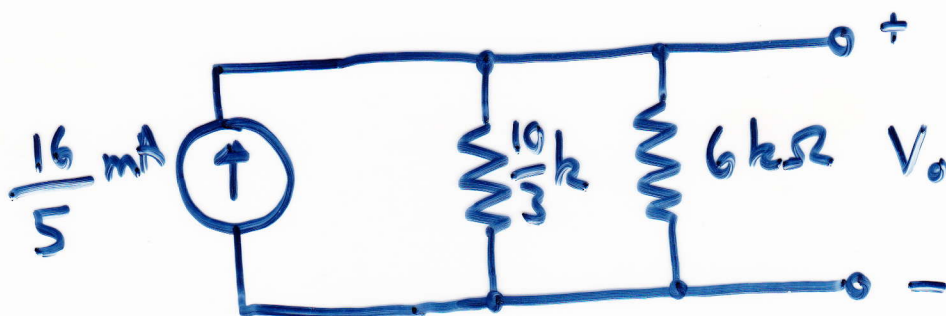

$$V_o = \frac{32}{3} \left( \frac{6}{6 + \frac{10}{3}} \right) = \frac{32}{3} \left( \frac{6}{\frac{28}{3}} \right)$$

$$= \frac{8}{32} \times \frac{6}{\frac{28}{3}}$$

$$= \underline{\underline{48}} V$$

