


Thevenin & Norton's Theorems II.

Circuits containing only dependent sources

For independent sources can calculate V_{oc} and i_{sc} and then R_{Th} . If circuit contains no independent sources, that is it has only dependent sources, there can be difficulties if introducing open or short circuits.


Approach : introduce a test source e.g. V_t or i_t and find either i_t or V_t , then determine $R_{Th} = V_t / i_t$. Easiest is to introduce a test value of 1V or 1A.

Example

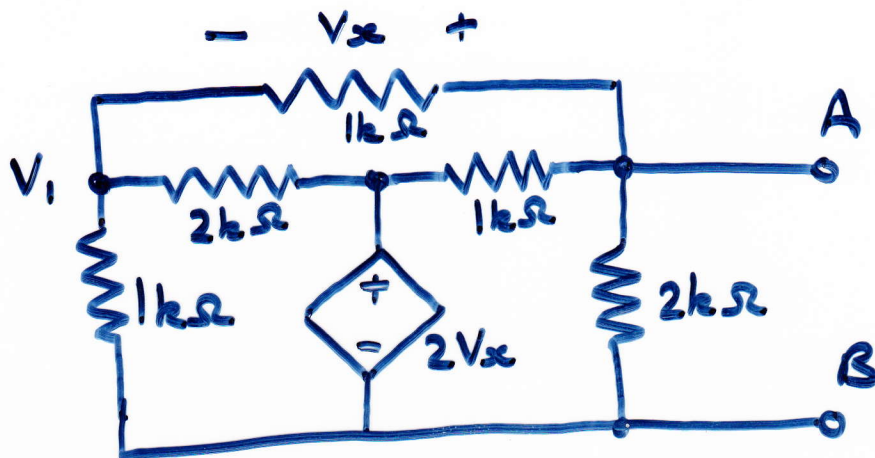

Thévenin equivalent at A-B.

Apply 1V across AB

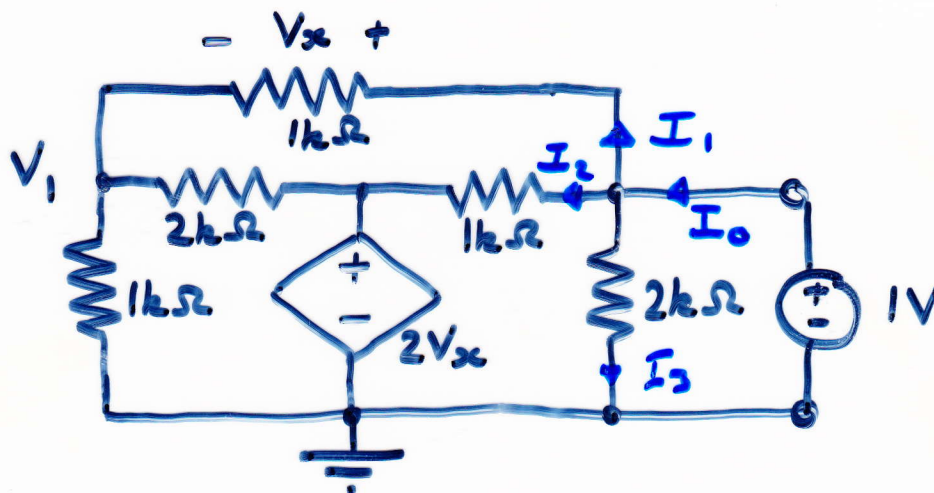

Apply KVL around outer loop

$$V_1 + V_{x} = 1$$

KCL at node labelled V_1

$$\frac{V_1}{1k} + \frac{V_1 - 2V_x}{2k} + \frac{V_1 - 1}{1k} = 0$$

Two simultaneous eqn. with two unknowns

$$\therefore \frac{1 - V_{oc}}{1k} + \frac{1 - 3V_{oc}}{2k} - \frac{V_{oc}}{1k} = 0$$

$$2 - 2V_{oc} + 1 - 3V_{oc} - 2V_{oc} = 0$$

$$7V_{oc} = 3$$

$$V_{oc} = 3/7 \text{ V}$$

$$\therefore I_1 = \frac{V_{oc}}{1k} = \frac{3}{7} \text{ mA}$$

$$I_2 = \frac{1 - 2V_{oc}}{1k} = \frac{1}{7} \text{ mA}$$

$$I_3 = \frac{1}{2k} = \frac{1}{2} \text{ mA}$$

$$\therefore I_o = I_1 + I_2 + I_3 = \frac{15}{14} \text{ mA}$$


$$R_{Th} = \frac{1}{I_o} = \frac{14}{15} \text{ k}\Omega$$

Ans.


Example 2

12.4

Determine R_{Th} at A-B.

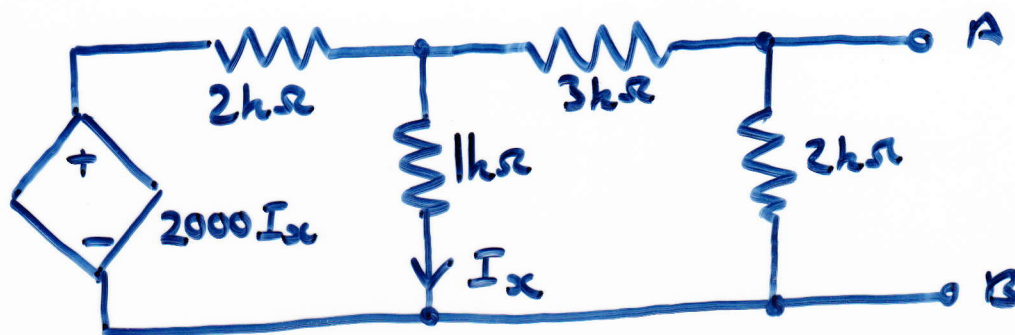

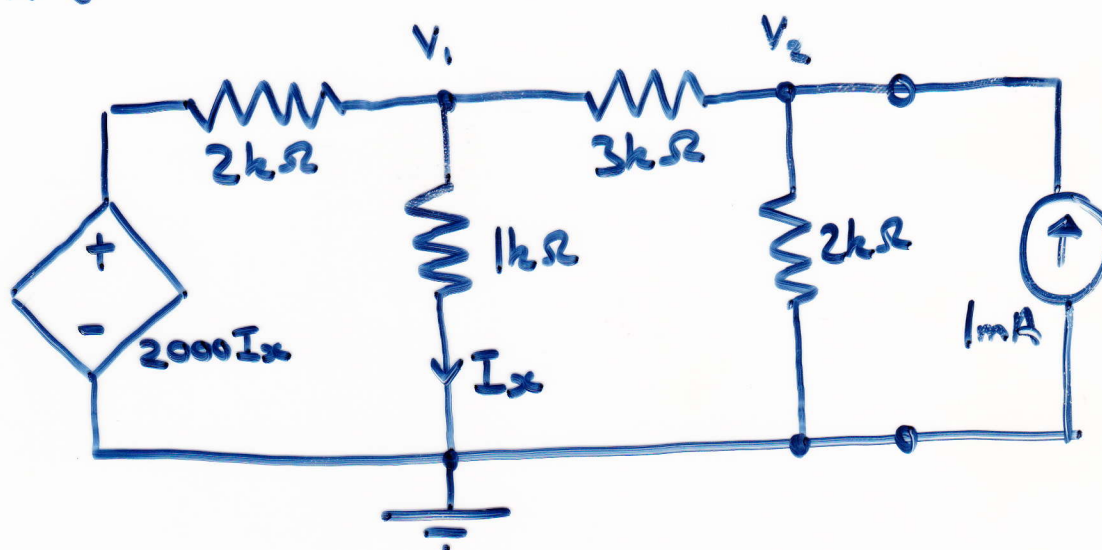Apply $1mA$ current source at terminals A-B



Node equations for the network are

$$\frac{V_1 - 2000I_x}{2k} + \frac{V_1}{1k} + \frac{V_1 - V_2}{3k} = 0 \quad (1)$$

$$\frac{V_2 - V_1}{3k} + \frac{V_2}{2k} = 1 \times 10^{-3} \quad (2)$$

$$I_x = \frac{V_1}{1k} \quad (3)$$

So from (2) $\frac{V_2}{3k} + \frac{V_2}{2k} = 1 \times 10^{-3} + \frac{V_1}{3k}$

$$\therefore \frac{5}{6k} V_2 = 1 \times 10^{-3} + \frac{V_1}{3k}$$

$$\text{So } V_2 = \frac{2}{5} V_1 + \frac{6}{5}$$

So (1) becomes

$$\frac{V_1 - 2000(V_1/1k)}{2k} + \frac{V_1}{1k} + \frac{V_1 - (2V_1 + 6)/5}{3k} = 0$$

$$\frac{V_1}{2} - \cancel{V_1} + \cancel{V_1} + \frac{V_1}{3} - \frac{2V_1}{15} - \frac{\cancel{6}}{\cancel{15}} \frac{2}{5} = 0$$

$$V_1 \left(\frac{1}{2} + \frac{1}{3} - \frac{2}{15} \right) = \frac{2}{5}$$

$$V_1 \left(\frac{15 + 10 - 4}{30} \right) = \frac{2}{5}$$

$$V_1 \left(\frac{\cancel{21}^7}{\cancel{30}_{10}} \right) = \frac{2}{5}$$

$$V_1 = \frac{2}{5} \times \frac{10}{7} = \frac{4}{7} \text{ V}$$

$$\text{So } V_2 = \frac{2}{5} \times \frac{4}{7} + \frac{6}{5}$$

$$= \frac{8}{35} + \frac{6}{5} = \frac{8 + 42}{35}$$


$$= \frac{50}{35} = \frac{10}{7} \text{ V}$$

$$\therefore R_{Th} = \left(\frac{10}{7} \right) / 1 \times 10^{-3} = \frac{10}{7} \text{ k}\Omega$$


Circuits with independent & dependent sources.

Calc. both the open-circuit voltage and short-circuit current, then calc. R_{Th} .

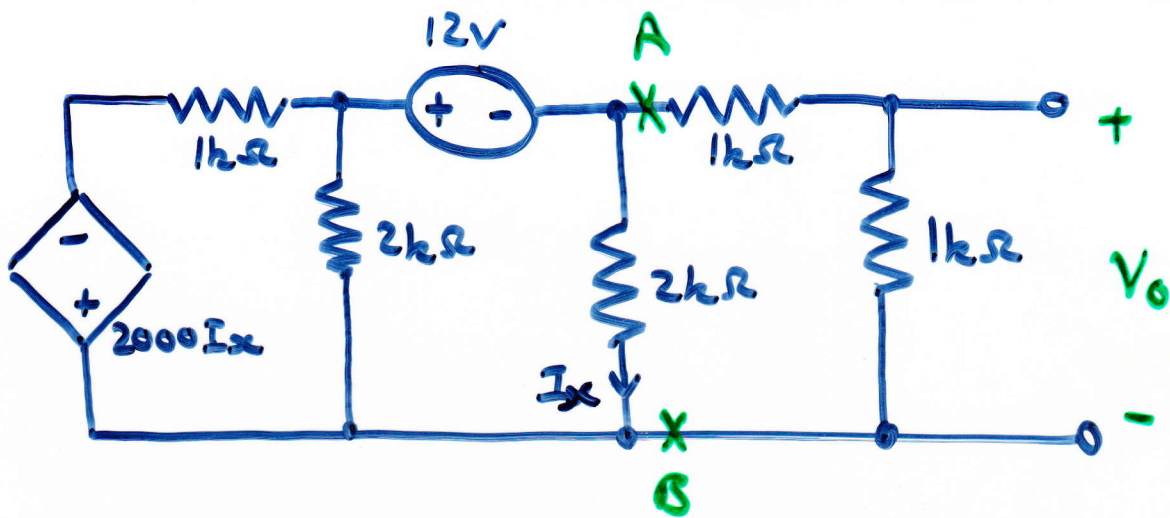Cannot split the dependent source and its controlling variable when finding T & N equivalent.



Break circuit at A B

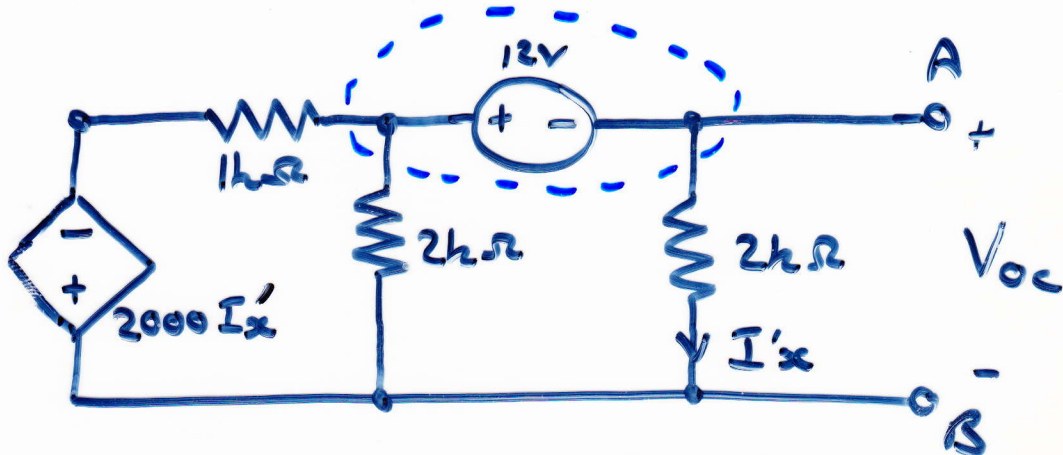

KCL for supernode around 12V source

$$\frac{(V_{oc} + 12) - (-2000 I'_x)}{1k} + \frac{V_{oc} + 12}{2k} + \frac{V_{oc}}{2k} = 0$$

Where $I'_x = \frac{V_{oc}}{2k}$

$$\frac{(V_{oc} + 12) + (\cancel{2000 V_{oc} / 2k})}{1k} + \frac{V_{oc} + 12}{2k} + \frac{V_{oc}}{2k} = 0$$


$$2V_{oc} + 12 + \frac{V_{oc}}{2} + 6 + \frac{V_{oc}}{2} = 0$$

$$3 V_{oc} = -18$$

$$V_{oc} = -6V$$



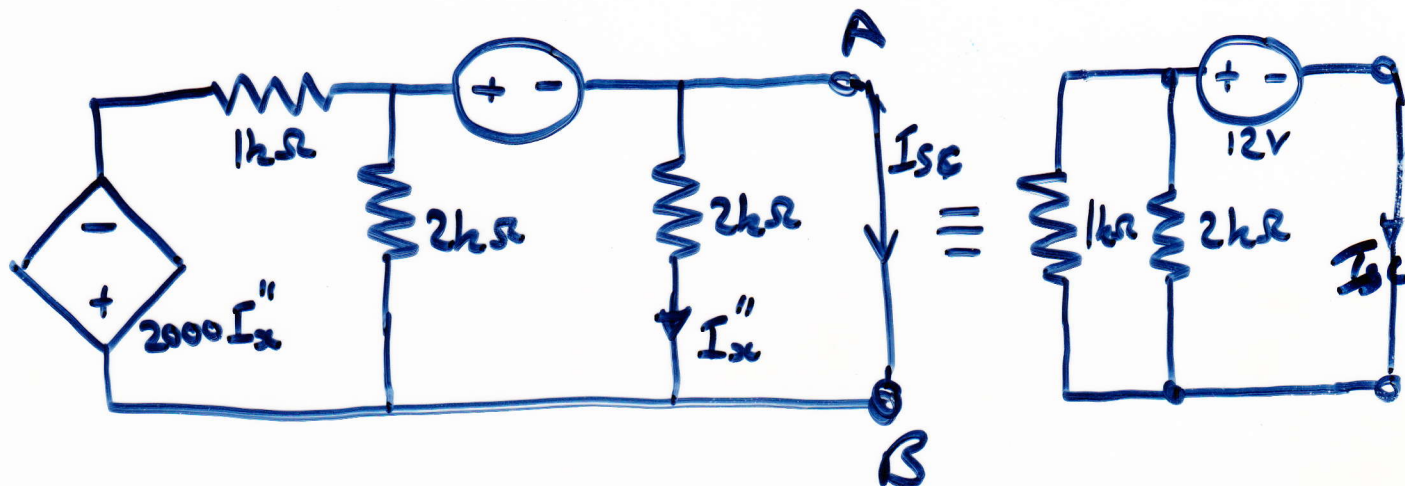
What about the short circuit current, I_{sc} ?



$$I_{sc} = \frac{-12}{2/3k} = -18mA$$

$$\therefore R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{-6}{-18 \times 10^{-3}} = \frac{1}{3}k\Omega$$

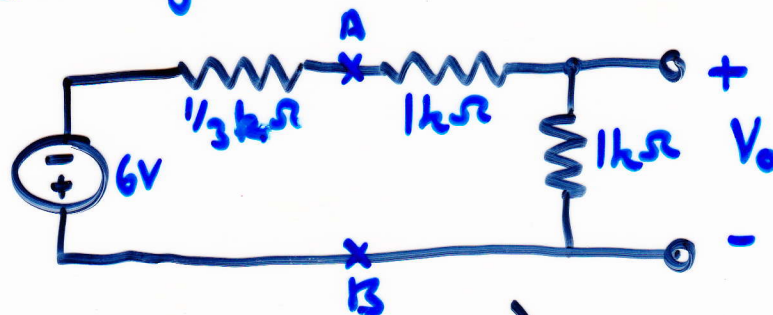
So connecting in the Thevenin eq. to the remainder of the network we have



$$V_o = (-6) \left(\frac{1k}{1/3k + 1k + 1k} \right) = -6 \times \frac{1}{7/3}$$

$$= -\frac{18V}{7}$$

Maximum Power Transfer.

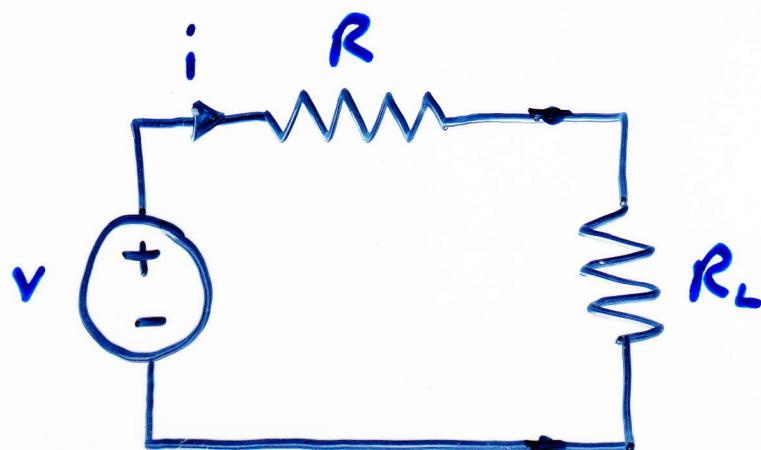

$$P_{\text{Load}} = i^2 R_L = \left(\frac{V}{R + R_L} \right)^2 R_L$$

What is the value of R_L that maximizes P_{Load} ?


$$\frac{dP_{\text{Load}}}{dR_L} = \frac{(R + R_L)^2 V^2 - 2V^2 R_L (R + R_L)}{(R + R_L)^4} = 0$$

Gives $R_L = R$


The above circuit is a very simple network. However, R and V represents the Thévenin equivalent circuit for a linear network.

Example

13.2

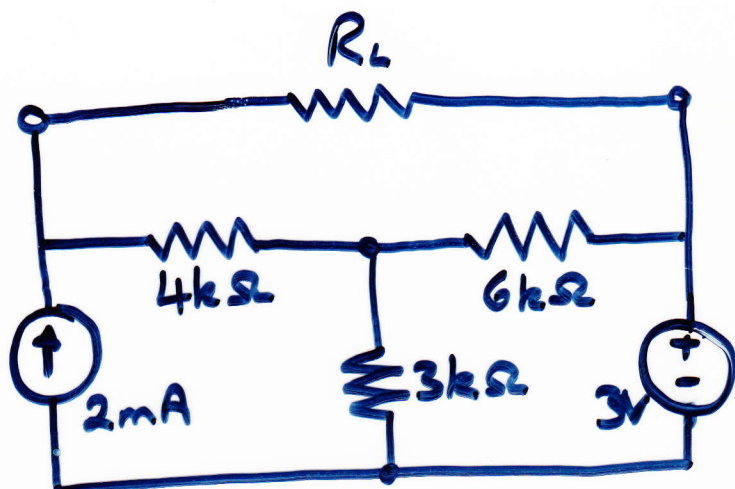

Determine V_{oc}

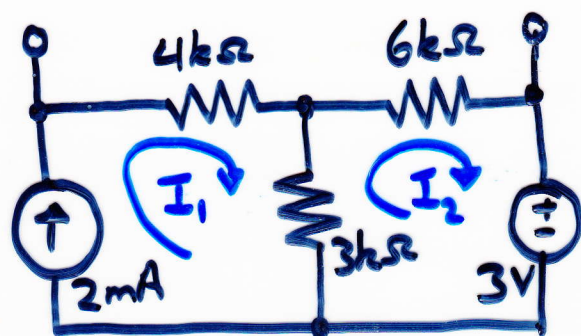

$$I_1 = 2 \times 10^{-3} \text{ A}$$

$$3\text{k} (I_2 - I_1) + 6\text{k} I_2 + 3 = 0$$


$$\therefore 3\text{k} I_2 - 6 + 6\text{k} I_2 + 3 = 0$$

$$9\text{k} I_2 = 3$$


$$I_2 = \frac{3}{9\text{k}} = \frac{1}{3} \text{ mA}$$

$$\begin{aligned}
 V_{oc} &= 4kI_1 + 6kI_2 \\
 &= 8 + 2 \\
 &= 10V
 \end{aligned}$$

Now for R_{Th}

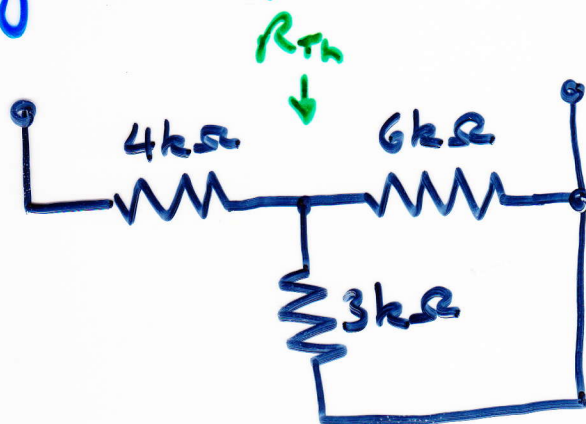
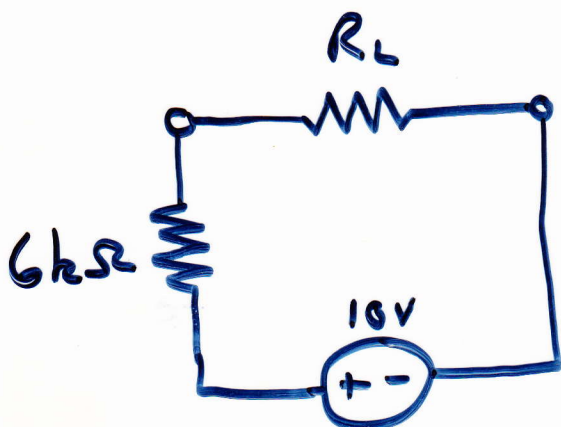
$$\begin{aligned}
 R_{Th} &= 4k + \frac{6 \times 3k}{(6+3)} \\
 &= 6k\Omega
 \end{aligned}$$





Where $R_L = R_{Th}$
for max. power transfer.


$$\begin{aligned}
 \therefore P_L &= \left(\frac{10}{12k} \right)^2 (6k) \\
 &= \frac{25}{6} \text{ mW}
 \end{aligned}$$

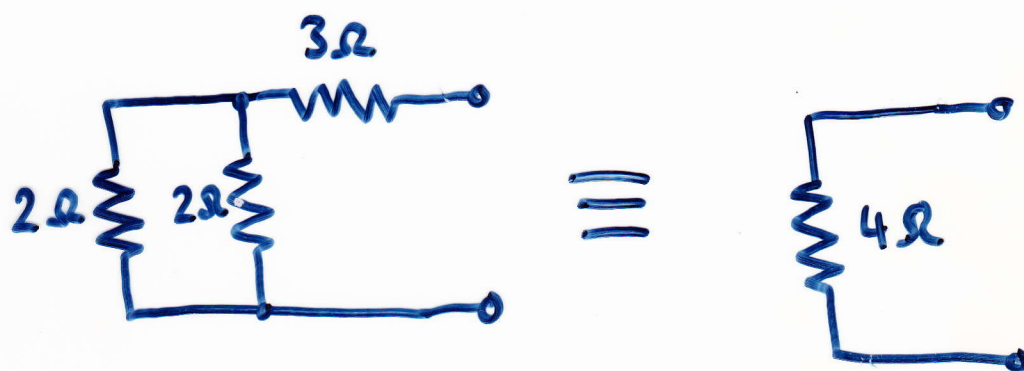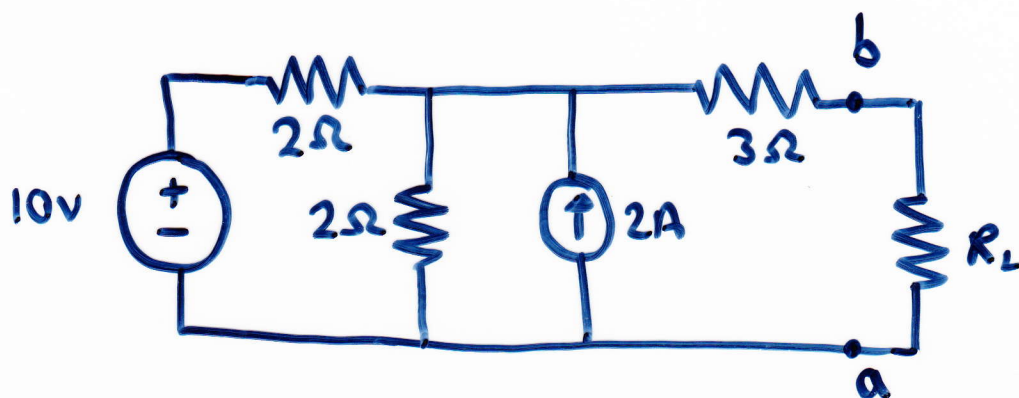Example

Determine the value of the load resistance to achieve max. power transfer.



$V_{oc}?$

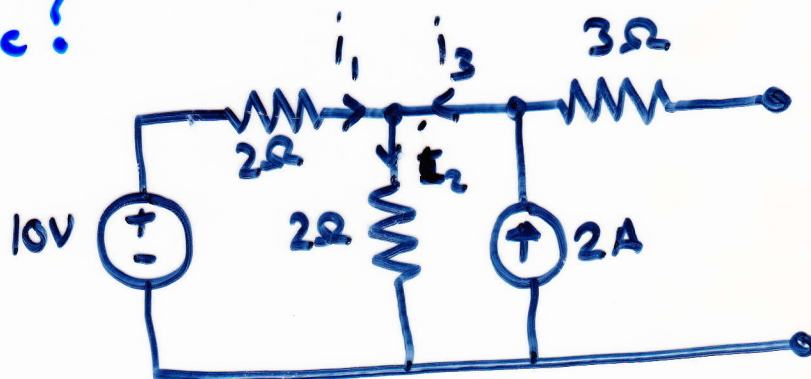

$$i_3 = 2A$$

$$-10 + i_1 \times 2 + i_2 \times 2 = 0$$

$$i_1 - i_2 + 2 = 0$$

$$i_1 = i_2 - 2$$


$$-10 + (i_2 - 2) \times 2 + i_2 \times 2 = 0$$

$$2i_2 - 4 + 2i_2 = 10$$

$$4i_2 = 14$$

$$i_2 = \frac{14}{4} \text{ A}$$
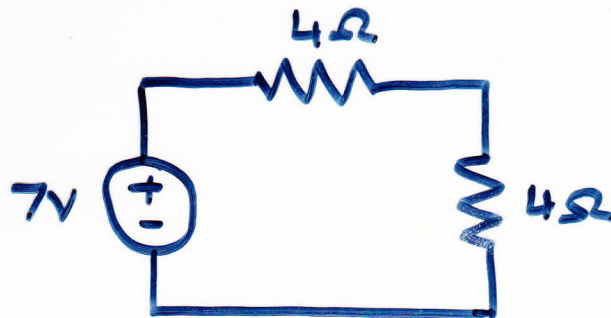
$$\therefore V_{oc} = \left(\frac{14}{4} \right) 2 = 7 \text{ V}$$



\therefore Max power:

$$i = 7/8$$

$$i^2 = 49/64$$

$$P_{max} = i^2 R_L = \frac{49}{64} \times 4 = \frac{49}{16} \text{ W.}$$