


Capacitors & Inductors.

Introduction

Two new circuit elements



Capacitor 

Inductor 

Devices can store energy.

Element	Stores energy...	Energy in form of...
Capacitor	when voltage across the element.	electric field
Inductor	when current passes through it.	magnetic field.

Capacitors.

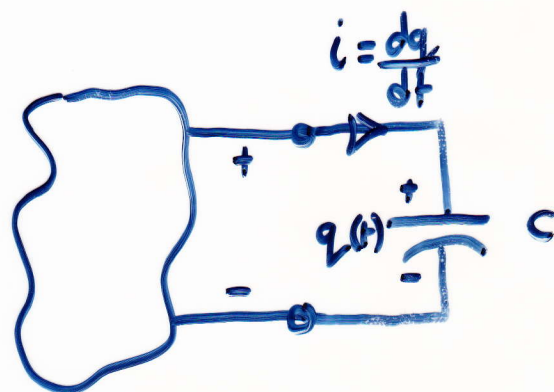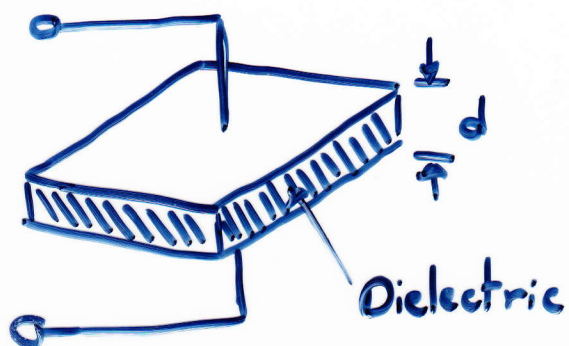

From physics know ...

$$C = \frac{\epsilon A}{d} \quad \text{for parallel plate capacitor}$$

$\epsilon = \epsilon_0 \epsilon_r$, permittivity of the dielectric

For vacuum $\epsilon_0 = 8.85 \times 10^{-12} \text{ Fm}^{-1}$ ($\approx \epsilon_{\text{air}}$)

Relative permittivity ϵ_r

e.g.	Material	ϵ_r
	air	~ 1
	mica	5.7-6.7
	polystyrene	2.55

Also

$$q = Cv$$

q is charge on capacitor.

What about current-voltage characteristics?

$$i = \frac{dq}{dt} = \frac{dCv}{dt}$$

$$i = C \frac{dv}{dt}$$

$$dv = \frac{1}{C} i dt$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx$$

rewriting

$$v(t) = \frac{1}{C} \int_{-\infty}^{t_0} i(x) dx + \frac{1}{C} \int_{t_0}^t i(x) dx$$

$$= v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

Energy stored ?

Considering power

$$p(t) = v(t)i(t) = C v(t) \frac{dv(t)}{dt}$$

Energy then is

$$W_c(t) = C \int_{-\infty}^t v(x) \frac{dv(x)}{dx} dx$$


$$= C \int_{v(-\infty)}^{v(t)} v(x) dv(x) = \left[\frac{1}{2} C v^2(x) \right]_{v(-\infty)}^{v(t)}$$

$$\underline{W_c(t) = \frac{1}{2} C v^2}$$

Since $v(-\infty) = 0$

$$\underline{W_c(t) = \frac{1}{2} \frac{q^2(t)}{C}}$$

Consider

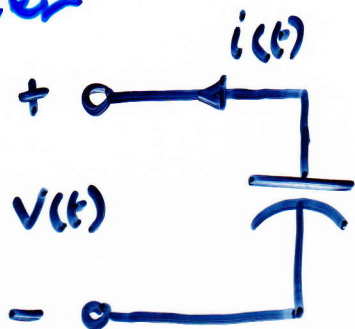


$i(t) ?$

$$i(t) = -C \frac{dv(t)}{dt}$$

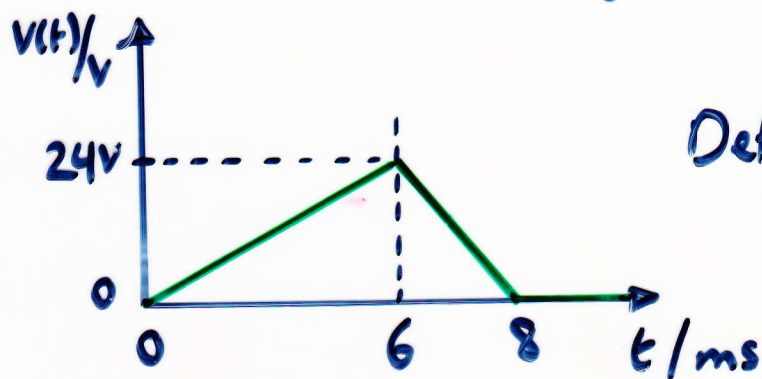Example

$5\mu\text{F}$ capacitor has following voltage waveform



Determine current waveform.

Irwin
Ex. 5.2

$$v(t) = \frac{24}{6 \times 10^{-3}} t \quad 0 \leq t < 6 \text{ ms}$$

$$\text{and} \quad = \frac{-24}{2 \times 10^{-3}} t + 96 \quad 6 \leq t < 8 \text{ ms}$$

$$= 0 \quad t \geq 8 \text{ ms}$$

$$\text{Now } i(t) = C \frac{dv(t)}{dt}$$


$$= 5 \times 10^{-6} \times 4 \times 10^3 \quad 0 \leq t < 6 \text{ ms}$$

$$= 20 \text{ mA} \quad 0 \leq t < 6 \text{ ms}$$

$$i(t) = 5 \times 10^{-6} \times (-12 \times 10^3) \quad 6 \leq t < 8 \text{ ms}$$

$$= -60 \text{ mA} \quad 6 \leq t < 8 \text{ ms}$$

$$i(t) = 0 \quad t \geq 8 \text{ ms}$$


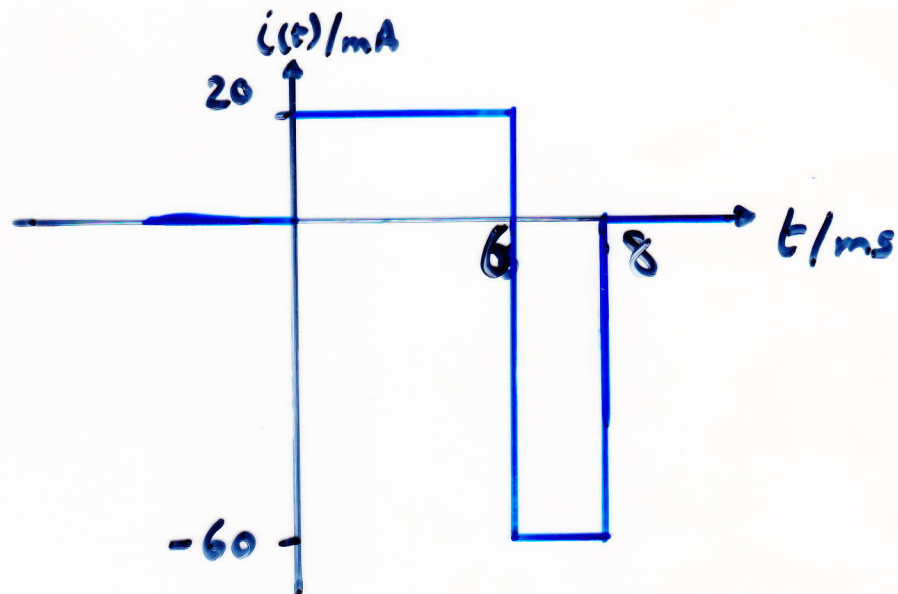


Inductors

Usually conducting wire in form of a coil.

Material on which they are wound does affect the inductance.

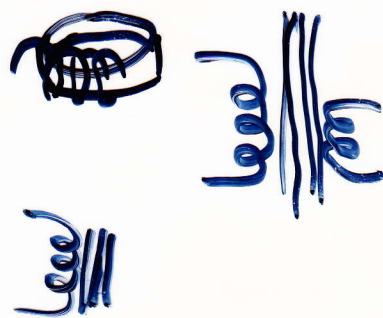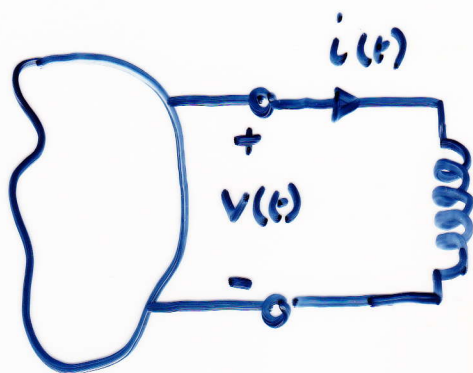Material can be air, non-magnetic, iron or ferrite.



$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(x) dx$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$

Power?

$$p(t) = v(t) i(t)$$


$$= L \frac{di(t)}{dt} i(t)$$

Energy?

$$w_L(t) = \int_{-\infty}^t L \left(\frac{di(x)}{dx} \right) i(x) dx$$


$$\therefore w_L(t) = \frac{1}{2} L i^2(t)$$

Consider

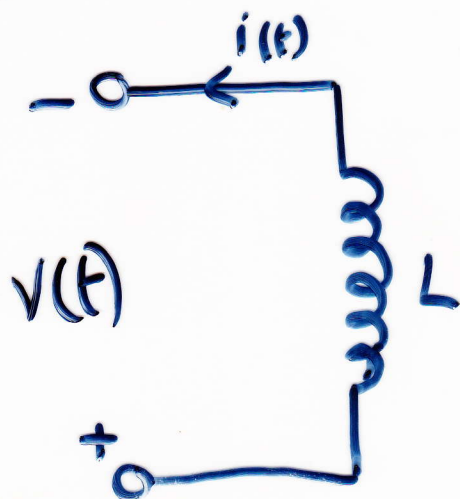

$$v(t) = L \frac{di(t)}{dt}$$

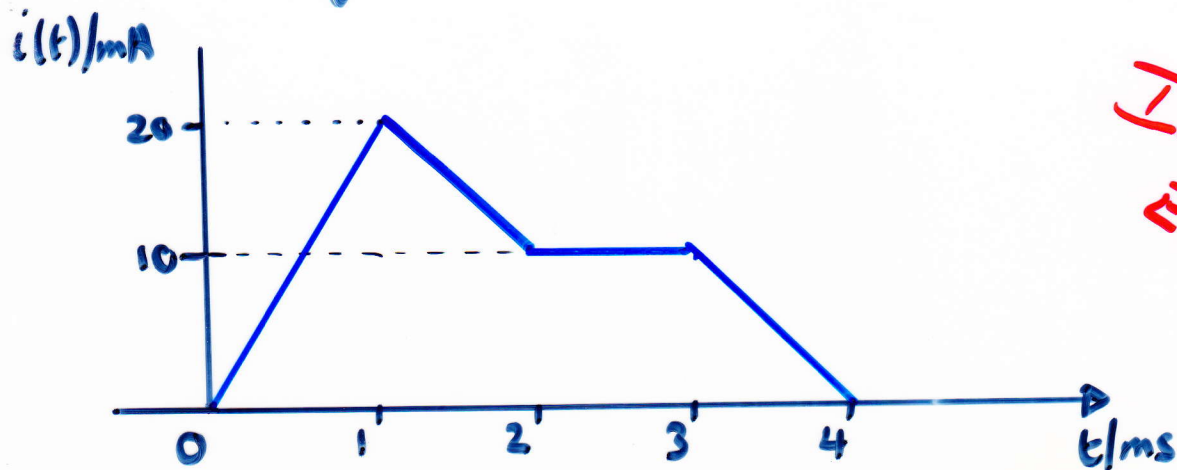Example 5mH inductor has following current waveform. Determine inductor voltage waveform.



Irwin
E6.4


$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = 20t \quad 0 \leq t < 1 \text{ ms}$$

$$i(t) = -10t + 30 \quad 1 \leq t < 2 \text{ ms}$$

$$i(t) = 10 \quad 2 \leq t < 3 \text{ ms}$$

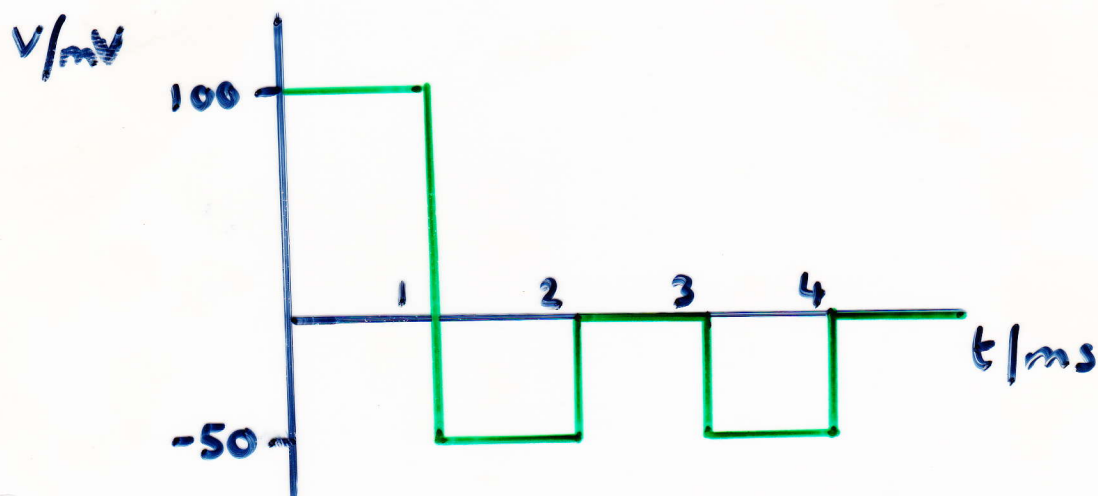
$$i(t) = -10t + 40 \quad 3 \leq t < 4 \text{ ms}$$



Capacitor & Inductor

Combinations

Series Capacitors

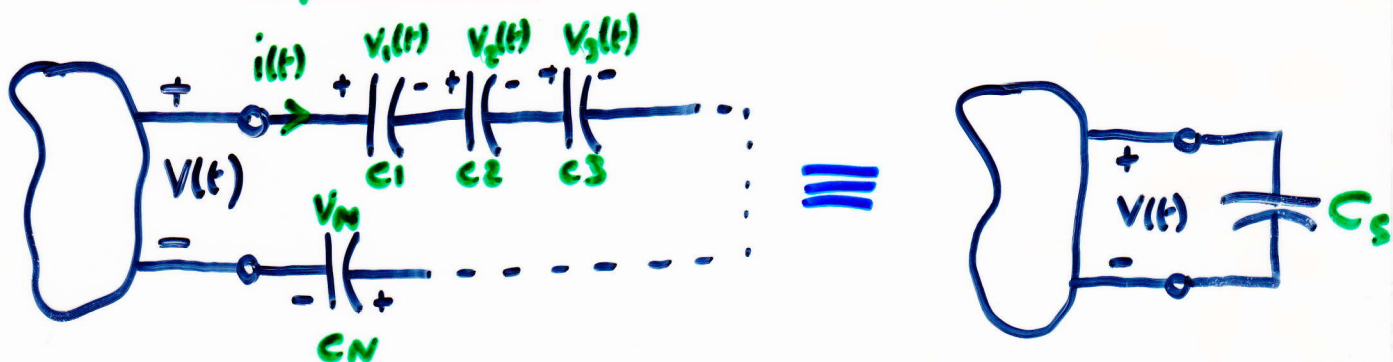

$$V(t) = V_1(t) + V_2(t) + V_3(t) + \dots + V_N(t)$$

$$V_i(t) = \frac{1}{C_i} \int_{t_0}^t i(t) dt + V_i(t_0)$$

$$V(t) = \left(\sum_{i=1}^N \frac{1}{C_i} \right) \int_{t_0}^t i(t) dt + \sum_{i=1}^N V_i(t_0)$$

$$= \frac{1}{C_s} \int_{t_0}^t i(t) dt + V(t_0)$$


where $V(t_0) = \sum_{i=1}^N V_i(t_0)$

and

$$\frac{1}{C_s} = \sum_{i=1}^N \frac{1}{C_i} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

Note: current same through each capacitor, so each capacitor gains same charge in the same time period. Voltage across each capacitor depends on this charge & capacitance of the element.

Parallel Capacitors

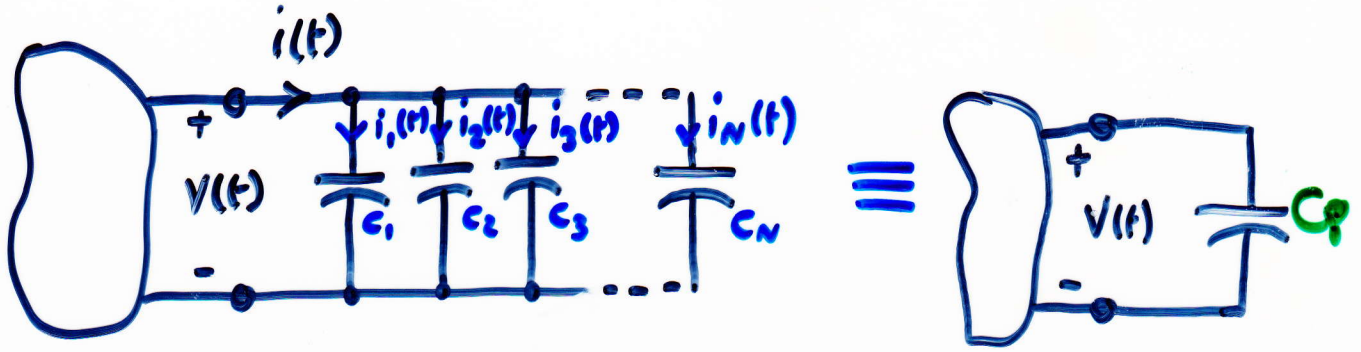

$$i(t) = i_1(t) + i_2(t) + i_3(t) + \dots + i_N(t)$$

$$= C_1 \frac{dv(t)}{dt} + C_2 \frac{dv(t)}{dt} + C_3 \frac{dv(t)}{dt} + \dots + C_N \frac{dv(t)}{dt}$$

$$= \left(\sum_{i=1}^N C_i \right) \frac{dv(t)}{dt}$$


$$= C_p \frac{dv(t)}{dt}$$

where

$$\underline{C_p = C_1 + C_2 + C_3 + \dots + C_N}$$

Example

16.4

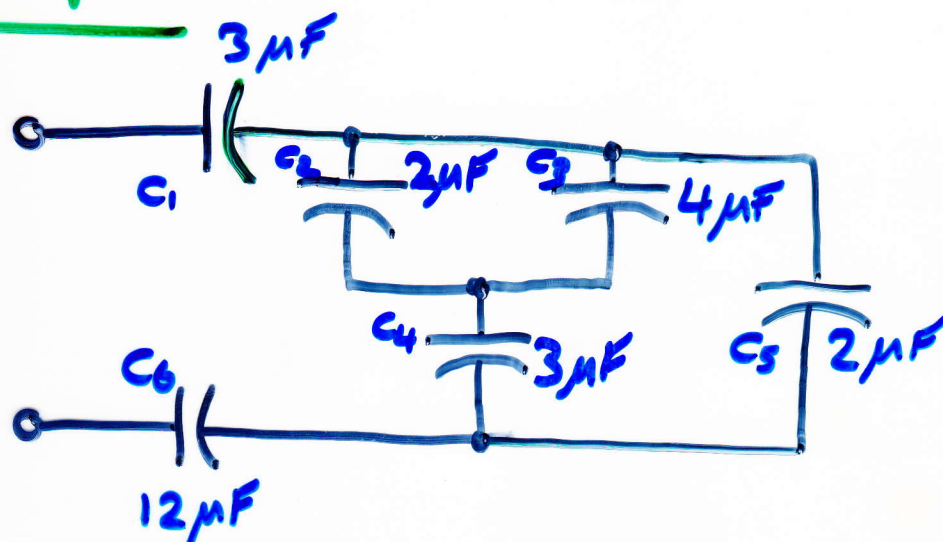


Combine C_2 & C_3 , $C_{23} = 2\mu F + 4\mu F = 6\mu F$

" $C_{23} + C_4$,

$$\frac{1}{C_{234}} = \frac{1}{C_{23}} + \frac{1}{C_4} = \frac{1}{6} + \frac{1}{3} = \frac{1}{2}$$


$$\therefore C_{234} = 2\mu F$$

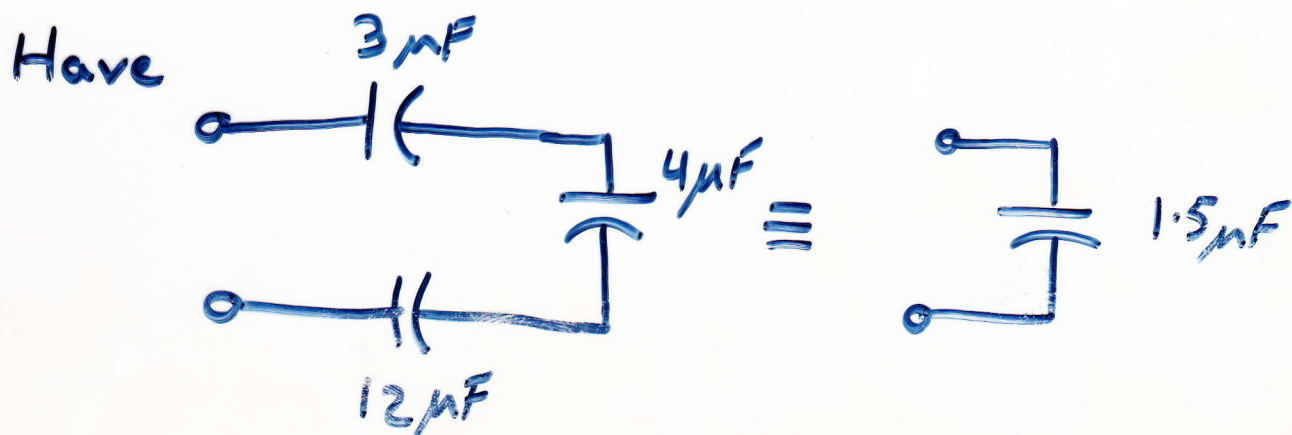Combine C_{234} with $C_5 = 2\mu F + 2\mu F = 4\mu F$



Series Inductors

16.5

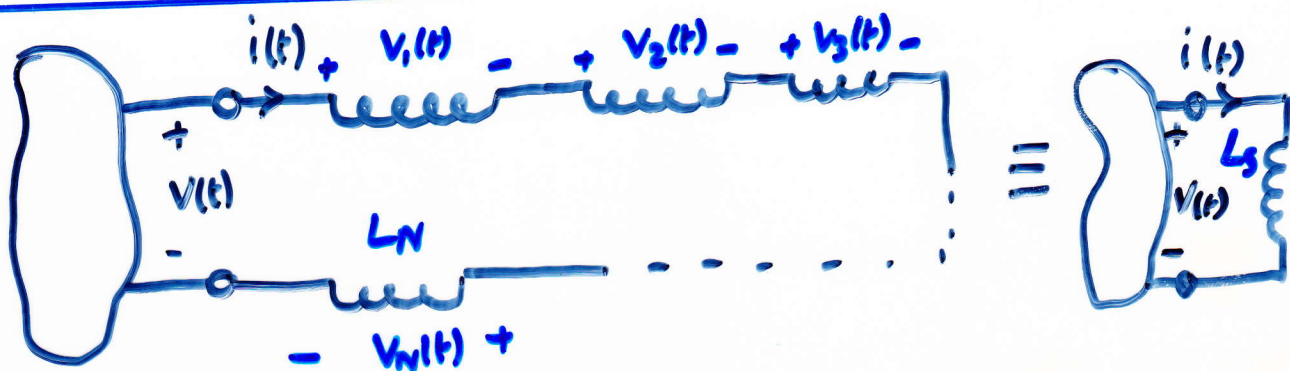

$$V(t) = V_1(t) + V_2(t) + V_3(t) + \dots + V_N(t)$$

$$V(t) = L_1 \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + L_3 \frac{di(t)}{dt} + \dots + L_N \frac{di(t)}{dt}$$


$$= \left(\sum_{i=1}^N L_i \right) \frac{di(t)}{dt}$$

$$= L_s \frac{di(t)}{dt}$$

where

$$L_s = \sum_{i=1}^N L_i = L_1 + L_2 + \dots + L_N$$

Parallel Inductors.

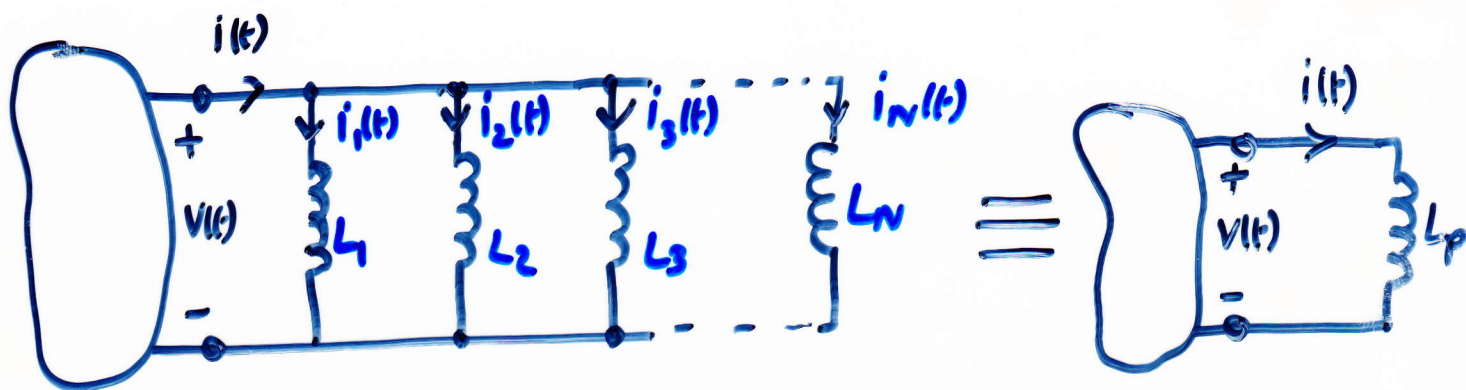

$$i(t) = i_1(t) + i_2(t) + i_3(t) + \dots + i_N(t)$$


$$i_j(t) = \frac{1}{L_j} \int_{t_0}^t v(x) dx + i_j(t_0)$$

$$\text{So } i(t) = \left(\sum_{j=1}^N \frac{1}{L_j} \right) \int_{t_0}^t v(x) dx + \sum_{j=1}^N i_j(t_0)$$

$$= \frac{1}{L_p} \int_{t_0}^t v(x) dx + i(t_0)$$

$$\text{where } \frac{1}{L_p} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$


Example

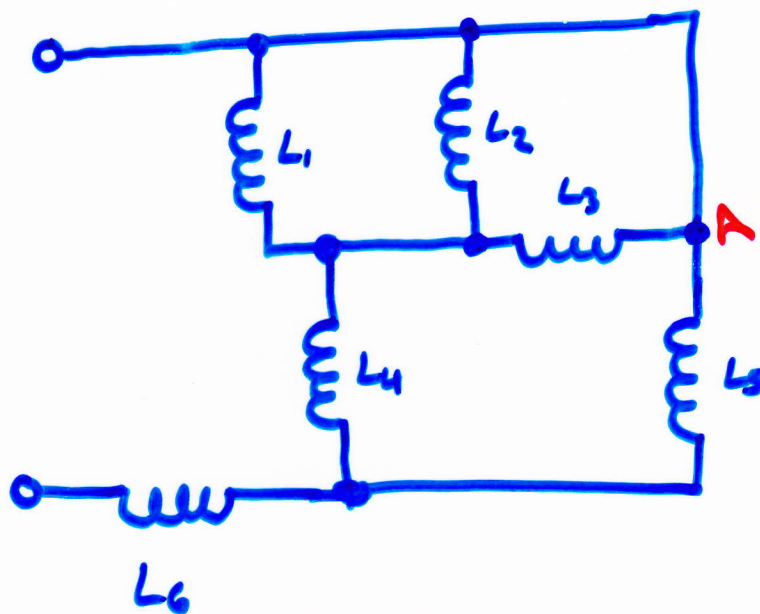

All inductors
are 6mH .

What is the value
of an equivalent
single inductor?

E 6.8

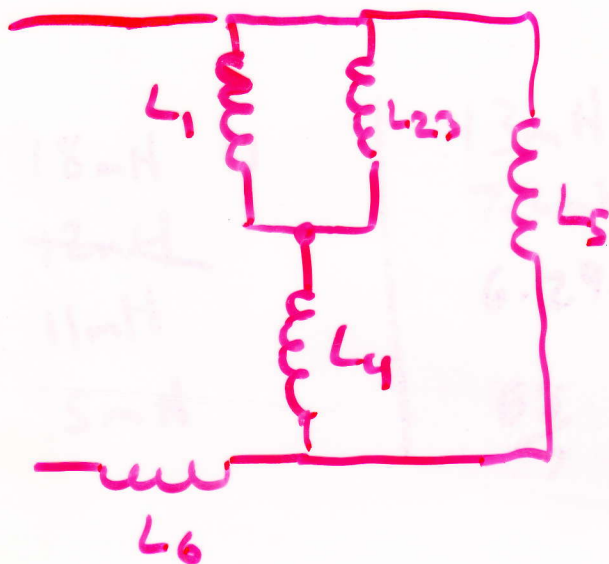

9.429mH .

Irwin E5.8