

# First-Order Circuits

## Transient response of RC & RL

### Introduction

We have seen previously that inductors and capacitors have current or voltage dependencies on the rate of change of the voltage or current.

i.e.

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = L \frac{di(t)}{dt}$$

Need to examine the effect of voltage or current changes in circuits containing capacitors or inductors.

# General Form of the Response Equations

(math revision)

Dealing with equations of the form

$$\frac{dx(t)}{dt} + ax(t) = f(t) \quad (1)$$

Solution?

$$x(t) = x_p(t)$$

Particular integral

is solution of (1). Also,

$$x(t) = x_c(t)$$

Complementary soln.

is solution of

$$\frac{dx(t)}{dt} + ax(t) = 0$$

So let

$$\frac{dx_p}{dt} + ax_p(t) = A \quad (2)$$

$$\frac{dx_c(t)}{dt} + ax_c(t) = 0 \quad (3)$$

If  $A$  is a constant assume soln to (2) is a constant,  $K_1$ .

$\therefore$  Sub.  $K_1$  for  $x_p$  into (2)

$$K_1 = \frac{A}{a}$$

Examining (3)

$$\frac{dx_c}{x_c} = -a dt$$

$$\therefore \ln x_c(t) = -at + c$$


$$x_c(t) = K_2 e^{-at}$$

Remember,  $x(t) = x_p + x_c(t)$

$$\text{So, } x(t) = \frac{A}{a} + K_2 e^{-at}$$


$$x(t) = K_1 + K_2 e^{-t/\tau}$$

$$x_c = K_2 e^{-t/\tau}$$

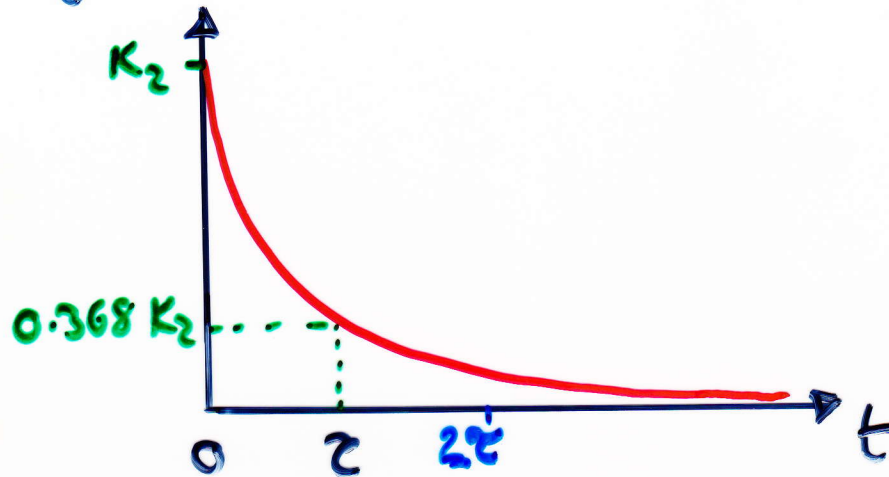

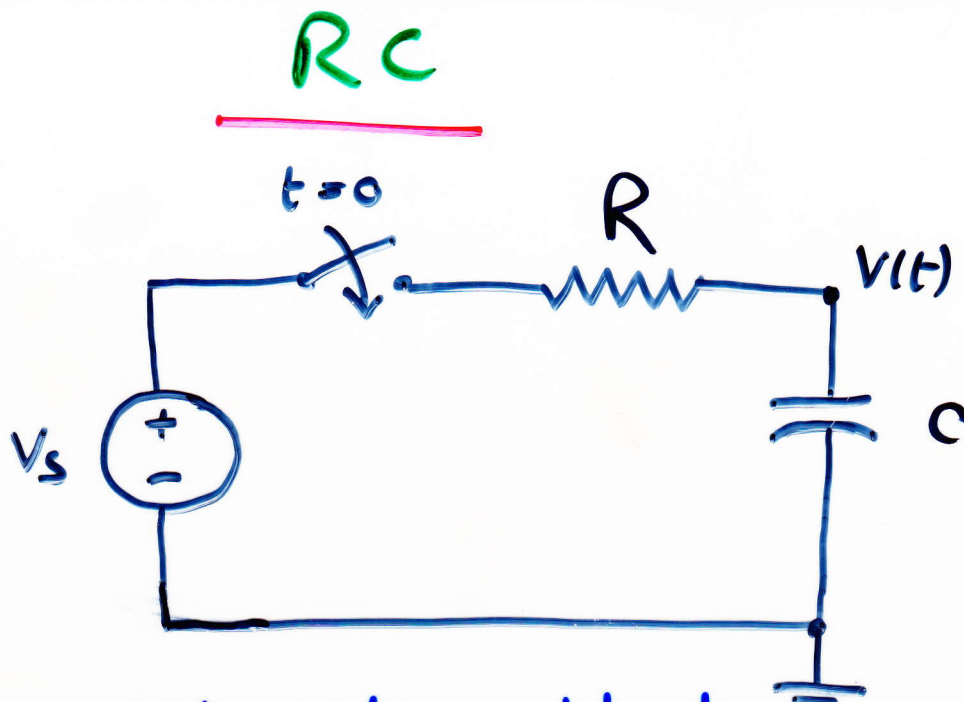Curve drops 63.2% each time constant  $\tau$ .





Apply KCL at  $t=0$  when switch closes

$$C \frac{dv(t)}{dt} + \frac{v(t) - V_s}{R} = 0$$

or

$$\frac{dv(t)}{dt} + \frac{v(t)}{RC} = \frac{V_s}{RC} \quad (4)$$

Solution of this equation is of form

$$v(t) = K_1 + K_2 e^{-t/\tau}$$

Substituting this solution into (4)

$$-\frac{K_2}{\tau} e^{-t/\tau} + \frac{K_1}{RC} + \frac{K_2}{RC} e^{-t/\tau} = \frac{V_s}{RC}$$

n.6

Equating constants and exponential terms:

$$K_1 = V_s$$

$$\tau = RC$$

$$\therefore V(t) = V_s + K_2 e^{-t/RC}$$

$V_s$  is steady-state value.

$K_2$  ? Consider initial conditions — cap. is uncharged.


$$0 = V_s + K_2$$

$$K_2 = -V_s$$

$\therefore$  Complete solution is

$$V(t) = V_s - V_s e^{-t/RC}$$

---

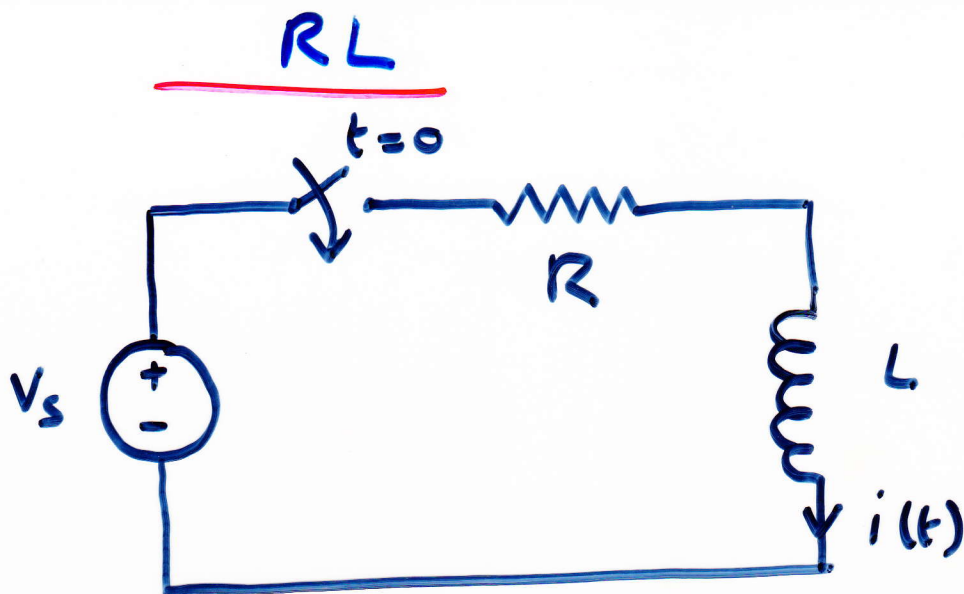

From KVL

$$L \frac{di(t)}{dt} + Ri(t) = V_s \quad \leftarrow$$

$$i(t) = \frac{V_s}{R} + K_2 e^{-(\frac{R}{L})t} \quad \triangleleft$$

Since

$$i(t) = K_1 + K_2 e^{-t/\tau} \quad \leftarrow \text{Apply..}$$

$$-\frac{L}{\tau} K_2 e^{-t/\tau} + RK_1 + RK_2 e^{-t/\tau} = V_s$$

$$K_1 = \frac{V_s}{R}$$

$$\tau = \frac{L}{R}$$

17.8  
 $\frac{V_s}{R}$  is steady state and  $\frac{L}{R}$  is circuit time constant.

So if no current at  $t=0$

$$0 = \frac{V_s}{R} + K_2$$

$$K_2 = -\frac{V_s}{R}$$


$$\therefore i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-\frac{R}{L} t}$$

---



# Examples: RC & RL Circuits.

①

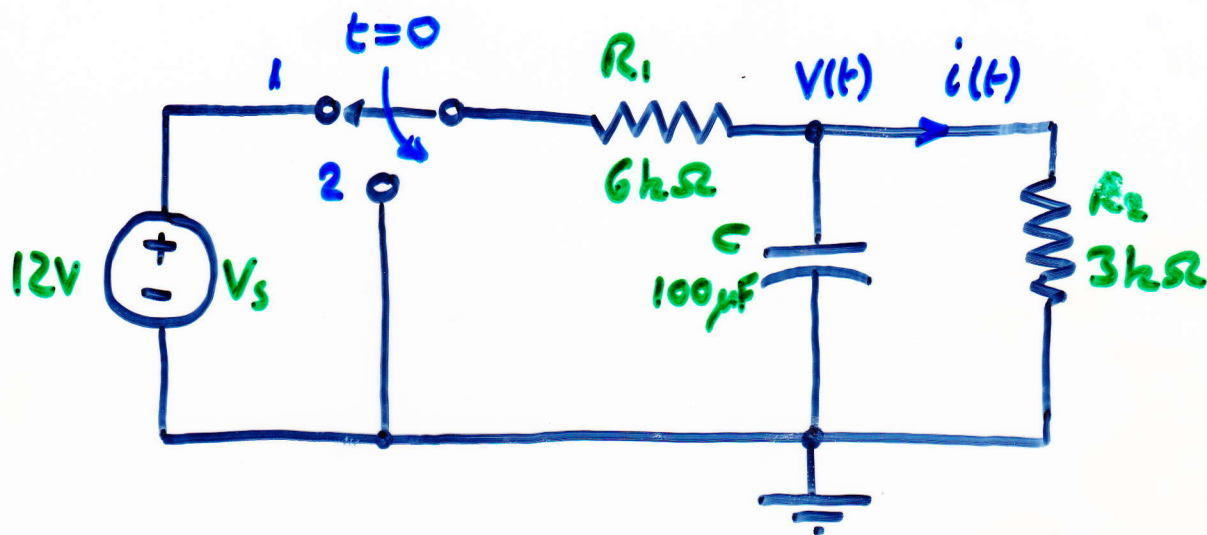Irwin  
Example 7.1


Determine  $i(t)$  for  $t > 0$ .

Switch in position 1 for long time. At  $t=0$  switched to position 2.

At  $t=0$   $C$  is fully charged.

No current passes through the capacitor (acts like open circuit to dc).
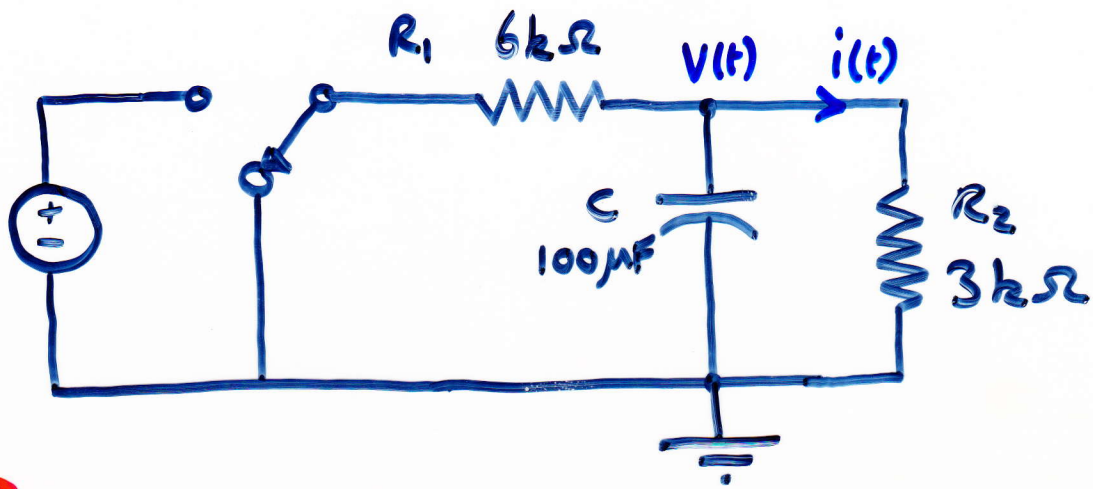
$$\therefore V_c(0) = 12 \left( \frac{3k}{6k+3k} \right) = 4V$$



$t > 0$

From KCL

$$\frac{V(t)}{R_1} + C \frac{dV(t)}{dt} + \frac{V(t)}{R_2} = 0$$

$$\frac{V(t)}{CR_1} + \frac{dV(t)}{dt} + \frac{V(t)}{CR_2} = 0$$

Sub. in values

$$\frac{V(t)}{0.6} + \frac{dV(t)}{dt} + \frac{V(t)}{0.3} = 0 = \frac{dV}{dt} + \frac{10V(t)}{6} + \frac{20V(t)}{6}$$

$$\frac{dV}{dt} + 5V(t) = 0$$

Soln. to this eqn is of the form  $V(t) = K_2 e^{-t/\tau}$

$$\text{So } \tau = \frac{1}{5} = 0.2 \text{ s}$$


$$v(t) = K_2 e^{-t/0.2} \text{ V}$$

Now initially

$$v(0) = 4 \text{ V}$$


$$\therefore v(t) = 4 e^{-t/0.2} \text{ V}$$

$$i(t) = v(t) / R_2$$

$$i(t) = \frac{4}{3} e^{-t/0.2} \text{ mA}$$


2

Irwin E6.2

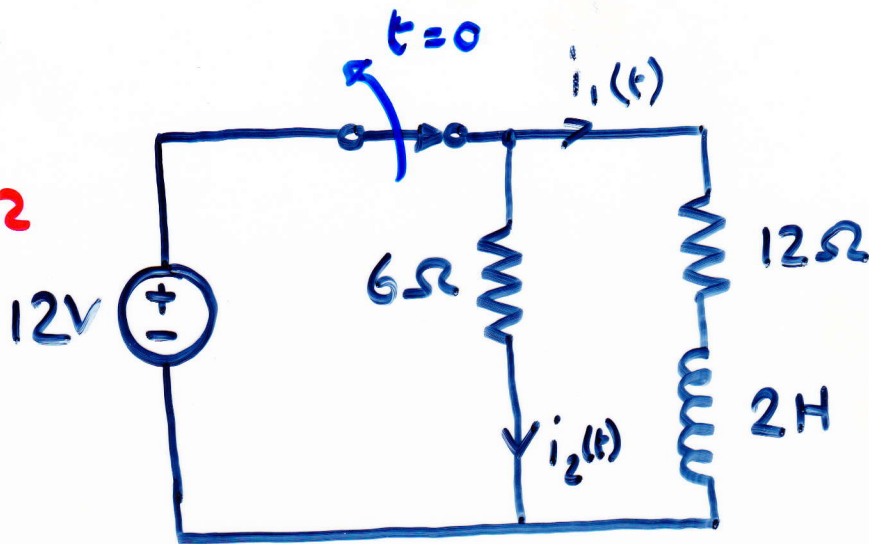

Switch opens at  $t=0$ . Find  $i_1(t)$  for  $t>0$


At  $t=0$  system in steady state so inductor is like a short circuit.

$$\therefore i_1(t) = 12/12 = 1 \text{ A}$$

$$i_2(t) = 12/6 = 2 \text{ A}$$



When switch opens have :

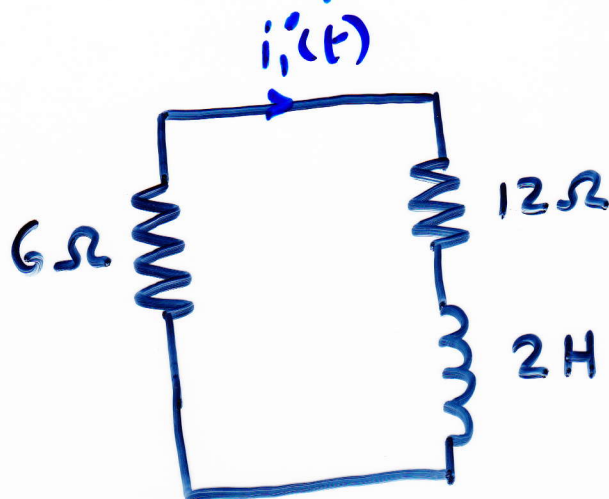

From KVL

$$6 i_1'(t) + 12 i_1'(t) + 2 \frac{d i_1'(t)}{dt} = 0$$

$$\frac{d i_1'(t)}{dt} + 9 i_1' = 0$$

Soln. of form  $i_1'(t) = K_2 e^{-t/\tau}$

$$\tau = \frac{1}{9}$$

Also at moment of switch opening  $K_2 = 1 \text{ A}$

$$\therefore i_1'(t) = 1 e^{-9t} \text{ A.}$$