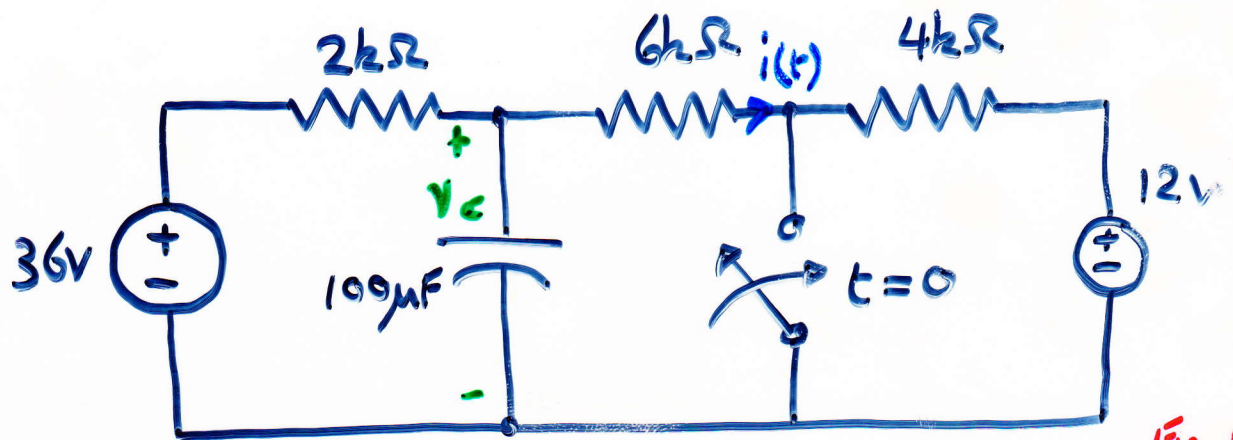


3

I in
Example 7.3

Circuit in steady state form before $t=0$.
Find $i(t)$ for $t > 0$

First find steady state voltage across capacitor

$$36 - V_c = 2k i(t)$$

$$\text{But } i(t) = (36 - 12) / 12k = 2mA$$

$$\begin{aligned} \therefore V_c &= 36 - 2k \times 2 \times 10^{-3} \\ &= \underline{32V} \quad (\text{at } t=0^-) \end{aligned}$$

When switch shuts, at $t = 0^+$, capacitor acts as a 32V supply momentarily.

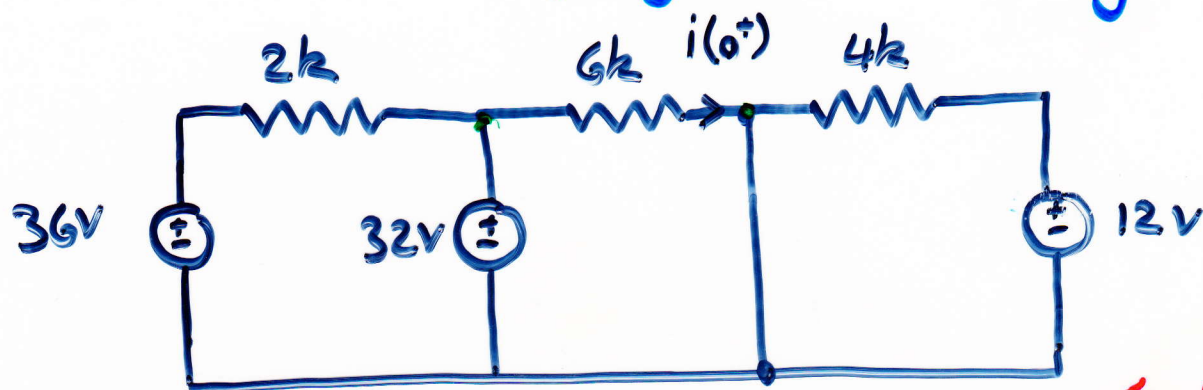


Fig 1a

$$\begin{aligned}\therefore i(0^+) &= \frac{32V}{6k} \\ &= \underline{\underline{\frac{16}{3} \text{ mA}}}\end{aligned}$$

At $t = \infty$


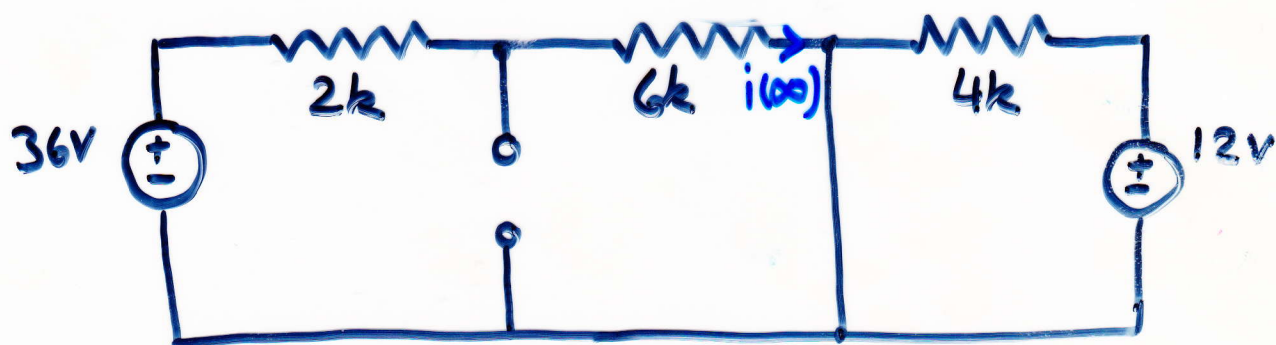


Fig 1b

$$\begin{aligned}\therefore i(\infty) &= \frac{36V}{8k} \\ &= \underline{\underline{\frac{9}{2} \text{ mA}}}\end{aligned}$$

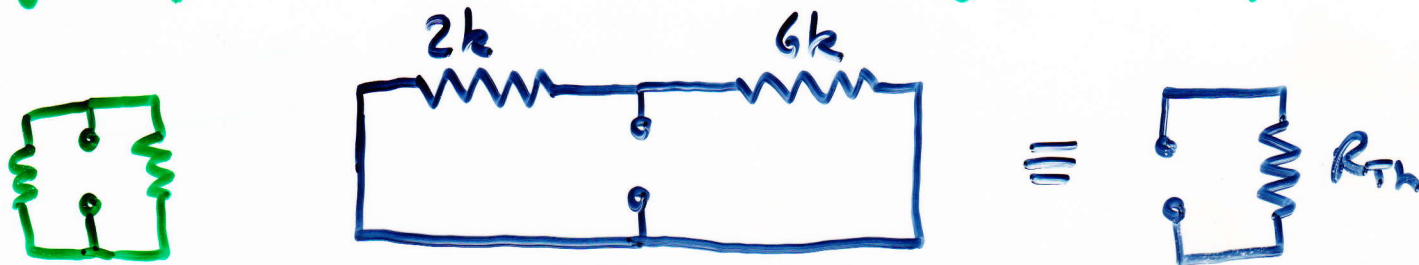Now consider the Thévenin equivalent resistance for open-circuit terminals of the capacitor



$$R_{Th} = \frac{2k \cdot 6k}{2k + 6k} = \frac{12k}{8}$$

$$R_{Th} = \frac{3}{2}k$$

Now, we know the effective resistance the capacitor sees, so the time constant is

$$\begin{aligned} \tau &= R_{Th} C \\ &= \frac{3}{2} \times 10^3 \times 100 \times 10^{-6} \\ &= 0.15s \end{aligned}$$

Making use of the solution of the form

$$i(t) = K_1 + K_2 e^{-t/\tau}$$


$$K_1 = i(\infty) = \frac{9}{2} \text{ mA}$$

$$K_2 = i(0^+) - K_1$$

$$= \frac{16}{3} - \frac{9}{2} = \frac{32 - 27}{6}$$

$$= \frac{5}{6} \text{ mA}$$




And we determine $\tau = 0.15 \text{ s}$

$$\therefore i(t) = \frac{36}{8} + \frac{5}{6} e^{-t/0.15} \text{ mA}$$

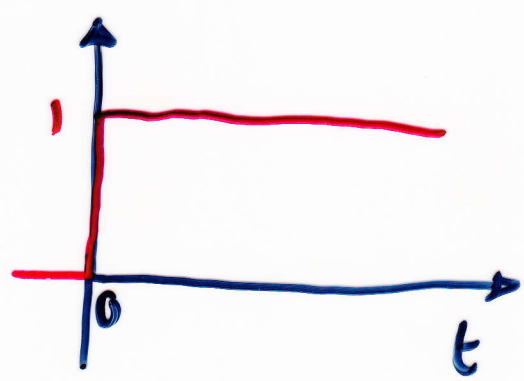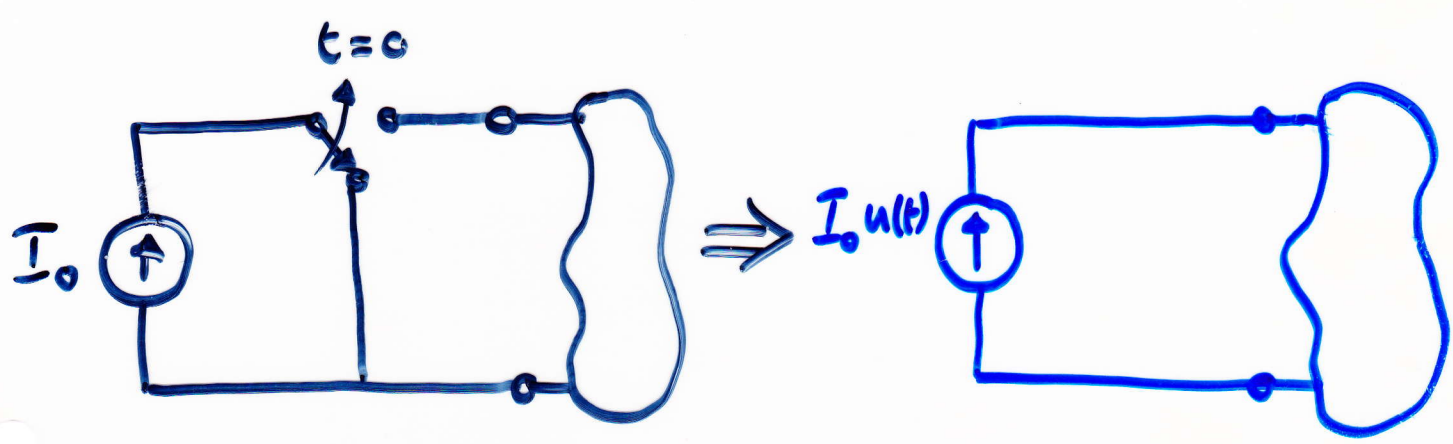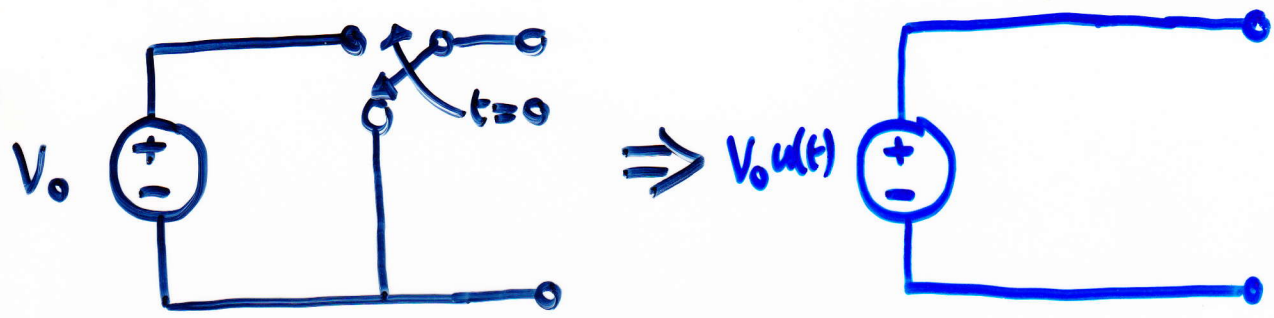
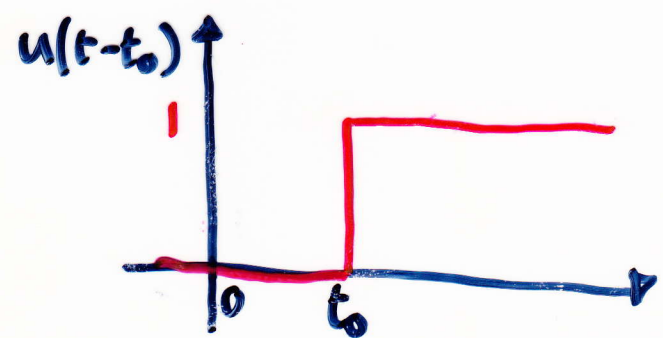
Pulse Response of RC & RL Circuits

19.1

So far have considered the abrupt application of a voltage or current. Can this discontinuous derivative be described mathematically?




$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$



$$u(t-t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$$



Step Function

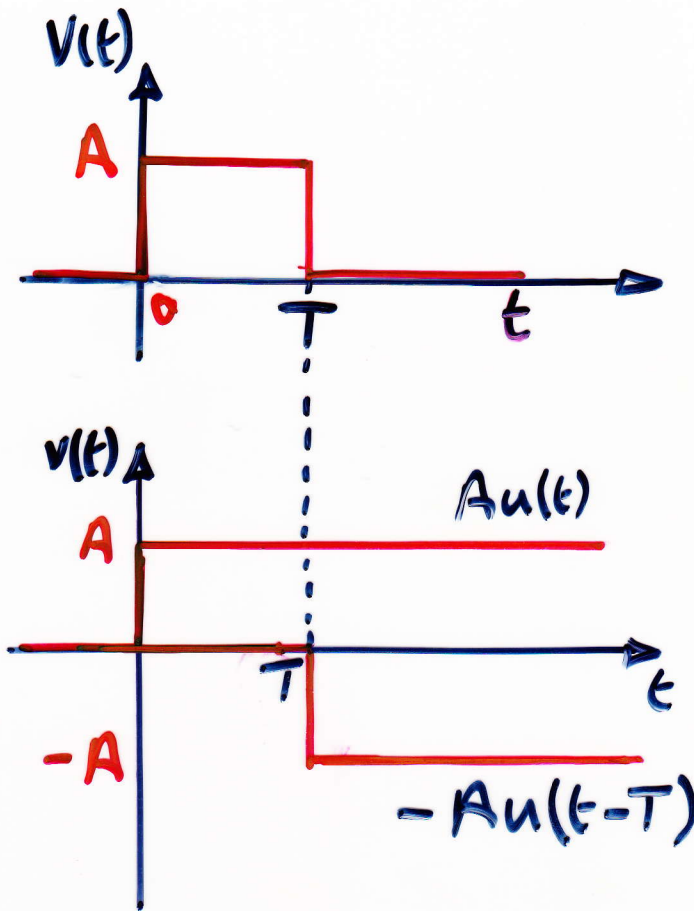


$$v(t) = A [u(t) - u(t-T)]$$

If the pulse starts at $t=t_0$ and with width T the equation is


$$v(t) = A \{ u(t-t_0) - u[t-(t_0+T)] \}$$

Example.

19.4

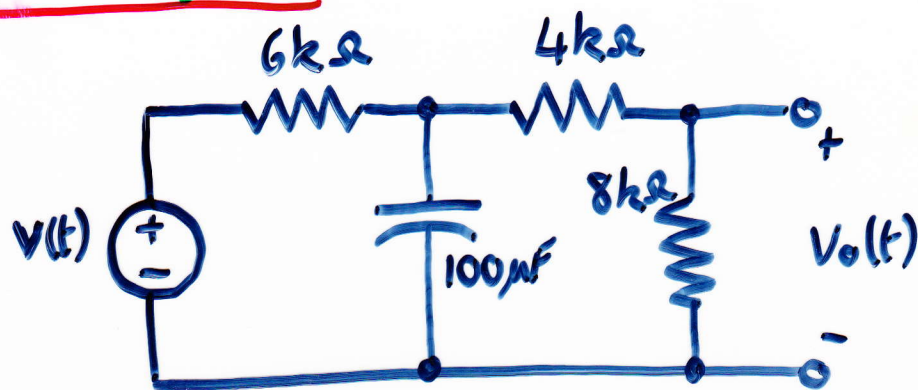

Input

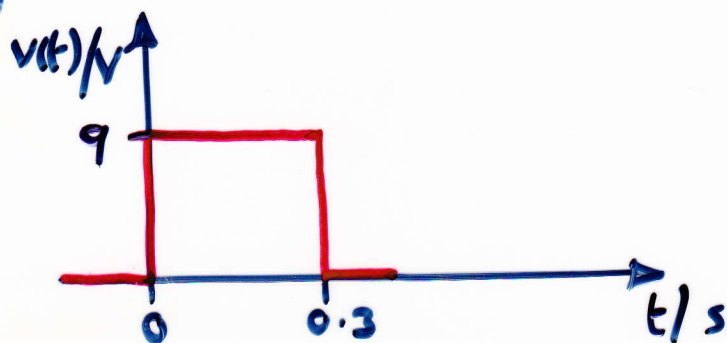

Determine the expression for $v_o(t)$

Initially voltage across capacitor is zero

$$v_o(0^+) = 0$$

If after $t=0$ and $v(t) = 9V$, consider situation that $v(t)$ is unchanged

In this situation

$$V_0(\infty) = \frac{9}{6k + 4k + 8k} (8k) = 4V$$

From the point of view of the capacitor the Thévenin equivalent resistance is

$$\begin{aligned} R_{Th} &= \frac{6k \times 12k}{6k + 12k} \\ &= 4k\Omega \end{aligned}$$

So circuit time constant is

$$\begin{aligned} \tau &= R_{Th} C \\ &= 4 \times 10^3 \times 100 \times 10^{-6} \\ &= 0.4s \end{aligned}$$

So response of $V_0(t)$ for $0 < t < 0.3s$

$$V_0 = 4 - 4e^{-t/0.4} V \quad 0 < t < 0.3s$$

Can see V_c relates to $V_o(t)$ through

$$V_o(t) = \frac{2}{3} V_c(t)$$

$$\text{So } V_c(t) = \frac{3}{2} (4 - 4e^{-t/0.4}) \text{ V}$$

Since the capacitor voltage is continuous

$$V_c(0.3^-) = V_c(0.3^+)$$

$$\begin{aligned} \therefore V_o(0.3^+) &= \frac{2}{3} V_c(0.3^-) \\ &= 4(1 - e^{-0.3/0.4}) \\ &= 2.11 \text{ V} \end{aligned}$$

When $t > 0.3 \text{ s}$ source is zero.

So when $t \rightarrow \infty$ $V_o = 0$.

$$V_o(t) = 2.11 e^{-(t-0.3)/0.4} \text{ V}$$

$$t > 0.3 \text{ s}$$

So solution

$$v_o(t) = 4(1 - e^{-t/0.4})u(t) - 4(1 - e^{-(t-0.3)/0.4})u(t-0.3) \text{ V}$$

or

$$v_o(t) = \begin{cases} 0 & t < 0 \\ 4(1 - e^{-t/0.4}) \text{ V} & 0 < t < 0.3 \text{ s} \\ 2.11 e^{-(t-0.3)/0.4} \text{ V} & t > 0.3 \text{ s} \end{cases}$$

or

$$v_o(t) = 4(1 - e^{-t/0.4})[u(t) - u(t-0.3)] + 2.11 e^{-(t-0.3)/0.4} u(t-0.3) \text{ V}$$

