

Sinusoids, sinusoidal forcing functions & phasors.

Introduction


So far considered circuit response to fixed value inputs or step inputs.

Now shall consider response to sinusoidal input or forcing function.

A number of approaches will be looked at, finishing with the phasor notation.

Sinusoids

Read section 7.1 - revision.

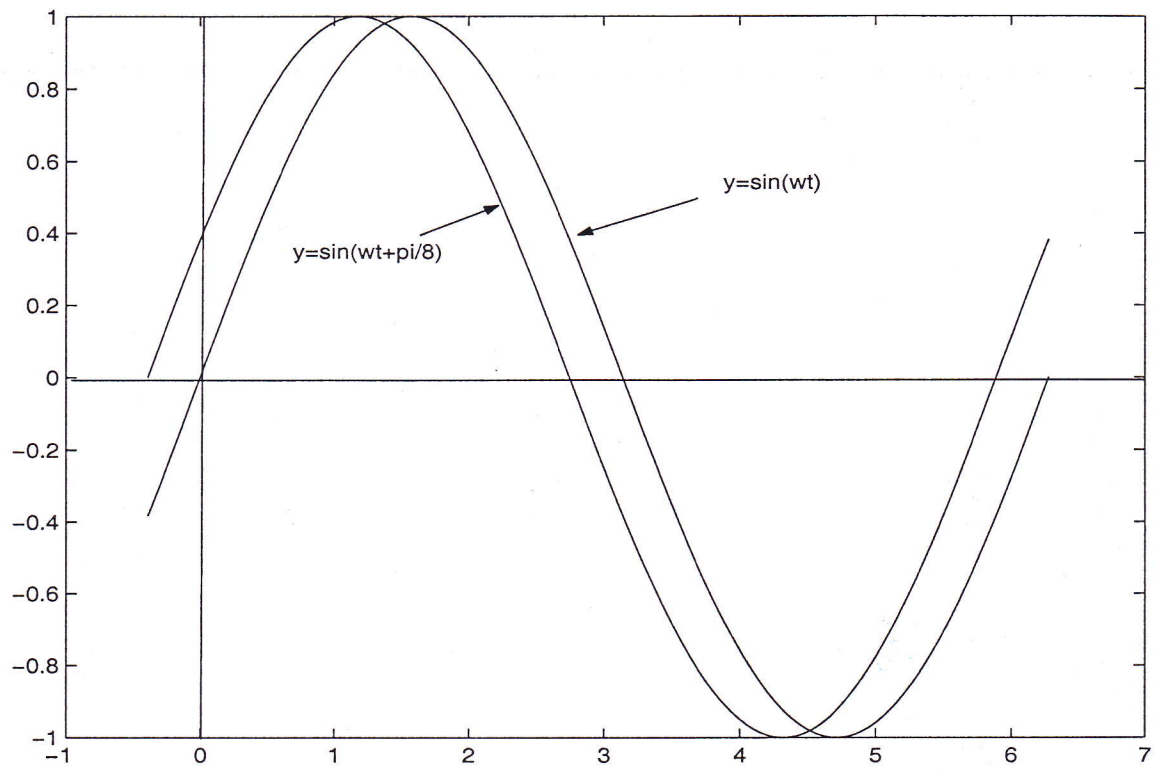


- $\omega = \frac{2\pi}{T} = 2\pi f$
- $\cos \omega t = \sin(\omega t + \frac{\pi}{2})$, $\sin \omega t = \cos(\omega t - \frac{\pi}{2})$

Sinusoidal Forcing Function.

Circuit source sinusoidal

↳ Output response?

Consider a simple circuit.

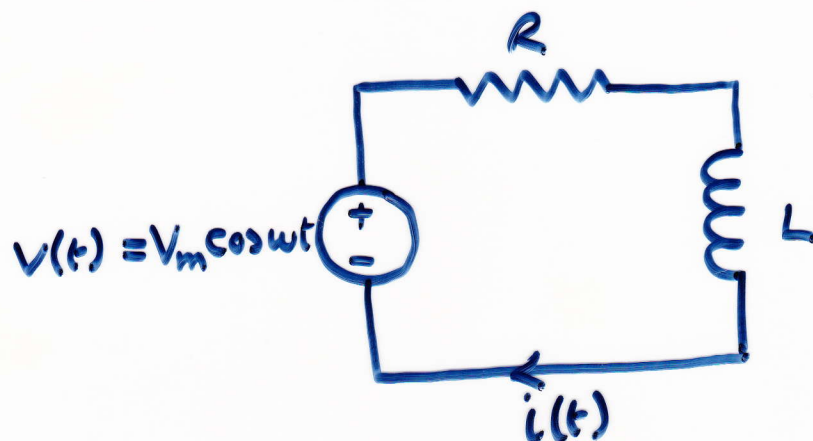

From KVL

$$L \frac{di(t)}{dt} + Ri(t) = V_m \cos \omega t \quad (1)$$

Assume forced response of circuit current $i(t)$ is of the form

$$i(t) = A \cos(\omega t + \phi)$$

$$\begin{aligned} \text{or } i(t) &= A \cos \phi \cos \omega t - A \sin \phi \sin \omega t \\ &= A_1 \cos \omega t + A_2 \sin \omega t \quad (2) \end{aligned}$$

\therefore substituting into (1)

$$L \frac{d}{dt} (A_1 \cos \omega t + A_2 \sin \omega t) + R (A_1 \cos \omega t + A_2 \sin \omega t) = V_m \cos \omega t$$

$$-A_1 \omega L \sin \omega t + A_2 \omega L \cos \omega t + R A_1 \cos \omega t + R A_2 \sin \omega t = V_m \cos \omega t$$

Equating coeffs of sine and cosines

$$-A_1 \omega L + A_2 R = 0$$

$$A_1 R + A_2 \omega L = V_m$$

$$\therefore A_1 = \frac{R V_m}{R^2 + \omega^2 L^2}$$

$$A_2 = \frac{\omega L V_m}{R^2 + \omega^2 L^2}$$

$$\therefore i(t) = \frac{R V_m}{R^2 + \omega^2 L^2} \cos \omega t + \frac{\omega L V_m}{R^2 + \omega^2 L^2} \sin \omega t$$

Comparing with (2) we have

$$A \cos \phi = \frac{R V_m}{R^2 + \omega^2 L^2}$$

$$A \sin \phi = \frac{-\omega L V_m}{R^2 + \omega^2 L^2}$$

- So $\tan \phi = \frac{A \sin \phi}{A \cos \phi} = -\frac{\omega L}{R}$

Since $(A \cos \phi)^2 + (A \sin \phi)^2 = A^2 (\cos^2 \phi + \sin^2 \phi) = A^2$

$$A^2 = \frac{R^2 V_m^2}{(R^2 + \omega^2 L^2)^2} + \frac{(\omega L)^2 V_m^2}{(R^2 + \omega^2 L^2)^2}$$

$$= \frac{V_m^2}{R^2 + \omega^2 L^2}$$

- So $A = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$

Using $i(t) = A \cos(\omega t + \phi)$ we have:

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

Insight from inspection

$$\phi = 0 \quad \text{if } L = 0$$

$$R = 0 \quad \text{if } \phi = -90^\circ$$

If L & R present current lags the voltage by between 0 to 90° .

Consider using complex numbers:

$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$

So input (in the simple RL circuit) becomes:

$$v(t) = V_m e^{j\omega t}$$

Expect response of form $i(t) = I_m e^{j(\omega t + \phi)}$

Working through example again

$$R I_m e^{j(\omega t + \phi)} + L \frac{d}{dt} (I_m e^{j(\omega t + \phi)}) = V_m e^{j\omega t}$$

$$R I_m e^{j(\omega t + \phi)} + j\omega L I_m e^{j(\omega t + \phi)} = V_m e^{j\omega t}$$

$$R I_m e^{j\phi} + j\omega L I_m e^{j\phi} = V_m$$

$$\therefore I_m e^{j\phi} = \frac{V_m}{R + j\omega L}$$

Recall

$$x + jy = r e^{j\phi}$$

$$r = \sqrt{x^2 + y^2}$$

$$\phi = \tan^{-1} y/x$$

$$\text{So } I_m e^{j\phi} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} e^{j[-\tan^{-1}(\frac{\omega L}{R})]}$$

Use form $i(t) = I_m \cos(\omega t + \phi)$

$$\text{then } i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left[\omega t - \tan^{-1}\left(\frac{\omega L}{R}\right)\right]$$


Phasors

Now look at another notation.

$$v(t) = V_m \cos(\omega t + \phi) = \text{Re} [V_m e^{j(\omega t + \phi)}]$$

or as a complex number
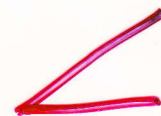
$$v(t) = \text{Re} (V_m \angle \phi e^{j\omega t})$$



Can drop the $\text{Re}(\cdot)$ and $e^{j\omega t}$ and work with $V_m \angle \phi$

$$\therefore v(t) = V_m \cos(\omega t + \phi) = \text{Re} [V_m e^{j(\omega t + \phi)}] \equiv \underline{V} = V_m \angle \phi$$

Correspondingly

$$i(t) = I_m \cos(\omega t + \phi) = \operatorname{Re} [I_m e^{j(\omega t + \phi)}]$$

$$\equiv \underline{I} = I_m \angle \phi$$

Using this notation consider the RL circuit again.

$$L \frac{di(t)}{dt} + Ri(t) = V_m \cos \omega t$$



Use $\underline{V} e^{j\omega t}$ where $\underline{V} = V_m \angle 0^\circ$

$$\text{so we have } L \frac{d\underline{I} e^{j\omega t}}{dt} + R \underline{I} e^{j\omega t} = \underline{V} e^{j\omega t}$$

$$j\omega L \underline{I} e^{j\omega t} + R \underline{I} e^{j\omega t} = \underline{V} e^{j\omega t}$$

$$j\omega L \underline{I} + R \underline{I} = \underline{V}$$


$$\therefore \underline{I} = \frac{\underline{V}}{R + j\omega L} = I_m \angle \phi = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle -\tan^{-1} \frac{\omega L}{R}$$

$$\therefore i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

Phasors applied to R, L & C.

Shall consider each type of component individually.

Resistor

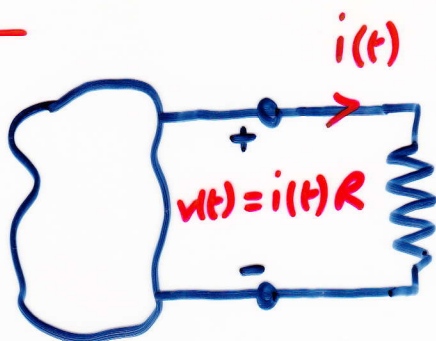


Applying the complex voltage $V_m e^{j(\omega t + \theta_v)}$

$$V_m e^{j(\omega t + \theta_v)} = R I_m e^{j(\omega t + \theta_i)}$$

$$V_m e^{j\theta_v} = R I_m e^{j\theta_i}$$


In phasor form

$$\underline{V} = R \underline{I}$$

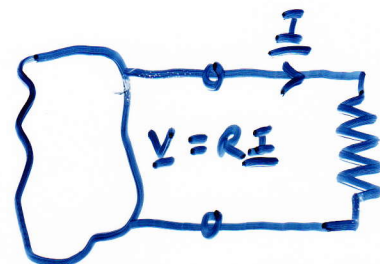


where $\underline{V} = V_m e^{j\theta_v} = V_m \angle \theta_v$

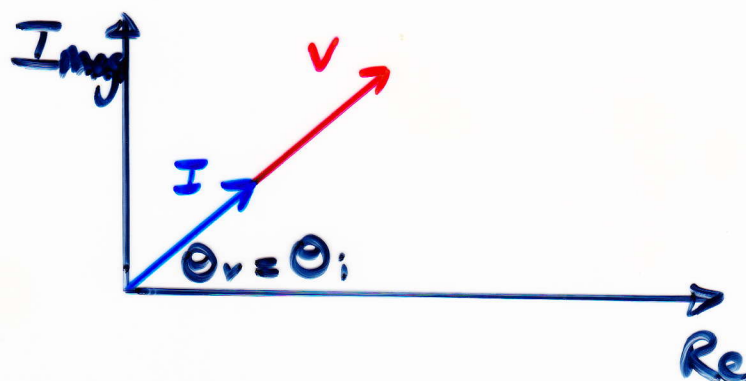and $\underline{I} = I_m e^{j\theta_i} = I_m \angle \theta_i$



Can see from equations, for a resistor,

$$\theta_v = \theta_i$$

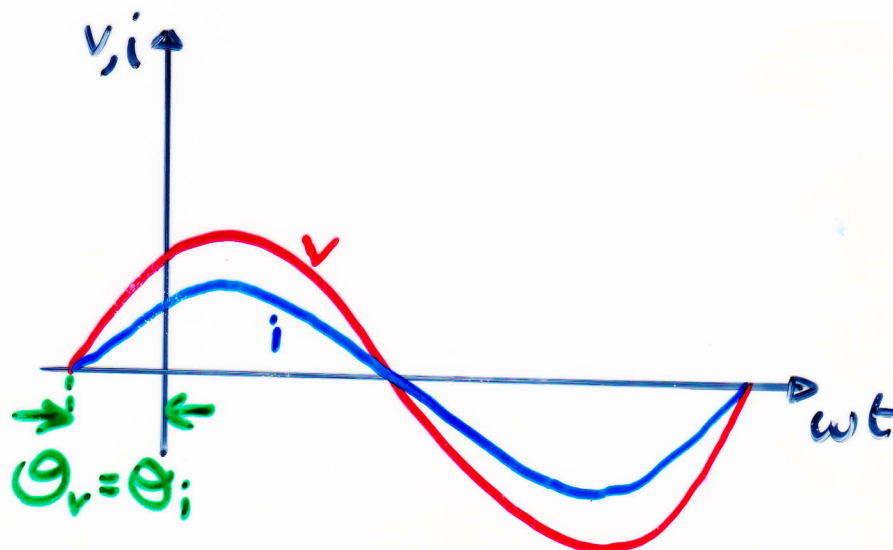

Example (E8.5)

Current in a 4Ω resistor is known to be $\underline{I} = 12 \angle 60^\circ$

Express the voltage across the resistor as a time function if the current freq. is 4 kHz .


$$\underline{V} = R \underline{I}$$

$$\therefore \underline{V} = 4 \times 12 \angle 60^\circ$$

$$\therefore V = 48 \cos(8000\pi t + 60^\circ)$$

$$\begin{aligned} \omega &= 2\pi f = 2\pi 4 \times 10^3 \\ &= 8000\pi \end{aligned}$$

Inductor

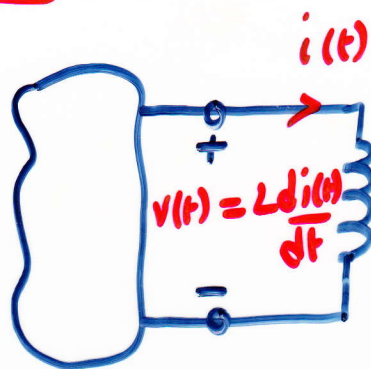

$$v(t) = L \frac{di(t)}{dt}$$


$$V_m e^{j(\omega t + \theta_v)} = L \frac{d}{dt} I_m e^{j(\omega t + \theta_i)}$$

→

$$V_m e^{j\theta_v} = j\omega L I_m e^{j\theta_i}$$




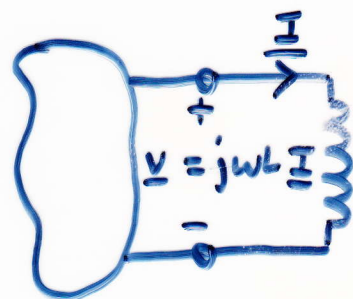
$$\underline{V} = j\omega L \underline{I}$$



$$\text{Now } j = 1e^{j90^\circ}$$

$$\begin{aligned} \therefore V_m e^{j\theta_v} &= \omega L I_m e^{j(\theta_i + 90^\circ)} \\ &= \omega L I_m e^{j\theta_i} e^{j90^\circ} \end{aligned}$$

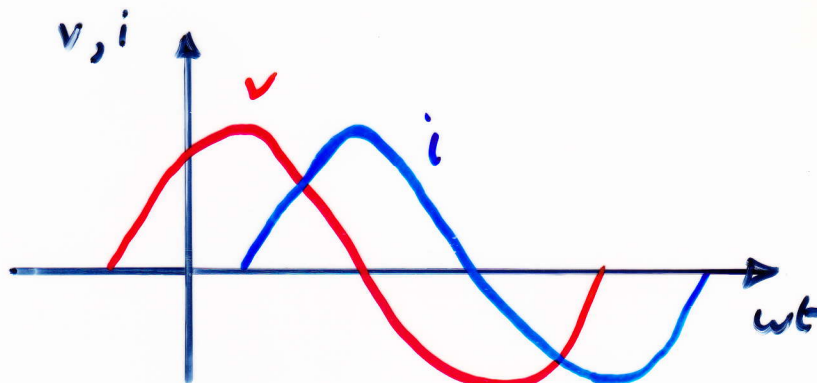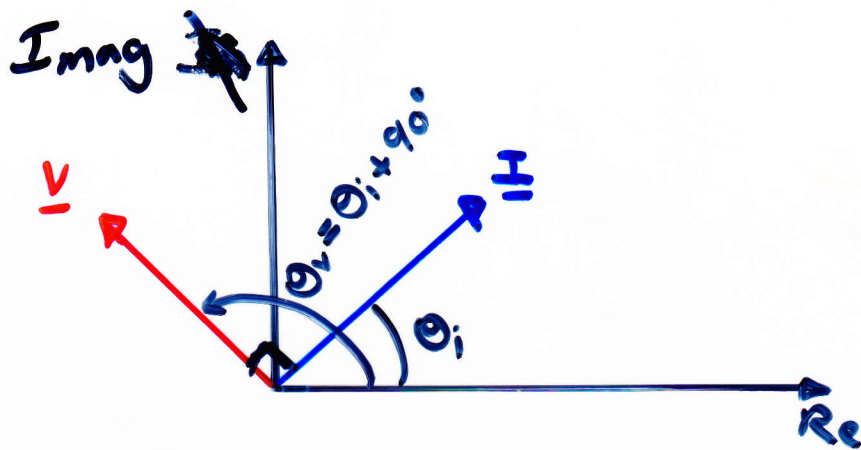

Example 8.6

Current in a 0.05 H inductor is $I = 4 \angle -30^\circ\text{ A}$.
If the freq. of the current is 60 Hz , determine the voltage across the inductor

$$\underline{V} = j\omega L \underline{I}$$


$$\underline{V} = j 120\pi \times 0.05 \times 4 \angle -30^\circ$$

$$= j 75.4 \angle -30^\circ = 75.4 \angle 90^\circ - 30^\circ$$

$$= 75.4 \angle 60^\circ$$

$$\therefore v_L = 75.4 \cos(120\pi t + 60^\circ) \text{ V}$$

Capacitor

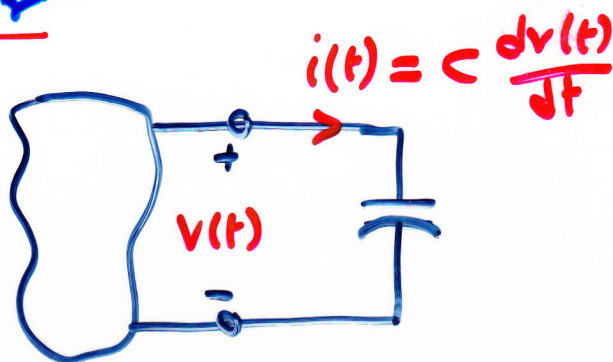

$$i(t) = C \frac{dv(t)}{dt}$$

$$I_m e^{j(\omega t + \theta_i)} = C \frac{d}{dt} V_m e^{j(\omega t + \theta_v)}$$


$$I_m e^{j\theta_i} = j\omega C V_m e^{j\theta_v}$$

$$\underline{I} = j\omega C \underline{V}$$

Sub. for $j = 1e^{j90^\circ}$

$$I_m e^{j\theta_i} = \omega C V_m e^{j(\theta_v + 90^\circ)}$$

voltage lags the current by 90°

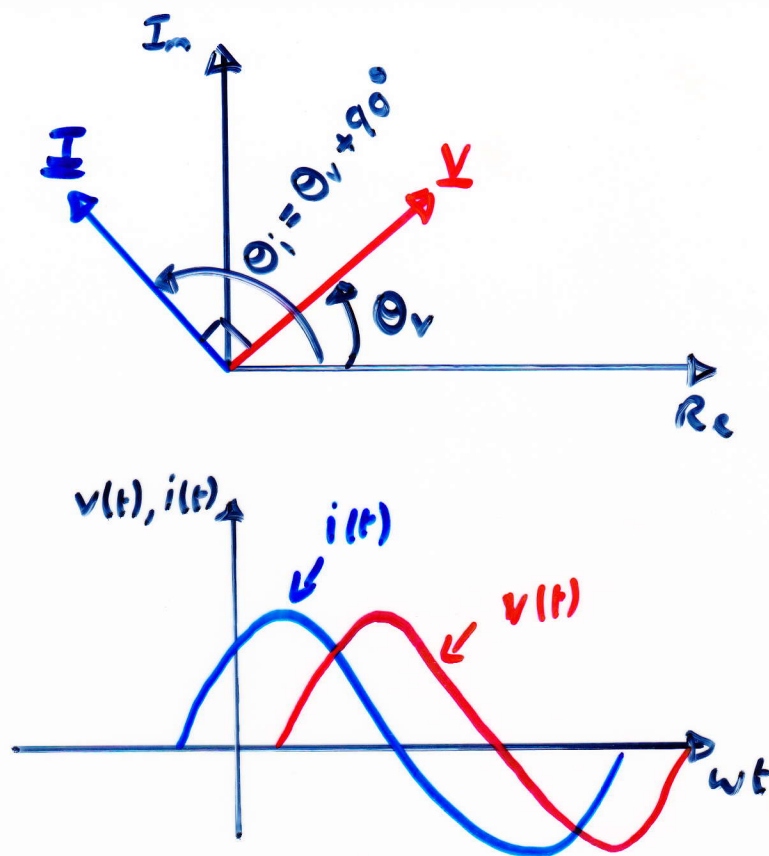

Example E8.7

The current in a $150\ \mu\text{F}$ capacitor is $\underline{I} = 3.6 \angle -145^\circ\ \text{A}$. If the frequency of the current is 60Hz determine the voltage across the capacitor.

$$\underline{I} = j\omega C \underline{V}$$

$$\underline{V} = \frac{\underline{I}}{j\omega C} = \frac{3.6 \angle -145^\circ}{120^\circ \cdot 120\pi \times 150 \times 10^{-6}}$$

$$= 63.66 \angle -235^\circ$$

$$V_c = 63.66 \cos(120\pi t - 235^\circ)$$