
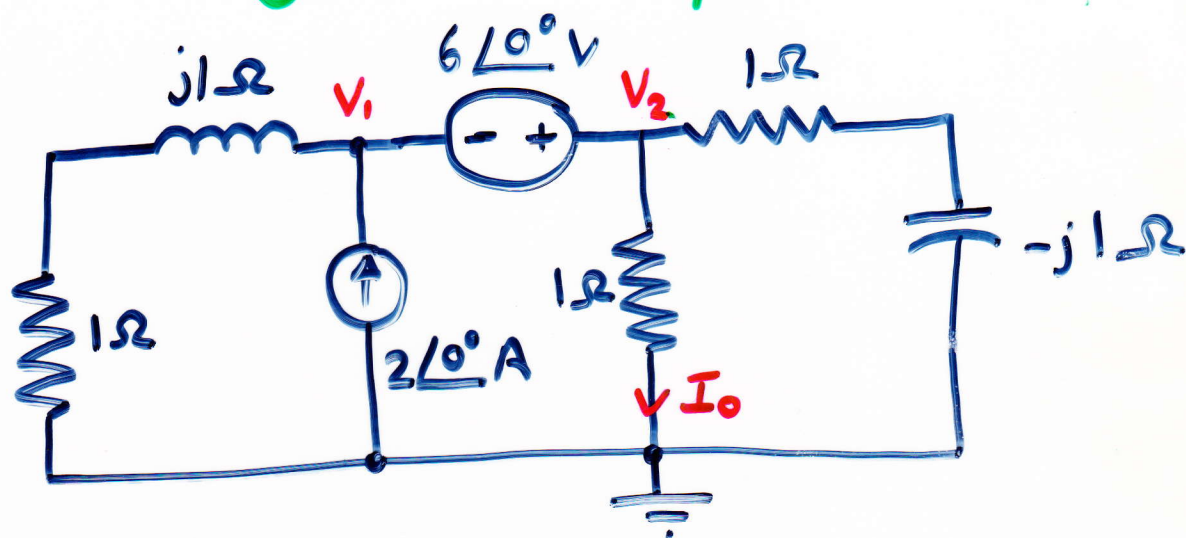


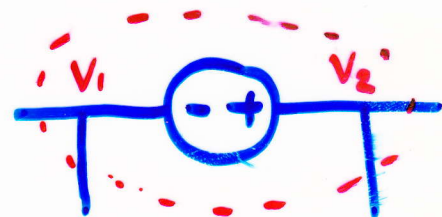Examples of Different Analysis Techniques with Phasors.



Employ nodal analysis.

Apply KCL to a supernode centred on the voltage source.



$$\frac{V_1}{1+j} - 2\angle 0^\circ + \frac{V_2}{1} + \frac{V_2}{1-j} = 0$$

Also $V_2 = V_1 + 6\angle 0^\circ$

$$\therefore \frac{V_2 - 6\angle 0^\circ}{1+j} - 2\angle 0^\circ + \frac{V_2}{1} + \frac{V_2}{1-j} = 0$$

$$V_2 \left[\frac{1}{1+j} + 1 + \frac{1}{1-j} \right] = \frac{6 + 2 + 2j}{1+j}$$

Considering L.H.S.

$$V_2 \left[\frac{1}{1+j} + \frac{1+j}{1+j} + \frac{j}{1+j} \right] = V_2 \left[\frac{2+2j}{1+j} \right]$$

$$\therefore V_2 = \frac{8+2j}{1+j} \times \frac{1+j}{2+2j}$$


$$= \frac{4+j}{1+j}$$

Since $I_0 = \frac{V_2}{1\Omega}$

$$I_0 = \frac{4+j}{1+j} = \frac{4+j}{1+j} \frac{(1-j)}{(1-j)}$$

$$= \frac{4+j-4j+1}{2} = \frac{5}{2} - \frac{3j}{2} \text{ A.}$$

Same problem but employ loop analysis

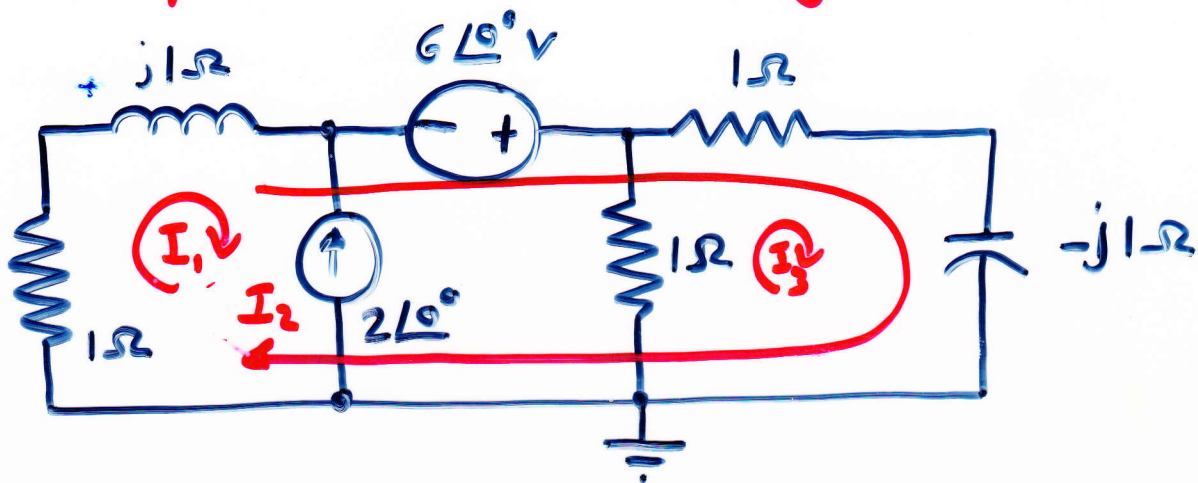

$$\underline{I}_1 = -2\angle 0^\circ \quad (1)$$

$$1(\underline{I}_1 + \underline{I}_2) + j1(\underline{I}_1 + \underline{I}_2) - 6\angle 0^\circ + 1(\underline{I}_2 + \underline{I}_3) - j1(\underline{I}_2 + \underline{I}_3) = 0 \quad (2)$$

$$1\underline{I}_3 + 1(\underline{I}_2 + \underline{I}_3) - j1(\underline{I}_2 + \underline{I}_3) = 0 \quad (3)$$

From (1) & (2)

$$-2 + \underline{I}_2 - 2j + j\underline{I}_2 - 6 + \underline{I}_2 + \underline{I}_3 - j\underline{I}_2 - j\underline{I}_3 = 0$$

$$2\underline{I}_2 + \underline{I}_3(1 - j) = 8 + 2j$$

Simplifying (3)

$$\underline{I}_2(1 - j) + \underline{I}_3(2 - j) = 0$$

$$\text{So } I_2 = -I_3 \frac{(2-j)}{(1-j)}$$

$$\therefore I_3 \left\{ \frac{-2(2-j)}{(1-j)} + 1-j \right\} = 8+2j$$

$$I_3 (-2-j)(1+j) + 1-j = 8+2j$$

$$I_3 (-2-2j+j-1+1-j) = 8+2j$$

$$I_3 (-2-2j) = 8+2j$$

$$I_3 = \frac{-(4+j)}{(1+j)} = \frac{-(4+j)(1-j)}{2}$$



$$= \frac{-5+3j}{2}$$

$$\underline{I_0} = -I_3 = \frac{5}{2} - \frac{3}{2}j$$



Apply Superposition to the circuit.

Consider first the current source.

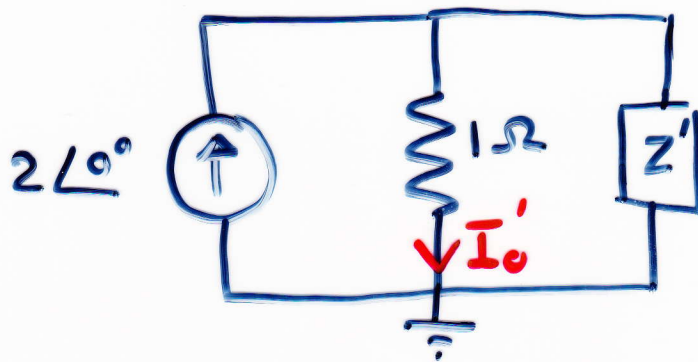
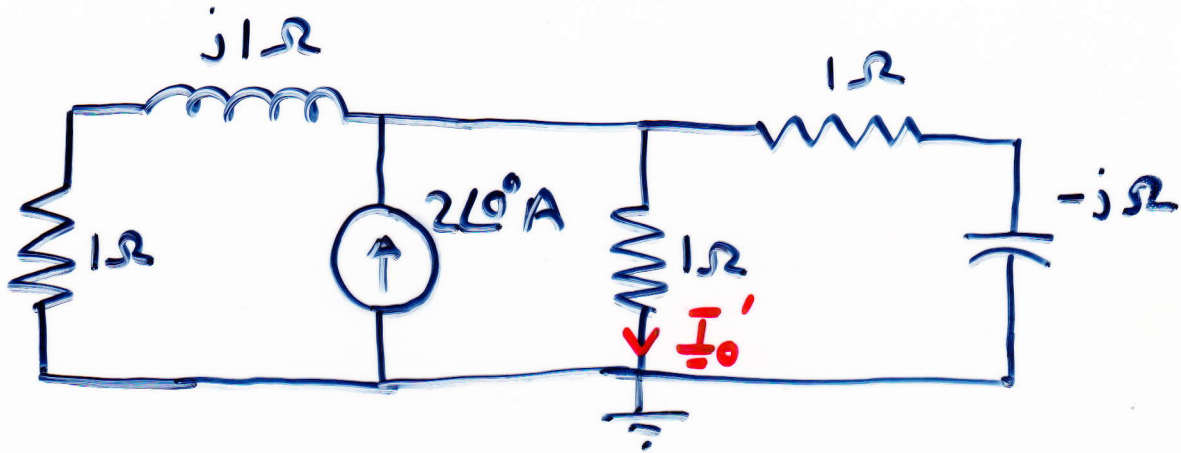


$$Z' = \frac{(1-j)(1+j)}{1-j+1+j}$$

$$Z' = 1\Omega$$

$$\therefore I_0' = 1\angle 0^\circ \text{ A}$$

Consider the voltage source (only).

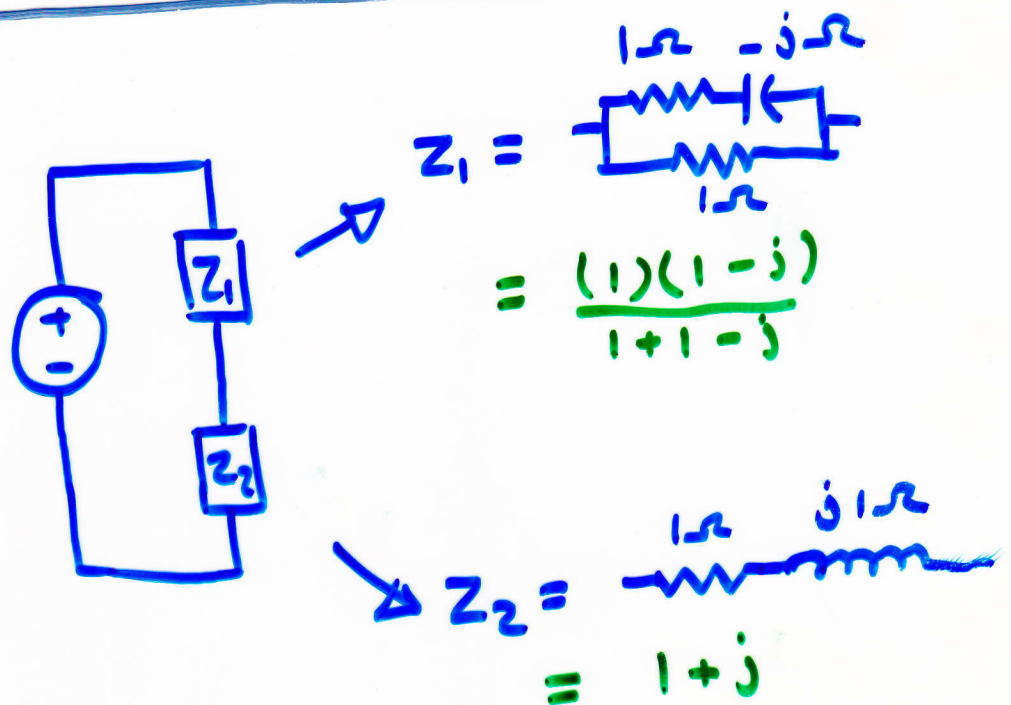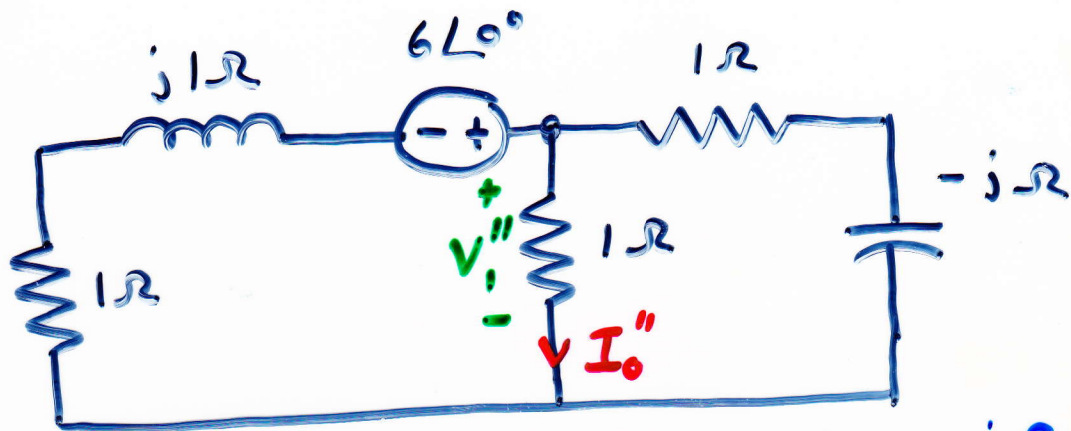

Voltage division

$$V_1'' = \frac{6\angle 0^\circ \times \left(\frac{1-j}{2-j}\right)}{1+j + \left(\frac{1-j}{2-j}\right)}$$

$$= \frac{6 \times \left(\frac{1-j}{2-j}\right)}{\frac{2+2j-j+1+1-j}{2-j}} = \frac{6(1-j)}{4}$$

$$\underline{I}_0'' = \frac{\underline{V}_1''}{1\Omega} = \frac{6}{4}(1-j)$$


Now combining results from the individual
Sources:

$$\underline{I}_0 = \underline{I}_0' + \underline{I}_0'' = 1 + \frac{6}{4}(1-j)$$

$$= \frac{5}{2} - \frac{3}{2}j$$




Analysis techniques (continued)

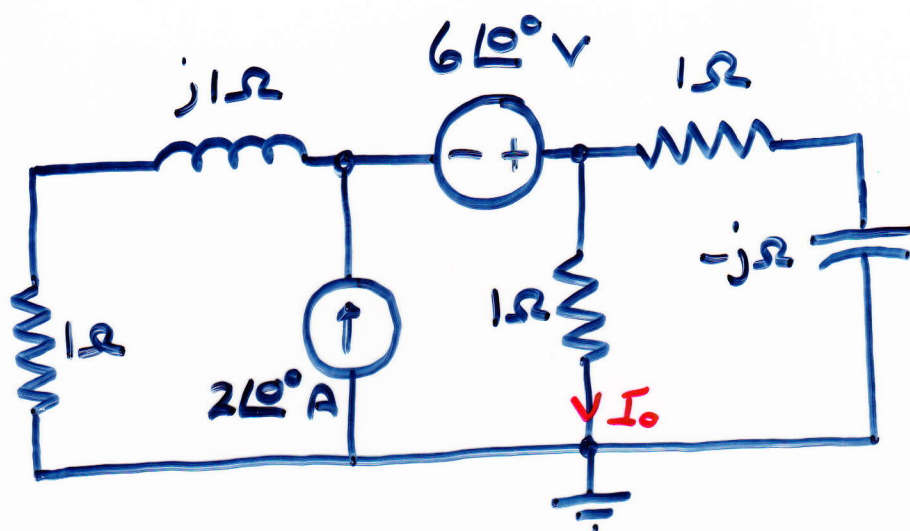

Source Exchange

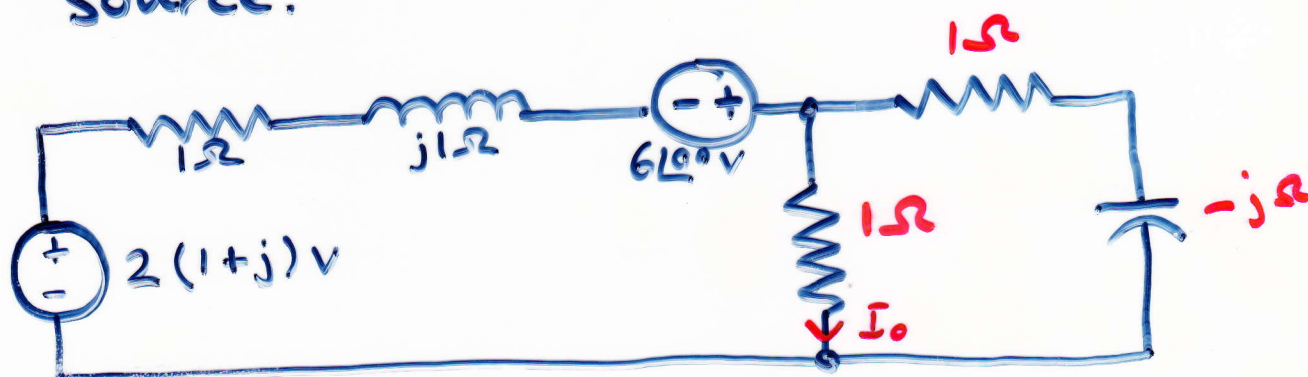- Replace current source with a voltage source.




- Combine voltage sources $6 + 2(1+j) \text{ V}$

- Transform

voltage source + series impedance




current source + parallel impedance

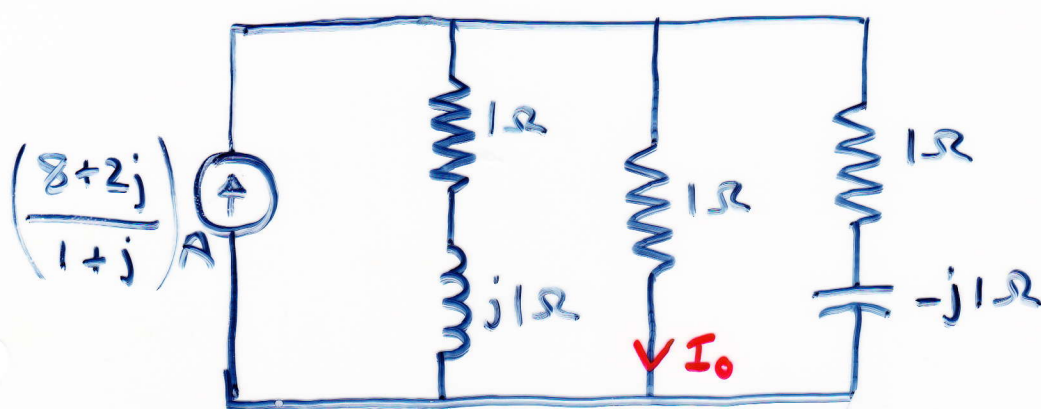

- Combine all impedances EXCEPT the 1Ω resistor that I_0 passes through.
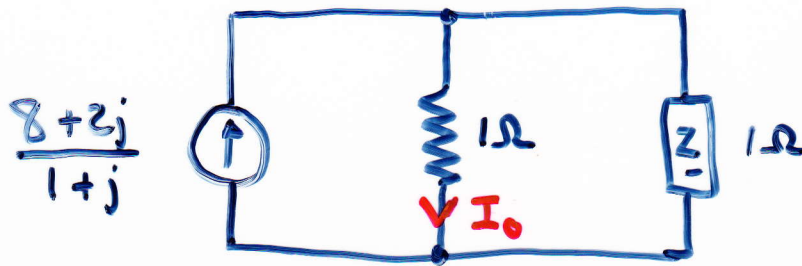
$$\underline{Z} = \frac{(1+j)(1-j)}{1+j+1-j} = 1\Omega$$




• \underline{I}_0 can be determined by current division

$$\underline{I}_0 = \left(\frac{8+2j}{1+j} \right) \left(\frac{1}{2} \right) = \frac{4+j}{1+j}$$


$$= \left(\frac{5}{2} - \frac{3}{2}j \right) \text{ A}$$

Thévenin analysis.



- Aim to obtain

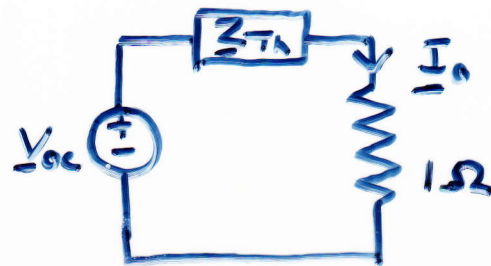

- Find V_{oc}

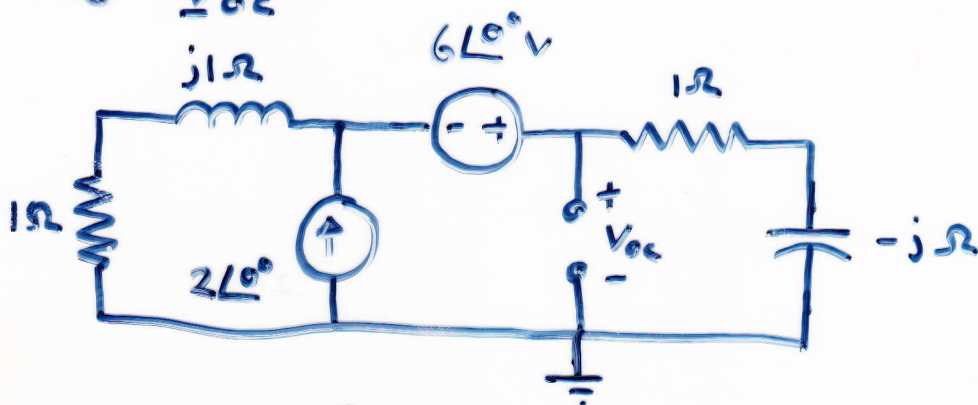

- Source transformation

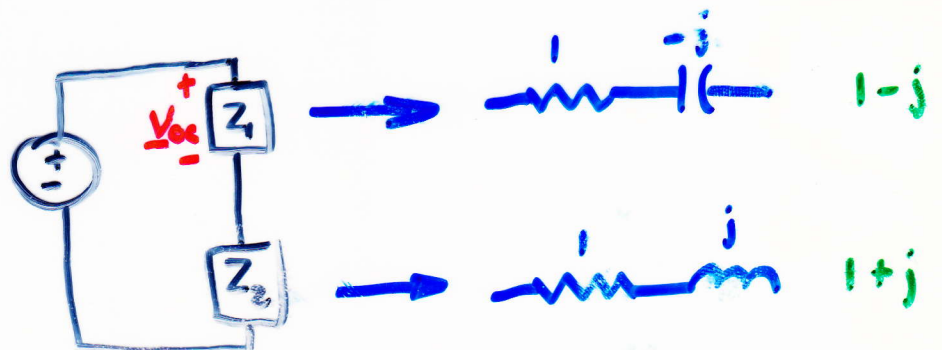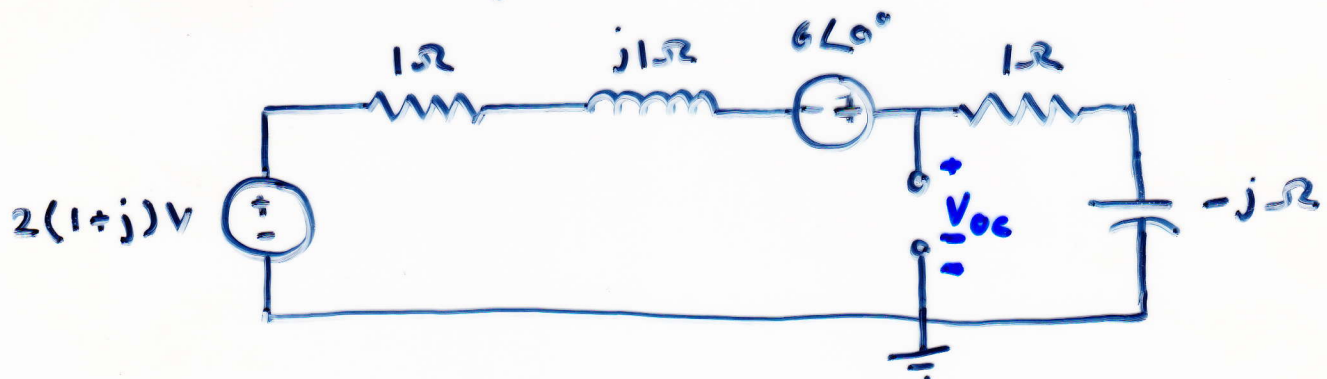


- Voltage division


$$\underline{V}_{oc} = (8 + 2j) \left(\frac{1-j}{1-j + 1+j} \right) = (4+j)(1-j)$$

$$= (5 - 3j) \text{ V}$$

- Determine Thevenin impedance, Z_{Th} .

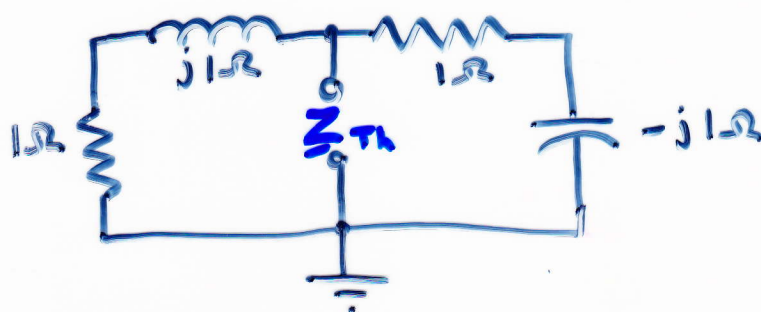

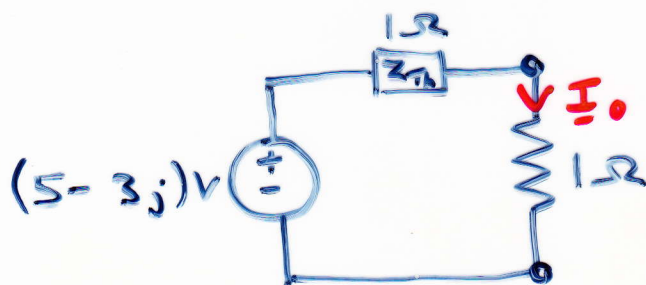
$$Z_{Th} = \frac{(1+j)(1-j)}{1+j + 1-j} = 1\Omega$$




$$\underline{I}_0 = \frac{(5-3j)}{2}$$

$$= \underline{\underline{\frac{5}{2} - \frac{3}{2}j}}$$

Norton Analysis

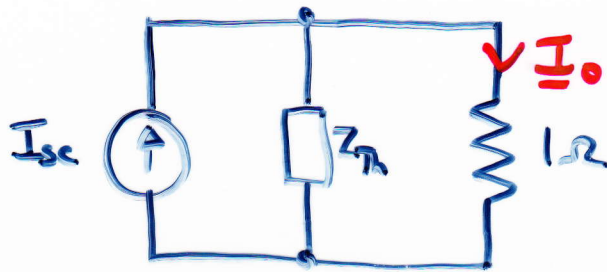


- Determine I_{sc}

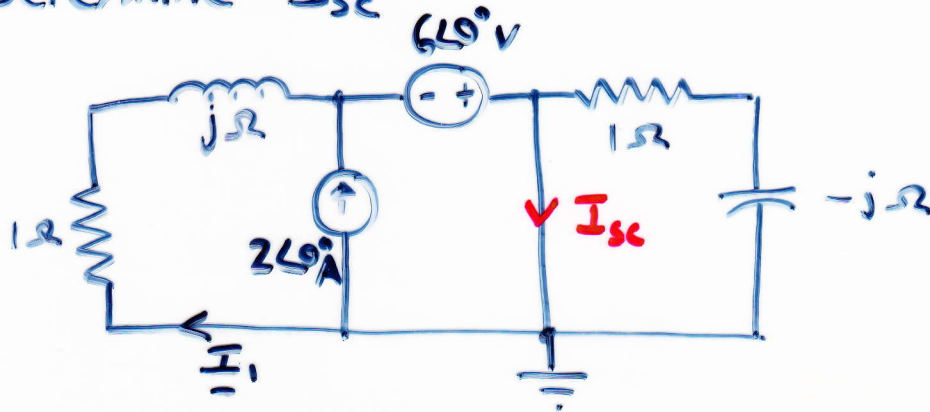

$$\underline{I}_1 = \frac{6\angle 0^\circ}{1+j} = \frac{6}{1+j}$$

$$\underline{I}_{sc} = \underline{I}_1 + 2\angle 90^\circ = 2 + \frac{6}{1+j}$$

$$= \frac{8 + 2j}{1+j} \text{ A}$$

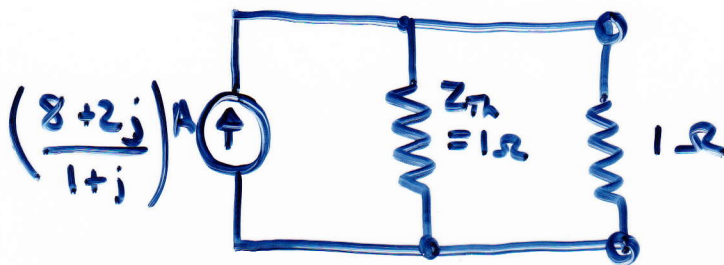

- Current division

$$\begin{aligned} I_o &= \frac{1}{2} \left(\frac{8+2j}{1+j} \right) \\ &= \left(\frac{5}{2} - \frac{3}{2} j \right) \text{ A} \end{aligned}$$