



# Frequency Response Analysis

Let us consider in turn

- resistor
- inductor
- capacitor



Resistor

$$Z_R = R = R \angle 0^\circ$$

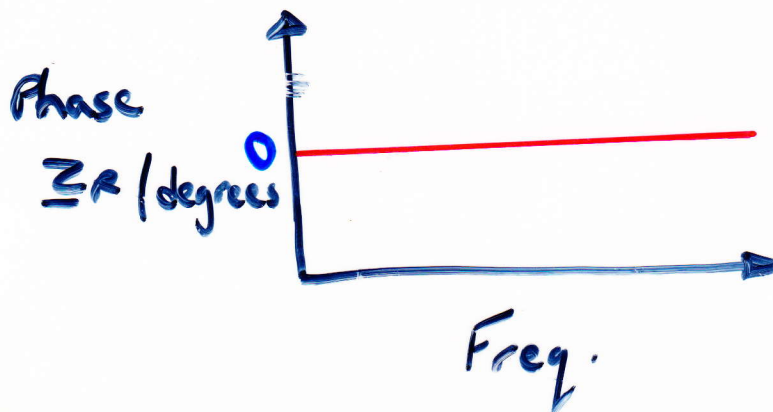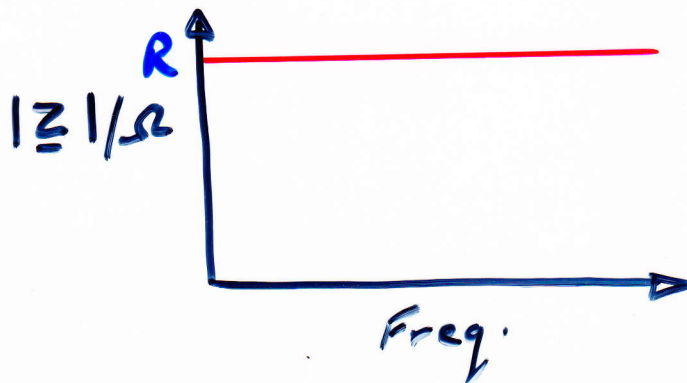

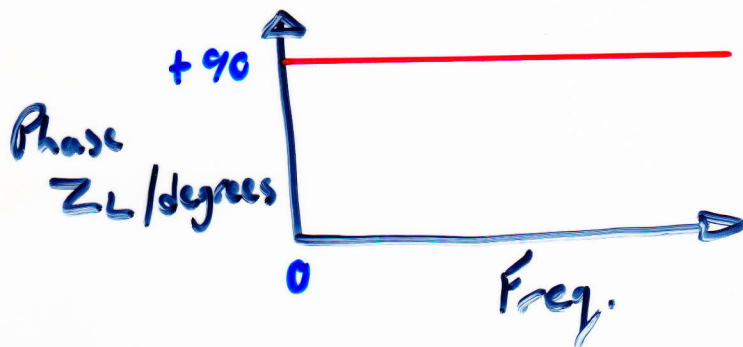
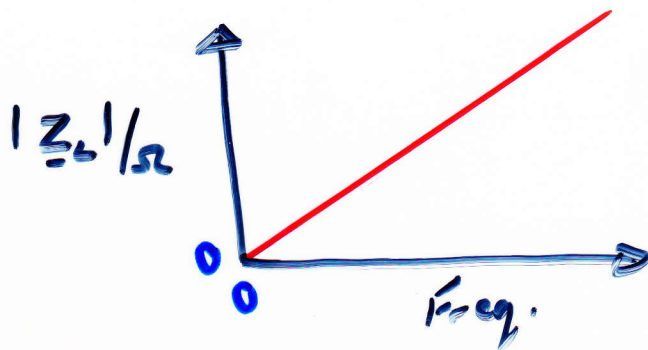
## Inductor

$$Z_L = j\omega L = \omega L \angle 90^\circ$$



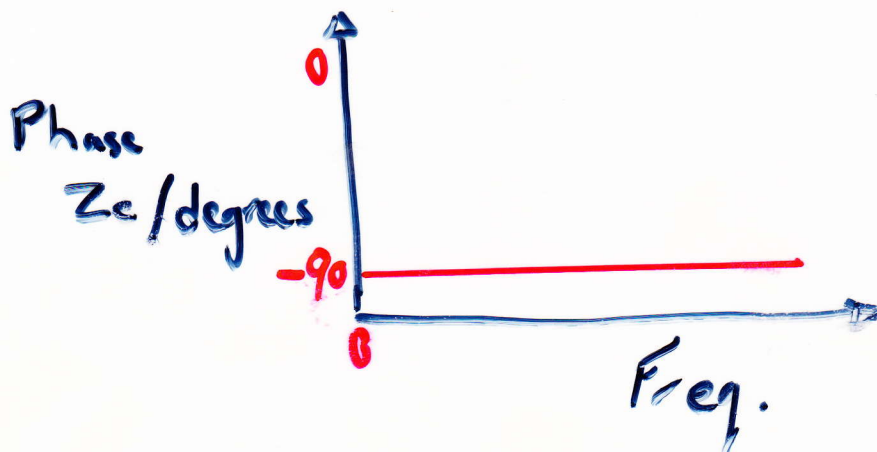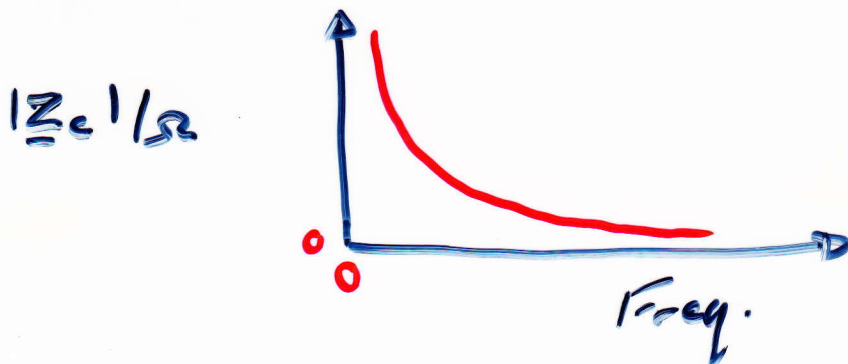
## Capacitor

$$Z_C = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$





Consider RLC in series

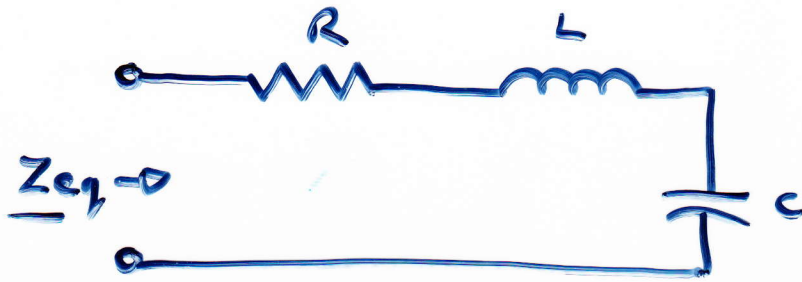

$$Z_{eq} = R + j\omega L + \frac{1}{j\omega C}$$
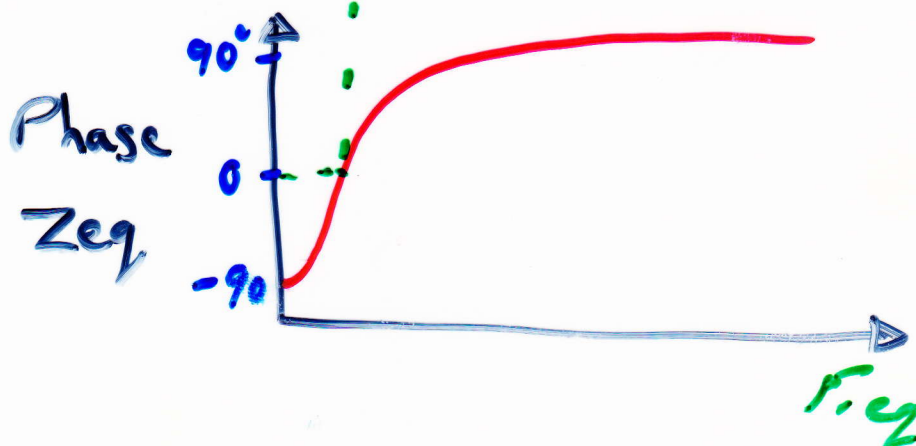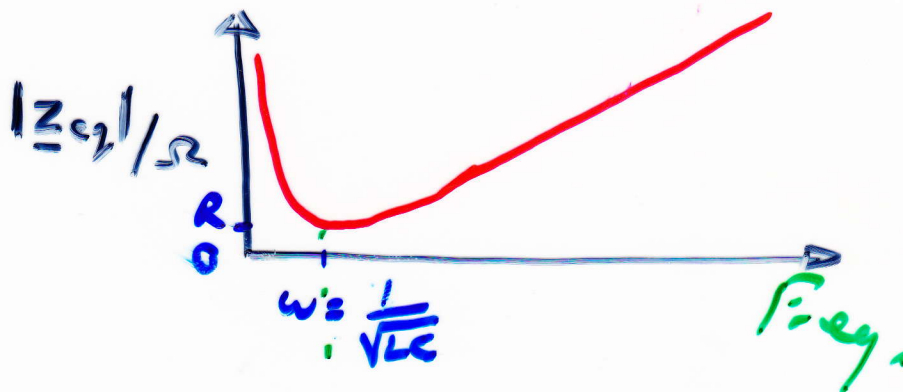
$$Z_{eq} = \frac{(j\omega)^2 LC + j\omega RC + 1}{j\omega C}$$



With

$$\underline{Z}_{eq} = \frac{(j\omega)^2 LC + j\omega RC + 1}{j\omega C}$$

Let us replace  $j\omega$  with  $s$

$$\therefore \underline{Z}_{eq} = \frac{s^2 LC + sRC + 1}{sC}$$


This ratio of two polynomials can be generalised to

$$\underline{Z}(s) = \frac{N(s)}{D(s)} = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}$$

This general form also holds for

- voltages
  - currents
  - admittances
  - gains
- of networks.

## Example

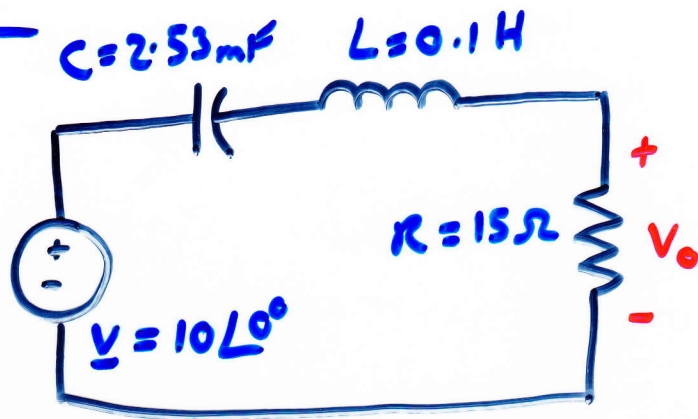

To find  $V_o$  use voltage division.

$$\underline{V_o} = \left( \frac{R}{R + j\omega L + \frac{1}{j\omega C}} \right) \underline{V_s}$$


$$\underline{V_o} = \left( \frac{j\omega C R}{(j\omega)^2 L C + j\omega C R + 1} \right) \underline{V_s}$$

$$V_o = \left( \frac{(j\omega)(37.95 \times 10^{-3})}{(j\omega)^2 (2.53 \times 10^{-4}) + j\omega(37.95 \times 10^{-3}) + 1} \right) 10\angle 0^\circ$$



$$V_o = \frac{S 37.95 \times 10^{-2}}{S^2 2.53 \times 10^{-4} + S 37.95 \times 10^{-3} + 1}$$

fregs(b,a),



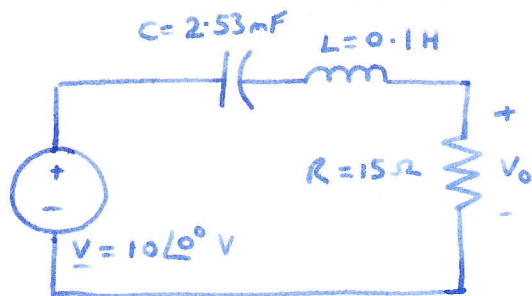

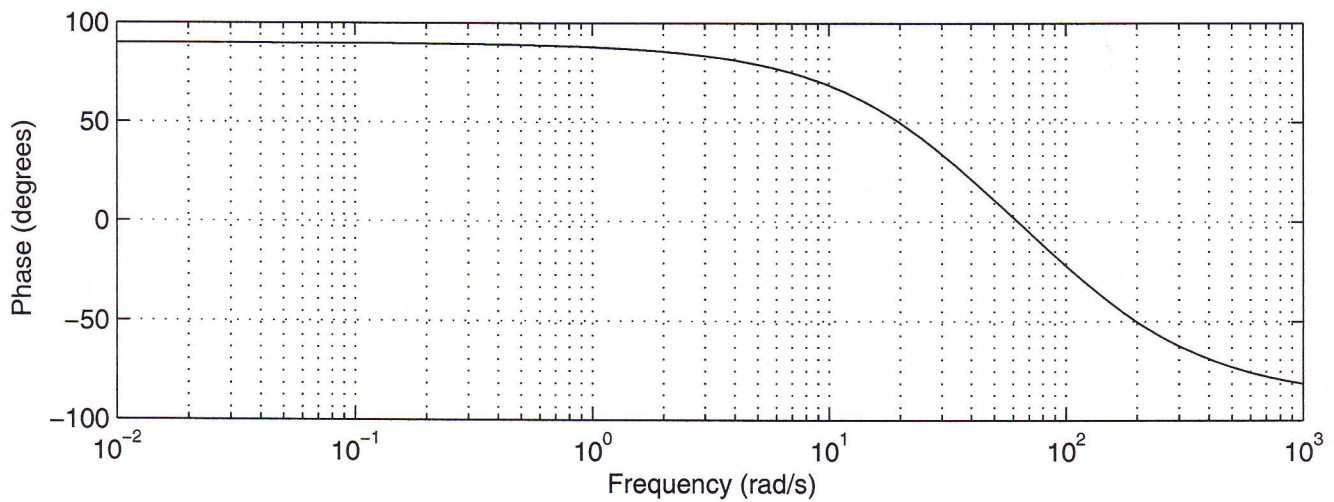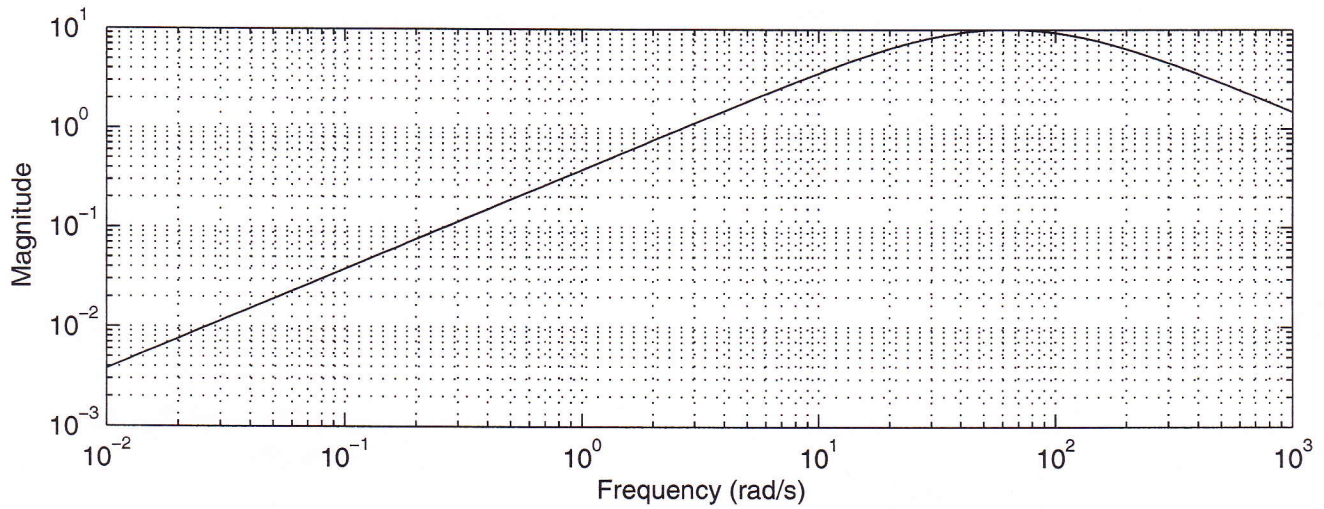
$$\underline{V}_o = \frac{537.95 \times 10^{-2}}{s^2 2.53 \times 10^{-4} + s 37.95 \times 10^{-3} + 1}$$



## Example

Gain of an audio amplifier

Equivalent circuit

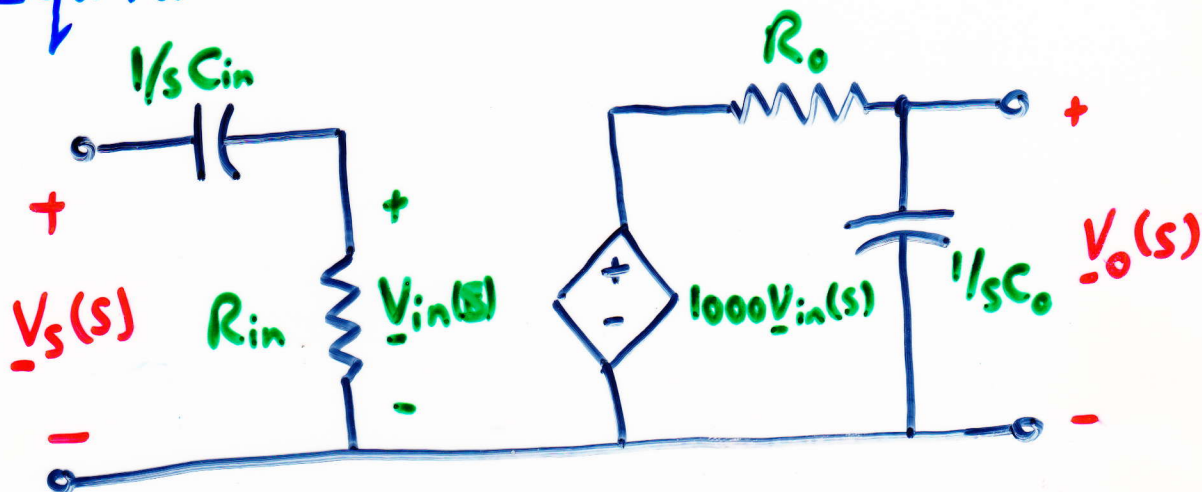


$$\underline{G}_v(s) = \frac{\underline{V}_o(s)}{\underline{V}_s(s)}$$

Voltage division

$$\underline{G}_v(s) = \frac{\underline{V}_o(s)}{\underline{V}_s(s)} = \frac{\underline{V}_{in}(s)}{\underline{V}_s(s)} \frac{\underline{V}_o(s)}{\underline{V}_{in}(s)} = \left[ \frac{R_{in}}{R_{in} + 1/sC_{in}} \right] (1000) \left[ \frac{1/sC_o}{R_o + 1/sC_o} \right]$$
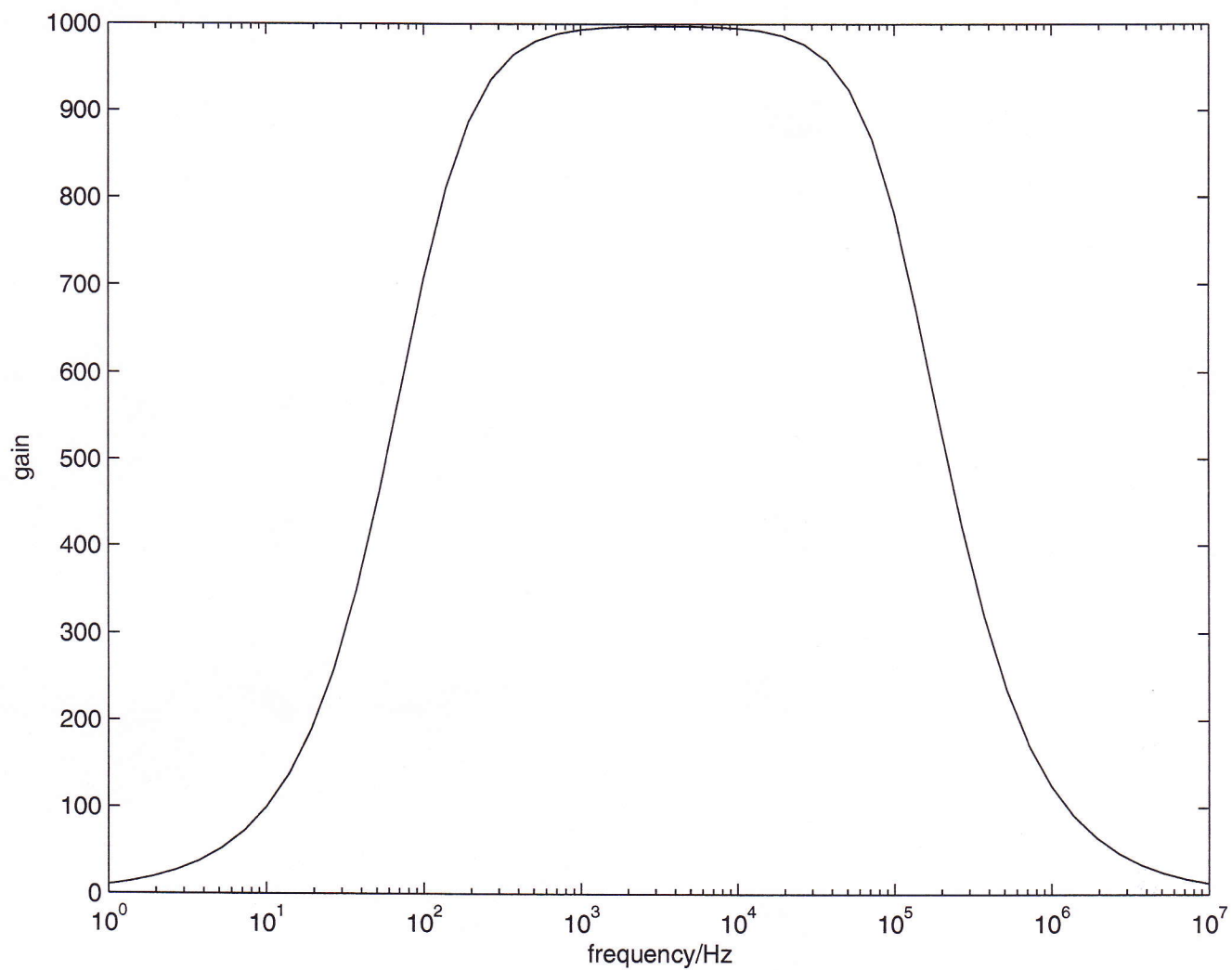
$$\underline{G}_v(s) = \left[ \frac{sC_{in}R_{in}}{1 + sC_{in}R_{in}} \right] (1000) \left[ \frac{1}{1 + sC_oR_o} \right]$$





# Sinusoidal Frequency Analysis

## Bode Plots

### Poles & Zeros

We have seen that the network transfer function can be expressed as the ratio of two polynomials.

$$\underline{H(s)} = \frac{\underline{N(s)}}{\underline{D(s)}} = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0} \quad (a)$$

Note: transfer functions are

Input	Output	Transfer Function	Symbol
voltage	voltage	voltage gain	$\underline{G}_v(s)$
current	voltage	transimpedance	$\underline{Z}(s)$
current	current	current gain	$\underline{G}_i(s)$
voltage	current	transadmittance	$\underline{Y}(s)$

Now (a) can be written in form

$$\underline{H(s)} = \frac{K_0 (s-z_1)(s-z_2) \dots (s-z_m)}{(s-p_1)(s-p_2) \dots (s-p_n)}$$

$$(e.g. s^2 - 5s + 6 = (s-2)(s-3))$$

$K_0$  - constant

$z_1, \dots, z_m$  are roots of  $N(s)$

$p_1, \dots, p_n$  are roots of  $D(s)$

If  $s = z_1$  or  $z_2, \dots, z_m$   $\underline{H(s)}$  becomes zero ZEROS

If  $s = p_1$  or  $p_2, \dots, p_n$   $\underline{H(s)}$  becomes  $\infty$  POLES

Zeros & poles can be complex, however, they must occur in conjugate pairs.

E.g.  $G_N(s) = \left[ \frac{s}{s+100\pi} \right]^{1000} \left[ \frac{40,000\pi}{s+40,000\pi} \right]$

$$\therefore K_0 = 4 \times 10^7 \pi$$



$$z_1 = 0$$

$$p_1 = -100\pi, p_2 = -40,000\pi$$

Putting into freq.,  $p_1 = -50 \text{ Hz}$ ,  $p_2 = -20,000 \text{ Hz}$

$$R_{in} = 1M\Omega, C_{in} = 3.18nF, R_o = 100\Omega, C_o = 79.58nF$$
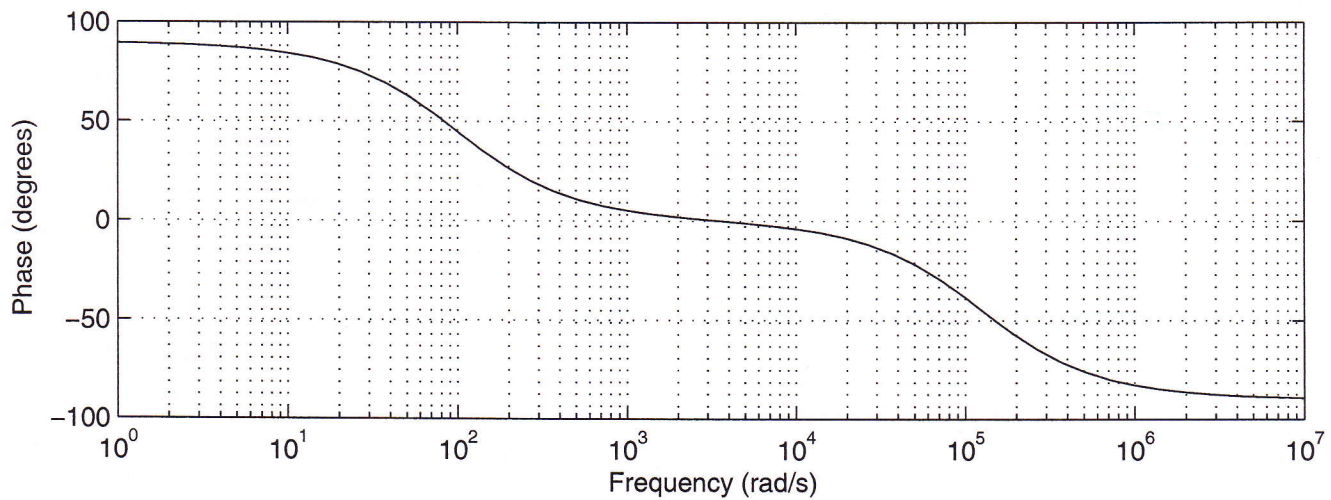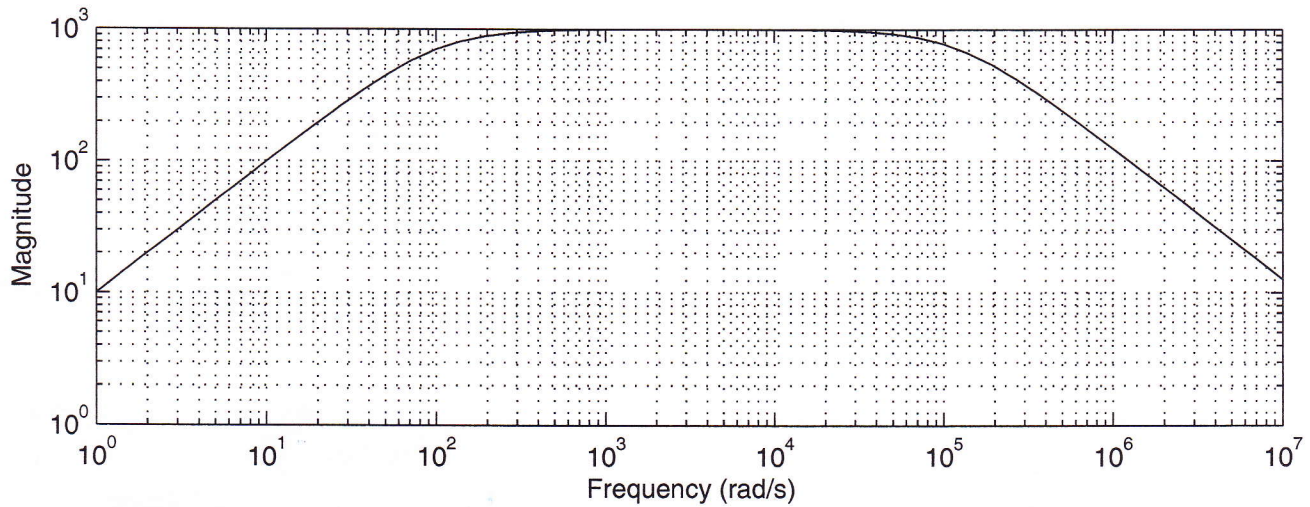
$$G_v(s) = \left[ \frac{s}{s + 100\pi} \right] (1000) \left[ \frac{40,000\pi}{s + 40,000\pi} \right]$$





## Frequency Analysis.

Can express transfer function as



$$\underline{H}(j\omega) = \underbrace{M(\omega)}_{\text{Magnitude}} e^{j\underbrace{\phi(\omega)}_{\text{Phase}}}$$

Aim is to examine magnitude & phase as functions of  $\omega$ .
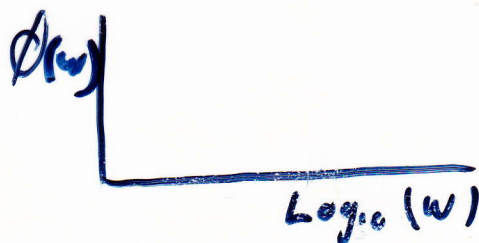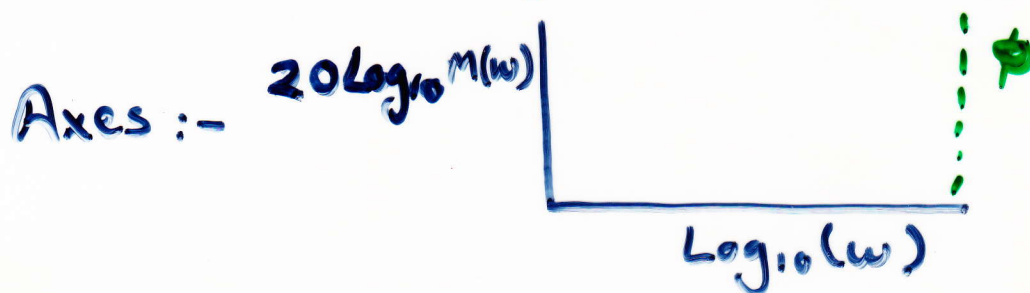
## Bode Plot

Tool for analysis and design of frequency dependent systems, filters, tuners & amplifiers.

Rather than plotting the characteristic point by point can use straight-line approximations.



Use decibels


$$dB = 10 \log_{10} \frac{P_2}{P_1}$$

$P_n$  is a power

Using  $P = I V$  and Ohm's law can see have

$$dB = 10 \log_{10} \frac{|V_2|^2 / R}{|V_1|^2 / R} = 10 \log_{10} \frac{|I_2|^2 R}{|I_1|^2 R}$$

$$= 20 \log_{10} \frac{|V_2|}{|V_1|} = 20 \log_{10} \frac{|I_2|}{|I_1|}$$

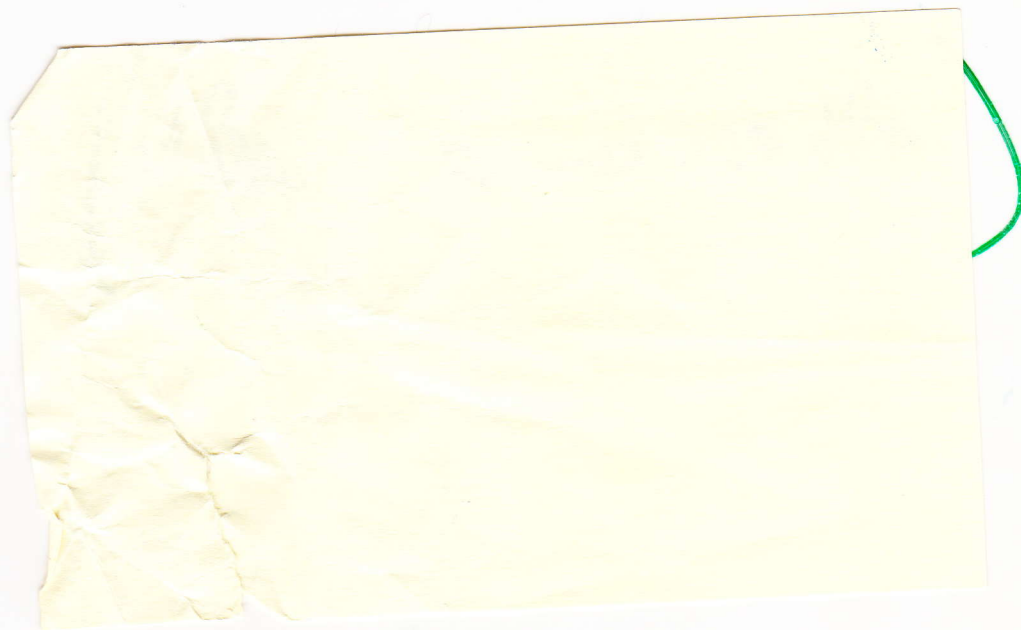



Returning to our transfer function. Use general expression

$$\underline{H}(j\omega) = \frac{K_0 (j\omega)^{\pm N} (1+j\omega\tau_1) [1+2\zeta_3(j\omega\tau_3) + (j\omega\tau_3)^2] \dots}{(1+j\omega\tau_a) [1+2\zeta_b(j\omega\tau_b) + (j\omega\tau_b)^2] \dots} \quad (b)$$

Have the following factors

1. Freq-independent factor  $K_0 > 0$
2. Poles  $(j\omega)^{-N}$ , zeros  $(j\omega)^{+N}$  at origin
3. Poles or zeros of form  $(1+j\omega\tau)$
4. Quadratic poles or zeros of form  $1+2\zeta(j\omega\tau) + (j\omega\tau)^2$


Manipulating (b)

$$\begin{aligned} 20 \log_{10} |\underline{H}(j\omega)| &= 20 \log_{10} K_0 \pm 20N \log_{10} |j\omega| \\ &\quad + 20 \log_{10} |1+j\omega\tau_1| \\ &\quad + 20 \log_{10} |1+2\zeta_3(j\omega\tau_3) + (j\omega\tau_3)^2| \\ &\quad + \dots - 20 \log_{10} |1+j\omega\tau_a| \\ &\quad - 20 \log_{10} |1+2\zeta_b(j\omega\tau_b) + (j\omega\tau_b)^2| \dots \end{aligned}$$

$$\begin{aligned} \angle \underline{H}(j\omega) &= 0 \pm N(90^\circ) + \tan^{-1} \omega\tau_1 + \tan^{-1} \left( \frac{2\zeta_3 \omega\tau_3}{1-\omega^2\tau_3^2} \right) \\ &\quad + \dots - \tan^{-1} \omega\tau_a - \tan^{-1} \left( \frac{2\zeta_b \omega\tau_b}{1-\omega^2\tau_b^2} \right) \dots \end{aligned}$$



Considering the individual factors.

### Constant Term

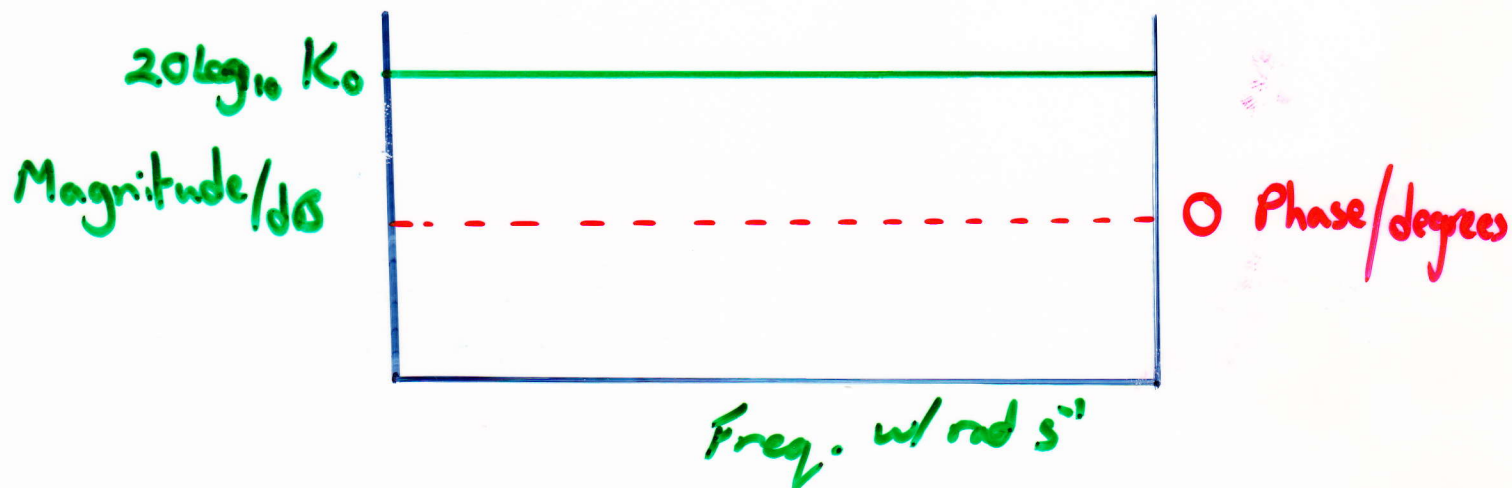
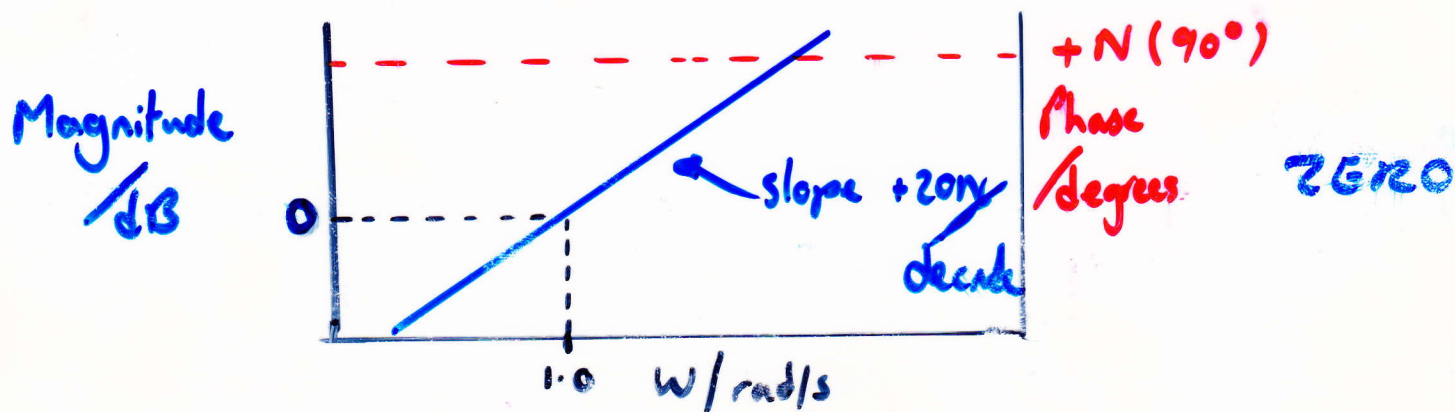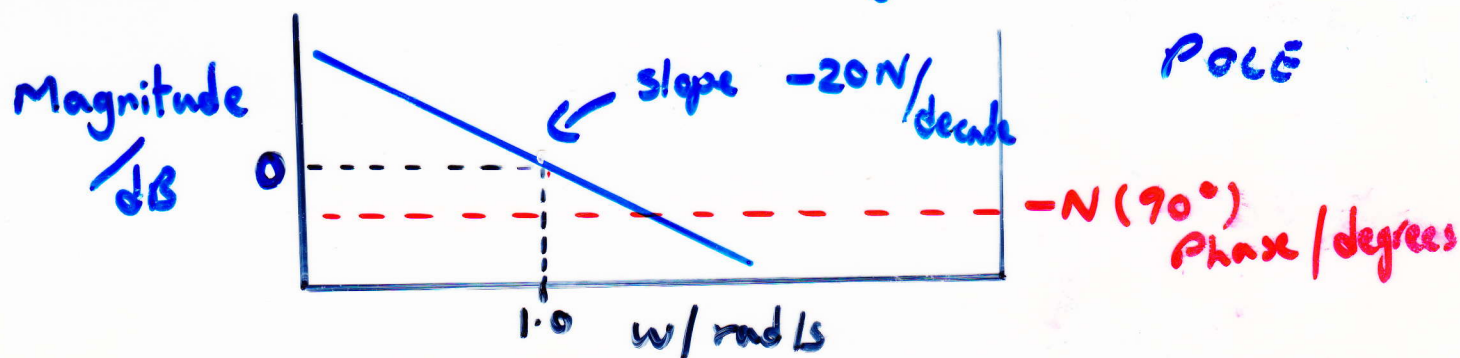
### Poles or Zeros at the origin

$$(j\omega)^{\pm N} \rightarrow \pm 20N \log_{10} \omega$$



## Simple Pole or Zero.

$$20 \log_{10} |1 + j\omega\tau|$$

For  $\omega\tau \ll 1$  then  $(1 + j\omega\tau) \approx 1 \rightarrow 0 \text{ dB}$

For  $\omega\tau \gg 1$  then  $(1 + j\omega\tau) \approx j\omega\tau \rightarrow 20 \log_{10} \omega\tau \text{ dB}$

$\omega\tau = 1$  Break Frequency  $20 \log_{10} |1 + j|$   
 $= 20 \log_{10} \sqrt{2} = 3 \text{ dB}.$


$$\phi = \tan^{-1} \omega\tau \quad \therefore \phi = 45^\circ \text{ at break freq.}$$

$\phi$  varies between  $0^\circ$  &  $90^\circ$

At twice break freq  $\phi = 63.4^\circ$ .

At half break freq  $\phi = 26.6^\circ$ .

## Simple Pole

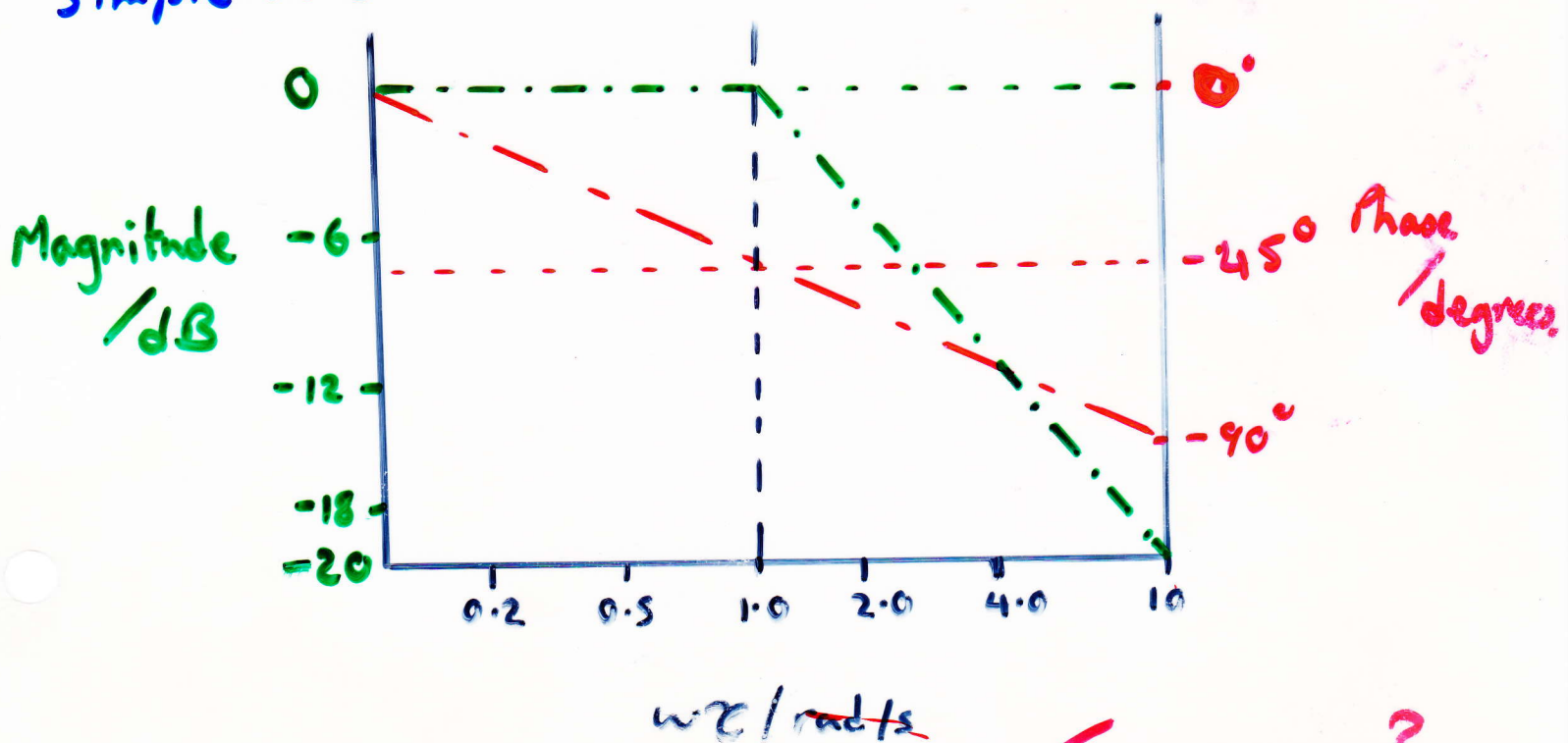

For zero?