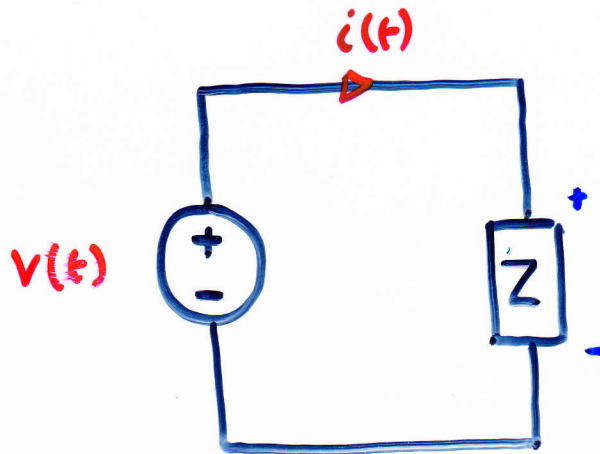


# Instantaneous & Average Power



Steady-state:

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$\therefore$  Instantaneous power

$$p(t) = v(t) i(t)$$

$$= V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

Now

$$\cos \phi_1 \cos \phi_2 = \frac{1}{2} [\cos(\phi_1 - \phi_2) + \cos(\phi_1 + \phi_2)]$$


$$\therefore p(t) = \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)]$$

Note:

Time independent

Twice freq. of input.

# Example (Irwin 9.1)

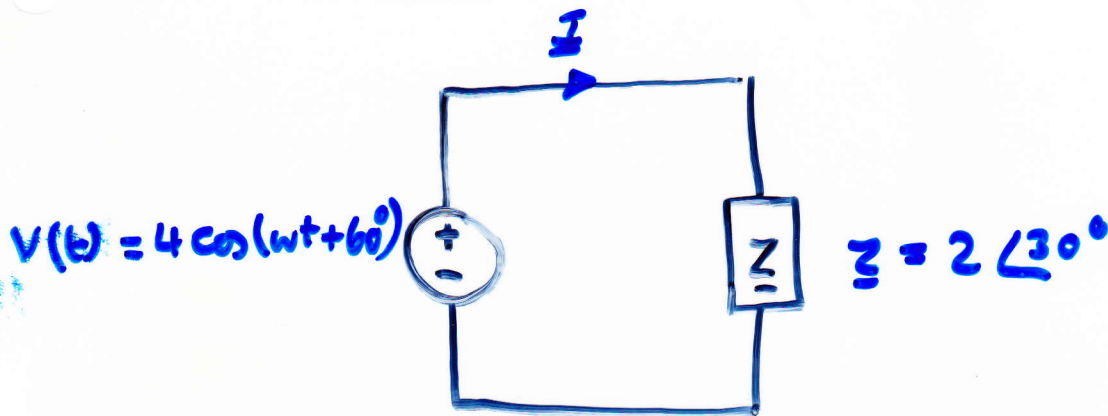


Determine

- i) current,
- ii) instantaneous power.

$$\begin{aligned} \text{i)} \quad \underline{I} &= \frac{4 \angle 60^\circ}{2 \angle 30^\circ} \\ &= 2 \angle 30^\circ \text{ A.} \end{aligned}$$

$$\text{So } i(t) = 2 \cos(\omega t + 30^\circ)$$

$$\begin{aligned} \text{ii)} \quad p(t) &= 4 [\cos(30^\circ) + \cos(2\omega t + 90^\circ)] \\ &= 3.46 + 4 \cos(2\omega t + 90^\circ) \text{ W} \end{aligned}$$

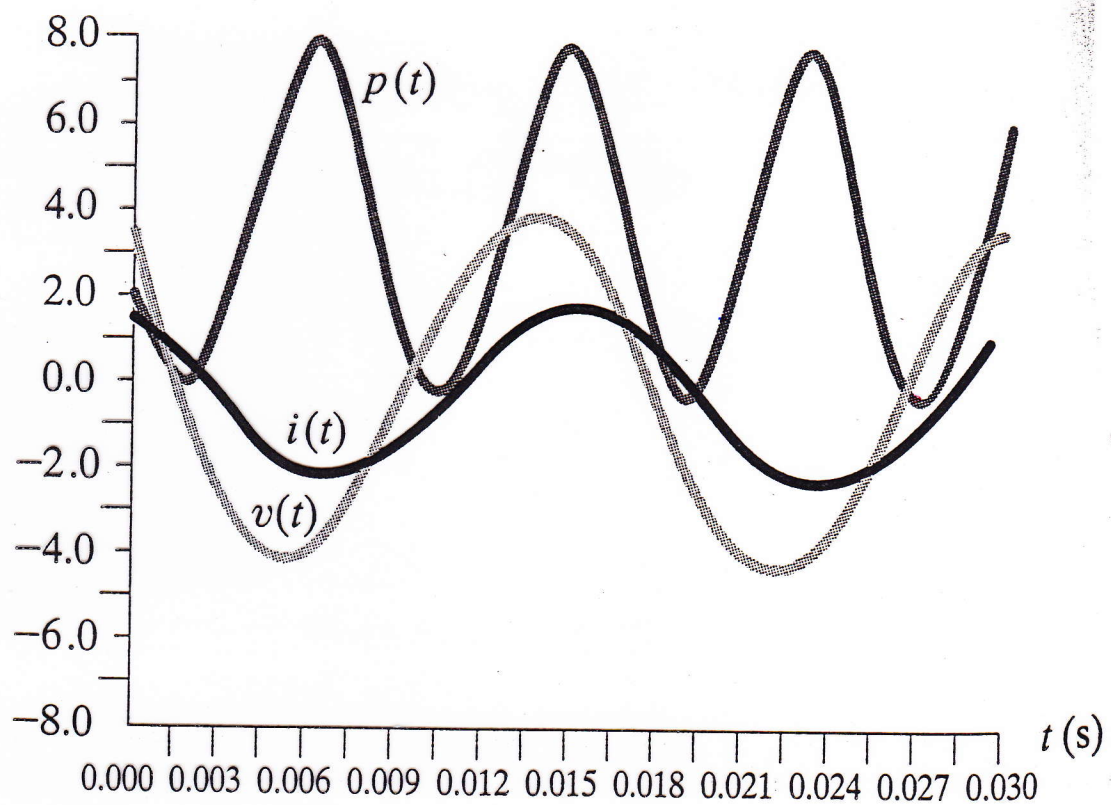

**Figure 9.2** Plots of  $v(t)$ ,  $i(t)$ , and  $p(t)$  for the circuit in Example 9.1 using  $f = 60$  Hz.

# Average Power.

Power is varying sinusoidally so ~~average~~ <sup>integrate</sup> over a period and divide by that period.

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt$$

$$= \frac{1}{T} \int_{t_0}^{t_0+T} V_m I_m \cos(\omega t + \theta_v) (\cos(\omega t + \theta_i)) dt$$

where  $T = \frac{2\pi}{\omega}$

Now

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} \frac{V_m I_m}{2} \left[ \underbrace{\cos(\theta_v - \theta_i)}_{\text{Independent of } t, \text{ so can be taken outside of integral.}} + \underbrace{\cos(2\omega t + \theta_v + \theta_i)}_{\text{zero over a period or integer number of periods.}} \right] dt$$

Independent of  $t$ ,  
so can be taken outside  
of integral.

zero over  
a period or integer  
number of periods.



$$\therefore P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Considering purely resistive circuit.

$$P = \frac{1}{2} V_m I_m$$

For purely reactive circuit

$$P = \frac{1}{2} V_m I_m \cos(90^\circ) \\ = 0.$$

Example.

i)  $\underline{V} = 2 \angle 30^\circ \text{ V}$  and  $\underline{I} = 2 \angle 30^\circ \text{ A}$

ii)  $\underline{V} = 2 \angle 30^\circ \text{ V}$  and  $\underline{I} = 2 \angle 120^\circ \text{ A}$


iii)  $\underline{V} = 2 \angle 30^\circ \text{ V}$  and  $\underline{I} = 2 \angle 60^\circ \text{ A}$

i) 2 W

ii) 0 W

iii) 1.732 W

# Example. (Irwin Example 9.3)

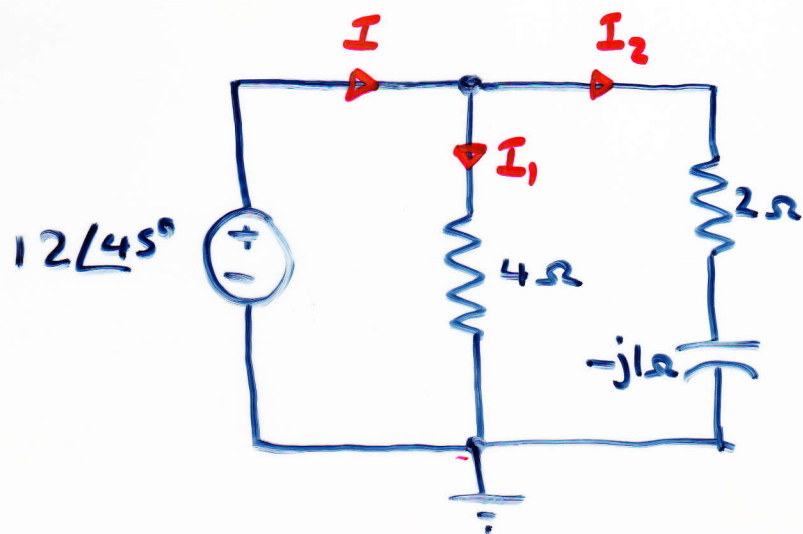

Determine total average power absorbed and total average power supplied.

$$\underline{I}_1 = \frac{12 \angle 45^\circ}{4} = 3 \angle 45^\circ \text{ A}$$

$$\underline{I}_2 = \frac{12 \angle 45^\circ}{2 - j1} = \frac{12 \angle 45^\circ}{2.24 \angle -26.57^\circ}$$

$$= 5.36 \angle 71.57^\circ \text{ A}$$

So  $\underline{I} = \underline{I}_1 + \underline{I}_2$

$$= 3 \angle 45^\circ + 5.36 \angle 71.57^\circ$$

$$= 8.15 \angle 62.10^\circ \text{ A}$$

Average power in  $4\Omega$  resistor

$$P_4 = \frac{1}{2} V_m I_m = \frac{12 \times 3}{2} = 18 \text{ W}$$

Average power of  $2\Omega$  resistor.

$$P_2 = \frac{1}{2} I_m^2 R = \frac{(5.36)^2 \times 2}{2} = 28.7 \text{ W}$$

$\therefore$  Total absorbed is

$$P_A = 18 + 28.7 = \underline{46.7 \text{ W}}$$

Total supplied

$$P_s = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \times 12 \times 8.15 \times \cos(45^\circ - 62.10^\circ)$$

$$= \underline{46.7 \text{ W}}$$

## Effective or RMS values.

So far have seen that the average power absorbed is dependent on the type of source

$$\text{dc supply} \rightarrow I^2 R$$

$$\text{sinusoidal} \rightarrow \frac{1}{2} I_m^2 R$$

What if another type of waveform is used?

Recall we looked at RMS values of waveforms



root mean squared.

This is what is used.



Define

$$P = I_{\text{eff}}^2 R \quad (1)$$

$I_{\text{eff}}$  is effective constant current of current waveform.

Considering the average power due to the waveform

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) R dt \quad (2)$$

$T$ . period.

Equating (1) & (2)

$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt}$$

RMS!

$$\therefore P = I_{\text{rms}}^2 R$$

Similarly

$$P = \frac{V_{\text{rms}}^2}{R}$$

## Example.

Determine the rms value of

$$i(t) = I_m \cos(\omega t - \theta)$$

Period,  $T = \frac{2\pi}{\omega}$

Now 
$$I_{rms} = \left[ \frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t - \theta) dt \right]^{\frac{1}{2}}$$

Using  $\cos^2 \phi = \frac{1}{2} + \frac{1}{2} \cos 2\phi$

$$\therefore I_{rms} = I_m \left\{ \frac{\omega}{2\pi} \int_0^{2\pi/\omega} \left[ \frac{1}{2} + \frac{1}{2} \cos(2\omega t - 2\theta) \right] dt \right\}^{\frac{1}{2}}$$


$$I_{rms} = I_m \left( \frac{\omega}{2\pi} \int_0^{2\pi/\omega} \frac{1}{2} dt \right)^{\frac{1}{2}}$$

$$= I_m \left\{ \left[ \frac{\omega}{2\pi} \left( \frac{t}{2} \right) \right]_0^{2\pi/\omega} \right\}^{\frac{1}{2}} = \frac{I_m}{\sqrt{2}}$$

Example.

~ 2.8

~ 2.0

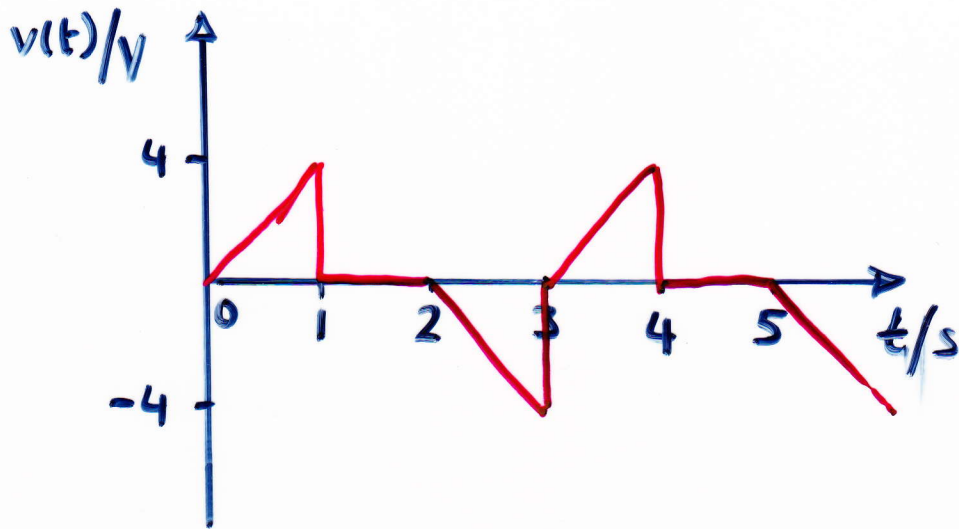

$$v(t) = \begin{cases} 4t \text{ V} & 0 \leq t \leq 1\text{s} \\ 0 \text{ V} & 1 < t \leq 2\text{s} \\ -4t + 8 \text{ V} & 2 < t \leq 3\text{s} \end{cases}$$

$$V_{\text{rms}} = \left\{ \frac{1}{3} \left[ \int_0^1 (4t)^2 dt + \int_1^2 (0)^2 dt + \int_2^3 (8-4t)^2 dt \right] \right\}^{1/2}$$

$$= \left\{ \frac{1}{3} \left( \left[ \frac{16t^3}{3} \right]_0^1 + \left[ 64t - \frac{64t^2}{2} + \frac{16t^3}{3} \right]_2^3 \right) \right\}^{1/2}$$

$$= 1.89 \text{ V}$$

