

Solution Set 10 (Fall 2011)

Use our step-by-step approach (Irwin pp. 202-204) (do not use diff'l eq'ns) for all of the following:



RC Circuits:

10.1

Step1 : $V_c(t) = K_1 + K_2 e^{-\frac{t}{\tau}}$

Step2 : $t = 0^-$

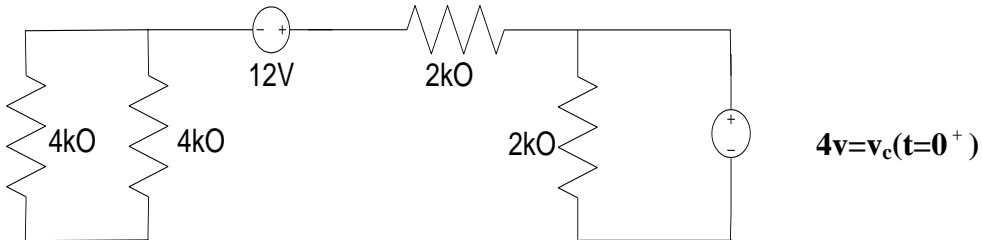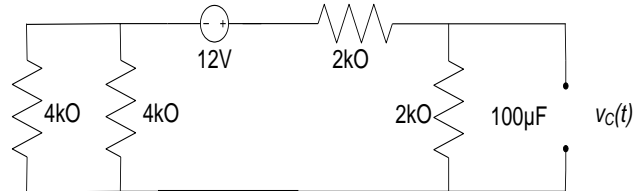Using voltage divider, $V_c(t = 0^-) = \frac{12V}{6k\Omega} \cdot 2k\Omega = 4V$



Step3 : $t = 0^+$

$V_c(t = 0^+) = V_c(t = 0^-) = 4V$

Step4: $t \rightarrow \infty$


Capacitor discharges through 2K resistance, $V_c(t \rightarrow \infty) = 0V$

Step5 : @ $t \rightarrow \infty$ capacitor becomes open ckt.

$R_{th} = 2k$

$\tau = R_{th} \cdot C = 2k \cdot 100 \times 10^{-6} = 0.2s$


Step6 $v_c(t = 0^+) = K_1 + K_2 = 4$

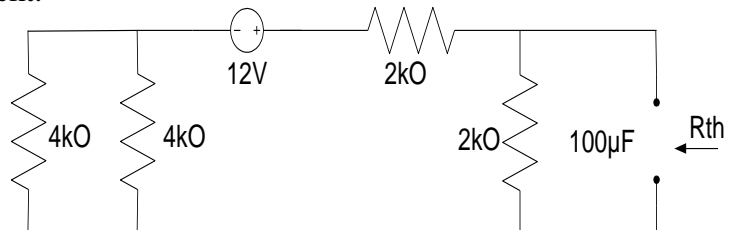

$$v_c(t \rightarrow \infty) = K_1 = 0$$

This gives $K_1=0$; $K_2=4$

$$v_c(t) = 4e^{\frac{-t}{0.2}} V$$

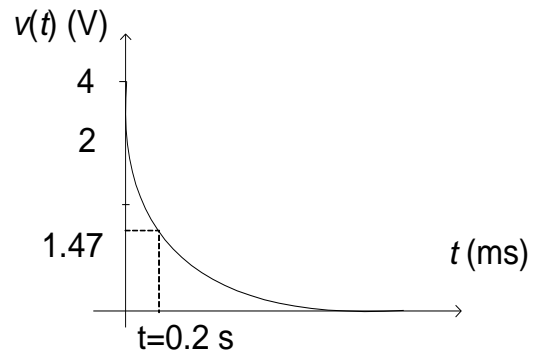


10.2

Step1 : $V_0(t) = K_1 + K_2 e^{\frac{-t}{\tau}}$

Step2 : $t = 0^-$

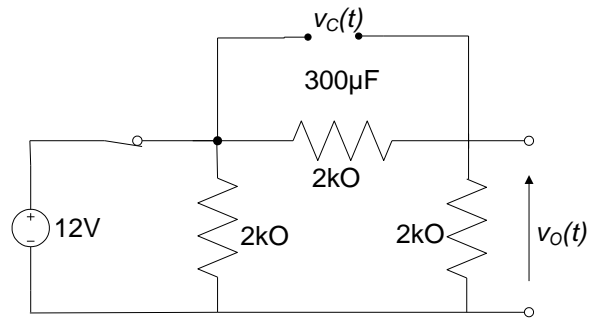
Using voltage divider, $V_c(t = 0^-) = \frac{12V}{2k + 2k\Omega} \cdot 2k\Omega = 6V$



Step3 : $t = 0^+$

$$V_c(t = 0^+) = V_c(t = 0^-) = 6V$$
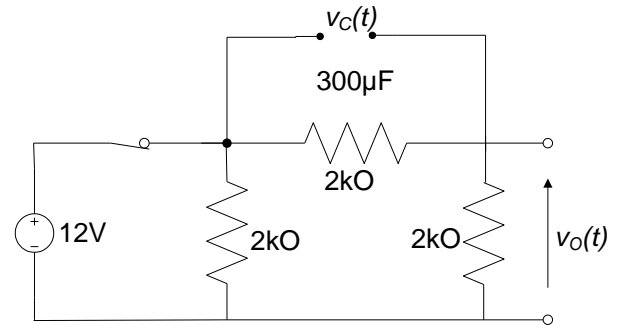
$$V_0(t = 0^+) = \frac{-V_c(t = 0^+)}{2k + 2k\Omega} \cdot 2k\Omega = -3V$$



Step4: $t \rightarrow \infty$

capacitor becomes open ckt, $V_c(t \rightarrow \infty) = 0V$

Step5 : $R_{th} = 2k // (2k + 2k) = \frac{4}{3} k\Omega$



$$\tau = R_{th} \cdot C = \frac{4}{3} k\Omega \cdot 300\mu = 0.4s$$


Step6 $v_c(t = 0^+) = K_1 + K_2 = -3$

$$v_c(t \rightarrow \infty) = K_1 = 0$$

This gives $K_1=0$; $K_2=-3$

$$v_c(t) = -3e^{\frac{-t}{0.4}} V$$

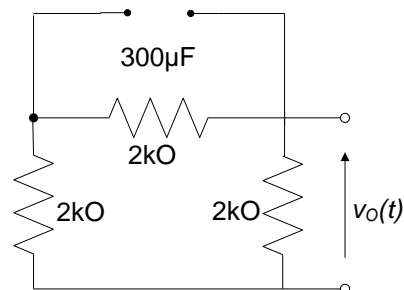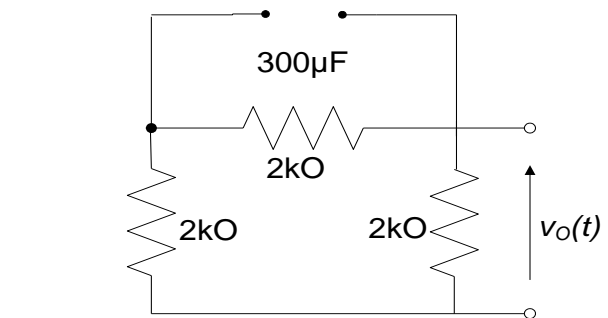

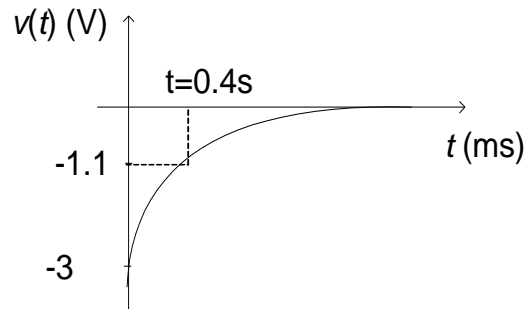


10.3

Step1 : $i_0(t) = K_1 + K_2 e^{\frac{-t}{\tau}}$

Step2 : $t = 0^-$

$$i_0(t = 0^-) = \frac{12\text{V}}{6\text{k}\Omega} = 2 \text{ mA}$$

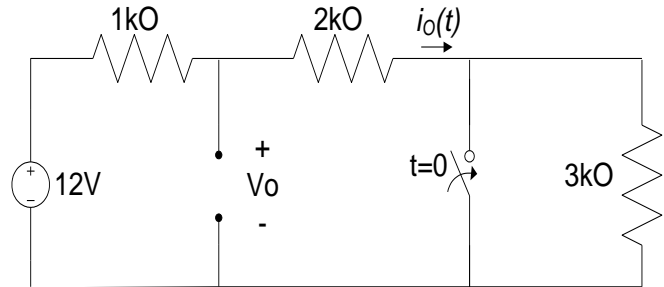
Voltage across the capacitor , $V_c(t = 0^-) = 2\text{mA} \cdot 5 \text{ k}\Omega = 10 \text{ V}$



Step3 : $t = 0^+$

The 3K resistor is shorted
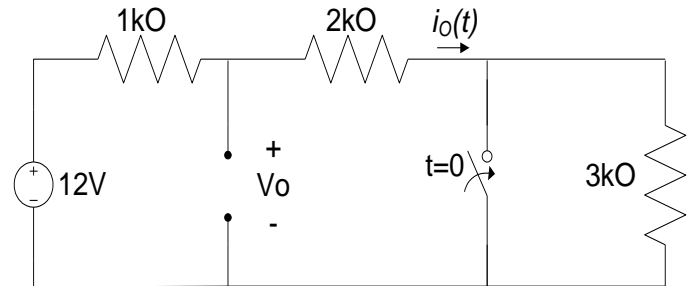
$$i_0(t = 0^+) = \frac{10\text{V}}{2\text{k}\Omega} = 5 \text{ mA}$$




Step4: $t \rightarrow \infty$

Capacitor becomes open circuit, $i_0(t \rightarrow \infty) = \frac{12\text{V}}{1\text{k} + 2\text{k}} = 4 \text{ mA}$

Step5 : .

$$R_{th} = 1\text{k} // 2\text{k} = \frac{2}{3} \text{ k}\Omega$$
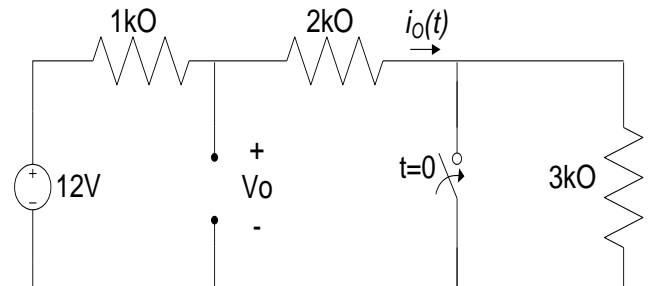
$$\tau = R_{th} \cdot C = \frac{2}{3} \text{ k}\Omega \cdot 400\mu = \frac{0.8}{3} = 0.2667 \text{ s}$$





Step6 $i_0(t = 0^+) = K_1 + K_2 = 5\text{mA}$

$$i_0(t \rightarrow \infty) = K_1 = 4\text{mA}$$

This gives $K_1=4\text{mA}$; $K_2=1\text{mA}$
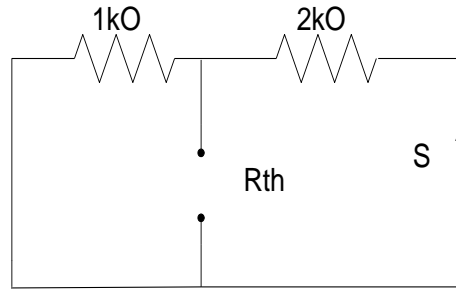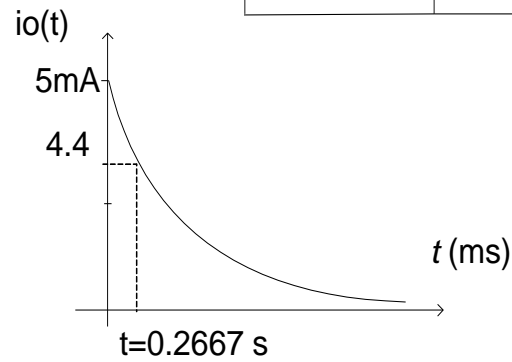
$$i_0(t) = 4 + e^{\frac{-t}{0.2667}} \text{mA}$$




10.4

Step1 : $i_0(t) = K_1 + K_2 e^{\frac{-t}{\tau}}$

Step2 : $t = 0^-$

Using voltage divider, $V_c(t = 0^-) = \frac{12\text{V}}{2\text{k}\Omega + 2\text{k}\Omega} \cdot 2\text{k}\Omega = 6\text{V}$
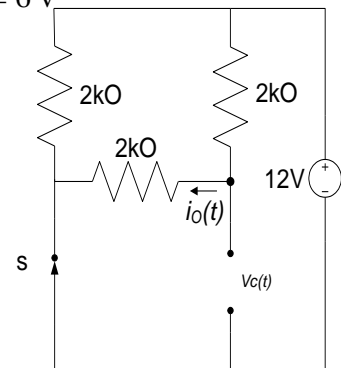
$$i_0(t = 0^-) = \frac{6\text{V}}{2\text{k}\Omega} = 3\text{mA}$$




Step3 : $t = 0^+$

$$V_c(t = 0^+) = V_c(t = 0^-) = 6\text{V}$$

KVL for loop 1: $V_1 + 6\text{V} - 12\text{V} = 0$

$$V_1 = 6\text{V}$$
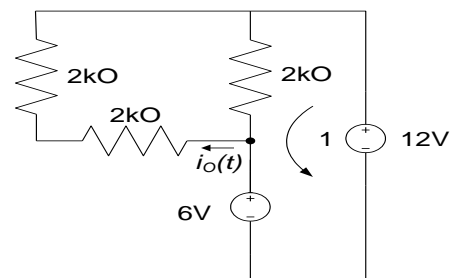
$$i_0(t = 0^+) = \frac{-6\text{V}}{4\text{k}\Omega} = -1.5\text{mA}$$



Step4: $t \rightarrow \infty$

$$i_0(t \rightarrow \infty) = 0$$

Step5 : .

$$R_{th} = 2k // (2k + 2k) = \frac{4}{3} k\Omega$$


$$\tau = R_{th} \cdot C = \frac{4}{3} k\Omega \cdot 100\mu = \frac{0.4}{3}$$

Step6 $i_0(t = 0^+) = K_1 + K_2 = -1.5mA$

$$i_0(t \rightarrow \infty) = K_1 = 0$$

This gives $K_1 = 0mA$; $K_2 = -1.50mA$

$$i_0(t) = -1.5e^{\frac{-t}{0.133}} mA$$

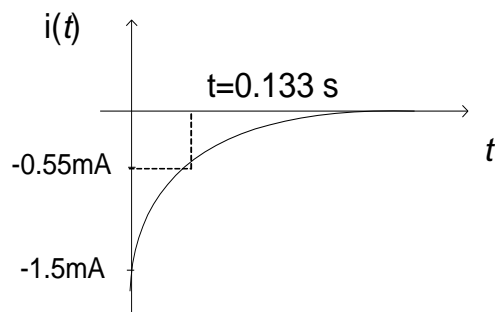

10.5



@t=0.5s , switch closes again

Step1 : $V_0(t) = K_1 + K_2 e^{\frac{-(t-0.5)}{\tau}}$

Step2 : $t = 0.5^-$

$$V_0(t = 0.5^-) = -3e^{\frac{-(0.5)}{0.4}} = -0.86v$$
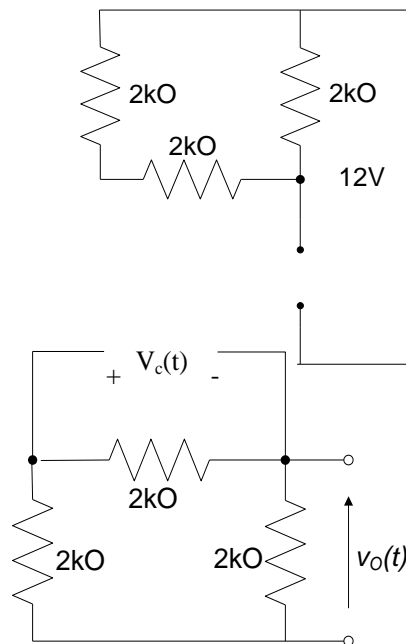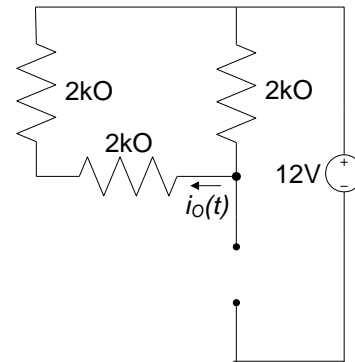
$$V_c(t = 0.5^-) = -2 V_0(t = 0.5^-) = 1.72 v$$




Step3 : $t = 0.5^+$

$$V_c(t = 0.5^+) = V_c(t = 0.5^-) = 1.72 \text{ v}$$

$$\text{KVL for outside loop : } -12 + 1.72 + V_0 = 0$$

$$V_0(t = 0.5^+) = 10.28 \text{ v}$$

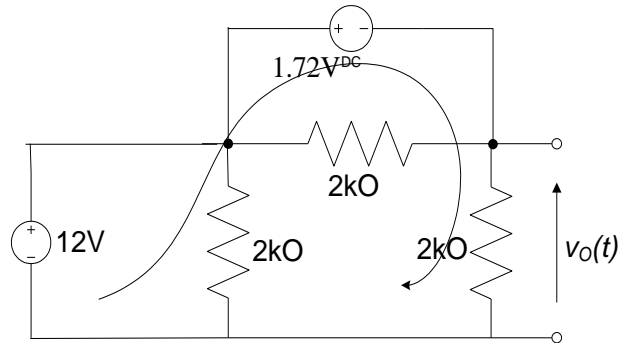

Step4: $t \rightarrow \infty$

$$V_o(t \rightarrow \infty) = 12 \text{ v} \cdot \frac{2k}{2k + 2k} = 6 \text{ v}$$

Step5 :

$$R_{th} = 2k // 2k = 1k$$


$$\tau = R_{th} \cdot C = 1k \cdot 300\mu = 0.3 \text{ s}$$

Step6: $V_0(t = 0.5^+) = K_1 + K_2 = 10.28 \text{ v}$

$$v_o(t \rightarrow \infty) = K_1 = 6$$

This gives $K_1 = 6$; $K_2 = 4.28$

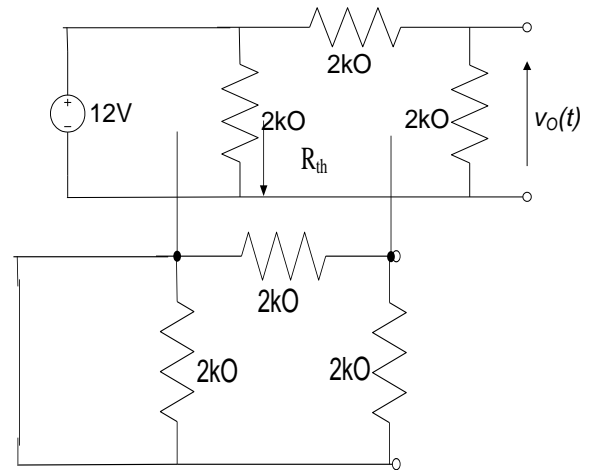
$$v_c(t) = \begin{cases} -3e^{\frac{-t}{0.4}} \text{ V} & (0 < t < 0.5) \\ 6 + 4.28e^{\frac{-(t-0.5)}{0.3}} & (t > 0.5 \text{ s}) \end{cases}$$



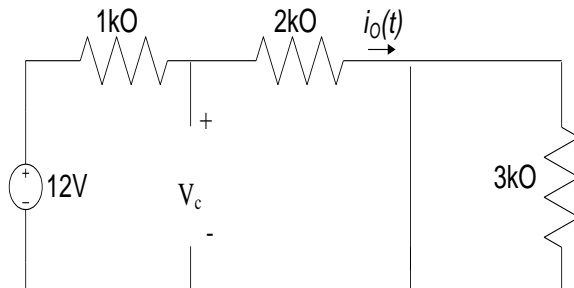10.6

@ $t = 0.5 \text{ s}$, switch closes again


Step1 : $i_0(t) = K_1 + K_2 e^{\frac{-t}{\tau}}$



Step2 : $t = 0.5^-$

$$i_0(t = 0.5^-) = 4 + e^{\frac{-0.5}{0.267}} = 4.15 \text{ mA}$$
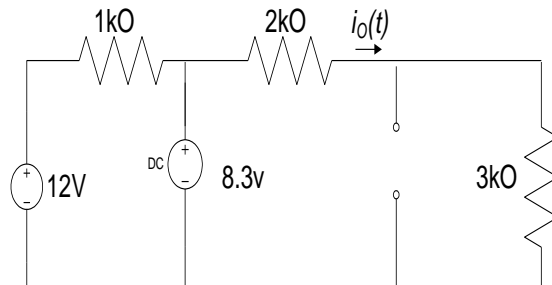
$$V_c(t = 0.5^-) = i_0 \cdot 2k = 8.3 \text{ v}$$



Step3 : $t = 0.5^+$

$$V_c(t = 0.5^+) = V_c(t = 0.5^-) = 8.3 \text{ v}$$

$$i_o(t = 0.5^+) = \frac{8.3v}{5k\Omega} = 1.66 \text{ mA}$$

Step4: $t \rightarrow \infty$

$$\text{Capacitor becomes open circuit, } i_o(t \rightarrow \infty) = \frac{12v}{6k} = 2 \text{ mA}$$

Step5 : .

$$R_{th} = 1k // 5k = 0.83k\Omega$$



$$\tau = R_{th} \cdot C = 0.83k\Omega \cdot 400\mu = 0.33s$$

$$\text{Step6 } i_o(t = 0^+) = K_1 + K_2 = 1.66mA$$

$$i_o(t \rightarrow \infty) = K_1 = 2mA$$

This gives $K_1 = 2mA$; $K_2 = -0.34mA$
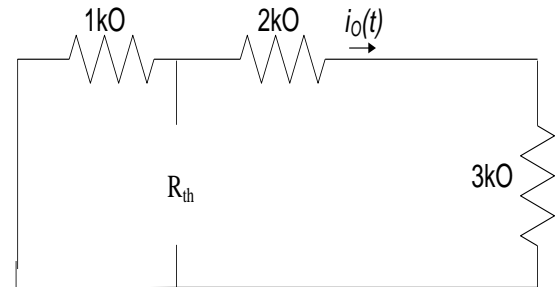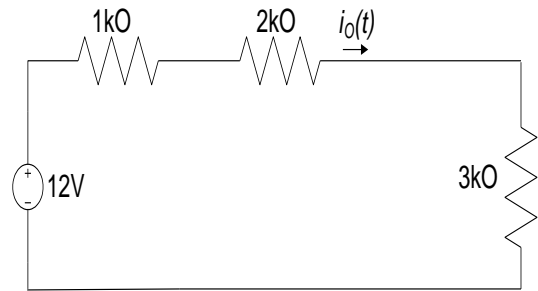
$$i_o(t) = \begin{cases} 4 + e^{\frac{-t}{0.2667}} mA & (0 < t < 0.5) \\ 2 - 0.34e^{\frac{-(t-0.5)}{0.33}} mA & (t > 0.5s) \end{cases}$$



RL Circuits:

10.7


$$\text{Step1 : } i_o(t) = K_1 + K_2 e^{\frac{-t}{\tau}}$$

Step2 : $t = 0^-$

$$i_o(t = 0^-) = 0 \text{ mA}$$

At dc inductor is short ckt. ($Z_L = j\omega L = 0$)

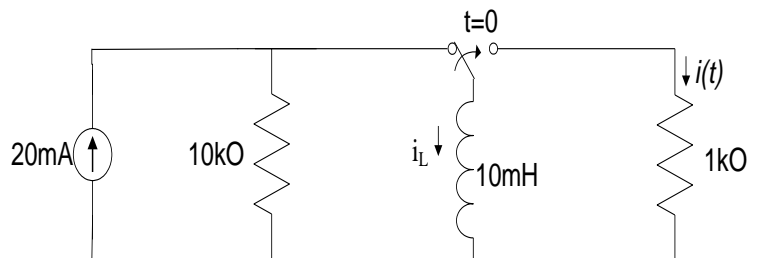
$$\text{Hence } i_L(t = 0^-) = 20 \text{ mA}$$



Step3 : $t = 0^+$

$$i_L(t = 0^-) = i_L(t = 0^+) = 20 \text{ mA}$$

$$i_o(t = 0^+) = -20 \text{ mA}$$

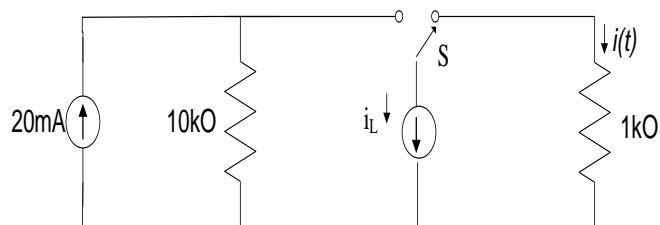

Step4: $t \rightarrow \infty$; inductor is short ckt

$$i_0(t \rightarrow \infty) = 0$$

Step5 : .

$$R_{th} = 1k\Omega$$




$$\tau = \frac{L}{R_{th}} = \frac{10mH}{1k} = 10\mu s$$

Step6 $i_0(t = 0^+) = K_1 + K_2 = -20mA$

$$i_0(t \rightarrow \infty) = K_1 = 0$$

This gives $K_1 = 0mA$; $K_2 = -20mA$

$$i_0(t) = -20e^{\frac{-t}{10\mu}} mA$$

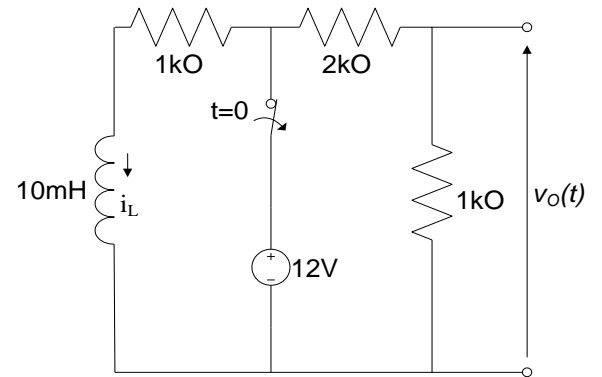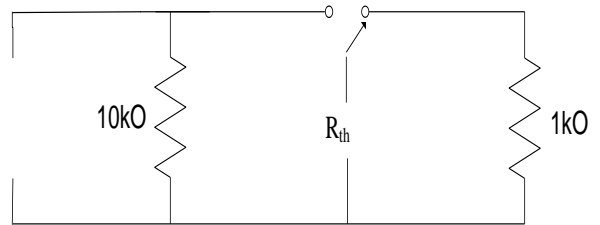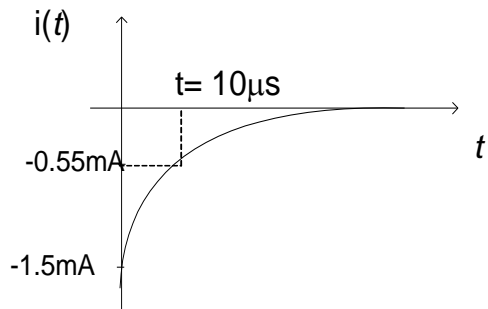

10.8

Step1 : $V_c(t) = K_1 + K_2 e^{\frac{-t}{\tau}}$

Step2 : $t = 0^-$

At dc inductor is short ckt., $Z_L = j\omega L = 0$

$$i_L(t = 0^-) = \frac{12V}{1k\Omega} = 12mA$$

Step3 : $t = 0^+$

$$i_L(t = 0^-) = i_L(t = 0^+) = 12 \text{ mA}$$

$$V_0(t = 0^+) = -12 \text{ mA} \cdot 1 \text{ k} = -12 \text{ V}$$

Step4: $t \rightarrow \infty$

$$i_L(t \rightarrow \infty) = 0 \text{ A}$$

$$V_0(t \rightarrow \infty) = 0 \text{ V}$$

Step5 :

$$R_{th} = 4 \text{ k}\Omega$$

$$\tau = \frac{L}{R_{th}} = \frac{10 \text{ mH}}{4 \text{ k}} = 2.5 \mu\text{s}$$

Step6 $v_c(t = 0^+) = K_1 + K_2 = -12$

$$v_c(t \rightarrow \infty) = K_1 = 0$$

This gives $K_1 = 0$; $K_2 = -12 \text{ V}$

$$v_c(t) = -12e^{\frac{-t}{2.5 \mu}} \text{ V}$$

