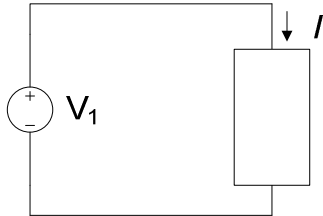


Solution Set 2 (Fall 2009)

2.1

a) $P_{\text{ABS}} = V \cdot I = 6 \cdot 3 = 18 \text{ Watts}$

b) $P_{\text{ABS}} = V \cdot I = (-6) \cdot (-3) = 18 \text{ Watts}$




2.2

a) $P_{\text{ABS}} = V \cdot I = (-8) \cdot 5 = -40 \text{ W}$, $P_{\text{SUPP}} = 40 \text{ Watts}$

b) $P_{\text{SUPP}} = -V \cdot I = -8 \cdot (-5) = 40 \text{ Watts}$


2.3

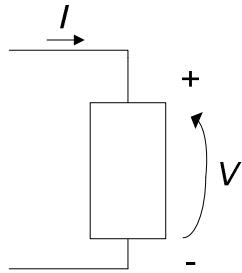a) $P = 25 \text{ W} = V \cdot I = 5 \cdot I$, $I = 5 \text{ A}$



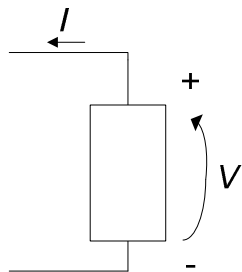b) $P_{\text{SUPP}} = V \cdot I = 3 \text{ A} \cdot 6 \text{ V} = 18 \text{ W}$


$P = -I \cdot V = -18 \text{ W}$ (ie. - power is supplied)




2.4

a) $P = V \cdot I = 6 \text{ W} = (-1)I$

$I = -6 \text{ A}$

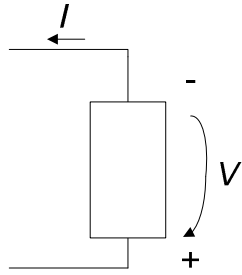

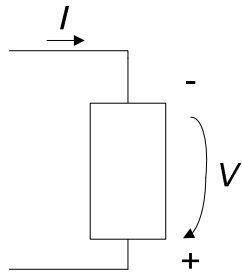b) $P = -I \cdot V = -30W = -(-3)V$
 $V = -10V$




2.5 If element 1 supplies 48W:



$$P_1 = -48 = I \cdot V = I \cdot 6, I = -8A$$

$$P_2 = I \cdot V = (-8A)(-12V) = 96W$$

So it absorbs 96W of power.

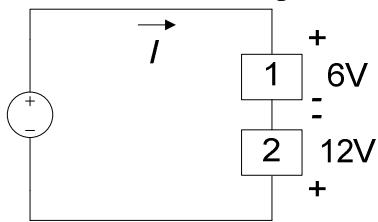

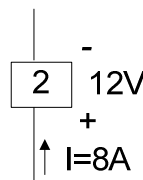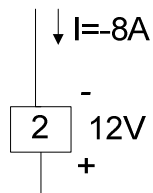If we only take the 12V element and rearrange the signs so that they are positive:



It is clear that power is absorbed.

2.6 Determine the power that is absorbed or supplied by the circuit elements below:

a)

$$P_1 = I \cdot V = 1A \cdot 5V = 5W \text{ (absorbed)}$$

$$P_2 = V \cdot I = 1 \cdot 7 = 7W \text{ (absorbed)}$$

$$P_{12V} = V \cdot I = 12(-1A) = -12W \text{ (12W Supplied)}$$

Note: total power supplied = total power absorbed.

b)

$$P_{24V} = 24V(-2A) = -48W \text{ (48W supplied)}$$

$$P_1 = 2A \cdot 8V = 16W$$

$$P_{16V} = 16V \cdot 2A = 32W$$

Note: absorbs even though it is a source.

2.7

$$P_1 = 3 \cdot 2 = 6W \text{ (absorbed)}$$

$$P_{7V} = 7 \cdot 2 = 14W \text{ (absorbed)}$$

$$P_{10V} = 10V \cdot 2A = 20W \text{ (supplied)}$$

2.8

Add all power absorbed and set to 0.

$$P_{6A} + P_1 + P_2 + P_3 + P_{8V} + P_4 = 0$$

$$(-6A)(6V) + (2A)(6V) + (1A)(6V) + I_X(2V) + I_X(4V) + (6V)(1A) = 0$$


$$-I_X(6V) = (-2A)(6V)$$

$$I_X = 2A$$

So the 4V source and element 3 are actually absorbing power.

2.9

Using KVL:

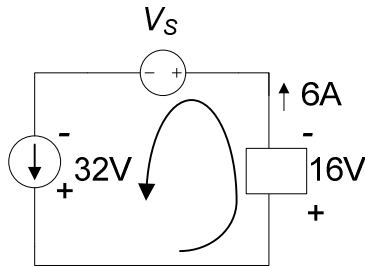

$$+V_S + 16V - 32V = 0$$

$$V_S = 16V$$


$$\text{So } P_{V_S} = (6A)(16V) = 96W$$

So V_S is absorbing 96 Watts.

2.10

$$V_{CS} = 6mA \cdot 2k\Omega = 12V$$

$$P_R = 12V \cdot 6mA = 72mW$$

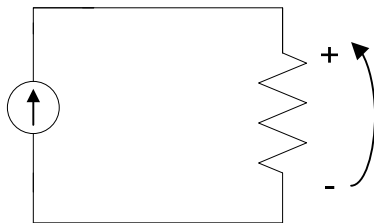


2.11

$$P_{Rx} = V \cdot I = 24mW = (8mA)(V)$$

$$V=3V$$

$$V=IR=8\text{mA}\cdot R=3V$$

$$R=(3/8)\text{k}\Omega$$

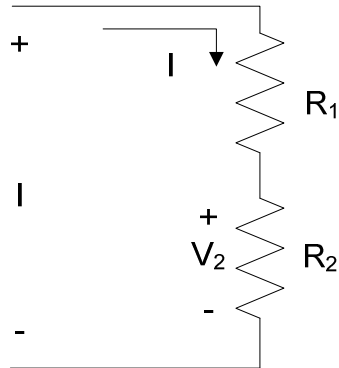


Voltage Divider:

$$V_2 = \frac{R_2}{R_1 + R_2} \cdot V_T, I = \frac{1}{R_1 + R_2} \cdot V_T$$

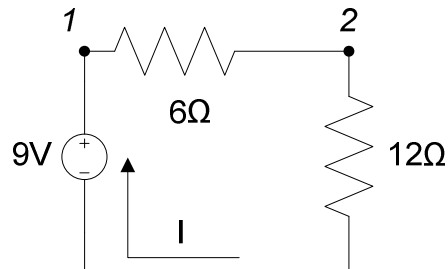2.12


$$I = V/R_T = 9V/(12+6)\Omega = 1/2 \text{ A}$$

$$V_{12} = I \cdot R = 1/2 \text{ A} \cdot 6 \Omega = 3V$$



-or- use voltage divider
 $V_{12} = 9V \cdot 6/(12+6) = 3V$

2.13 Find V_2 in the circuit below.

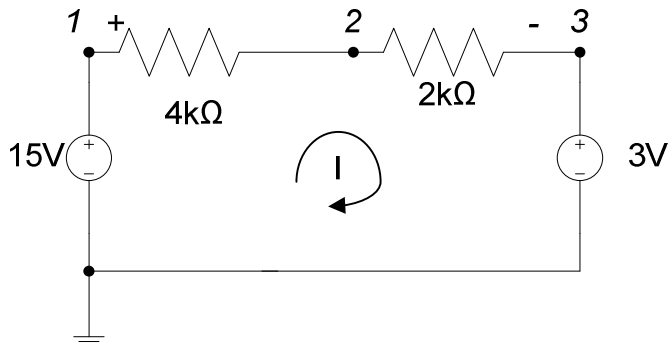

$$V_{13} + 3V - 15V = 0$$

$$V_{13} = 12V$$

$$I = V_{13}/(4k + 2k) = 2\text{mA}$$


$$V_{23} = 2\text{mA} \cdot 2k = 4V$$

-or-

$$V_{23} = V_{13} \cdot 2k/(2k + 4k) = 4V$$

$$V_2 = V_{23} + V_3 = 4V + 3V = 7V$$

2.14 Find V_x in the circuit below.

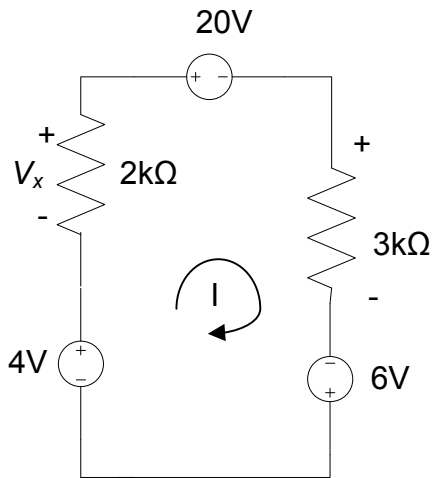

KVL:

$$-4V - V_x + 20 + V_{3k} - 6V = 0$$

Note: $V_x = -I \cdot 2k$, $V_{3k} = I \cdot 3k$

$$I(2k + 3k) = -10V$$

$$I = -2mA$$

$$\text{So } V_x = -I \cdot 2k = -(-2mA)(2k) = 4V$$

$$P_{4V} = -I \cdot V = -(-2mA)(4V) = 8 \text{ mW (absorbed)}$$