

Solution Set 3 (Fall 2010)

3.1 Find V_{14} in the network below:

Solution:


$$V_{14} = V_{12} + V_{23} + V_{34};$$

$$V_{14} = (-3)V + (-2)V + (+12)V = 7V;$$


or

$$V_{14} = V_{10} + V_{04};$$

$$V_{14} = (+4)V + (+3)V = 7V;$$

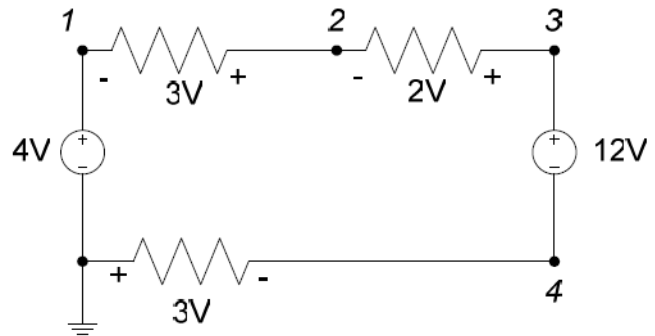

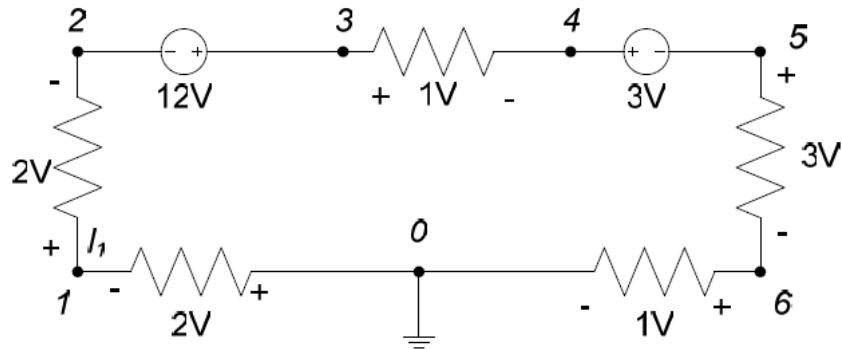3.2 Find V_{20} and V_{64} in the network below:



Solution:

$$V_{20} = V_{21} + V_{10} = (-2)V + (-2)V = -4V$$

$$V_{64} = V_{65} + V_{54} = (-3)V + (-3)V = -6V;$$

3.3 Repeat 2.12 and find the power in each:


i) 6Ω resistor;

ii) 12Ω resistor;

iii) 9 volt source

a) when the source is +9V DC

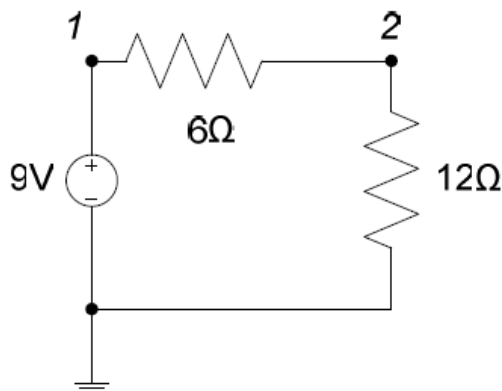b) when the source is $+9\sqrt{2} \sin 100t$



Solution:

(a) $V_s = 9V$, DC source

$$I = \frac{V_s}{6\Omega + 12\Omega} = \frac{9V}{18\Omega} = 0.5A;$$

Power absorbed by 12Ω resistor: $P = I^2 R_{12\Omega} = 0.5^2 A \cdot 12\Omega = 3W$;

Power absorbed by 6Ω resistor: $P = I^2 R_{6\Omega} = 0.5^2 A \cdot 6\Omega = 1.5W$;

Voltage source: $P = V_s \cdot (-I) = 9V \cdot (-0.5A) = -4.5W$

(Negative sign indicates supplied power)

(b) $V_s = 9\sqrt{2} \sin(100t)$, AC source

$$V_{peak} = 9\sqrt{2}V;$$

$$V_{rms} = \frac{V_{peak}}{\sqrt{2}} = 9V;$$


$$I_{rms} = \frac{V_{rms}}{6\Omega + 12\Omega} = \frac{9V}{18\Omega} = 0.5A$$

Power absorbed by 12Ω resistor: $P = I_{rms}^2 R_{12\Omega} = 0.5A^2 \cdot 12\Omega = 3W$;

Power absorbed by 6Ω resistor: $P = I_{rms}^2 R_{6\Omega} = 0.5A^2 \cdot 6\Omega = 1.5W$;

Voltage source: $P = V_{s_{rms}} \cdot (-I_{rms}) = 9V \cdot (-0.5A) = -4.5W$;

3.4 Find I_1 in the network below:

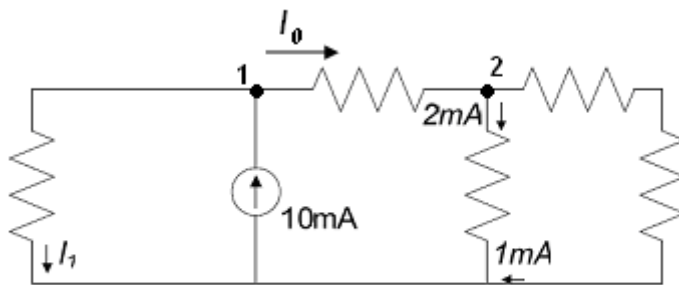

Solution:


Let's apply KCL at the node 2:

$$I_0 - 2mA - 1mA = 0 \longrightarrow I_0 = 3mA;$$

Let's apply KCL at the node 1:

$$10mA - I_1 - I_0 = 0 \longrightarrow I_1 = 7mA;$$

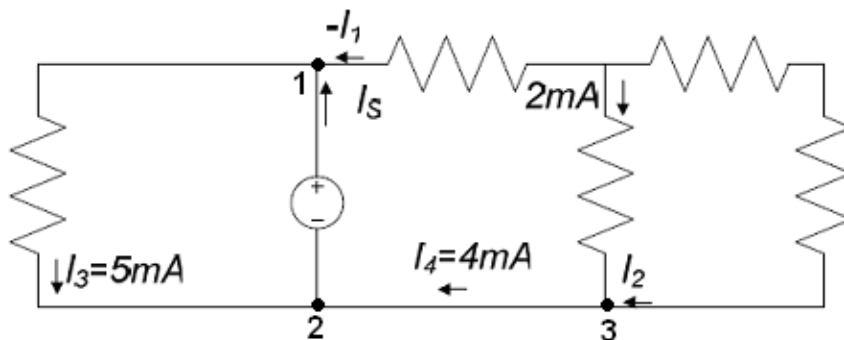3.5 Find I_1 and I_2 in the network below:



Solution:

Let's apply KCL at the node 2:

$$5mA + 4mA - I_s = 0 \longrightarrow I_s = 9mA;$$


Let's apply KCL at the node 1:

$$I_s - I_1 - 5mA = 0 \longrightarrow I_1 = 4mA;$$

Let's apply KCL at the node 3:

$$I_2 + 2mA - 4mA = 0 \longrightarrow I_2 = 2mA;$$

3.6 Find I_1 , I_2 and I_3 in the network below:

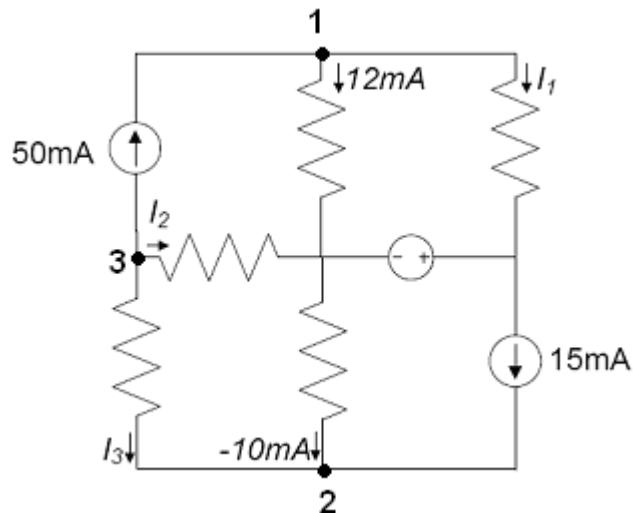**Solution:**

Let's apply KCL at the node 1:

$$50mA - 12mA - I_1 = 0 \longrightarrow I_1 = 38mA;$$


Let's apply KCL at the node 2:

$$15mA - 10mA + I_3 = 0 \longrightarrow I_3 = -5mA;$$

KCL@3:

$$-50mA - I_3 - I_2 = 0 \longrightarrow I_2 = -45mA;$$

3.7 Find I_0 in the network below:

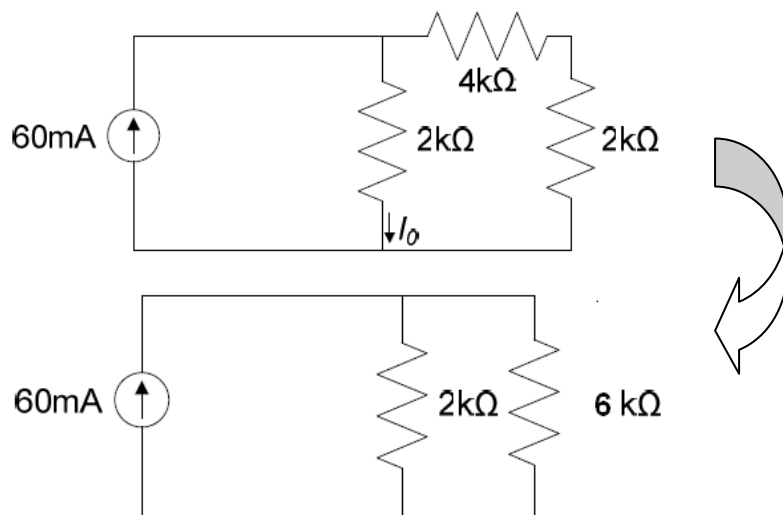
Solution:

Using current division: $I_0 = 60mA \frac{6\Omega}{6\Omega + 2\Omega} = 45mA$;

3.8 Find I_0 in the network below:

Solution:

The network can be redrawn as:

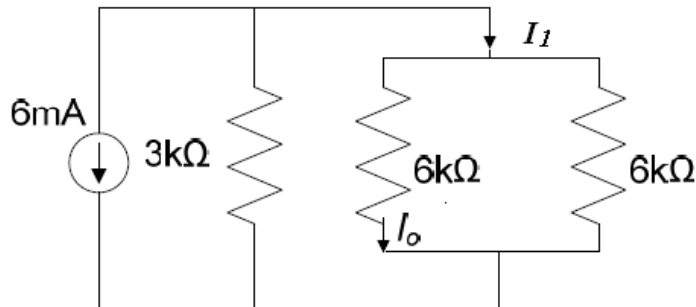

Where I_1 can be found with help of current division rule:


$$I_1 = -6mA * \frac{3k\Omega}{3k\Omega + (6k\Omega \parallel k\Omega)} = -3mA;$$

Applying the same rule I_0 can be found:


$$I_0 = -3mA * \frac{6k\Omega}{6k\Omega + 6k\Omega} = -1.5mA;$$

3.9 Find R_{AB} in the network below:


Solution:

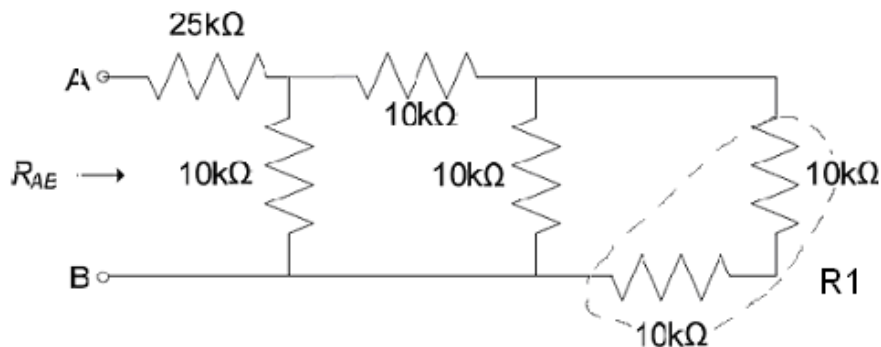

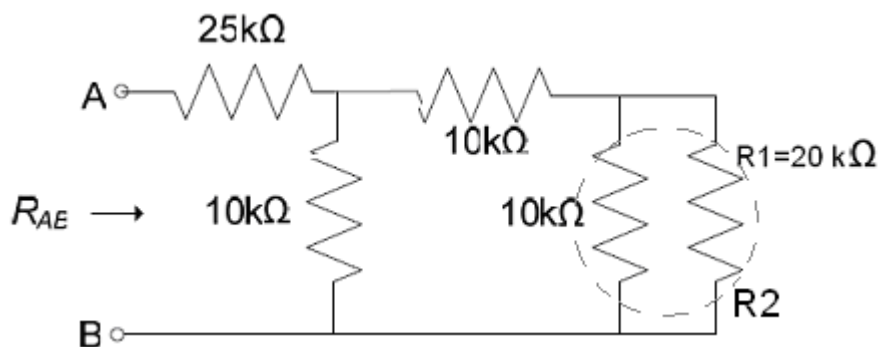
$$R1 = 10k\Omega + 10k\Omega = 20k\Omega;$$



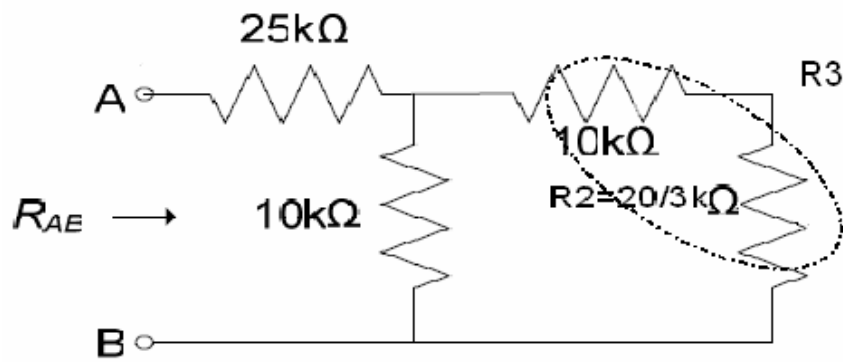
$$R2 = R1 \parallel 10k\Omega = 20k\Omega \cdot 10k\Omega / (20k\Omega + 10k\Omega) = 20/3k\Omega;$$


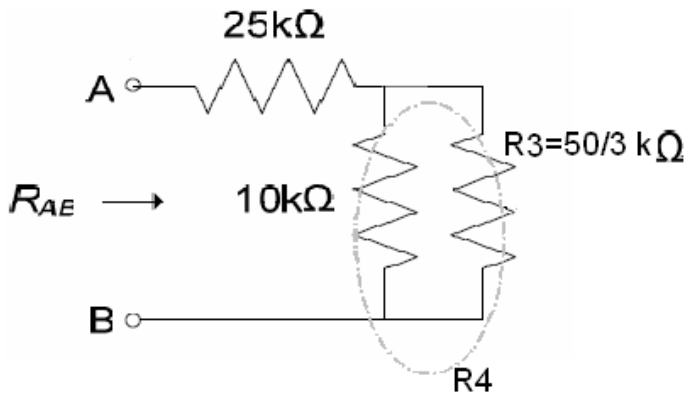
$$R_3 = R_2 + 10k\Omega = 20/3k\Omega + 10k\Omega = 50/3k\Omega;$$



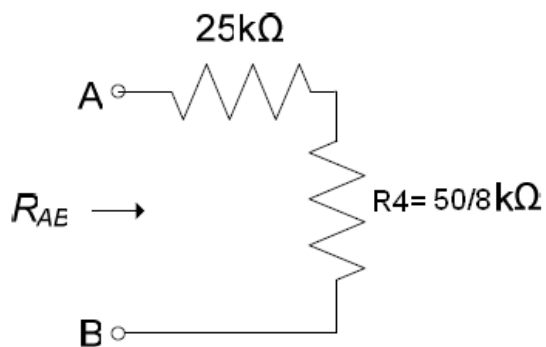
$$R_4 = 10k\Omega \parallel 50/3k\Omega = \frac{10k\Omega * 50k\Omega}{3(10k\Omega + 50/3k\Omega)} = 50/8k\Omega;$$




$$R_{AB} = 25k\Omega + 50/8k\Omega = 125/4k\Omega$$


3.10 Find R_{AB} in the network below:

Solution:

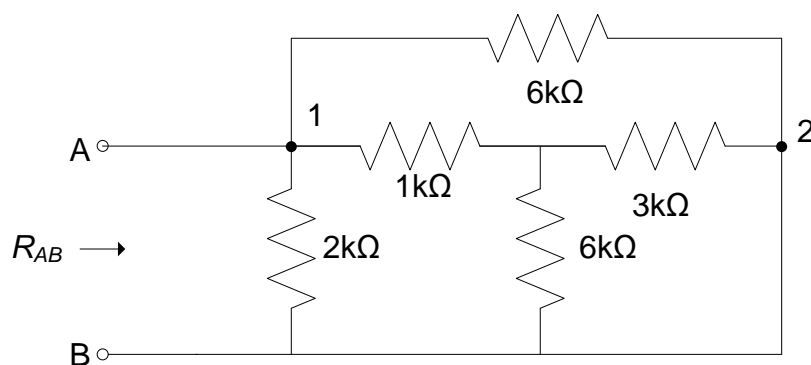


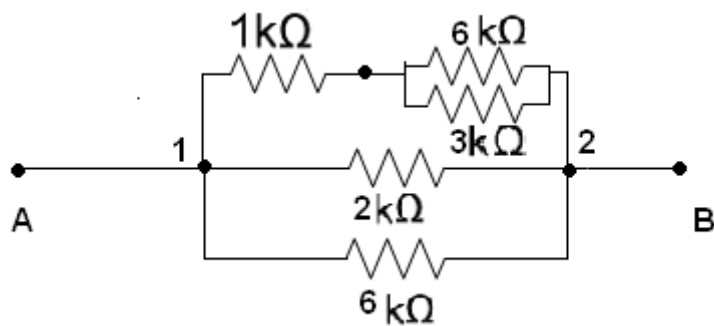
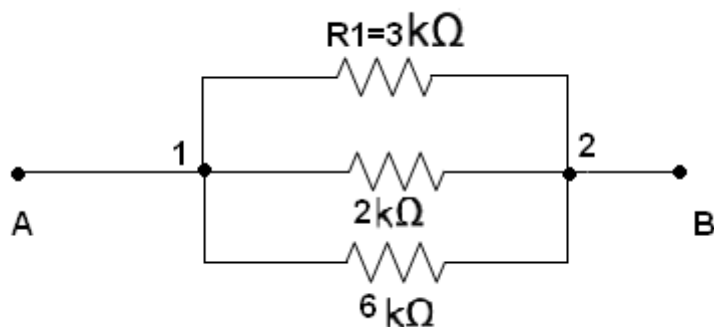
$$R1 = 1k\Omega + 6k\Omega \parallel 3k\Omega = 1k\Omega + \frac{6k\Omega * 3k\Omega}{6k\Omega + 3k\Omega} = 3k\Omega;$$


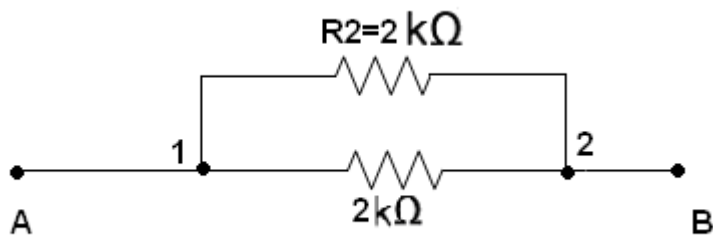
$$R2 = R1 \parallel 6k\Omega = \frac{3k\Omega * 6k\Omega}{3k\Omega + 6k\Omega} = 2k\Omega;$$




$$R_{AB} = 2k\Omega \parallel 2k\Omega = \frac{2k\Omega + 2k\Omega}{2k\Omega * k\Omega} = 1k\Omega$$

3.11 Find V_o in the network below:


Solution:

$$V_o = I * R_{eq};$$

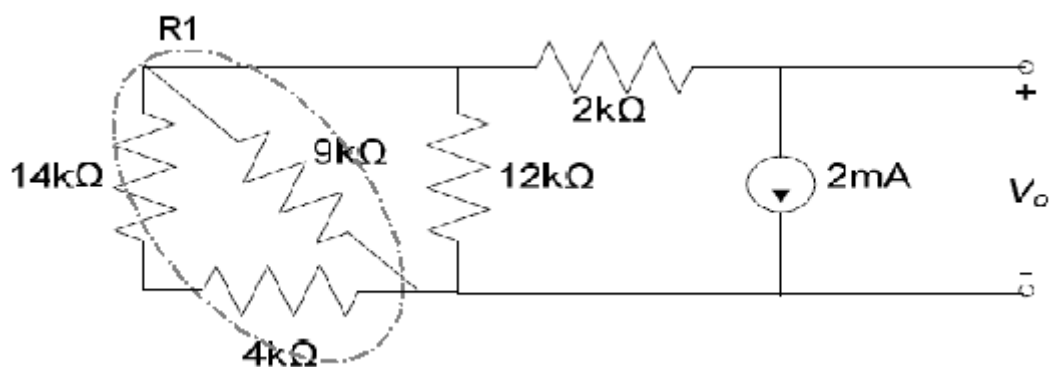

$$R1 = 9k\Omega \parallel (14k\Omega + 4k\Omega) = 9k\Omega \parallel 18k\Omega = \frac{9k\Omega * 18k\Omega}{9k\Omega + 18k\Omega} = 6k\Omega;$$
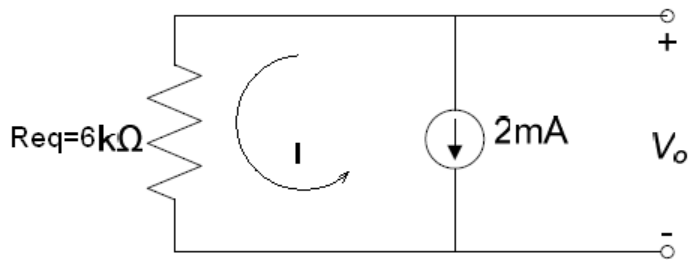
$$R_{eq} = 2k\Omega + R1 \parallel 12k\Omega = 2k\Omega + \frac{6k\Omega * 12k\Omega}{6k\Omega + 12k\Omega} = 6k\Omega;$$




$$I = -2mA;$$

$$V_o = I * R_{eq} = -2mA * 6k\Omega = -12V;$$

3.12 Find I_1 and V_o in the following network:

Solution:

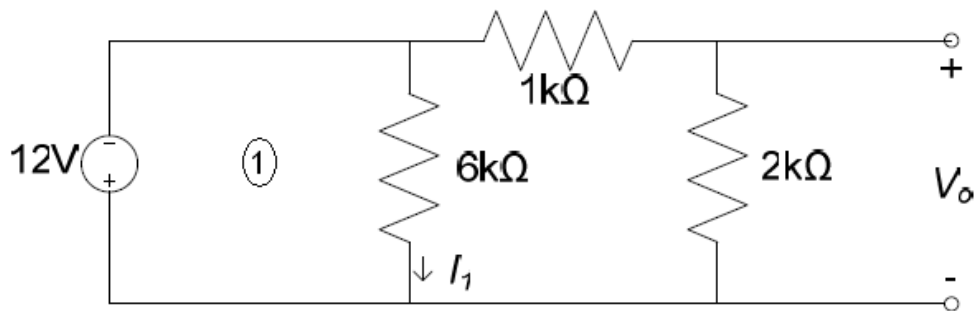

Ohm's law in the loop 1:

$$I_1 * 6k\Omega + 12V = 0 \longrightarrow I_1 = -2mA;$$


Using voltage division:

$$V_o = -12 \frac{2k\Omega}{2k\Omega + 1k\Omega} = -8V;$$

Negative sign is due to the fact that source and V_o have opposite sign.

3.13 Find V_o in the following network:

Solution:

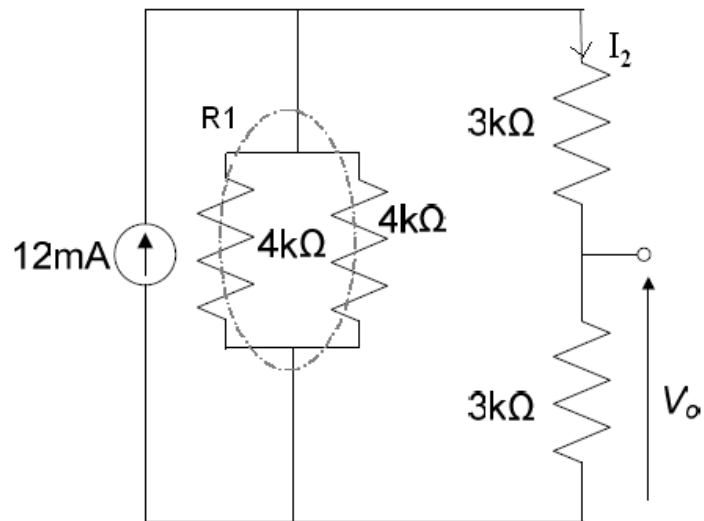

$$R1 = 4k\Omega \parallel 4k\Omega = 2k\Omega;$$

$$\text{Using current division: } I_2 = 12mA \frac{2k\Omega}{2k\Omega + (3k\Omega + 3k\Omega)} = 3mA;$$

$$V_0 = I_2 * 3k\Omega = 9V$$