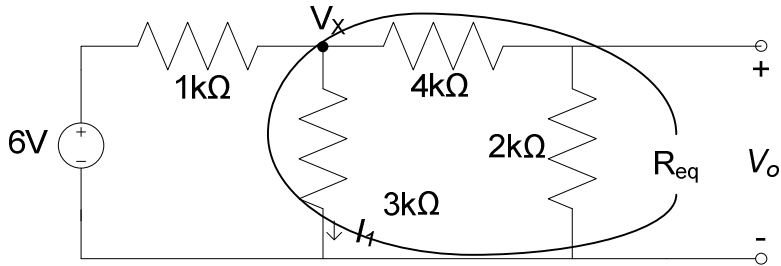


Solution Set 4 (Fall 2008)

4.1



$$\begin{aligned}
 R_{eq} &= 3k \parallel (4k + 2K) \\
 &= 3k \parallel 6k \\
 &= \frac{3 \cdot 6}{3 + 6} = 2k\Omega
 \end{aligned}$$

Voltage divider:


$$\begin{aligned}
 V_x &= 6v \cdot \frac{R_{eq}}{R_{eq} + 1K} = 6v \cdot \frac{2}{2 + 1} \\
 \underline{\underline{V_x = 4v}}
 \end{aligned}$$

Voltage divider:

$$\begin{aligned}
 V_o &= V_x \cdot \frac{4}{4 + 8} = 4 \cdot \frac{2}{3} \\
 V_o &= \frac{8}{3} v \\
 I_1 &= \frac{V_x}{3k\Omega} = \frac{4}{3} \text{ mA} = 1.33 \text{ mA}
 \end{aligned}$$

*Note: V_o is not a voltage division directly of 6v as the current through the $1k\Omega$ resistor is different than through $4k\Omega$ & $2k\Omega$ resistor.

4.2

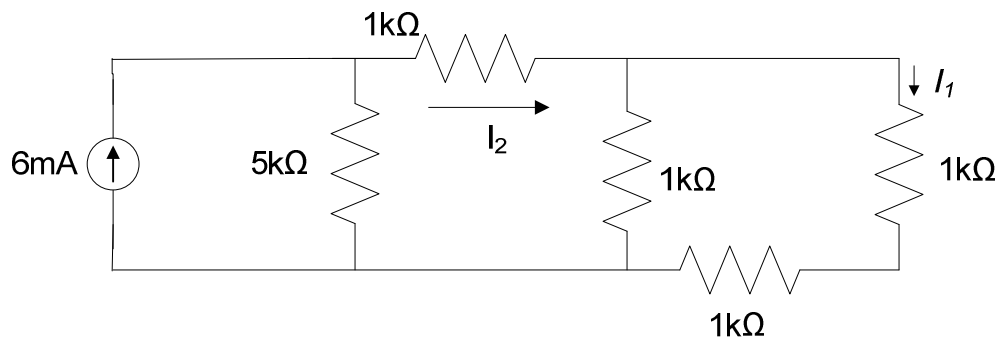



Current divider:

$$I_2 = 6\text{mA} \cdot \frac{5\text{k}\Omega}{5\text{k}\Omega + (1\text{k}\Omega + 2\text{k} // 1\text{k})} = 3\text{mA} \cdot \frac{3}{2} = \frac{9}{2} \text{mA}$$

$$I_1 = I_2 \cdot \frac{1\text{k}}{1\text{k} + 2\text{k}} = \frac{9}{2} \cdot \frac{1}{3} \text{mA}$$

$$\Rightarrow I_1 = \frac{3}{2} \text{mA}$$

4.3

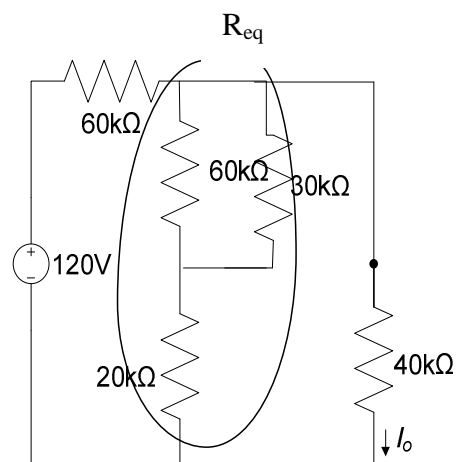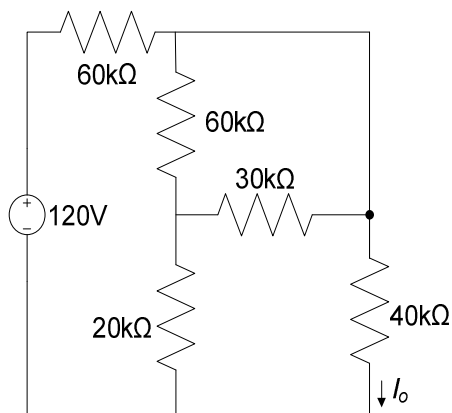

Voltage Divider:

$$R_{eq} = (60\text{k} // 30\text{k} + 20\text{k}) // 40\text{k}$$

$$V_x = 120V * \frac{R_{eq}}{R_{eq} + 60k\Omega} \quad = 40k // 40k$$

$$= 120V * \frac{20k\Omega}{20k\Omega + 60k\Omega} \quad \Rightarrow R_{eq} = 20k\Omega$$

$$\Rightarrow V_x = \underline{\underline{30V}}$$

$$I_0 = \frac{V_x}{40k\Omega} = \frac{30V}{40k\Omega}$$


$$\Rightarrow I_0 = \underline{\underline{0.75mA}}$$

OR

$$I_T = \frac{120V}{R_{eq} + 60k\Omega} = \frac{120V}{20k\Omega + 60k\Omega} = 1.5mA$$

$$I_0 = I_T * \frac{60k // 30k + 20k}{60k // 30k + 20k + 40k} = I_T * \frac{1}{2} = \underline{\underline{0.75mA}}$$

4.4

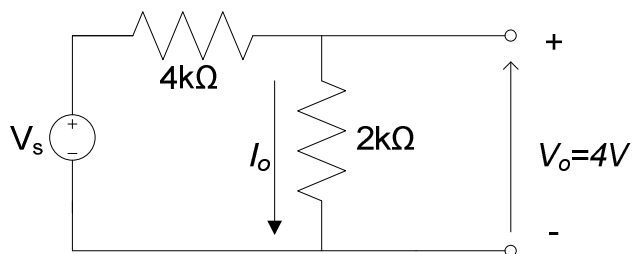

Voltage Divider:

$$\text{OR} \quad I_0 = \frac{V_0}{2k\Omega} = 2mA \text{ [Ohm's Law]}$$

$$V_0 = V_s * \frac{2k\Omega}{2k\Omega + 4k\Omega}$$

$$\Rightarrow V_s = V_0 * \frac{6k\Omega}{2k\Omega}$$


$$= 4V * 3$$

$$\Rightarrow V_s = \underline{\underline{12V}}$$

$$V_s = I_0 (4k + 2k) = 2mA * 6k\Omega$$

$$\Rightarrow V_s = \underline{\underline{12V}}$$

4.5

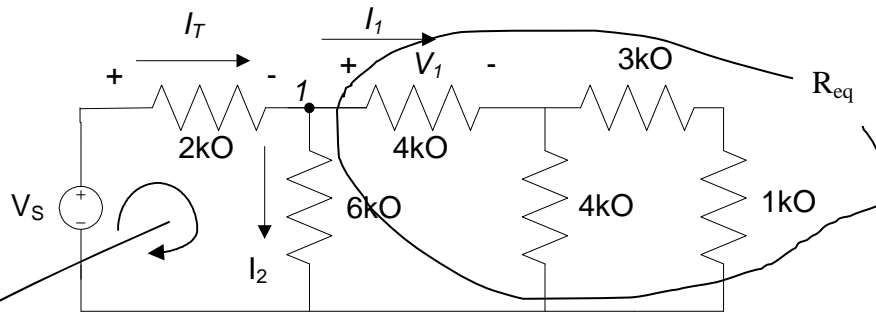

(N.B. The “O”s in the above diagram are actually Ω s, for some reason Word will no longer show them correctly in two of this solution set’s visio diagrams.)

$$V_1 = 12V$$

$$I_1 = \frac{12V}{4k} = 3mA$$

$$R_{eq} = 4k + (4k // 4k) = 6k$$

$$I_1 = \frac{6k}{6k + R_{eq}} \cdot I_T = \frac{1}{2} I_T$$

$$I_T = 6mA$$


$$\text{KCL @ node 1: } I_T - I_1 - I_2 = 0$$

$$I_2 = I_T - I_1 = 3mA$$

$$\text{KVL: } -V_S + 2k \cdot I_T + 6k \cdot I_2 = 0$$

$$V_S = 2k(6mA) + 6k(3mA) = \underline{\underline{30V}}$$

4.6

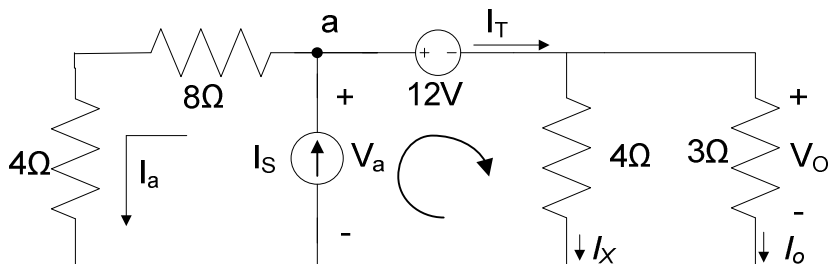

$$I_o = 2A$$

$$\text{So } V_o = 2A \cdot 3\Omega = 6V$$

$$I_x = \frac{6V}{4\Omega} = 1.5A$$

$$I_T = I_o + I_x = 3.5A$$

$$\text{KVL: } -V_a + 12V + I_o \cdot 3\Omega = 0$$


$$V_a = 12V + 6V = 18V$$

$$I_a = \frac{V_a}{12} = 1.5A$$

$$\text{KCL @ a: } -I_a + I_s - I_T = 0$$

$$I_s = I_a + I_T = 1.5A + 3.5A = 5A$$

4.7

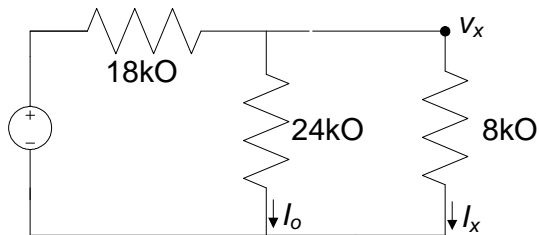

(Change 4kΩ in problem statement to 8kΩ)

$$P_{8k} = I_x \cdot V_x = 36mW$$


$$\text{But: } I_x = \frac{V_x}{8k}$$

$$P_{8k} = \frac{V_x^2}{8k} \text{ or } P_{8k} = I_x^2 \cdot 8k$$

$$I_x = \sqrt{\frac{36mW}{8k}} = \frac{6}{\sqrt{8}} mA, \quad V_x = \frac{6}{\sqrt{8}} mA \cdot 8k\Omega \cong 17V$$

$$\text{So } I_o = \frac{V_x}{24k} \cong \frac{17V}{24k\Omega} = 0.707mA$$

4.8

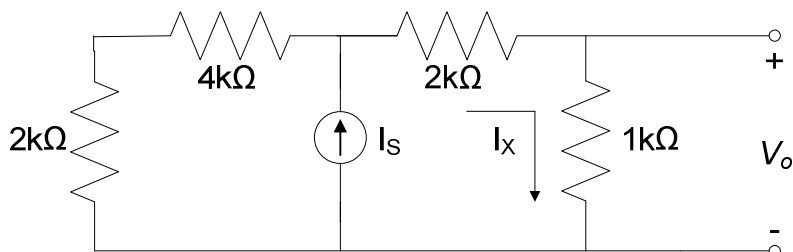


$$I_x = \frac{V_o}{1k} = \frac{6V}{1k} = 6mA$$

$$I_x = \frac{(4k + 2k)}{(4k + 2k) + (2k + 1k)} \cdot I_s = 6mA$$

$$I_s = \frac{9}{6} \cdot 6mA = 9mA$$

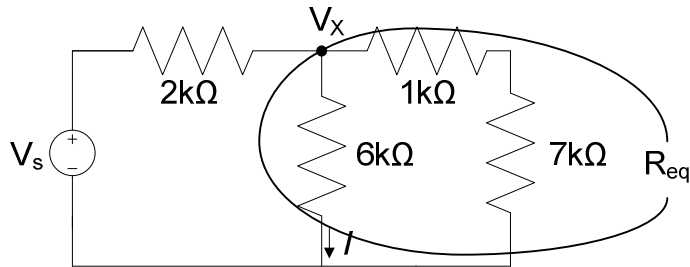4.9 If $I = 4mA$ in the circuit below, find V_s .




$$V_x = I \cdot 6k = 4mA \cdot 6k \Omega = 24V$$

$$V_x = V_s \cdot \frac{R_{eq}}{R_{eq} + 2k}$$

$$R_{eq} = (1k + 7k) // 6k = 3.43k \Omega$$

$$V_s = 24V \cdot \frac{(3.43 + 2)}{3.43} = 38V$$

4.10

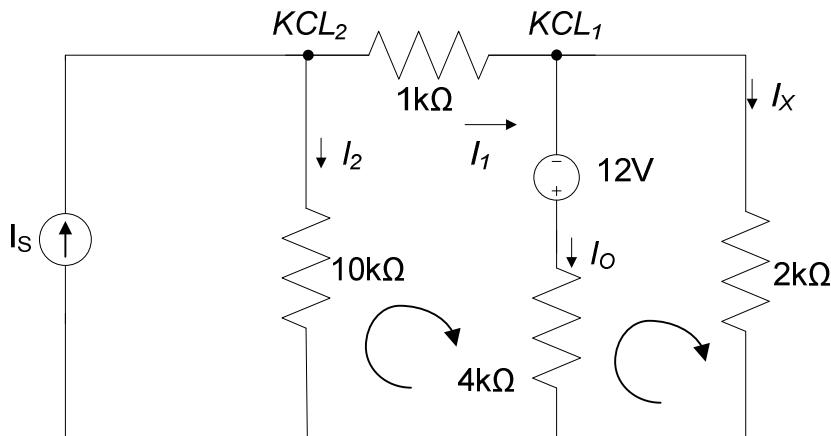

$$I_o = 4mA$$

$$KVL: 12V - I_o \cdot 4k + I_x \cdot 2k = 0$$

$$V_x = I_x \cdot 2k = I_o \cdot 4k - 12V$$

$$= 4mA \cdot 4k - 12V = 4V$$

$$I_x = \frac{4V}{2k} = 2mA$$

$$KCL: I_1 - I_o - I_x = 0 \Rightarrow I_1 = 2mA + 4mA = 6mA$$

$$KVL: -I_2 \cdot 10k + I_1 \cdot 1k + I_o \cdot 4k - 12V = 0$$

$$I_2 \cdot 10k = 6V + 16V - 12V = 10V$$

$$I_2 = 1mA$$

$$KCL: I_s - I_2 - I_1 \Rightarrow I_s = 1mA + 6mA = 7mA$$