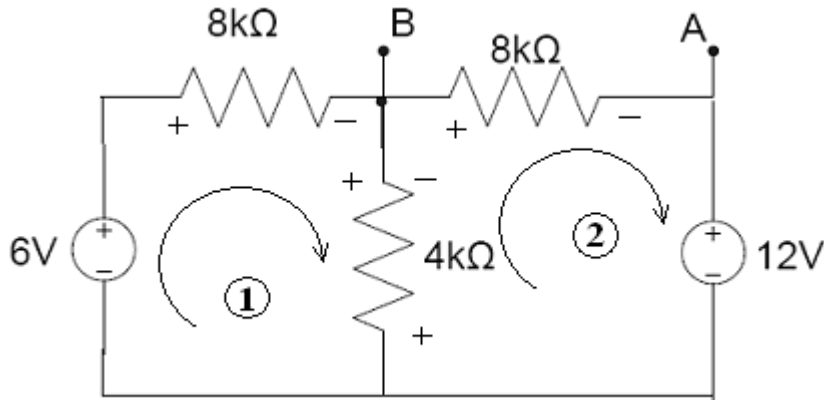


Solution Set 5 (Fall 2008)

5.1 Use Thevenin's theorem using KVL around 2 loops to find V_{ab} in the following network.

Solution:



To find let's consider V_{ab}

$$\text{Loop 1: } -6V + I_1 * 8k\Omega + (I_1 - I_2) * 4k\Omega = 0, \quad (1)$$

$$\text{Loop 2: } I_2 * 8k\Omega + (I_2 - I_1) * 4k\Omega + 12V = 0, \quad (2)$$

$$(1): I_1 * 12k\Omega - I_2 * 4k\Omega = 6V, \quad I_1 = \frac{1}{12k\Omega} (I_2 * 4k\Omega + 6V).$$

$$(2): I_2 * 12k\Omega - I_1 * 4k\Omega = -12V$$


By substituting (1) into (2):

$$I_2 * 12k\Omega - \frac{4k\Omega}{12k\Omega} (I_2 * 4k\Omega + 6V) = -12V,$$

$$I_2 = -15/16mA;$$


$$V_{AB} = -I_2 * 8k\Omega = 7.5V;$$

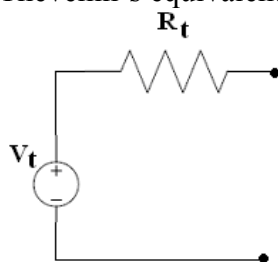
Thevenin's equivalent circuit can be presented as:



To find R_t set all voltage sources to be equal zero (short circuit) and all current sources to be equal zero (open circuit):

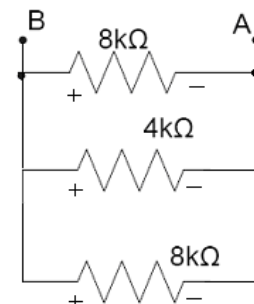
$$R_t = 8k\Omega \parallel 4k\Omega \parallel 8k\Omega = 2k\Omega;$$



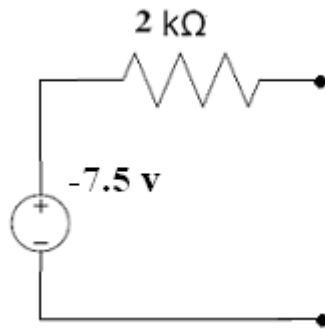

So the Thevenin's circuit is

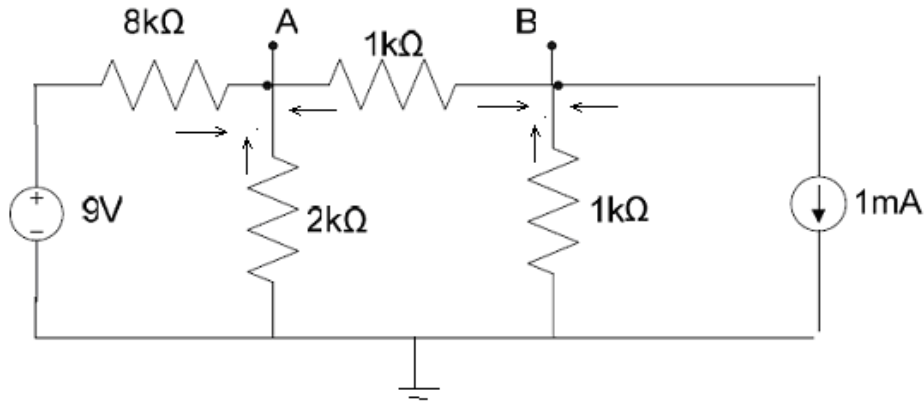5.2 Use Thevenin's theorem using KCL at nodes A and B to find V_{ab} in the following network. (check the solution at node B))



Solution:

$$\text{KCL at the node A: } \frac{9V - V_A}{8k\Omega} + \frac{0 - V_A}{2k\Omega} + \frac{V_B - V_A}{1k\Omega} = 0, \quad (1)$$

$$\text{KCL at the node B: } -1mA + \frac{0 - V_B}{1k\Omega} + \frac{V_A - V_B}{1k\Omega} = 0, \quad (2)$$

Let's express V_a from (1): $V_A = 2V_B + 1V$,

And substitute it into (2):

$$9V - V_A - V_A * 4k\Omega + V_B * 8k\Omega - V_A * 8k\Omega = 0,$$

$$8V_B = 13V_A - 9V,$$


$$8V_B = 13(2V_B + 1V) - 9V$$

$$V_B = -4/18V,$$

Hence $V_A = 5/9V$;


$$V_{AB} = V_A - V_B = 5/9V + 4/18V = 7/9V$$

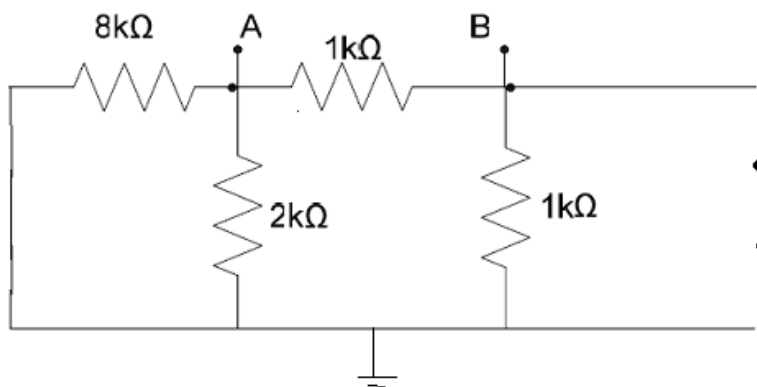To find R_t set all voltage sources to be equal zero (short circuit) and all current sources to be equal zero (open circuit):




So $R_T = 1k\Omega \parallel (1k\Omega + 2k\Omega \parallel 8k\Omega) = 0.722k\Omega$;

The Thevenin's equivalent is:

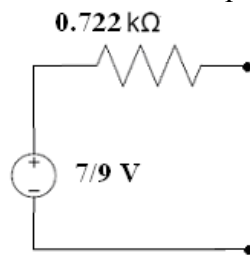

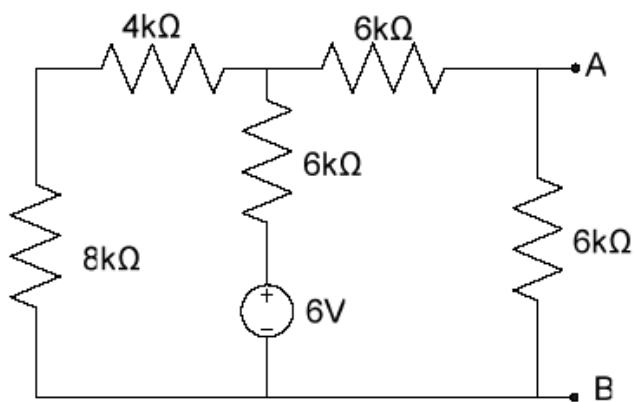
5.3 Find the Norton equivalent source for each of the following circuits



Solution:

1. Find I_S

Redraw circuit:

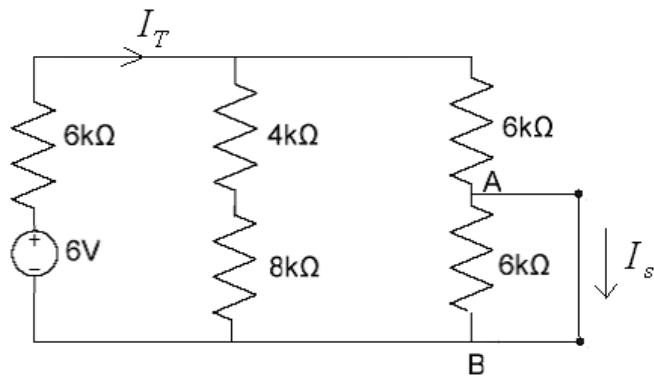

(The $6k\Omega$ resistor shorted out)

$$I_T = \frac{6v}{R_T} = \frac{6v}{6k\Omega + (4k\Omega + 8k\Omega) \parallel 6k\Omega}$$



$$= \frac{6v}{6k\Omega + 4k\Omega} = 0.6mA$$

$$I_s = I_T \cdot \frac{4k\Omega + 8k\Omega}{(4k\Omega + 8k\Omega) + 6k\Omega} \quad \text{(Current divider)}$$

$$= 0.6mA \cdot \frac{12k\Omega}{18k\Omega} = 0.4mA$$

2. Find R_s , set Vsource = 0

Redraw circuit:

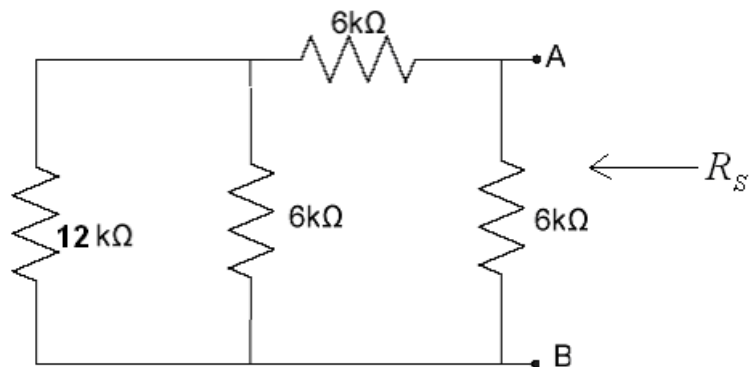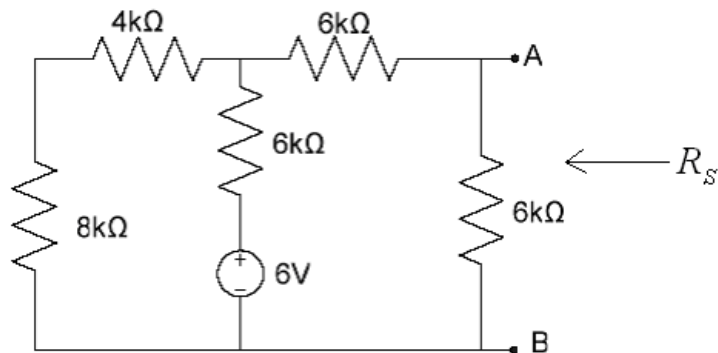


$$R_s = 6k\Omega \parallel [(12k\Omega \parallel 6k\Omega) + 6k]$$

$$= 6k\Omega \parallel 10k\Omega$$

$$= 3.75k\Omega$$


3. Draw the Norton equivalent source:

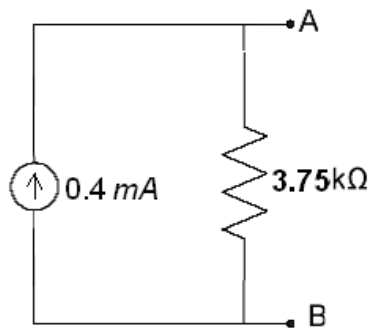


5.4 Find Norton equivalent source for the following circuit.

Solution:

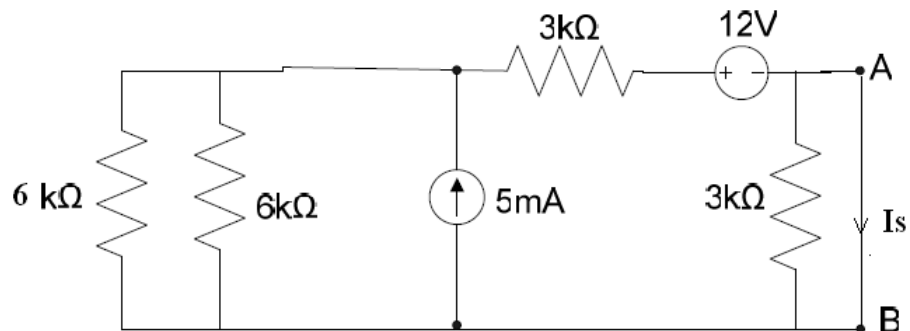1. The original circuit can be redrawn as:



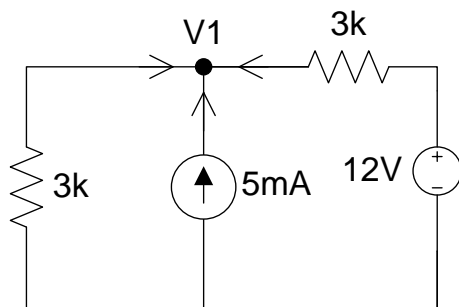To find I_s let's apply KCL at the node V1:




$$\frac{0 - V1}{3k\Omega} + 5mA + \frac{12V - V1}{3k\Omega} = 0,$$


$$V1 = 13.5V$$

$$I_s = \frac{V1 - 12V}{3k\Omega} = 0.5mA,$$

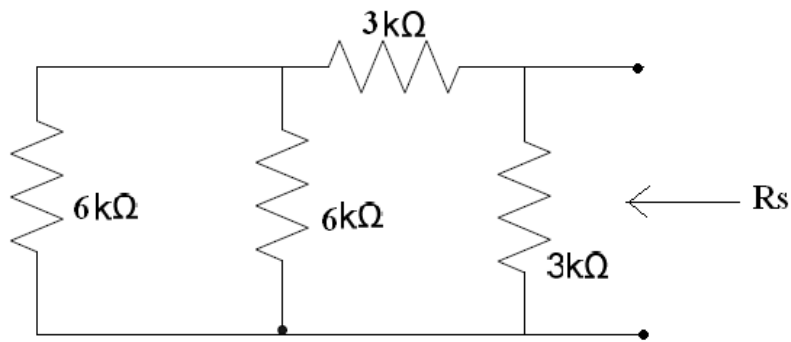
2. Find R_s (set all voltage sources to be equal zero (short circuit) and all current sources to be equal zero (open circuit)):



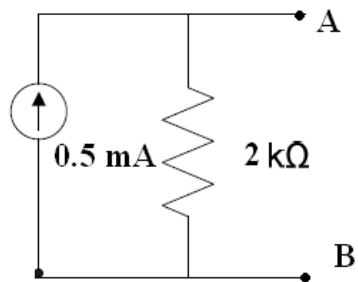$R_s = 3k\Omega \parallel [3k\Omega + 6k\Omega \parallel 6k\Omega] = 2k\Omega$;
 Hence the Norton equivalent source is:




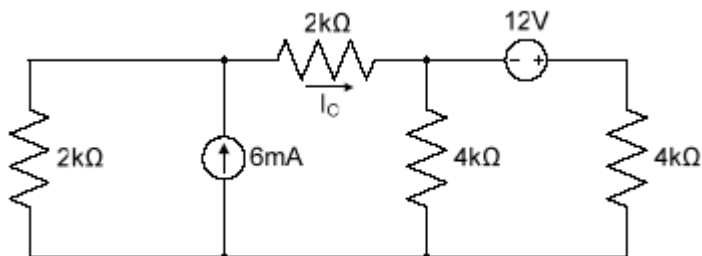5.5 Find I_o in the following network using superposition.




Solution:

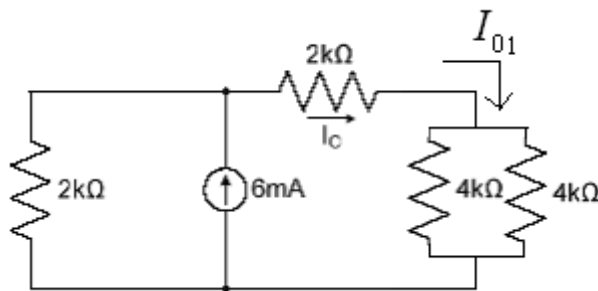Consider the current source (voltage source = short)
 Redraw without the voltage source



$$\begin{aligned}
 I_{01} &= 6mA \cdot \frac{2k\Omega}{2k\Omega + (2k\Omega + 4k\Omega \parallel 4k\Omega)} \\
 &= 6mA \cdot \frac{2k\Omega}{2k\Omega + 2k\Omega + 2k\Omega} \\
 &= 6mA \cdot \frac{2k\Omega}{6k\Omega} \\
 &= 2mA
 \end{aligned}$$

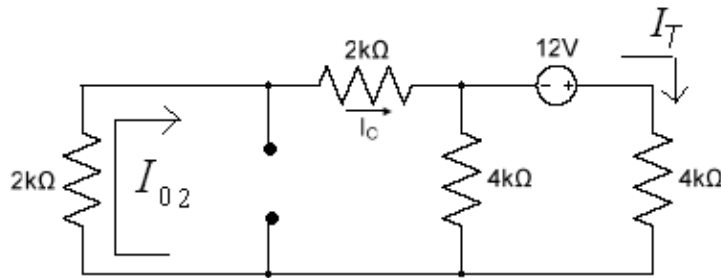Consider the voltage source (Current source = open)
Redraw without the current source.




$$\begin{aligned}
 I_T &= \frac{12V}{4k\Omega + (4k\Omega \parallel (2k\Omega + 2k\Omega))} \\
 &= \frac{12V}{4k\Omega + 2k\Omega} \\
 &= 2mA
 \end{aligned}$$

$$\begin{aligned}
 I_{02} &= 2mA \cdot \frac{4k\Omega}{4k\Omega + (2k\Omega + 2k\Omega)} \\
 &= 2mA \cdot \frac{4k\Omega}{8k\Omega} \\
 &= 1mA
 \end{aligned}$$

$$\begin{aligned}
 I_0 &= I_{01} + I_{02} \\
 &= 2mA + 1mA \\
 &= 3mA
 \end{aligned}$$

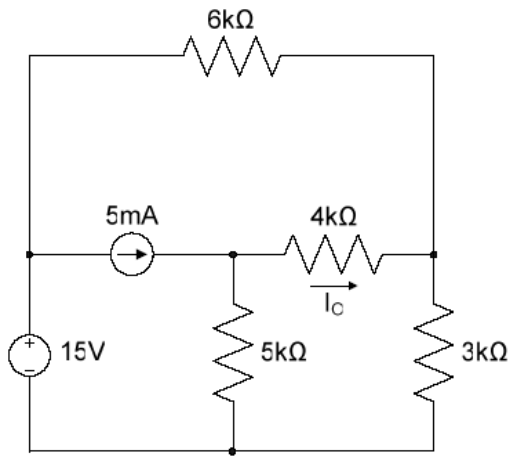
5.6 Find I_0 in the following network using superposition (Hint: At some point: $3k\Omega \parallel 6k\Omega$)



Solution:

Consider the current source (Voltage source = short)

Redraw without the voltage source

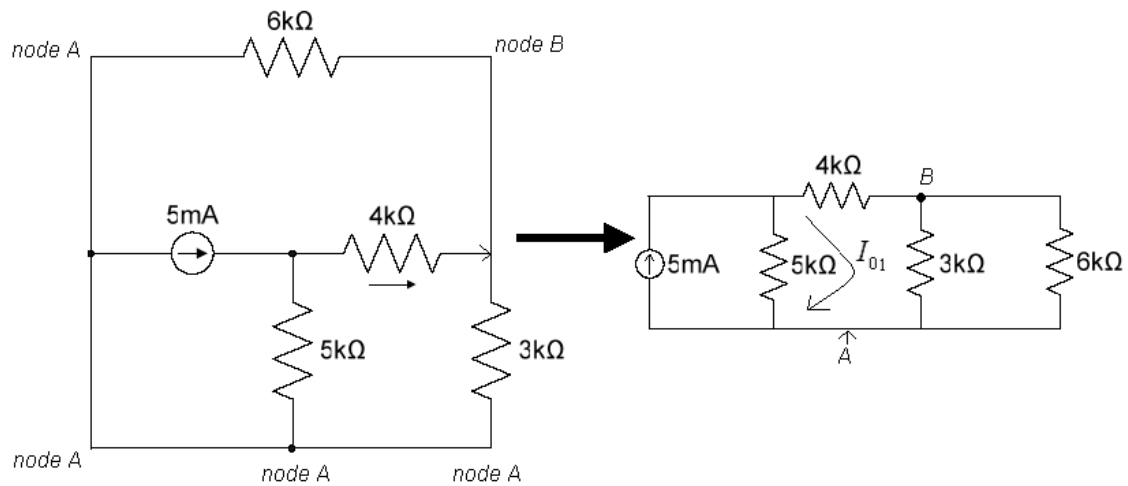


$$I_{01} = 5mA \frac{5k\Omega}{5k\Omega + (4k\Omega + 3k\Omega \parallel 6k\Omega)}$$

$$I_{01} = 5mA \frac{5k\Omega}{5k\Omega + 4k\Omega + 2k\Omega}$$

$$I_{01} = 5mA * 0.455 = 2.275mA$$

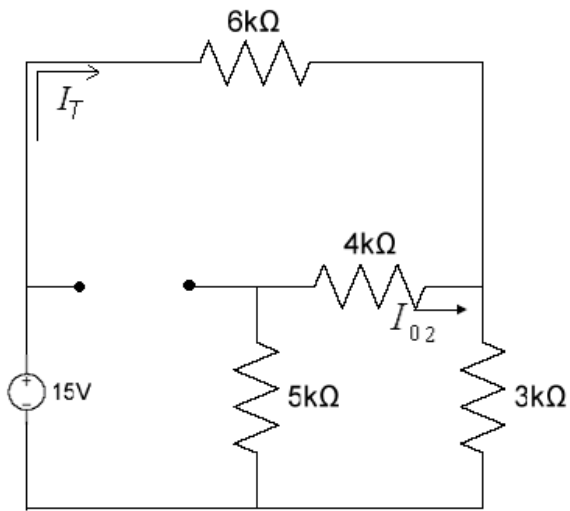Consider the voltage source (current source is open):



Note: I_{02} points in the opposite direction than I_T

$$I_T = \frac{15V}{6k\Omega + (3k\Omega \parallel (4k\Omega + 5k\Omega))} = 1.82mA$$

$$I_{02} = -1.82mA * \frac{3k\Omega}{3k\Omega + (4k\Omega + 5k\Omega)} = -0.455mA$$

$$I_0 = I_{01} + I_{02} = 2.275 + (-0.455mA) = 1.82mA$$