

Solution Set 7 (Fall 2011)

7.1 Determine the phase angles by which $v_1(t)$ leads $i_1(t)$ and $v_1(t)$ leads $i_2(t)$, where :

$$v_1(t) = 6\sin(377t + 25^\circ)V$$

$$i_1(t) = 0.04\cos(377t - 10^\circ)A$$

$$i_2(t) = -0.2\sin(377t - 75^\circ)A$$

Solution:

$$i_1(t) = 0.04\cos(377t - 10^\circ)A = 0.04\sin(377t - 10^\circ + 90^\circ)A = 0.04\sin(377 + 80^\circ)A$$

It means that $v_1(t)$ leads $i_1(t)$ by $25^\circ - 80^\circ = -55^\circ$.


$$i_2(t) = -0.2\sin(377t - 75^\circ)A = 0.2\sin(377 - 75^\circ + 180^\circ)A = 0.2\sin(377 + 105^\circ)A$$

It means that $25^\circ - 105^\circ = -80^\circ$

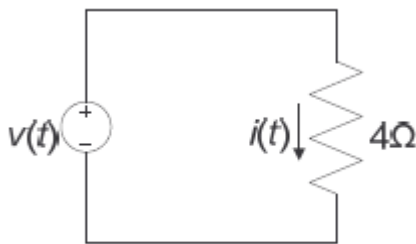7.2 Calculate $i(t)$, the time-domain current in the resistor in the following circuit if the input voltage is:

$$1) \quad v_1(t) = 12\cos(377t + 180^\circ)V$$

$$2) \quad v_2(t) = 16\sin(377t + 45^\circ)V$$



Solution:

This is a purely resistive network: $i(t)$ and $v(t)$ are in phase


$$1) \quad i_1(t) = v_1(t)/R = \frac{12\cos(377t + 180^\circ)}{4}A = 3\cos(377t + 180^\circ)A$$

$$2) \quad i_2(t) = v_2(t)/R = \frac{16}{4}\sin(377t + 45^\circ)A = 4\sin(377t + 45^\circ)A$$

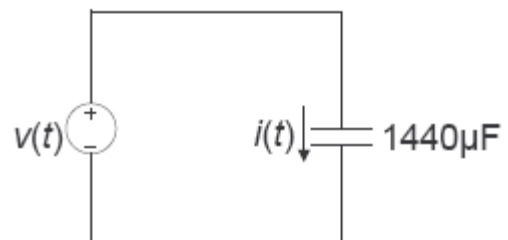7.3 Calculate $i(t)$, the time-domain current in the capacitor in the following circuit if the input voltage is:

$$1) \quad v_1(t) = 8\cos(377t - 30^\circ)V$$

$$2) \quad v_2(t) = 4\sin(377t + 60^\circ)V$$



Solution:

This is purely Capacitive network: $i(t)$ leads $v(t)$ by 90° .

$i(t) = C \frac{dv(t)}{dt}$, However, this equation can be rewritten as $I = j\omega CV$ (eq.7.29 Irwin)

1) $I_1 = j\omega C(8\angle -30^\circ)A$, where $v_1(t) = 8\cos(377t - 30^\circ)V$

$$I_1 = 377 * 1440 * 10^{-6} \angle 90^\circ * 8\angle -30^\circ A = 4.34\angle 60^\circ A$$

$$i_1(t) = 4.34\cos(377 + 60^\circ)A$$

2) $v_2(t) = 4\sin(377t + 60^\circ)V = 4\cos(377t + 60^\circ - 90^\circ)V = 4\cos(377 - 30^\circ)V$


$$I_2 = j\omega C(4\angle -30^\circ)A = 377 * 1440 * 10^{-6} \angle 90^\circ * 4\angle -30^\circ A = 2.17\angle 60^\circ A$$

$$i_2(t) = 2.17\cos(377 + 60^\circ)A$$

7.4 Calculate $i(t)$, the time-domain current in the inductor in the following circuit if the input voltage is:

1) $v_1(t) = 24\cos(377t + 12^\circ)V$

2) $v_2(t) = 18\sin(377t + 48^\circ)V$

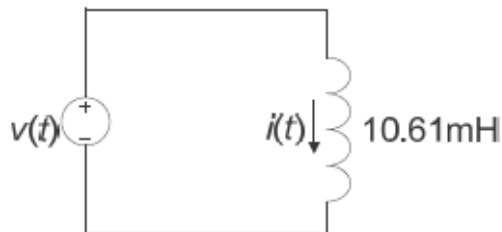

Solution:

This purely Inductive network:

$i(t)$ by 90°

$$v(t) = L \frac{di(t)}{dt} \quad \text{This can be simplified to } V = j\omega LI$$

1) $v_1(t) = 24\cos(377t + 12^\circ)V$

$$I = \frac{V_1}{j\omega L} = \frac{24\angle 12^\circ}{377 * 10.61 * 10^{-3} \angle 90^\circ} = 6\angle (12^\circ - 90^\circ) = 6\angle -78^\circ$$

$$i(t) = 6\cos(377 - 78^\circ)A$$

2) $v_2(t) = 18\sin(377t + 48^\circ)V = 18\cos(377t + 48^\circ - 90^\circ)V = 18\cos(377t - 42^\circ)V$;

$$I_2 = \frac{18\angle -42^\circ}{377 * 10.61 * 10^{-3} \angle 90^\circ} A = 4.5\angle (-42^\circ - 90^\circ) = 4.5\angle -132^\circ$$

$$i(t) = 4.5\cos(377t - 132^\circ)A$$

7.5 Find the frequency-domain impedance Z of the following network:



Solution:


This is a series RLC network:

$$\text{Impedance } Z = Z_R + Z_C + Z_L$$

$$Z = Z_R + Z_C + Z_L = 0.5\Omega - j2\Omega + j5\Omega = 0.5 + j3(\Omega) = \sqrt{0.5^2 + 3^2} \angle \tan^{-1}\left(\frac{3}{0.5}\right) = 3.04 \angle 80.54^\circ$$

$$Z = 3.04 \angle 80.54^\circ$$

7.6 Find the frequency-domain impedance Z of the following network:

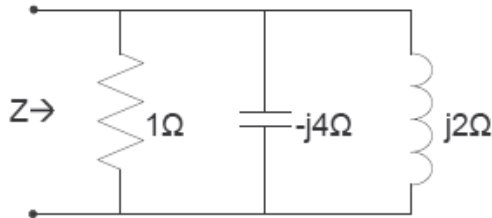**Solution:**

This is a Parallel RLC network

$$\text{Impedance } Z = \left(\frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L} \right)^{-1}$$


$$\frac{1}{Z} = \frac{1}{1\Omega} + \frac{1}{-j4\Omega} + \frac{1}{j2\Omega} = 1 + j0.25 - j0.5 = 1 - j0.25$$

$$Z = \frac{1}{1 - j0.25} \Omega = \frac{1}{\sqrt{1 + (-0.25)^2} \angle \tan^{-1}(-0.25/1)} \Omega \approx \frac{1}{1.03 \angle -14.04^\circ} \Omega = 0.97 \angle 14.04^\circ \Omega$$

$$Z = 0.97 \angle 14.04^\circ \Omega \quad \text{or} \quad Z^{-1} = Y \approx 1.03 \angle -14.04^\circ$$

7.7 The voltages $v_R(t)$ and $v_L(t)$ in the following circuit can be redrawn as phasors in a phasor diagram. Use a phasor diagram to show that $v_R(t) + v_L(t) = v_s(t)$ where


$$v_s(t) = 120 \cos(377t) V$$

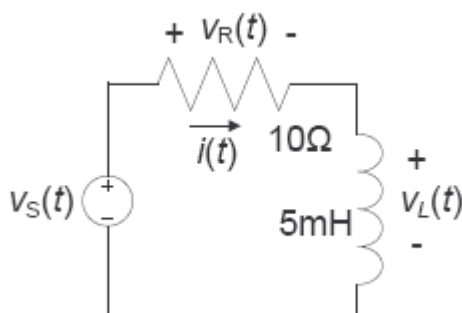**Solution:**

$$I = \frac{V_s}{R + j\omega L} = \frac{120 \angle 0^\circ}{10 + j(377 \times 5m)} = 11.79 \angle -10.67^\circ$$

$$V_L = j\omega L I = 377 \times 5 \times 10^{-3} \angle 90^\circ \times 11.79 \angle -10.67^\circ = 22.22 \angle 79.33^\circ$$
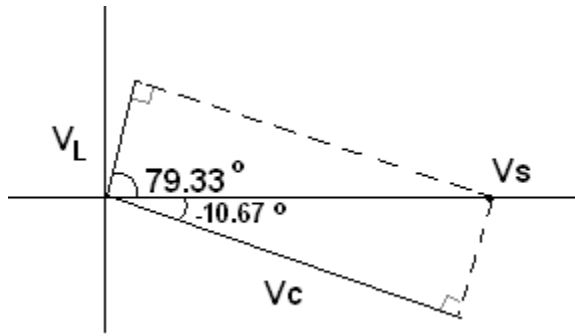
$$v_L(t) = 22.22 \cos(377t + 79.33^\circ) V$$



$$\Delta\angle = \tan^{-1}\left(\frac{V_L}{V_R}\right) = \tan^{-1}\frac{22.22}{117.9} = 10.67$$


$$V_S^2 = V_R^2 + V_L^2 = 117.9^2 + 22.22^2 = 14394.14$$

$$V_S = 120$$

$$\angle V_S = \angle V_R + \Delta\angle = -10.67 + 10.67 = 0$$

7.8 The currents $i_R(t)$ and $i_C(t)$ in the following circuit can be drawn as phasors in a phasor diagram. Use such a phasor diagram to show that $i_C(t) + i_R(t) = i_s(t)$ where:

$$i_s(t) = 20 \cos(377t + 30^\circ) A$$

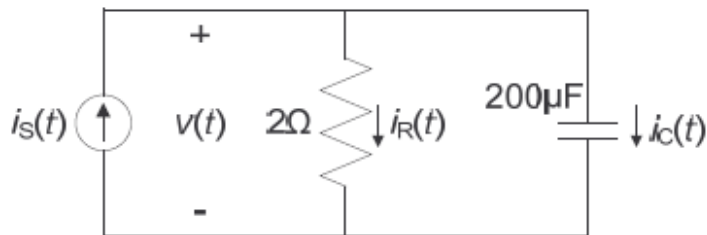

Solution:

This is a parallel network:

$$Z_c = \frac{1}{j\omega C} = \frac{1}{j * 377 * 200 * 10^{-6}} = -j13.26 = 13.26 \angle -90^\circ$$

Using a current divider,

$$I_R = I_s * \frac{Z_C}{Z_r + Z_C} = 20 \angle 30^\circ \frac{13.26 \angle -90^\circ}{2 - j13.26} =$$


$$= 20 \angle 30^\circ \frac{13.26 \angle -90^\circ}{13.41 \angle -81.42^\circ} = 20 \frac{13.26}{13.41} \angle 30^\circ - 90^\circ + 81.42^\circ =$$

$$= 19.78 \angle 21.42^\circ$$

$$I_R = I_s * \frac{Z_R}{Z_R + Z_C} = 20 \angle 30^\circ \frac{2}{13.41 \angle -81.42^\circ} =$$

$$= 20 \frac{2}{13.41} \angle 30^\circ + 81.42^\circ$$
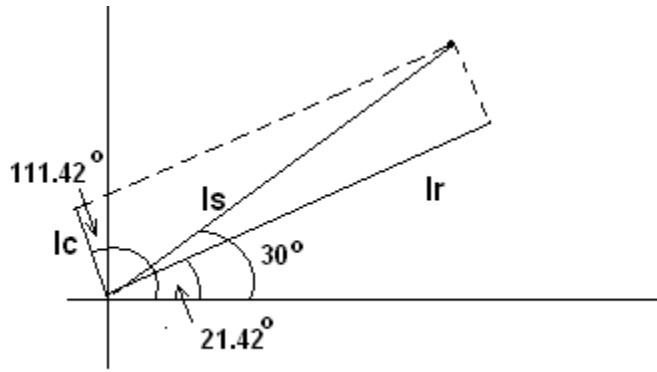
$$I_s = \sqrt{I_C^2 + I_R^2} = \sqrt{19.78^2 + 2.98^2} = 20;$$




$$\Delta L = \tan^{-1}\left(\frac{I_C}{I_R}\right) = \tan^{-1}\left(\frac{2.98}{19.78}\right) = 8.57^\circ$$

$$\angle I_S = \angle I_R + \Delta L = 21.42^\circ + 8.57^\circ \approx 30^\circ$$

$$\angle I_S = \angle I_R + \Delta L = 21.42^\circ + 8.57^\circ \approx 29.9 \approx 30^\circ$$

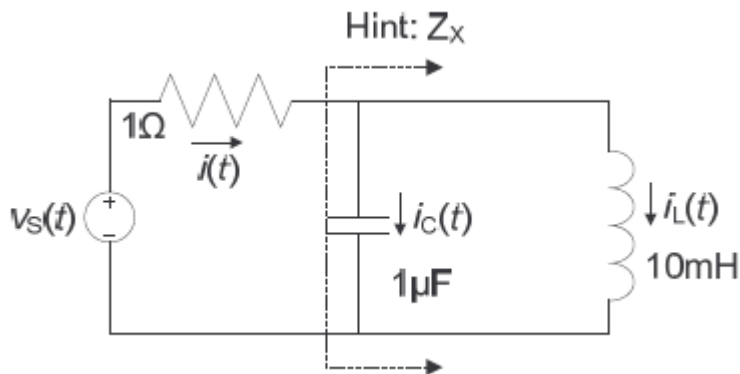7.9 The currents $i_L(t)$ and $i_C(t)$ of the inductor and capacitor, respectively, in the following circuit can be drawn as phasors in a phasor diagram. Show in the phasor diagram that $i_L(t) + i_C(t) = i_S(t)$ where:

$$v_s(t) = 10 \cos(10^3 t + 30^\circ) V$$



Solution:

Z_x is a parallel network $Z_x = Z_L \parallel Z_C$

$$Z_C = 1 / j\omega C = \frac{1}{j10^3 * 10^{-6}} = -j10^3$$

$$Z_L = j\omega L = j10^3 (10 * 10^{-3}) = j10$$


$$Z_x = \frac{Z_C * Z_L}{Z_L + Z_C} = \frac{-j10^3 * j10}{-j10^3 + j10} = j10.1$$

Voltage divider:

$$V_a = V_s \frac{Z_x}{Z_x + Z_R} = 10 \angle 30^\circ \frac{j10.1}{1 + j10.1} = 10 \angle 30^\circ \frac{10.1 \angle 90^\circ}{10.15 \angle 84.35^\circ} = 9.95 \angle 35.65^\circ$$

$$I_L = \frac{V}{Z_L} = \frac{9.95 \angle 35.65^\circ}{j10} = \frac{9.95 \angle 35.65^\circ}{10 \angle 90^\circ} = 0.995 \angle -54.35^\circ (A)$$
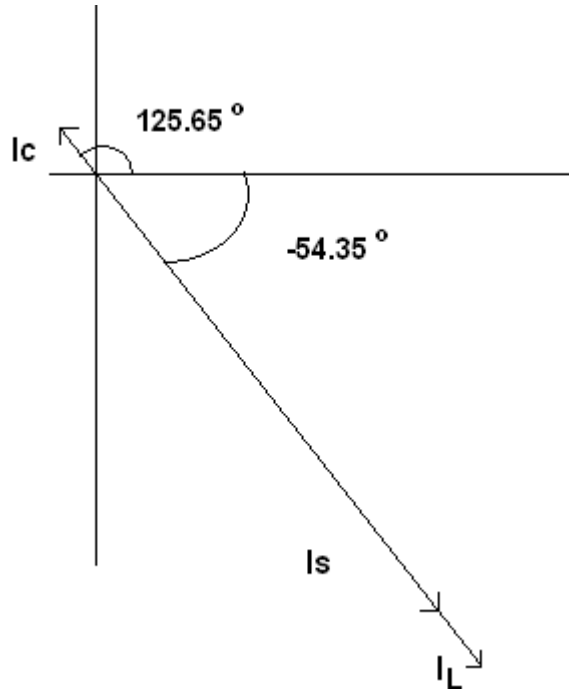
$$I_C = V / Z_C = 9.95 \angle 35.65^\circ \left(\frac{1}{-j10^3} \right) = 9.95 \angle 35.65^\circ \left(\frac{1}{10^3 \angle -90^\circ} \right) = 9.95 * 10^{-3} \angle 125.65^\circ$$



$$I_S = 0.995 \angle -54.35^\circ + 9.95 * 10^{-3} \angle 125.65^\circ = 0.995 \angle -54.35^\circ - 9.95 * 10^{-3} \angle -54.35^\circ = 0.985 \angle -54.35^\circ$$

Verification:

$$V_S = 10 \angle 30^\circ = 10 \cos 30 + j10 \sin 30 = 8.66 + j5.00$$

$$V_a = 9.95 \angle 35.65^\circ = 8.09 + j5.80$$

$$I_S = \frac{V_S - V_a}{R} = \frac{8.66 + j5.0 - (8.09 + j5.8)}{1} = 0.57 - 0.8j = 0.982 \angle -54.53^\circ$$

$$I_{S_{phasor}} = I_{S_{calculated}}$$

7.10. Repeat 7.9 for $v_s(t) = 10 \cos(10^4 t + 30^\circ) V$ (surprising result called ‘resonance’).

Solution:

$$Z_C = 1 / j\omega C = \frac{1}{j10^4 * 10^{-6}} = -j100$$

$$Z_L = j\omega L = j10^4 (10 * 10^{-3}) = j100$$

$$Z_x = \frac{Z_c * Z_L}{Z_c + Z_L} = \frac{-j100 * j100}{-j100 + j100} = \frac{10^4}{0} j = +\infty$$

$$\text{Voltage divider: } V_a = V_s \frac{Z_x}{Z_x + Z_R} = V_s \frac{1}{1 + Z_R / Z_x} = V_s(1/(1+0))$$

$$V_a = V_s$$


LC is in resonance

This is very large impedance (Z_x) –it is like an open circuit

Since $V_a = V_s$ there is no current through the resistor

$$I_L = V_s / Z_L = \frac{10 \angle 30^\circ}{j100} = \frac{10 \angle 30^\circ}{100 \angle 90^\circ} = 0.1 \angle -60^\circ$$
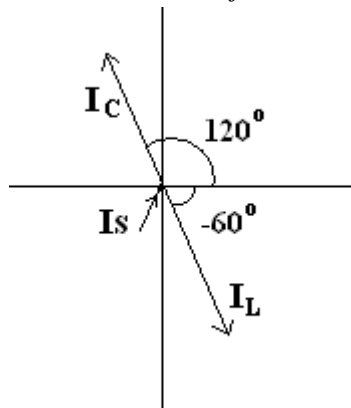
$$I_C = V_s / Z_C = \frac{10 \angle 30^\circ}{-j100} = \frac{10 \angle 30^\circ}{100 \angle -90^\circ} = 0.1 \angle -120^\circ$$



$$I_s = \frac{V_s - V_a}{R} (A) = 0 / R (A) = 0(A)$$

Note: the currents are identical in magnitude, but 180° out of phase. This means the I_s is zero.

This is the same value as the current which passes through the resistor.

The currents flow between L and C, but never escape the resonant network. The energy is exchanged between the electric field of the capacitor and the magnetic field of the inductor.