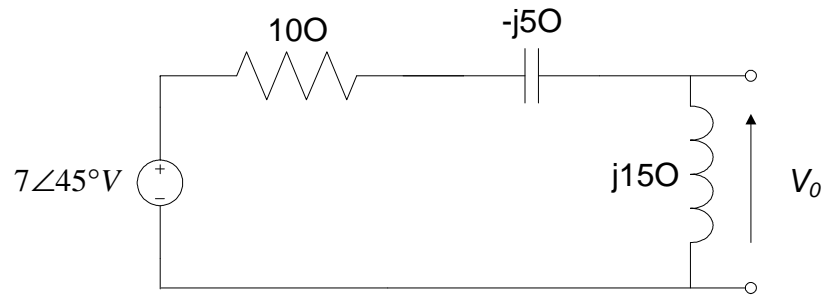


Problem Set 8 (Fall 2011)

8.1 Using voltage divider :


$$\begin{aligned}
 V_o &= 7 \angle 45^\circ \cdot \frac{Z_L}{Z_R + Z_C + Z_L} \\
 &= 7 \angle 45^\circ \cdot \frac{j15}{10 - 5 + 15} \\
 &= 7 \angle 45^\circ \cdot \frac{15 \angle 90^\circ}{10 + j10} \\
 &= 7 \angle 45^\circ \cdot \frac{15 \angle 90^\circ}{10\sqrt{2} \angle 45^\circ} \\
 &= 5.25 \sqrt{2} \angle 90^\circ \text{ V}
 \end{aligned}$$



(* Note : According to the convention in this course, the arrow point to the higher potential , which might be the opposite to those physics background)

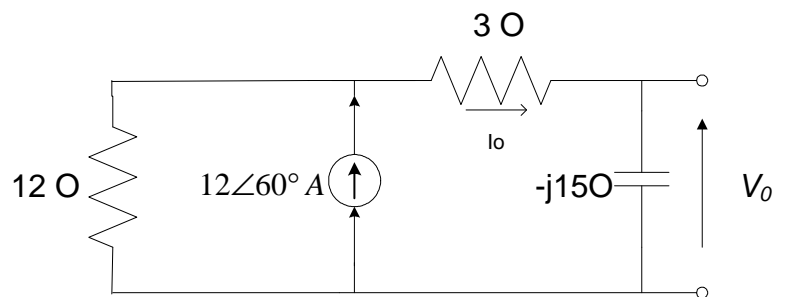8.2 Using current divider:

$$\begin{aligned}
 I_o &= 12 \angle 60^\circ \cdot \frac{12}{12 + 3 - j15} \\
 &= 12 \angle 60^\circ \cdot \frac{12}{15\sqrt{2} \angle -45^\circ} \\
 &= \frac{24\sqrt{2}}{5} \angle 105^\circ \text{ A}
 \end{aligned}$$



$$\begin{aligned}
 V_o &= I_o (-j15\Omega) \\
 &= \frac{24\sqrt{2}}{5} \angle 105^\circ \cdot 15 \angle -90^\circ \\
 &= 72 \sqrt{2} \angle 15^\circ \text{ V}
 \end{aligned}$$

$$8. Z_o = -2j \parallel 1 = \frac{-2j}{1-2j} = \frac{-2j(1+2j)}{1-2j(1+2j)}$$

$$= \frac{4-2j}{5} = 0.8 - 0.4j \, \Omega$$


Using voltage divider:

$$V_o = 100 \angle 90^\circ \cdot \frac{Z_o}{Z_o + 2 + j}$$

$$= 100 \angle 90^\circ \cdot \frac{0.8 - 0.4j}{0.8 - 0.4j + 2 + j} = 100 \angle 90^\circ \cdot \frac{0.894 \angle -26.6^\circ}{2.86 \angle 12.1^\circ}$$

$$= 31.26 \angle 51.3^\circ \, \text{V}$$
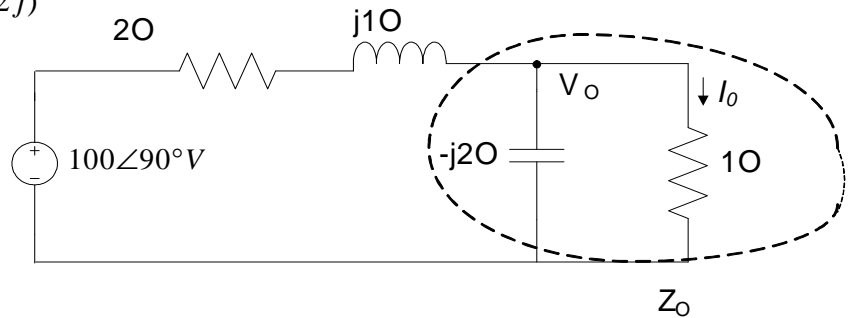
$$I_o = \frac{V_o}{1\Omega} = 31.26 \angle 51.3^\circ \, \text{A}$$



8.4 Power is absorbed only by the resistor. Inductors and capacitors only store energy. They do not consume.


Using current divider:

$$I_R = 10 \angle 45^\circ \cdot \frac{2j - 4j}{2j - 4j + 4}$$

$$= 10 \angle 45^\circ \cdot \frac{-2j}{4 - 2j}$$


$$= 10 \angle 45^\circ \cdot \frac{2 \angle -90^\circ}{4.47 \angle -26.6^\circ}$$

$$= 4.47 \angle -18.4^\circ$$

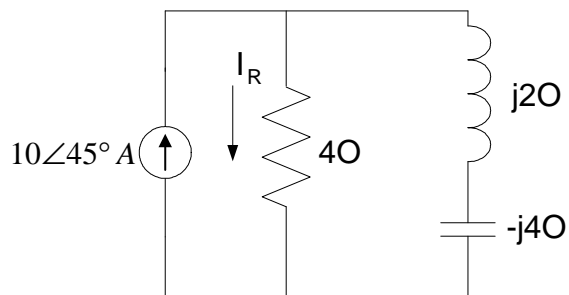

$$\text{Average power } P_A = \frac{1}{2} |I_R|^2 R = \frac{1}{2} (4.47)^2 \cdot 4 \approx 40 \, \text{W}$$

8.5

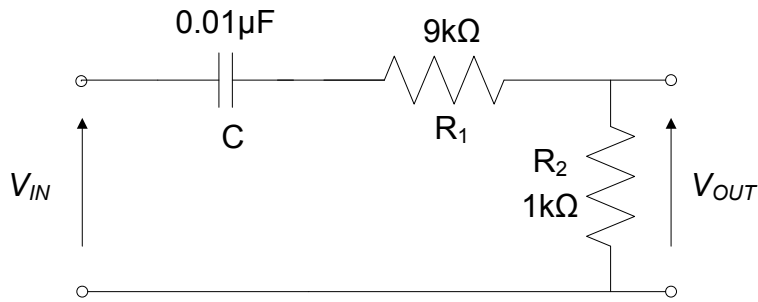

$$Z_c = \frac{1}{j\omega C}$$

Using Voltage Divider

$$V_{out} = \frac{R_2}{R_2 + R_1 + \frac{1}{j\omega C}} \cdot V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{j\omega C R_2}{1 + j\omega C(R_1 + R_2)} = \frac{j\omega \frac{R_2}{R_2 + R_1}}{j\omega + \frac{1}{C(R_1 + R_2)}}$$

Examine the denominator:

$$D(\omega) = j\omega + \frac{1}{C(R_1 + R_2)}$$

At very low frequency $|j\omega| \ll \frac{1}{C(R_1 + R_2)}$, $D(\omega) = \frac{1}{C(R_1 + R_2)}$

At very high frequency $|j\omega| \gg \frac{1}{C(R_1 + R_2)}$, $D(\omega) = j\omega$


Somewhere in between when $|j\omega| = \frac{1}{C(R_1 + R_2)}$ we call this cut off frequency ω_0 . In this

example $\omega_0 = \frac{1}{C(R_1 + R_2)} = 10k \text{ rad/s}$

Therefore


When $\omega_0 \ll \frac{1}{C(R_1 + R_2)}$; $\frac{V_{out}}{V_{in}} = \frac{j\omega \frac{R_2}{R_1 + R_2}}{\frac{1}{C(R_1 + R_2)}} \approx j\omega R_2 C$

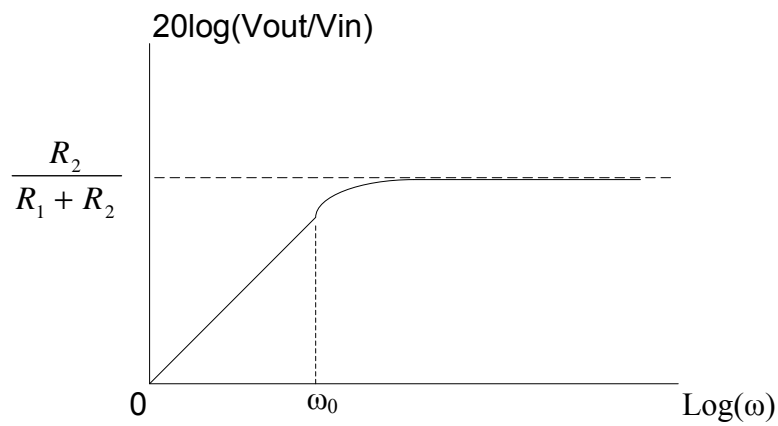When $\omega_0 \gg \frac{1}{C(R_1 + R_2)}$; $\frac{V_{out}}{V_{in}} = \frac{j\omega \frac{R_2}{R_1 + R_2}}{j\omega} \approx \frac{R_2}{R_1 + R_2}$



High pass filter

8.6

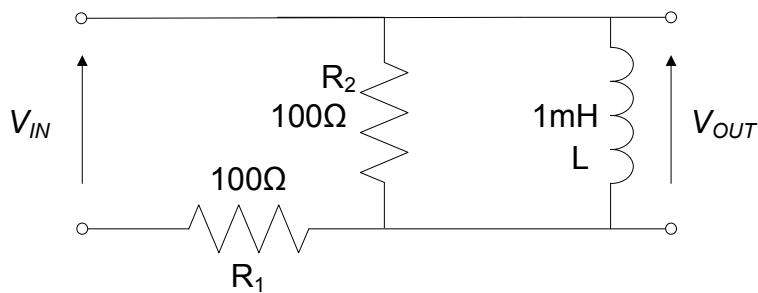

$$V_s = (1/2)V_{in}$$

$$R_s = 100 // 100 = 50\Omega$$

Using Voltage Divider


$$V_{out} = \frac{j\omega(1mH)}{50\Omega + j\omega(1mH)} \cdot \frac{V_{in}}{2}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{2} \cdot \frac{j\omega}{\frac{50}{1m} + j\omega} = \frac{0.5j\omega}{j\omega + 50000}$$

$$\therefore \omega_0 = 50000 \text{ rad/s}$$


$$\text{When } \omega \ll 50000 \text{ rad/s} ; \frac{V_{out}}{V_{in}} \approx \frac{0.5j\omega}{50000} \propto \omega$$
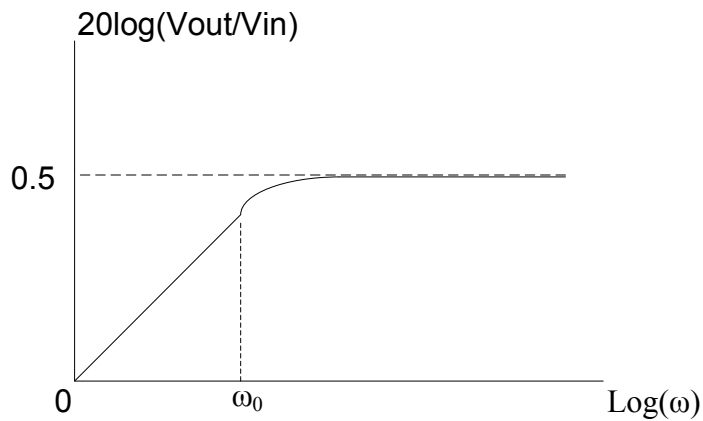
$$\text{When } \omega \gg 50000 \text{ rad/s} ; \frac{V_{out}}{V_{in}} = \frac{0.5j\omega}{j\omega} = 0.5$$



High pass filter

8.7

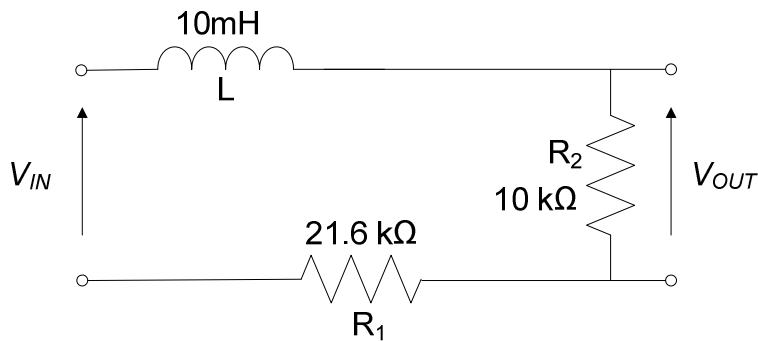

Using Voltage Divider

$$V_{out} = \frac{10k}{10k + 21.6k + 10m \cdot j\omega} \cdot V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{10k}{31.6k + 10m \cdot j\omega}$$


$$= \frac{1M}{3.16M + j\omega}$$

$$\therefore \omega_0 = 3.16 \times 10^6 \text{ rad / s}$$

$$\text{When } \omega \ll 3.16 \times 10^6 \text{ rad / s} ; \frac{V_{out}}{V_{in}} = \frac{1 \times 10^6}{3.16 \times 10^6} \approx \frac{1}{3.16}$$

$$\text{When } \omega \gg 3.16 \times 10^6 \text{ rad / s} ; \frac{V_{out}}{V_{in}} = \frac{1 \times 10^6}{j\omega} \propto \frac{1}{\omega}$$

It's a low pass filter

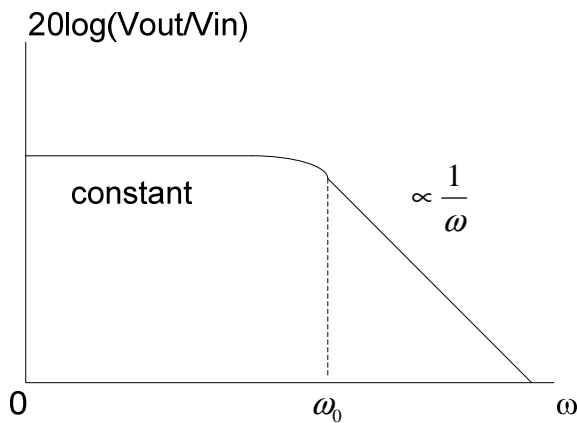


$$8.8 \quad \frac{V_{out}}{V_{in}} = \frac{10}{1 + 10 \bullet j\omega} = \frac{1}{\frac{1}{10} + j\omega} \quad \therefore \omega_0 = \frac{1}{10} = 0.1 \text{ rad / s}$$

$$\text{When } \omega \gg \omega_0 ; \frac{V_{out}}{V_{in}} \approx \frac{1}{j\omega} = \frac{1}{\omega} \angle -90$$


$$\text{When } \omega = \omega_0 ; \frac{V_{out}}{V_{in}} = \frac{1}{\frac{1}{10} + j\frac{1}{10}} = \frac{10}{1 + j} = \frac{10}{\sqrt{2}} \angle -45$$

$$\text{When } \omega \ll \omega_0 ; \frac{V_{out}}{V_{in}} \approx \frac{1}{\frac{1}{10}} = 10 \angle 0$$

Magnitude plot:

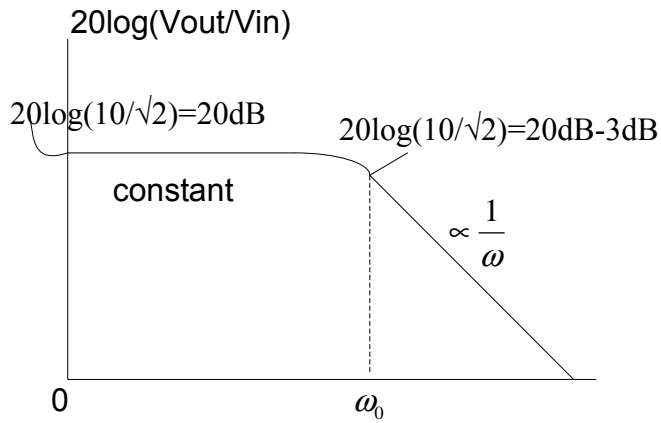

Phase plot:

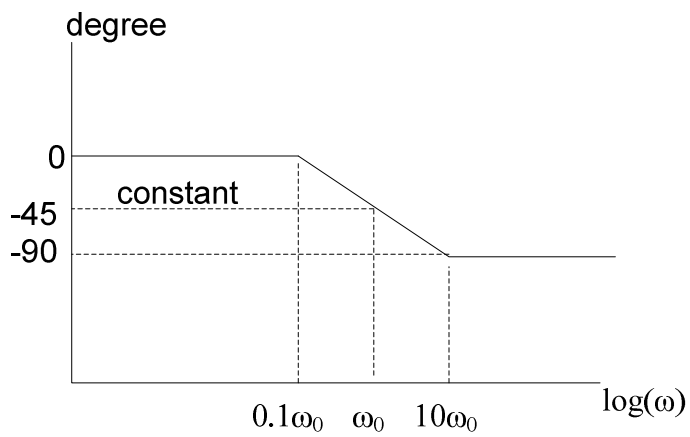


$$8.9 \frac{V_{OUT}}{V_{IN}} = \frac{100}{j\omega - 10} \quad \therefore \omega_0 = 10 \text{ rad/s}$$


$$\text{When } \omega \gg \omega_0 ; \frac{V_{out}}{V_{in}} \approx \frac{100}{j\omega} = \frac{100}{\omega} \angle -90$$

$$\text{When } \omega \ll \omega_0 ; \frac{V_{out}}{V_{in}} \approx \frac{100}{-10} = 10 \angle -180$$

Magnitude plot:

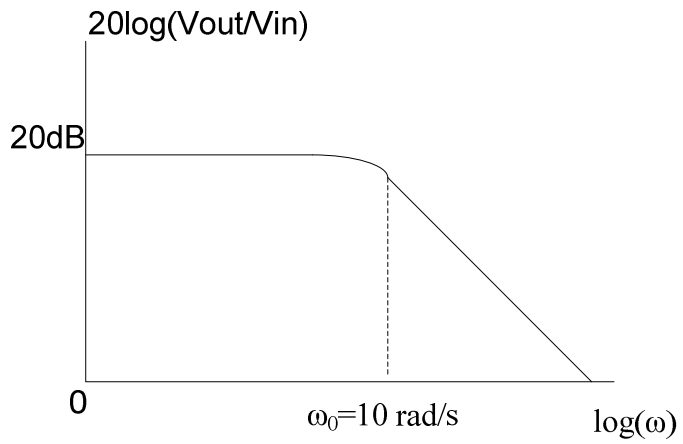

Phase plot:

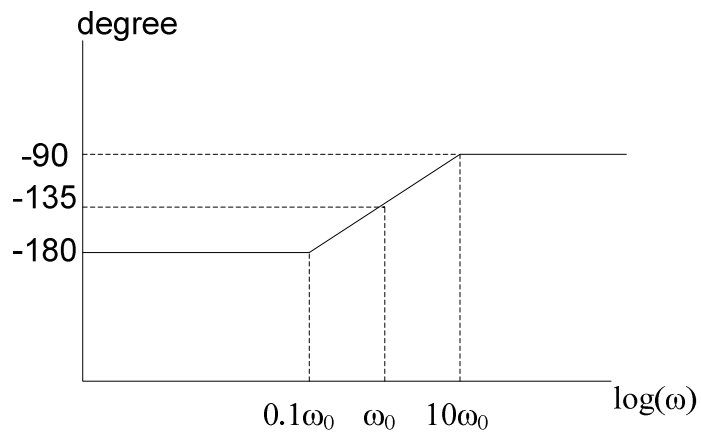

$$8.10 \quad \frac{V_{OUT}}{V_{IN}} = \frac{1}{1 + \frac{1}{j10\omega}} = \frac{j\omega}{j\omega + \frac{1}{10}} = \frac{j\omega}{j\omega + 0.1}$$


$$\therefore \omega_0 = 0.1 \text{ rad/s}$$

$$\text{When } \omega \gg \omega_0 ; \quad \frac{V_{out}}{V_{in}} \approx \frac{j\omega}{j\omega} = 1$$


When $\omega = \omega_0$; $\frac{V_{out}}{V_{in}} = \frac{0.1j}{0.1(j+1)} = \frac{1\angle 90}{\sqrt{2}\angle 45} = \frac{1}{\sqrt{2}}\angle 45$

When $\omega \ll \omega_0$; $\frac{V_{out}}{V_{in}} \approx \frac{j\omega}{0.1} = 10j\omega = 10\omega\angle 90$

Magnitude plot:

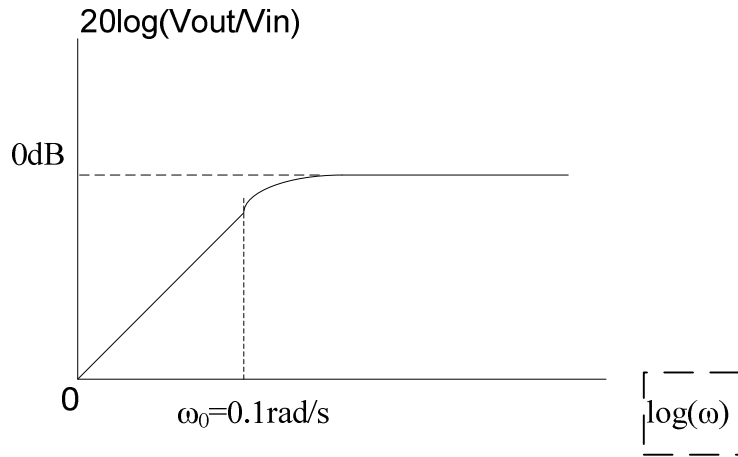

Phase plot:

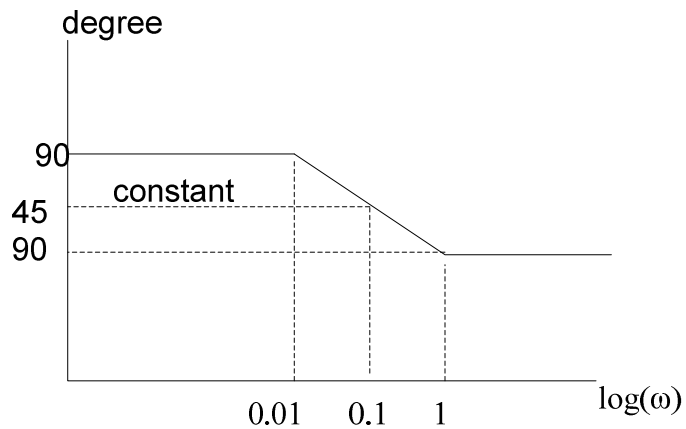

8.11 $\frac{V_{OUT}}{V_{IN}} = \frac{200j\omega}{1+20j\omega} = \frac{10j\omega}{0.05+j\omega}$


$\therefore \omega_0 = 0.05 \text{ rad/s}$

When $\omega \gg \omega_0$; $\frac{V_{out}}{V_{in}} \approx \frac{10j\omega}{j\omega} = 10\angle 0$


When $\omega = \omega_0$; $\frac{V_{out}}{V_{in}} = \frac{10j(0.05)}{0.05 + j(0.05)} = \frac{10j}{1+j} = \frac{10}{\sqrt{2}} \angle 45$

When $\omega \ll \omega_0$; $\frac{V_{out}}{V_{in}} \approx \frac{10j\omega}{0.05} = 200j\omega = 200\omega \angle 90$

Magnitude plot:

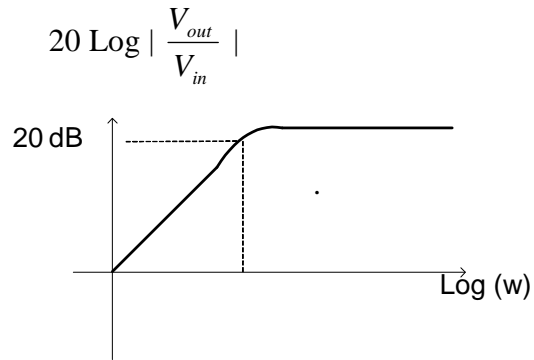

Phase plot:

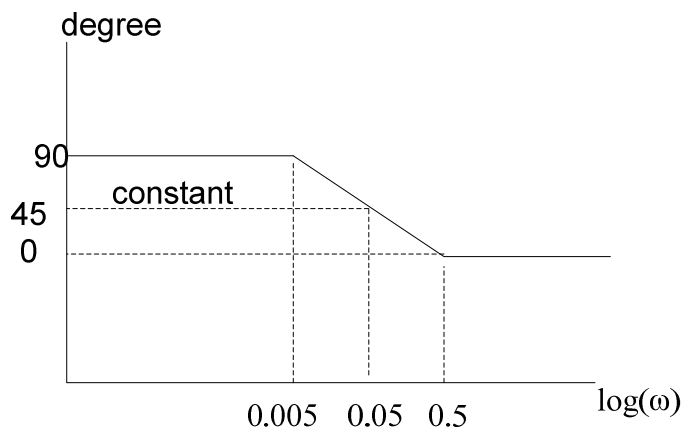

8.12

$$8.8 \quad V_{out} = 10\angle 135 \cdot \frac{10}{1 + j10} = \frac{100\angle 135}{10.05\angle 84} = 9.95\angle 51$$

$$8.9 \quad V_{out} = 10\angle 135 \cdot \frac{100}{j - 10} = \frac{100\angle 135}{10.05\angle 174.3} = 9.95\angle -39.3$$

$$8.10 \quad V_{out} = 10\angle 135 \cdot \frac{j}{j + 0.10} = 10\angle 135 \bullet \frac{1\angle 90}{1.004\angle 84} = 9.95\angle 141$$

$$8.11 \quad V_{out} = 10\angle 135 \cdot \frac{10j}{0.05 + j} = 10\angle 135 \bullet \frac{10\angle 90}{1.0012\angle 87} = 99.9\angle 138$$