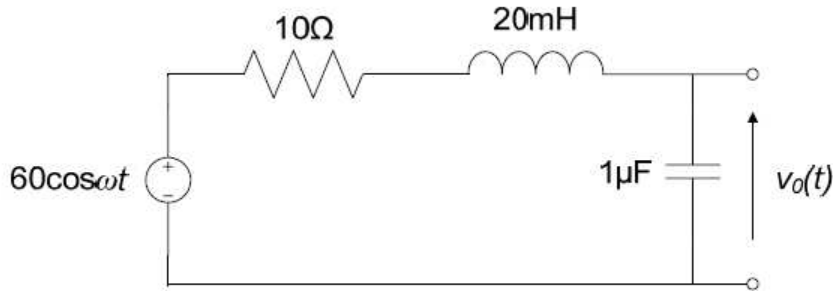


## Solution Set 9 (Fall 2011)

9.1 Given the network below find  $\omega_0$ ,  $|V_o(\omega_0)|$  and Q.



**Solution:**

Resonance occurs when  $\omega L = \frac{1}{\omega C} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$

$$\omega_0 = \frac{1}{\sqrt{20mH * 1\mu F}} = 7071 rad / s$$

During the resonance:

$$I(\omega_0) = \frac{60\angle 0^\circ}{10} = 6\angle 0^\circ$$

$$V(\omega_0) = I(\omega_0) * Z_C = 6\angle 0^\circ * \left(\frac{1}{j\omega C}\right) = 6\angle 0^\circ * 141.426\angle -90^\circ = 848.546\angle -90^\circ (V)$$

$$Q = \frac{|V_C|}{|V_S|} = \frac{|V_o(\omega_s)|}{|V_s|} = \frac{848.54}{60} = 14.14$$

Note: in this case  $|V_C| = \frac{|V_s|}{R} * \frac{1}{\omega C} \rightarrow \frac{|V_C|}{|V_s|} = Q = \frac{1}{\omega CR}$ ;

9.2 Repeat the problem 9.1 if the value of R is changed to 1 ohm.


**Solution:**

$\omega_0 = 7071 rad / s$  (as L and C are unchanged)

$$I(\omega_0) = \frac{60\angle 0^\circ}{1} = 60\angle 0^\circ$$

$$V_o(\omega_0) = I(\omega_0) * Z_C = 60\angle 0^\circ * 141.42\angle -90^\circ = 8485.36\angle -90^\circ (V)$$


$$|V_o(\omega_0)| = 8485.36 (V)$$

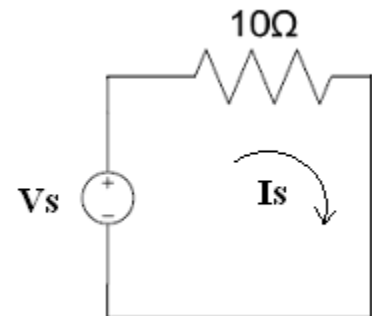

$$Q = \frac{|V_0(\omega_0)|}{|V_s|} = \frac{8485.36}{60} = 141.42$$

Note that since  $Q \propto 1/R$  (in this case)  
 $R \downarrow \times 10 \quad Q \uparrow \times 10$

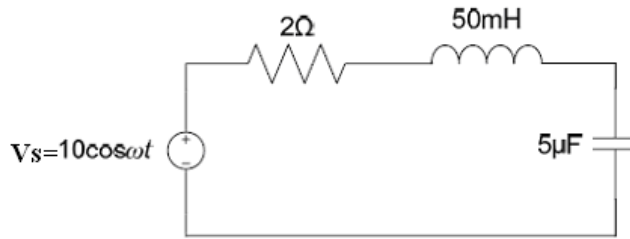**9.3** Determine the resonant frequency, Q, BW and the average power dissipated by the network at resonance.



**Solution:**


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{50mH * 5\mu F}} = 2000 rad / s$$

$$|V_L| = I_s * \omega_0 * L = \frac{|V_s|}{R} * \omega_0 L$$

$$Q = \frac{|V_L|}{|V_s|} = \frac{|V_s|}{R} * \omega_0 L / |V_s| = \omega_0 L / R = 2000 * 50mH / 2\Omega = 50$$

$$\text{Bandwidth BW} = \Delta\omega = \frac{\omega_0}{Q} = \frac{2000}{50} = 40 rad / s$$


Power resonance:

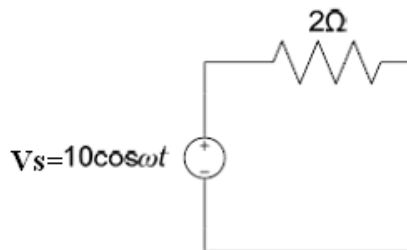

$$V_{rms} = R.M.S(10 \cos \omega t) = 10 / \sqrt{2}$$

$$P_{avg} = V_{rms}^2 / R = \left( \frac{10}{\sqrt{2}} \right)^2 \cdot \frac{1}{2} = 25 Watt$$

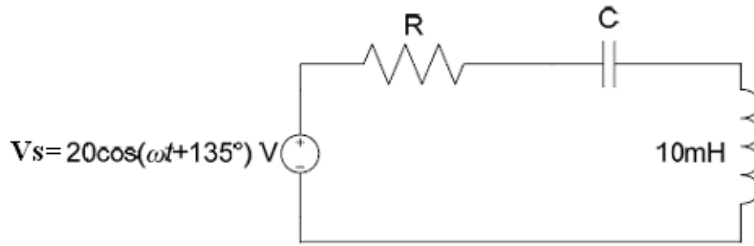**9.4** In the circuit below, if magnitude of the current at resonance is 10A,  
 $\omega_0 = 1000 \text{ rad/s}$ , find  $Q$  and the bandwidth of the circuit.



**Solution:**

Given  $\omega_0 = 1000 \text{ rad/s}$       $I_0 = 10 \text{ A}$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow C = \frac{1}{L\omega_0^2} = \frac{1}{10 \text{ mH} * (1000)^2} = 100 \mu\text{F}$$


$$\text{Resonance: } |I_0| = 10 \text{ A} \Rightarrow R = \frac{|V_s|}{|I_0|} = 20 / 10 = 2 \Omega$$

$$|V_L| = I_d \omega L = 10 * 1000 * 10 \text{ mH} = 100 \text{ V}$$


$$Q = \frac{|V_L|}{|V_s|} = 100 / 20 = 5$$

$$BW = \frac{\omega_0}{Q} = 1000 / 5 = 200 \text{ rad/s}$$

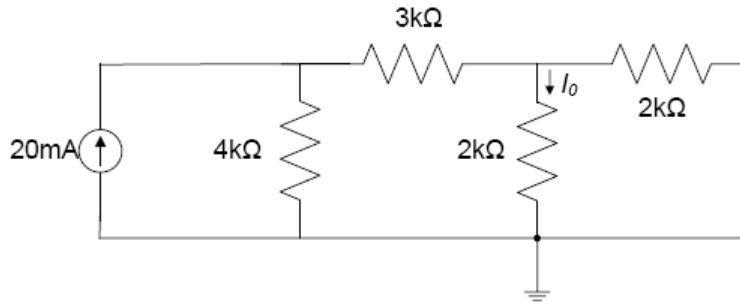**9.5** Find  $I_0$  in the circuit below using nodal analysis.



Solution:

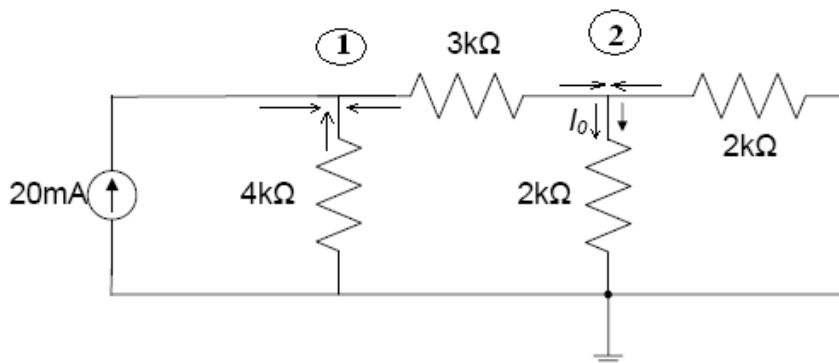

At the node#1:

$$20m + \left( \frac{0 - V_1}{4k\Omega} \right) + \left( \frac{V_2 - V_1}{3k\Omega} \right) = 0$$

$$240 + (-3V_1) + 4V_2 + (-4V_1) = 0$$

$$4V_2 = 7V_1 - 240$$

$$V_2 = 7V_1 / 4 - 60 \quad ; [1]$$

At the node#2:

$$\left( \frac{V_1 - V_2}{3k\Omega} \right) - \left( \frac{V_2 - 0}{2k\Omega} \right) + \left( \frac{0 - V_2}{2k\Omega} \right) = 0$$

$$2V_1 - 2V_2 - 3V_2 - 3V_2 = 0$$

$$2V_1 = 8V_2$$

$$V_1 = 4V_2 \quad ; [2]$$


Let's substitute eq.[2] into eq.[1]:

$$V_2 = \frac{7}{4}(4V_2) - 60$$


$$V_2 = 10V$$

$$I_0 = 10V / 2k\Omega = 5mA$$

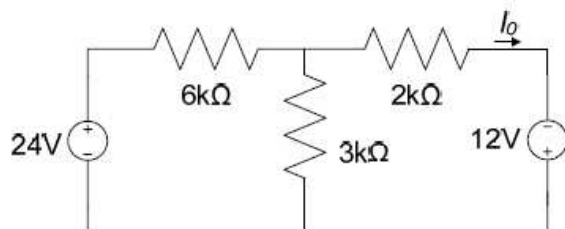**9.6** Find  $I_0$  in the circuit below using nodal analysis



**Solution:**

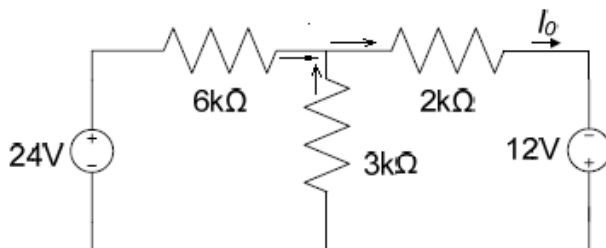


$$\left(\frac{24V - V_1}{6k\Omega}\right) + \left(\frac{0 - V_1}{3k\Omega}\right) - \left(\frac{V_1 - (-12V)}{2k\Omega}\right) = 0$$

$$24V - V_1 - 2V_1 - 3V_1 - 36 = 0$$


$$V_1 = -2V$$

$$I_0 = \frac{V_1 - (-12V)}{2k\Omega} = \frac{-2V + 12V}{2k\Omega} = 5mA$$

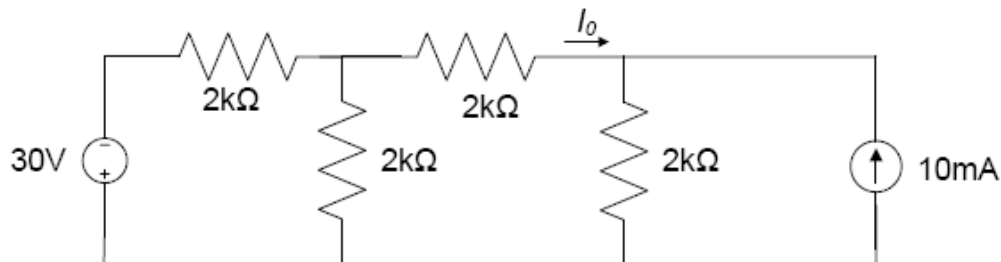**9.7** Find  $I_0$  in the circuit below using nodal analysis



**Solution:**

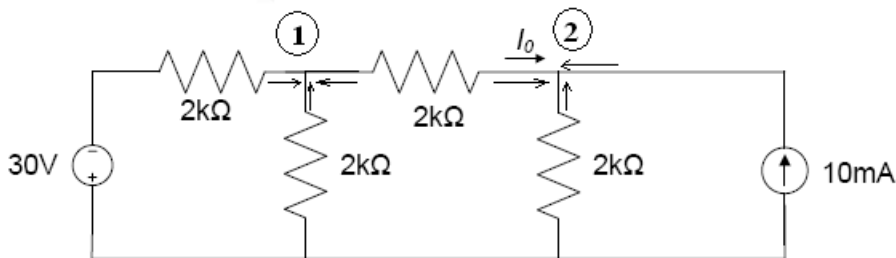

At the node#1:

$$\left(\frac{-30V - V_1}{2k\Omega}\right) + \left(\frac{0 - V_1}{2k\Omega}\right) + \left(\frac{V_2 - V_1}{2k\Omega}\right) = 0$$

$$-30V - V_1 - V_1 + V_2 - V_1 = 0;$$

$$V_2 = 3V_1 + 30V ; [3]$$

At the node#2:

$$\left(\frac{V_1 - V_2}{2k\Omega}\right) + \left(\frac{0 - V_2}{2k\Omega}\right) + 10mA = 0;$$

$$V_1 - V_2 - V_2 + 20V = 0;$$

$$V_1 = 2V_2 - 20V ; [4]$$

Let's substitute [4] into [3]:

$$V_2 = 3(2V_2 - 20V) + 30V$$


$$V_2 = 6V$$

Let's substitute  $V_2$  into eq. [4]:


$$V_1 = 2(6V) - 20V = -8V$$

$$I_0 = \frac{V_1 - V_2}{2k\Omega} = -7mA$$

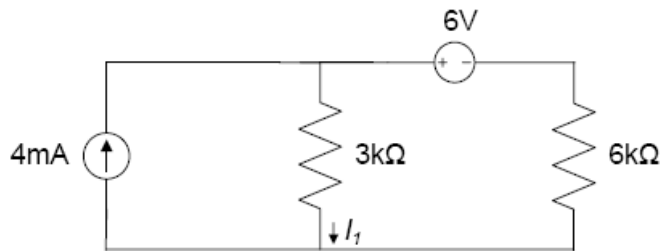**9.8** Find  $I_1$  in the circuit below using nodal analysis



**Solution:**

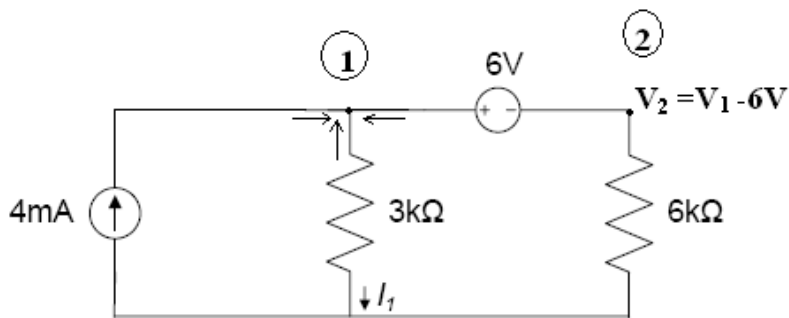

It can be noted that node#2 is just  $(V_1 - 6V)$

Node#1:


$$4mA + \left( \frac{0 - V_1}{3k\Omega} \right) - \left( \frac{0 - (V_1 - 6V)}{6k\Omega} \right) = 0;$$

$$24V - 2V_1 - V_1 + 6V = 0;$$

$$V_1 = 10V$$

$$I_1 = \frac{V_1 - 0}{3k\Omega} = 10V / 3k\Omega = 3.33mA$$

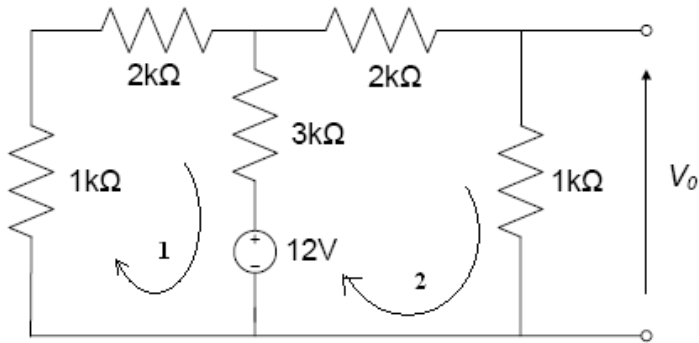**9.9** Use loop analysis to find  $V_0$  in the circuit below:



**Solution:**

Loop 1:

$$1k\Omega I_1 + 2k\Omega I_1 + 3k\Omega(I_1 - I_2) + 12V = 0;$$

$$6k\Omega I_1 - 3k\Omega I_2 + 12V = 0;$$

$$I_1 - 0.5I_2 + 2mA = 0; \quad [5]$$

Loop 2:

$$-12V + 3k\Omega(I_2 - I_1) + 2k\Omega I_2 + 1k\Omega I_2 = 0;$$

$$6k\Omega I_2 - 3k\Omega I_1 - 12V = 0;$$

$$I_2 = 0.5I_1 + 2mA; \quad [6]$$

Let's substitute eq.[6] into eq.[5]:


$$I_1 - 0.5(0.5I_1 + 2mA) + 2mA = 0;$$

$$I_1 = -1.33mA$$

$$I_2 = 0.5(4/3)mA + 2mA = 1.333mA$$

$$V_0 = 1.333mA * 1k\Omega = 1.333V$$

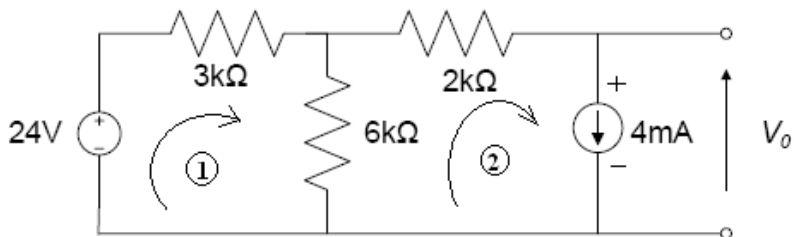**9.10** Use loop analysis to find  $V_0$  in the circuit below:



**Solution:**

Loop 1:

$$-24V + 3k\Omega I_1 + 6k\Omega(I_1 - I_2) = 0;$$

$$9k\Omega I_1 - 6k\Omega I_2 - 24V = 0;$$

$$I_1 = \frac{2}{3}I_2 + \frac{8}{3}mA$$

But  $I_2$  is known to be 4mA:

$$I_1 = \frac{2}{3}4mA + \frac{8}{3}mA = \frac{16}{3}mA$$

Loop 2:


$$6k\Omega(I_2 - I_1) + 2k\Omega I_2 + V_0 = 0$$

$$6k\Omega(4mA - \frac{16}{3}mA) + 2k\Omega 4mA + V_0 = 0$$

$$6k\Omega(-1.333mA) + 2k\Omega 4mA + V_0 = 0$$

$$V_0 = 0V$$

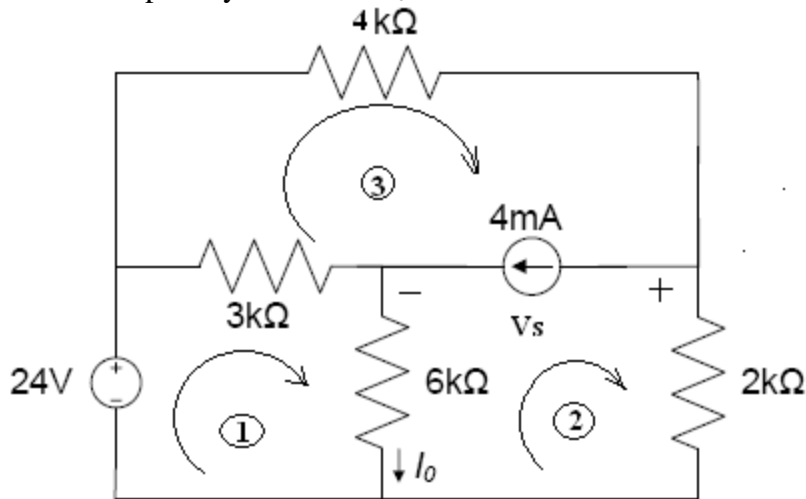**9.11** Use loop analysis to find  $V_0$  in the circuit below:



**Solution:**

$$\text{Loop 1: } -24V + 3k\Omega(I_1 - I_3) + 6k\Omega(I_1 - I_2) = 0; [1]$$

$$\text{Loop 2: } 6k\Omega(I_2 - I_1) - V_s + 2k\Omega I_2 = 0; [2]$$

$$\text{Loop 3: } 3k\Omega(I_3 - I_1) + 4k\Omega I_3 + V_s; [3]$$

$$I_3 - I_2 = 4mA \rightarrow I_3 = I_2 + 4mA \quad [4]$$

Let's insert eq. [4] into eq. [3]:

$$3k\Omega((I_2 + 4mA) - I_1) + 4k\Omega(I_2 + 4mA) + V_s = 0$$

$$3k\Omega I_2 + 12V - 3k\Omega I_1 + 4k\Omega I_2 + 16V + V_s = 0$$

$$7k\Omega I_2 - 3k\Omega I_1 + 28V + V_s = 0; [5]$$

Let's substitute [4] into [1]:



$$\begin{aligned}
-24V + 3k\Omega(I_1 - (I_2 + 4mA)) + 6k\Omega(I_1 - I_2) &= 0 \\
-24V + 3k\Omega I_1 - 3k\Omega I_2 - 12V + 6k\Omega I_1 - 6k\Omega I_2 &= 0 \\
9k\Omega I_1 - 9k\Omega I_2 - 36V &= 0; \quad [6]
\end{aligned}$$

When eq. [2]:

$$\begin{aligned}
6k\Omega(I_2 - I_1) - V_s + 2k\Omega I_2 &= 0; \\
8k\Omega I_2 - 6k\Omega I_1 - V_s &= 0
\end{aligned}$$

Eq. [5] and [2] together:

$$15k\Omega I_2 - 9k\Omega I_1 + 28V = 0; \quad [7]$$

Eq. [6] and [7] together:

$$6k\Omega I_2 - 8V = 0$$

$$I_2 = 8/6mA = 1.333mA; \quad [8]$$

Let's substitute eq. [8] into eq. [6]:

$$9k\Omega I_1 - 9k\Omega(1.333mA) - 36V = 0;$$

$$9k\Omega I_1 = 12V + 36V$$

$$I_1 = 5.333mA$$

$$I_0 = I_1 - I_2 = 5.333mA - 1.333mA = 4mA$$