

* Assume entering +ve end of component is +ve in equation

Find V_{eq} KVLs

$$0 = V_1 - V_b + V_c + V_2 - V_a$$

Move voltage sources to other side of equation

$$V_a + V_b - V_c = V_1 + V_2$$

$$\text{OR } V_{eq} = V_1 + V_2$$

* V_{eq} is the summation of the 3 voltage sources:


$$V_{eq} = V_a + V_b - V_c$$

Find R_{eq}

* R_1 and R_2 are in series


$$\therefore R_{eq} = R_1 + R_2$$

New Circuit:

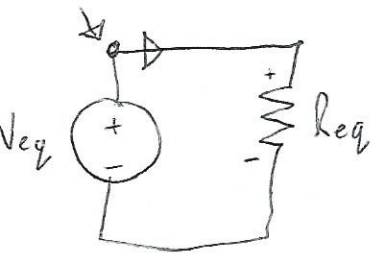

$$\text{New KVL: } 0 = V_{Req} - V_{eq}$$

06)

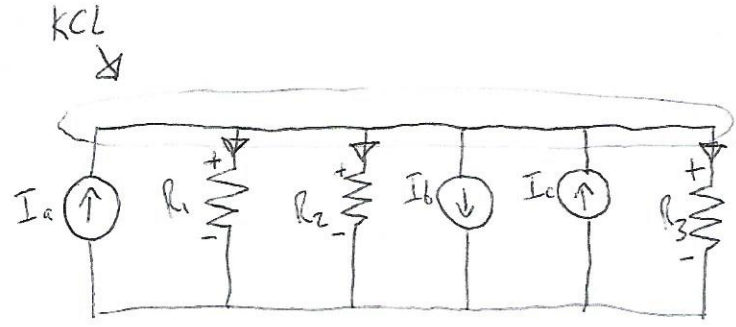

★ According to PSC assume currents are entering +ve end of each resistor

★ Assume current entering the node is +ve

Find I_{eq} KCL:


$$0 = I_a - I_1 - I_2 - I_b + I_c - I_3$$

Isolate current source terms:

$$0 = \underbrace{(I_a - I_b + I_c)}_{I_{eq}} - I_1 - I_2 - I_3$$

$$0 = I_{eq} - I_1 - I_2 - I_3$$

\Rightarrow

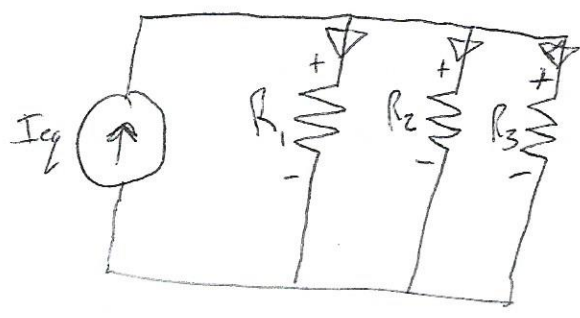


Find R_{eq}

$$R_{eq} = R_1 \parallel R_2 \parallel R_3 \text{ (all 3 in parallel)}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


$$R_{eq} = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}$$

New Circuits:

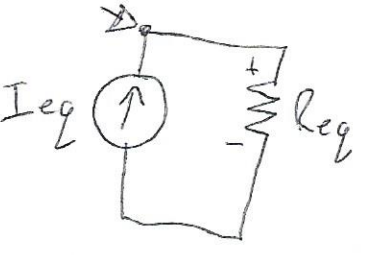

New KCL: $0 = I_{eq} - I_{R_{eq}}$

① c)

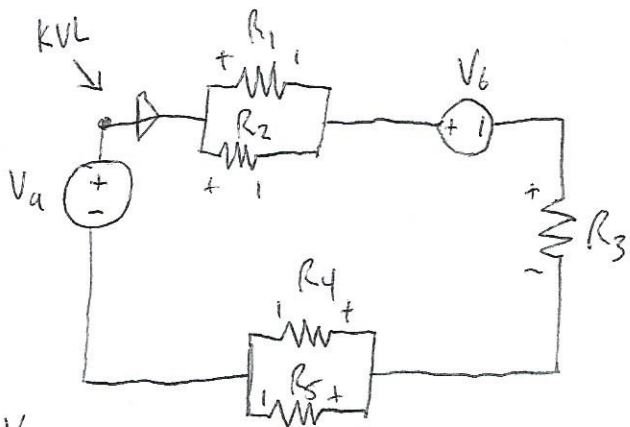

* Assume entering the +ve end of the component is +ve in the equation

Find V_{eq}

* We know $V_1 = V_2$ and $V_4 = V_5$ (the resistor pairs are in parallel)


KVL:

$$0 = V_1 + V_6 + V_3 + V_4 - V_a$$

$$\underbrace{V_a - V_6}_{V_{eq}} = V_1 + V_3 + V_4$$

$$V_{eq} = V_1 + V_3 + V_4$$

$$0 = V_1 + V_3 + V_4 - V_{eq}$$

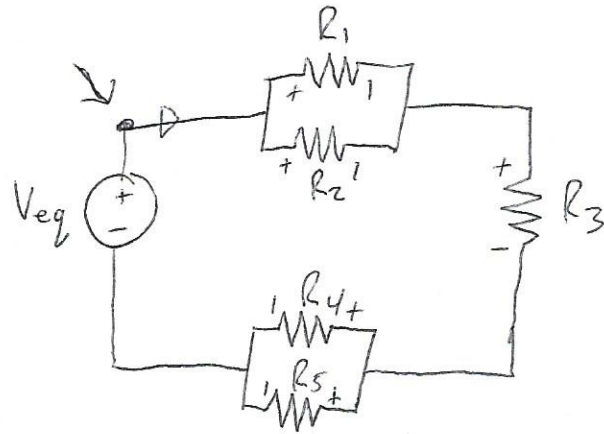


Find R_{eq}

$$R_{eq} = (R_1 || R_2) + R_3 + (R_4 || R_5)$$


$$R_{eq} = \left[\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \right] + R_3 + \left[\frac{1}{\frac{1}{R_4} + \frac{1}{R_5}} \right]$$

New Circuit:

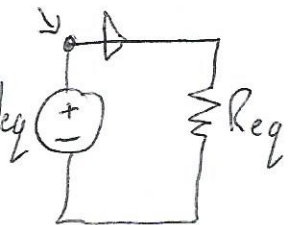

New KVL: $0 = V_{Req} - V_{eq}$

2) a)

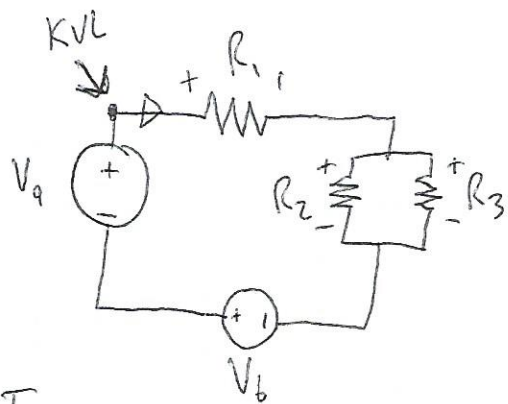

* Assume entering the +ve end of the component is +ve in the equation

* We know $V_1 = I \times R_1$ (1)
and $V_2 = V_3 = I \times (R_2 || R_3)$ (2)

Find I_x
KVL:

3) $0 = V_{R_1} + V_2 - V_b - V_q$

sub in equation (1) and (2) into (3)

$$0 = I_x R_1 + I_x (R_2 || R_3) - V_b - V_q$$

$$0 = I_x R_1 + I_x \left[\frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} \right] - V_b - V_q$$

sub in values

$$0 = I_x (5k\Omega) + I_x \left[\frac{1}{\frac{1}{12k\Omega} + \frac{1}{4k\Omega}} \right] - 3V - 1V$$

$$0 = I_x (5k\Omega) + I_x (3k\Omega) - 4V$$

$$I_x = \frac{4V}{8k\Omega} = 0.5mA$$

Find V_1, V_2, V_3

$$V_1 = (0.5mA)(5k\Omega) = 2.5V$$

From (3) (KVL)


$$0 = V_1 + V_2 - V_b - V_q$$

$$\begin{aligned} \rightarrow V_2 &= V_q + V_b - V_1 \\ &= 3V + 1V - 2.5V \\ &= 1.5V \end{aligned}$$

From (2)


$$V_2 = V_3 = 1.5V$$

(2) b)

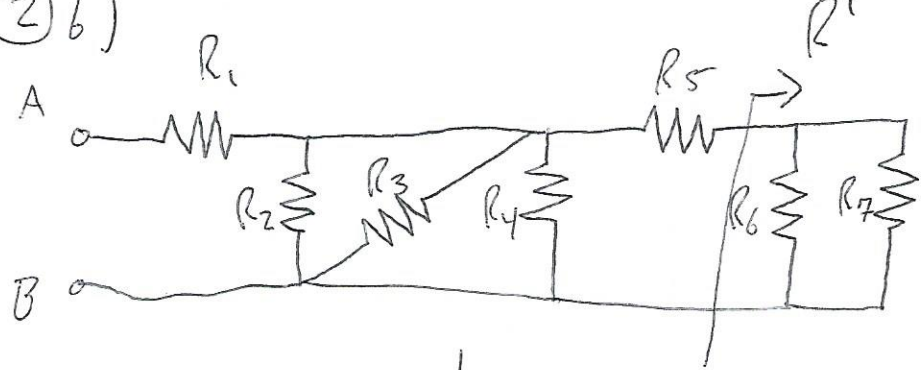


$$R' = R_6 \parallel R_7 = \frac{1}{\frac{1}{8\text{k}\Omega} + \frac{1}{8\text{k}\Omega}} = 4\text{k}\Omega$$

Redraw: (i)

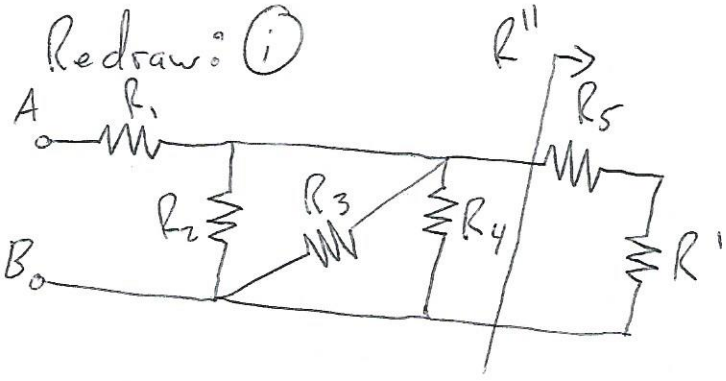


$$\begin{aligned} R'' &= R_5 + R' \\ &= 8\text{k}\Omega + 4\text{k}\Omega \\ &= 12\text{k}\Omega \end{aligned}$$

Redraw: (ii)

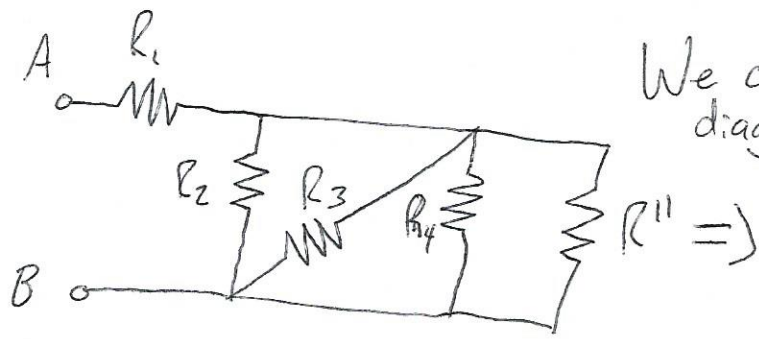

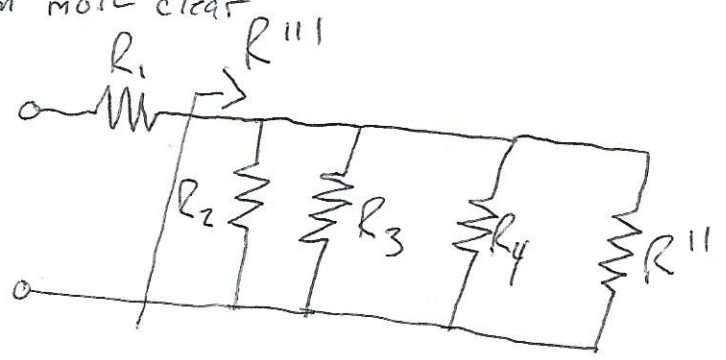
We can redraw again to make the diagram more clear



$$R''' = R_2 \parallel R_3 \parallel R_4 \parallel R''$$

$$R''' = \frac{1}{\left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R''} \right]} = 1\text{k}\Omega$$

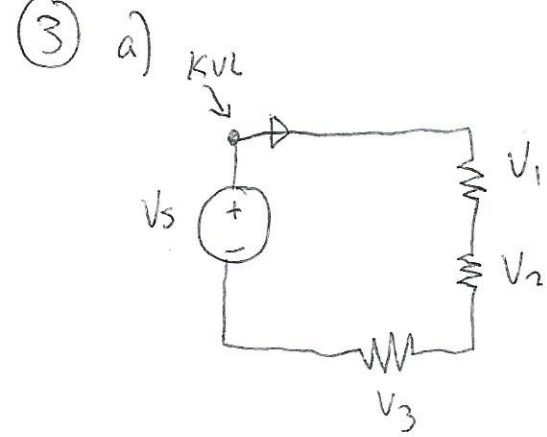Lastly: $R_{AB} = R_1 + R''' = 6\text{k}\Omega$



$$V_1 = V_s \left(\frac{R_1}{R_1 + R_2 + R_3} \right) = (25V) \left(\frac{2k\Omega}{2k\Omega + 3k\Omega + 6k\Omega} \right)$$

$$\approx 4.54V$$


$$V_2 = V_s \left(\frac{R_2}{R_1 + R_2 + R_3} \right) = (25V) \left(\frac{3k\Omega}{2k\Omega + 3k\Omega + 6k\Omega} \right)$$

$$\approx 6.82V$$

$$V_3 = V_s \left(\frac{6k\Omega}{2k\Omega + 3k\Omega + 6k\Omega} \right) (25V) \approx 13.64V$$

Check with KVL:
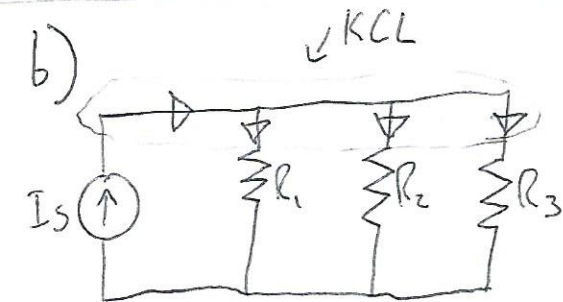
$$0 = V_1 + V_2 + V_3 - V_s \Rightarrow 0 = 4.54V + 6.82V + 13.64V - 25V = 0 \quad \therefore \text{LHS} = \text{RHS}$$



Find R_p

$$R_p = R_1 \parallel R_2 \parallel R_3$$

$$= \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)} = 1.69k\Omega$$

$$\star I_k = I_s \frac{R_p}{R_k}$$

$$I_1 = I_s \left(\frac{1.69k\Omega}{5k\Omega} \right) = 1.69mA$$

$$I_2 = I_s \left(\frac{1.69k\Omega}{4k\Omega} \right) \approx 2.11mA$$

$$I_3 = I_s \left(\frac{1.69k\Omega}{7k\Omega} \right) \approx 1.21mA$$

Check with KCL:

$$0 = I_s - I_1 - I_2 - I_3$$

$$0 = 5mA - 1.21mA - 2.11mA - 1.69mA = -0.01mA$$

→ \star small error of 0.01mA due to rounding

$$\frac{0.01mA}{5mA} (100\%) = 0.2\% \text{ error}$$

(very small)