





ITI1100 Section Z

Digital Systems I





Chapter 5: Synchronous Sequential Logic (2)

Prof. Mohammad Alja'afreh

Flip-Flop Full Description

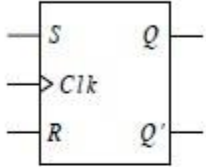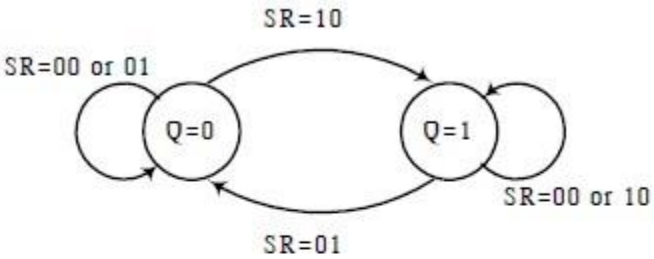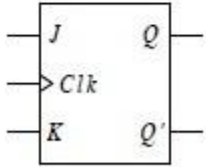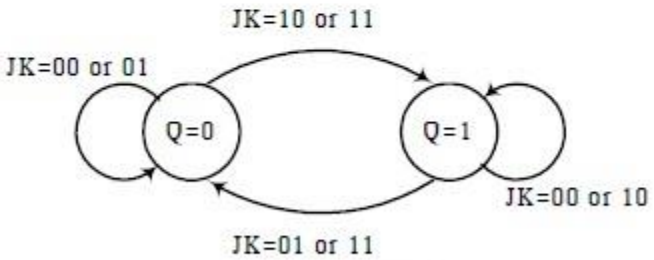Name / Symbol	Characteristic (Truth) Table	State Diagram / Characteristic Equations	Excitation Table																																																								
<p>SR</p> 	<table border="1"> <thead> <tr> <th>S</th> <th>R</th> <th>Q</th> <th>Q_{next}</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>×</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>×</td></tr> </tbody> </table>	S	R	Q	Q _{next}	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	×	1	1	1	×	 <p style="text-align: center;">$Q_{next} = S + R'Q$</p>	<table border="1"> <thead> <tr> <th>Q</th> <th>Q_{next}</th> <th>S</th> <th>R</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>×</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>×</td><td>0</td></tr> </tbody> </table>	Q	Q _{next}	S	R	0	0	0	×	0	1	1	0	1	0	0	1	1	1	×	0
S	R	Q	Q _{next}																																																								
0	0	0	0																																																								
0	0	1	1																																																								
0	1	0	0																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	0	1	1																																																								
1	1	0	×																																																								
1	1	1	×																																																								
Q	Q _{next}	S	R																																																								
0	0	0	×																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	1	×	0																																																								
<p>JK</p> 	<table border="1"> <thead> <tr> <th>J</th> <th>K</th> <th>Q</th> <th>Q_{next}</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	J	K	Q	Q _{next}	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	0	 <p style="text-align: center;"> $Q_{next} = J'K'Q + JK' + JKQ'$ $= J'K'Q + JK'Q + JK'Q' + JKQ'$ $= K'Q(J' + J) + JQ'(K' + K)$ $= K'Q + JQ'$ </p>	<table border="1"> <thead> <tr> <th>Q</th> <th>Q_{next}</th> <th>J</th> <th>K</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>×</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>×</td></tr> <tr><td>1</td><td>0</td><td>×</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>×</td><td>0</td></tr> </tbody> </table>	Q	Q _{next}	J	K	0	0	0	×	0	1	1	×	1	0	×	1	1	1	×	0
J	K	Q	Q _{next}																																																								
0	0	0	0																																																								
0	0	1	1																																																								
0	1	0	0																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	0	1	1																																																								
1	1	0	1																																																								
1	1	1	0																																																								
Q	Q _{next}	J	K																																																								
0	0	0	×																																																								
0	1	1	×																																																								
1	0	×	1																																																								
1	1	×	0																																																								

Flip-Flop Full Description (cont'd)

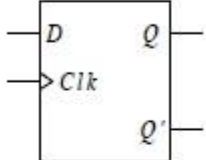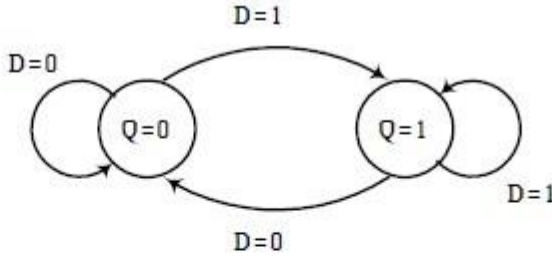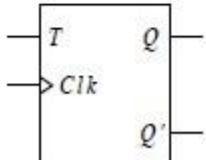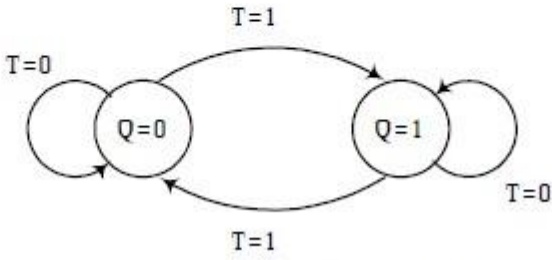
Name / Symbol	Characteristic (Truth) Table	State Diagram / Characteristic Equations	Excitation Table																														
<p>D</p> 	<table border="1"> <thead> <tr> <th>D</th> <th>Q</th> <th>Q_{next}</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>x</td> <td>0</td> </tr> <tr> <td>1</td> <td>x</td> <td>1</td> </tr> </tbody> </table>	D	Q	Q_{next}	0	x	0	1	x	1	 <p style="text-align: center;">$Q_{next} = D$</p>	<table border="1"> <thead> <tr> <th>Q</th> <th>Q_{next}</th> <th>D</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	Q	Q_{next}	D	0	0	0	0	1	1	1	0	0	1	1	1						
D	Q	Q_{next}																															
0	x	0																															
1	x	1																															
Q	Q_{next}	D																															
0	0	0																															
0	1	1																															
1	0	0																															
1	1	1																															
<p>T</p> 	<table border="1"> <thead> <tr> <th>T</th> <th>Q</th> <th>Q_{next}</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	T	Q	Q_{next}	0	0	0	0	1	1	1	0	1	1	1	0	 <p style="text-align: center;">$Q_{next} = TQ' + T'Q = T \oplus Q$</p>	<table border="1"> <thead> <tr> <th>Q</th> <th>Q_{next}</th> <th>T</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	Q	Q_{next}	T	0	0	0	0	1	1	1	0	1	1	1	0
T	Q	Q_{next}																															
0	0	0																															
0	1	1																															
1	0	1																															
1	1	0																															
Q	Q_{next}	T																															
0	0	0																															
0	1	1																															
1	0	1																															
1	1	0																															

Analysis of Synchronous Sequential Circuits

- **Analysis** describes what **a given circuit will do under certain conditions**
- **Behavior** of synchronous sequential circuit can be **determined** from
 - **Its inputs**
 - **Its outputs**
 - **Flip-Flop states**

Analysis of Synchronous Sequential Circuits (cont'd)

- Example of clocked sequential circuit:

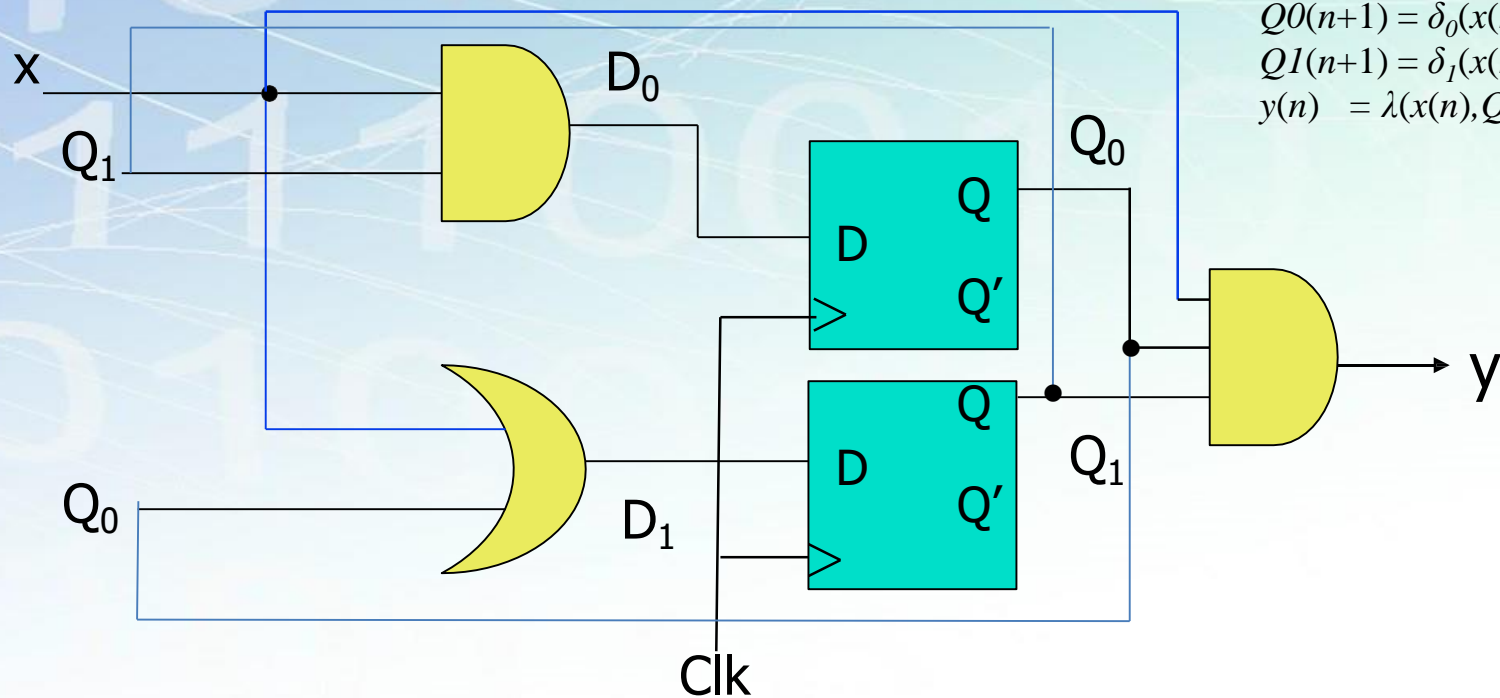

from circuit = find

$$Q0(n+1) = \delta_0(x(n), Q0(n), Q1(n))$$

$$Q1(n+1) = \delta_1(x(n), Q0(n), Q1(n))$$

$$y(n) = \lambda(x(n), Q0(n), Q1(n))$$

Output equation $\rightarrow y(t) = x(t)Q_1(t)Q_0(t)$

FF input equations

- $\rightarrow D_0(t) = x(t)Q_1(t)$
- $\rightarrow D_1(t) = x(t) + Q_0(t)$

State equations

- $\rightarrow Q_0(t+1) = D_0(t)$
- $\rightarrow Q_1(t+1) = D_1(t)$

State Table

- Sequence of **outputs**, **inputs**, and **flip-flop states** enumerated in state table
- **Present state** indicates current value of flip-flops
- **Next state** indicates state after next clock edge
- **Output** is output value on current clock edge


State Table

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0 0	00	10	0	0
0 1	10	10	0	0
1 0	00	11	0	0
1 1	10	11	0	1

$$y(t) = x(t)Q_1(t)Q_0(t)$$

$$Q_0(t+1) = D_0(t) = x(t)Q_1(t)$$

$$Q_1(t+1) = D_1(t) = x(t) + Q_0(t)$$

 

State Table (cont'd)


- All possible **input** combinations enumerated
- All possible **state** combinations enumerated
- Separate columns for **each output value**
- Sometimes easier to **designate a symbol for each state**

Let:	Present State	Next State		Output	
		x=0	x=1	x=0	x=1
$s_0 = 00$	s_0	s_0	s_2	0	0
$s_1 = 01$	s_1	s_2	s_2	0	0
$s_2 = 10$	s_2	s_0	s_3	0	0
$s_3 = 11$	s_3	s_2	s_3	0	1

State Diagram


- Circles indicate **current state**
- Arrows point to **next state**
- For x/y , x is **input** and y is **output**

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
00	00	10	0	0
01	10	10	0	0
10	00	11	0	0
11	10	11	0	1

 

State Diagram (cont'd)

 - Each state has two arrows leaving
 - One for $x = 0$ and one for $x = 1$
- Unlimited arrows can enter a state
- Use of state names is easier to identify



SEQUENTIAL CIRCUITS ANALYSIS

from circuit to state diagram = find

$$A(n+1) = \delta_A(x(n), A(n), B(n))$$

$$B(n+1) = \delta_B(x(n), A(n), B(n))$$


$$y(n) = \lambda(x(n), A(n), B(n))$$

$$\left. \begin{aligned} D_A &= \underline{x A + x B = A^+} \\ D_B &= \underline{x A' = B^+} \end{aligned} \right\} \text{Transition function } \delta$$

$$y = \underline{x' A + x' B} \text{ Output function } \lambda$$

State Table



Present State	B	In	Next State	Out
A	B	x	A ⁺	B ⁺
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	0
1	1	0	0	0
1	1	1	1	0

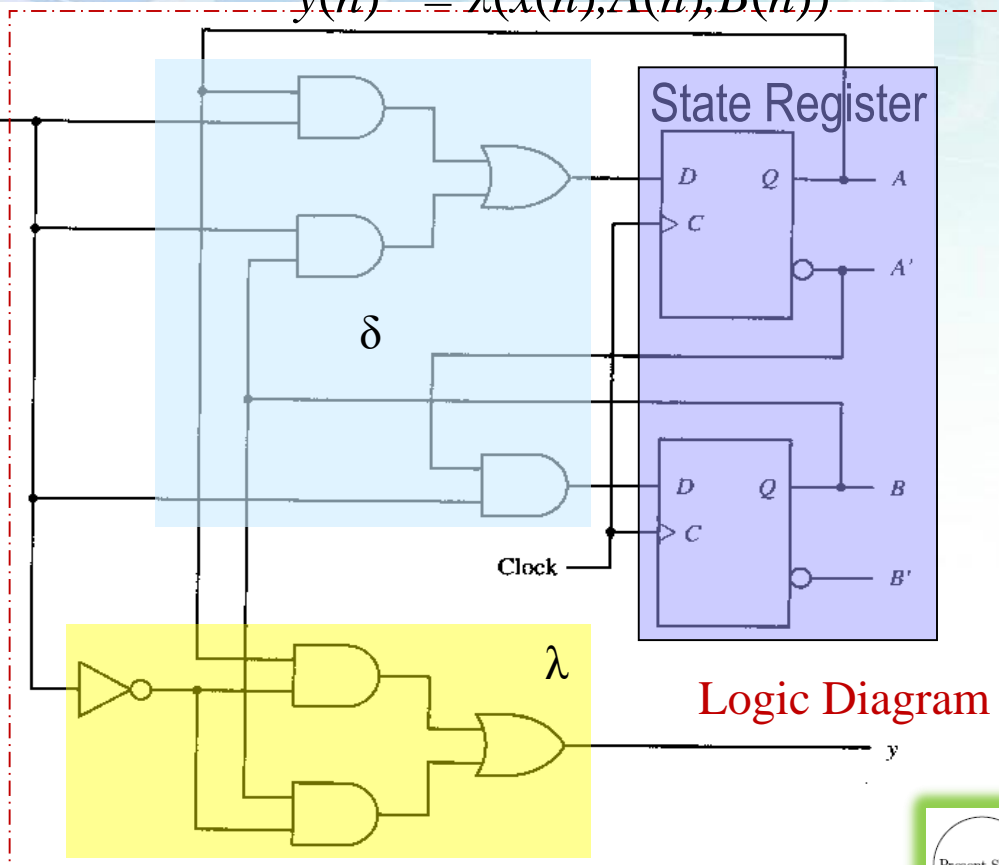

Logic Diagram

State Diagram

- nodes = states
- arcs = transitions

  


Mealy and More Models

- A general model of a Sequential Circuit has
 - **Inputs**
 - **Outputs**
 - **Internal States**
- There are two “**standard models**”
 - **Mealy Model**, known as Mealy Finite State Machine (FSM) (or Mealy machine)
 - **Moore Model** known as Moore FSM (or Moore Machine)


Mealy Machine

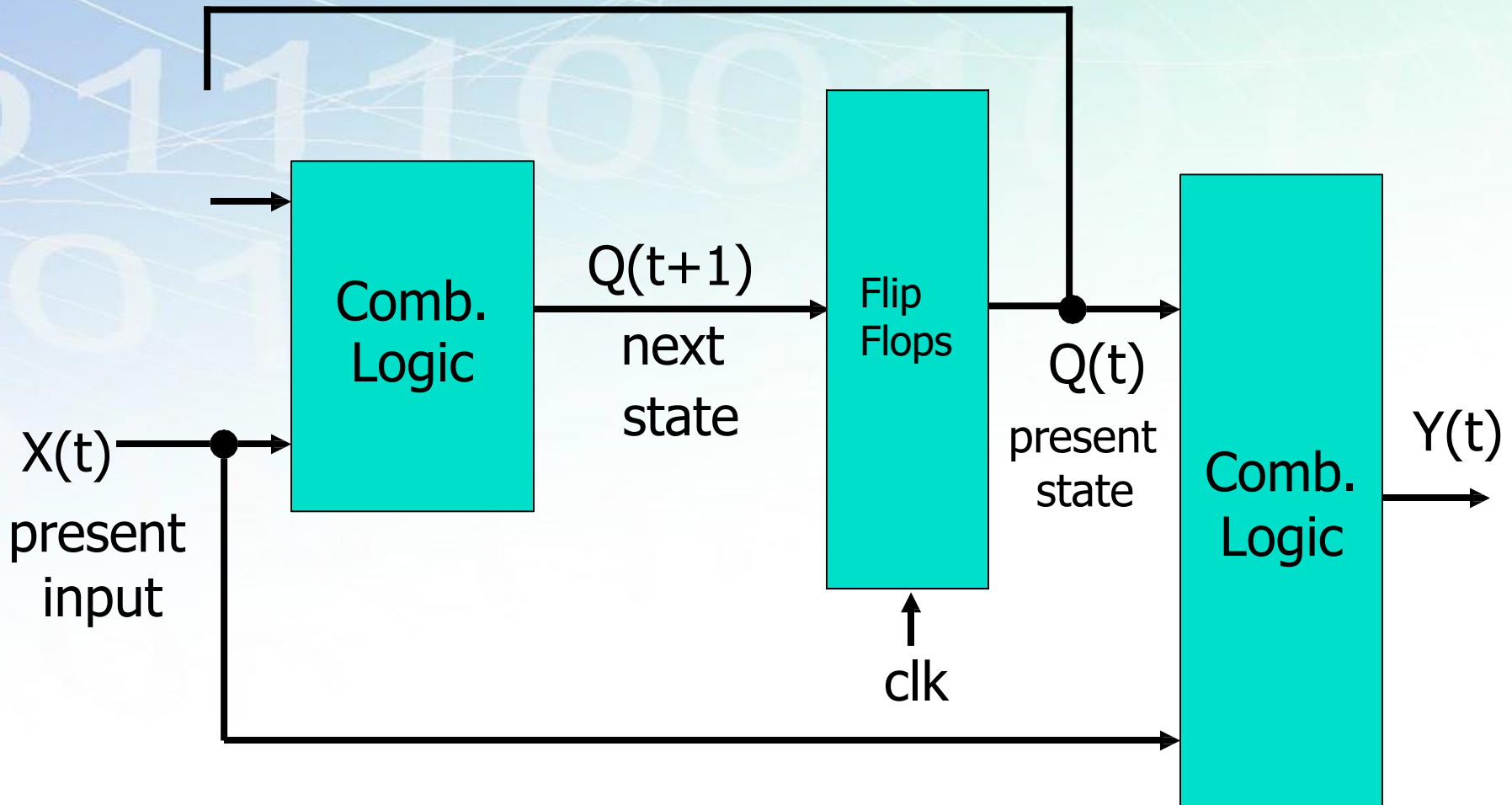- **Output** based on **state** and **present input**




Mealy Machine (cont'd)

- Example:

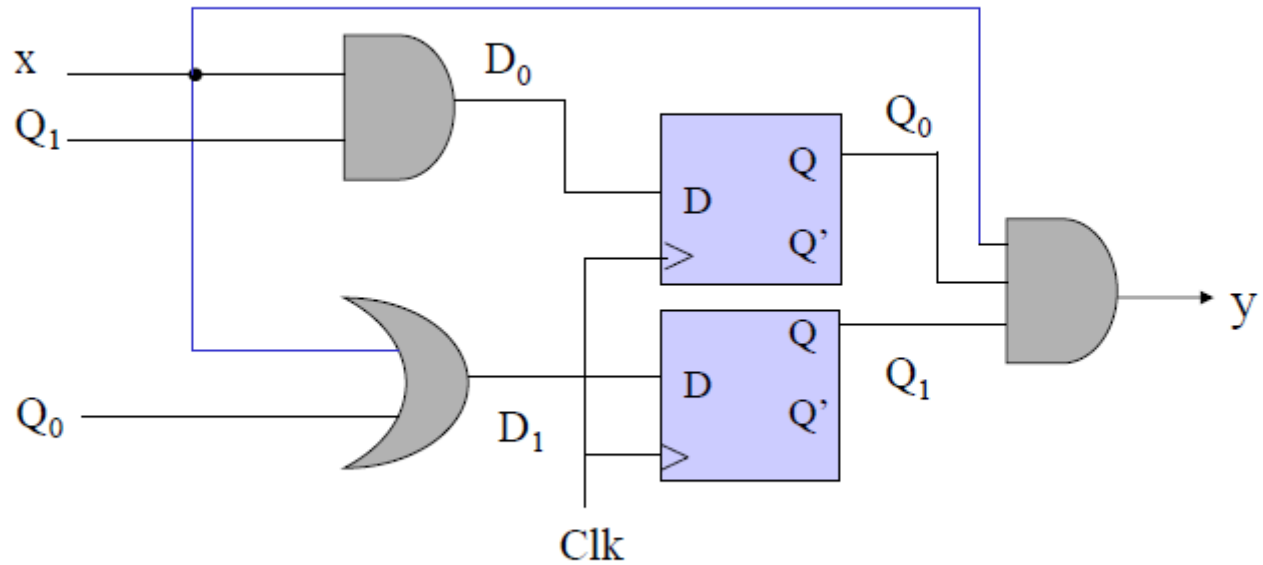


Moore Machine

- **Output** based on **state** only

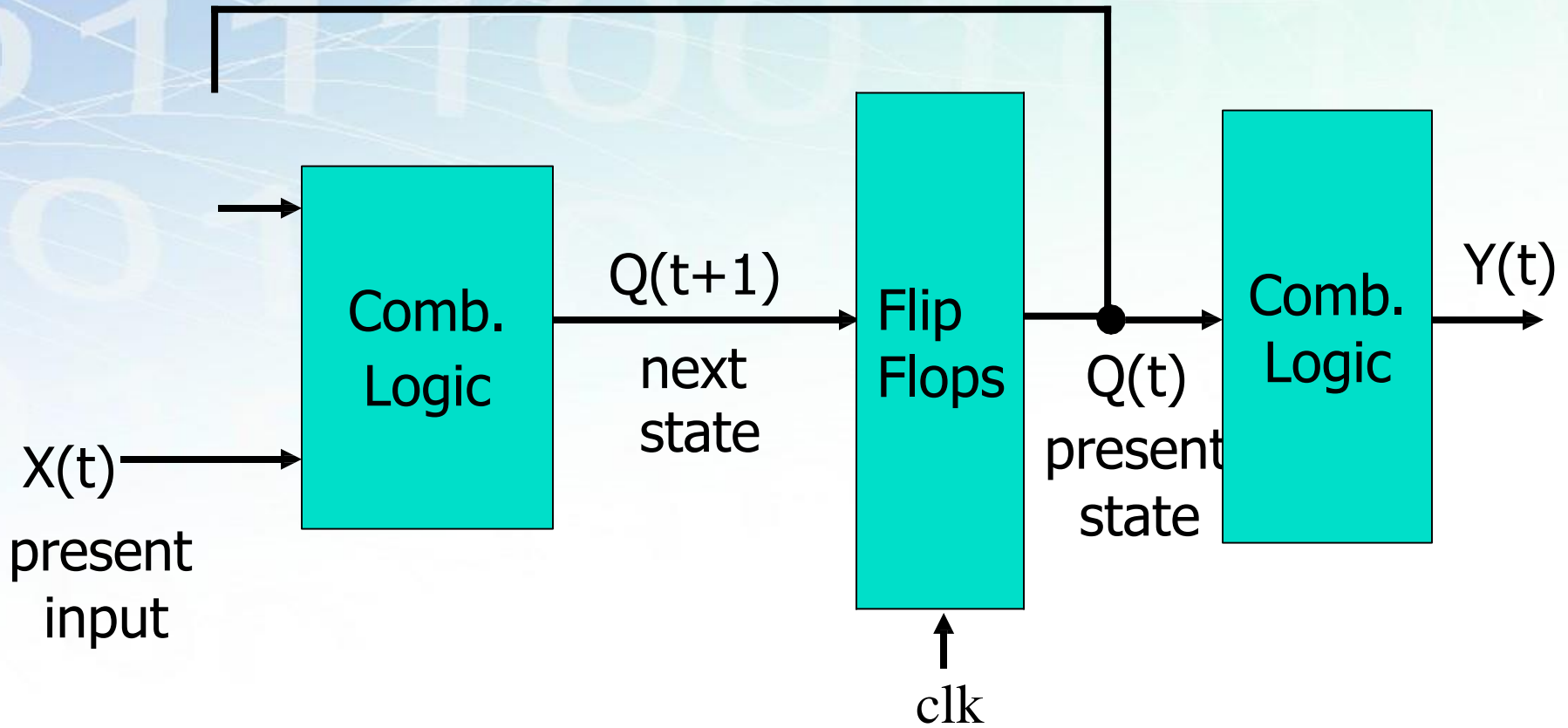


Moore Machine (cont'd)

- Example:

 

State Reduction

 - In general, **reducing the number of states reduces the number of gates and flip-flops**
- Consider a sequential circuit with the following **State diagram**:



State Reduction (cont'd)

- Obtaining the State table from State diagram of the previous slide

State *e* and *g* are equivalent \rightarrow have the same next states and same output when $x=0$, $x=1$

State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
\rightarrow <i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
\rightarrow <i>g</i>	<i>a</i>	<i>f</i>	0	1

Reducing the State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1

\swarrow Remove *g* and replace it by *e* in remaining next states

State Reduction (cont'd)

Reducing the State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
→ <i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
→ <i>f</i>	<i>e</i>	<i>f</i>	0	1

f and *d* are
equivalent

Reduced State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

Sequential Circuit **Design** = from **Finite State Machine FSM** => **Logic Circuit**

Sequential Circuit Design Procedure

Step 0: From the **problem specification**, create the **state diagram** which shows all of the states that the **FSM** can be in, and how to switch from one state to another

Step 1: State Table - transition (δ) and output (λ) functions

Make a **state table** based on the problem specification or state diagram. It may show the next states S^{n+1} and outputs Z^n as **functions** of present states S^n and inputs X^n (transition function: $S^{n+1} = \delta(S^n, X^n)$, output function $Z_n = \lambda(S_n, X_n)$).

State minimization = reduce the number of states in the table

Step 2: State Assignment (Encoding). Assign binary codes to the states in the state table, if they were not assigned already. If you have N states, your binary codes will have at least $\lceil \log_2 N \rceil$ digits, and your circuit will have at least $\lceil \log_2 N \rceil$ flip-flops →

Transition table (i.e., binary-coded state table) = a state table with encoded states.

Step 3: Excitation Table and Equations. Choose the type of flip-flops to be used. For each flip-flop and each row of your transition table, find the flip-flop input values that are needed to generate the next state from the present state. You may use flip-flop excitation tables.

Step 4: Find simplified equations for the flip-flops inputs & the circuit outputs Z .

Step 5: Build the circuit!

Design Procedure

From the word description and specifications of the desired operation, derive a state diagram for the circuit

Develop a state table

Reduce the number of states if necessary

Assign binary values to the states

Obtain the binary-coded state table


Choose the type of flip-flops to be used

Derive the simplified flip-flop input and output equations

Draw the logic diagram

 Example 1

- Design a circuit that **detects** a **sequence of 3 or more consecutive 1's** in a string of bits coming through an input line



State diagram

- State S_0** : zero 1s detected
- State S_1** : one 1 detected
- State S_2** : two 1s detected
- State S_3** : \geq three 1s detected
- Each state has 2 output arrows
- x**: input
- y**: output

Example 1 (cont'd)

Present State	Next State		y	
	x=0	x=1	x=0	x=1
S_0	S_0	S_1	0	0
S_1	S_0	S_2	0	0
S_2	S_0	S_3	0	0
S_3	S_0	S_3	1	1

State table

- Sequence of outputs, inputs, and flip-flop states enumerated in State table
- **Present state:** indicates current value of flip-flops
- **Next state:** indicates state after next clock edge
- **Output:** is output value on current clock edge

No equivalent states \Rightarrow no reduction in State diagram

Example 1 (cont'd)

Present State			Input	Next State		Output
A	B	A		B	y	
0	0	0	0	0	0	
0	0	1	0	1	0	
0	1	0	0	0	0	
0	1	1	1	0	0	
1	0	0	0	0	0	
1	0	1	1	1	0	
1	1	0	0	0	1	
1	1	1	1	1	1	

- Assign binary values to states, 2 bits needed to encode state:

- $S_0 = \underline{00}$
- $S_1 = 01$
- $S_2 = 10$
- $S_3 = 11$

Binary-coded State table

Example 1 (cont'd)

- Using **D flip-flops**: **2 D flip-flops** to represent the **4 states**

Present State			Input	Next State		FF Inputs		Output
A	B	A		B	D_A	D_B		
0	0	0	0	0	0	0	0	
0	0	1	0	1	0	1	0	
0	1	0	0	0	0	0	0	
0	1	1	1	0	1	0	0	
1	0	0	0	0	0	0	0	
1	0	1	1	1	1	1	0	
1	1	0	0	0	0	0	1	
1	1	1	1	1	1	1	1	

State table and D flip-flop inputs

D flip-flop Excitation Table

Q	Q_{next}	D
0	0	0
0	1	1
1	0	0
1	1	1


$$A(t+1) = D_A(A, B, x) = \sum m(3, 5, 7)$$

$$B(t+1) = D_B(A, B, x) = \sum m(1, 5, 7)$$

State or Characteristic equations

 Example 1 (cont'd)

- Create K-map directly from State table (3 columns = 3 K-maps)
- Minimize K-maps to find SOP representations
- Separate circuit for each next state and output value




FF input equations Maps for Sequence Detector

Output equation

K-maps for sequence detector

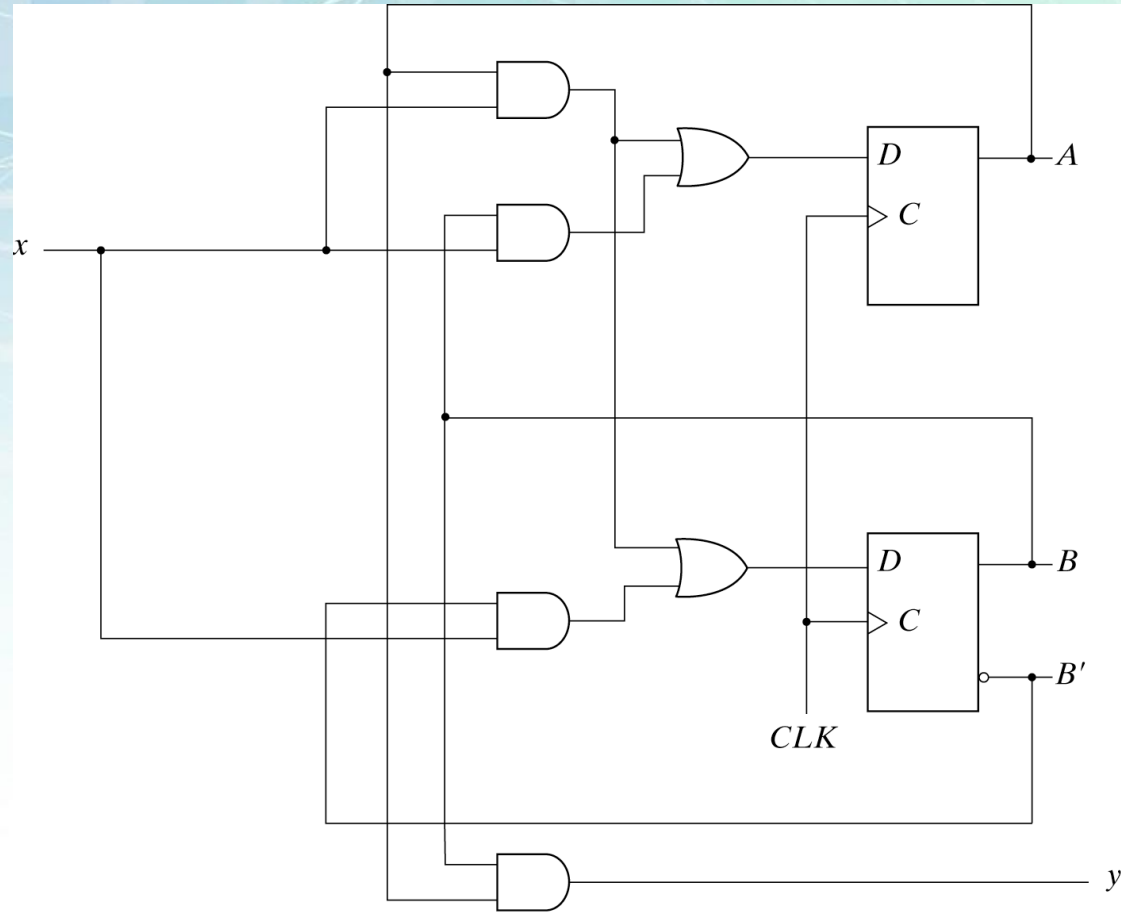Example 1 (cont'd)

- Output value (**y**) is **function of state**
 - This is a **Moore machine**



Logic Diagram of Sequence Detector