

ITI1100 Section Z

Digital Systems I


Chapter 5:

Synchronous Sequential Logic (1)


Prof. Mohammad Alja'afreh

Summer 2019

Logic Circuits

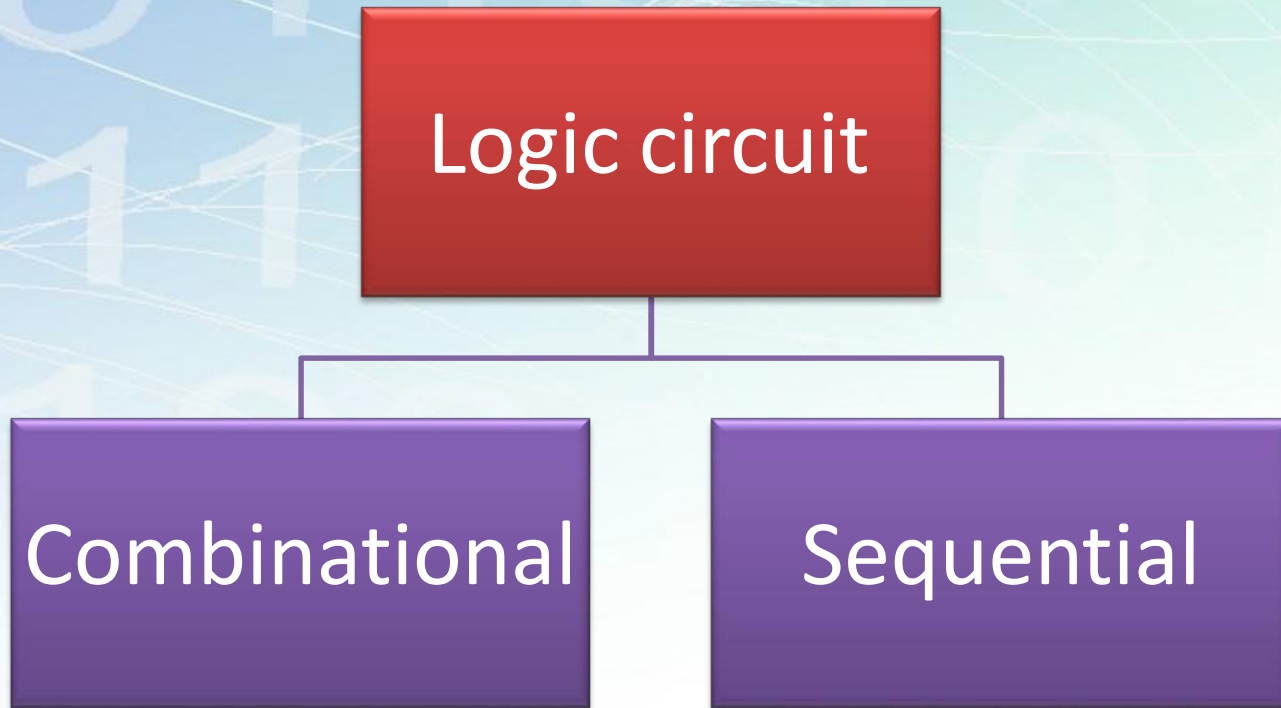

Sequential Circuits

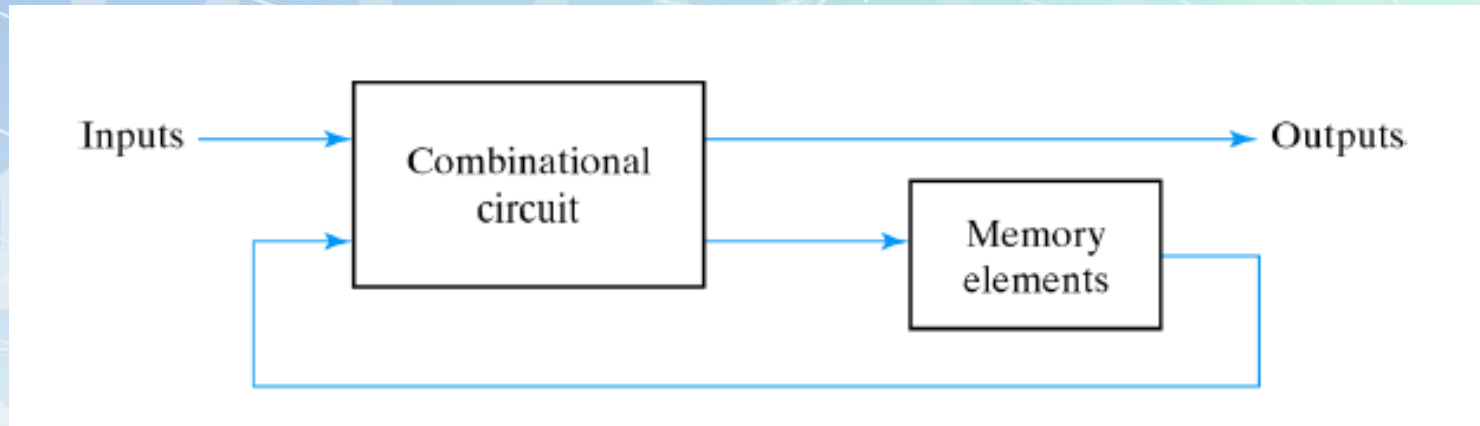

- **Outputs** are **functions** of **inputs** and **previous history of circuit** (memory)
- **Feedback** loops

Sequential Circuits (cont'd)



- In contrast to the combinational circuits, **two new parameters** are to be considered
 - **Memory Element:**
 - The function performed by the memory element is to **store previous results in a binary form**
 - **Time:**
 - We have to consider the **propagation delay** of the circuits

Sequential Circuits (cont'd)

- The **memory cell** that stores one "**bit**" of information is called **flip-flop**
- A **set of flip-flops** can be used to **store several bits** in a **REGISTER**
- Two different **modes**:
 - Asynchronous
 - Synchronous



Sequential Circuits (cont'd): Asynchronous

  - In this mode of operation, the **output reacts "immediately"** to the **changes** of the **input variables**
 - **Propagation delay**, t_p , of the **gates** are to be **considered**




Sequential Circuits (cont'd): Synchronous

  - In this mode of operation, **changes** of the **input variables** will be become **“effective”** when the **clock input is active**
 - Clock signals are periodic signals



Synchronous Clocked Sequential Circuits

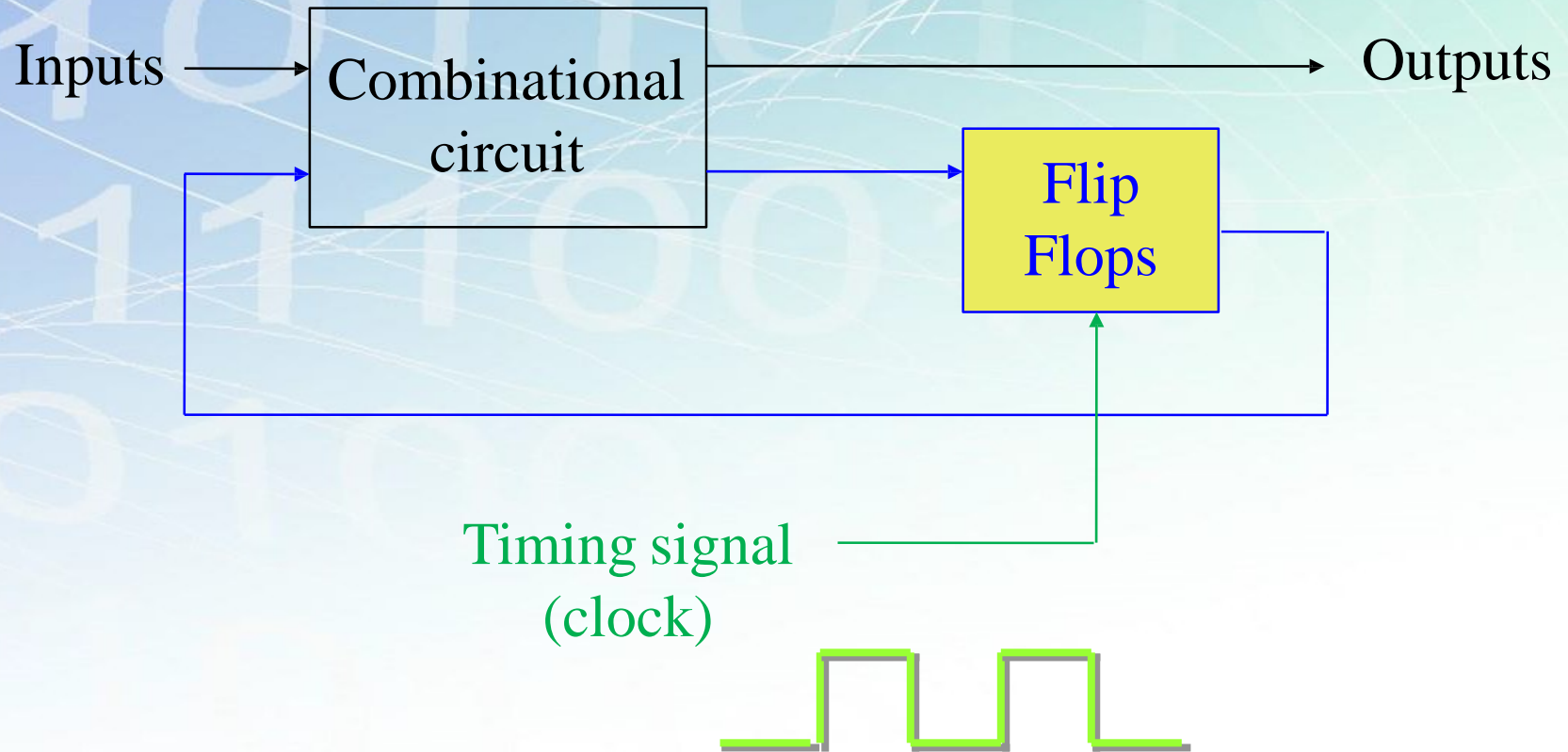

After changed inputs, new outputs appear in the next clock cycle

Clock Signal

- Clock is used in synchronous logic circuits to **trigger the circuit (flip-flop)** allowing it to **switch its states**
- Clock signal can **trigger a flip-flop** in **three ways**:
 - **During Positive level**
 - **During Positive transition (or positive edge)**
 - **During Negative transition (or negative edge)**


Clock Signal (cont'd)

- **Positive level:**
 - The **flip-flop** is **triggered** while the **clock pulse** is at **logic '1'**
 - The **logic '0'** is therefore **inactive state** where changes to the flip-flop's states are not allowed




Clock Signal (cont'd)

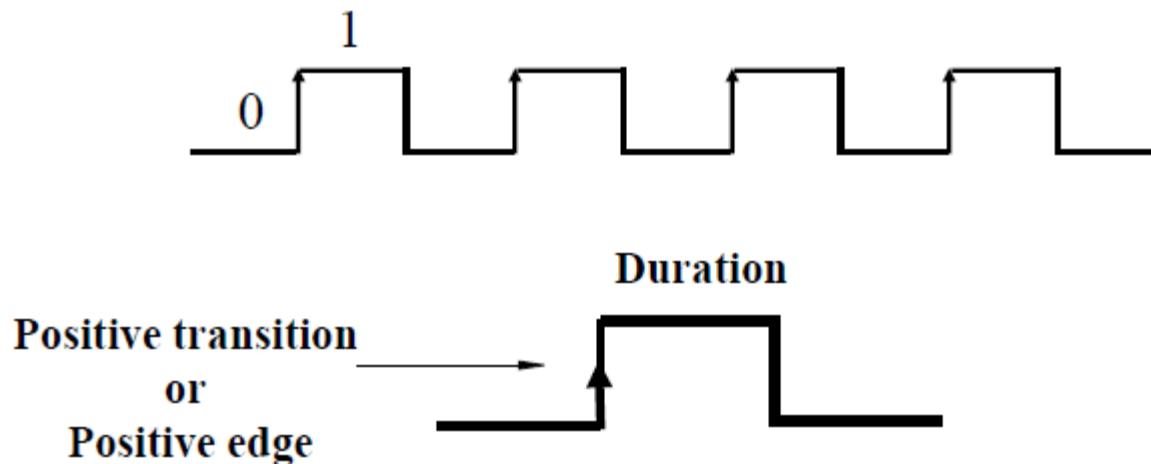- **During positive transition (or positive edge):**
 - The **flip-flop** is triggered only during the **signal transition from 0 to 1**; this transition is defined as **positive edge**



Clock Signal (cont'd)

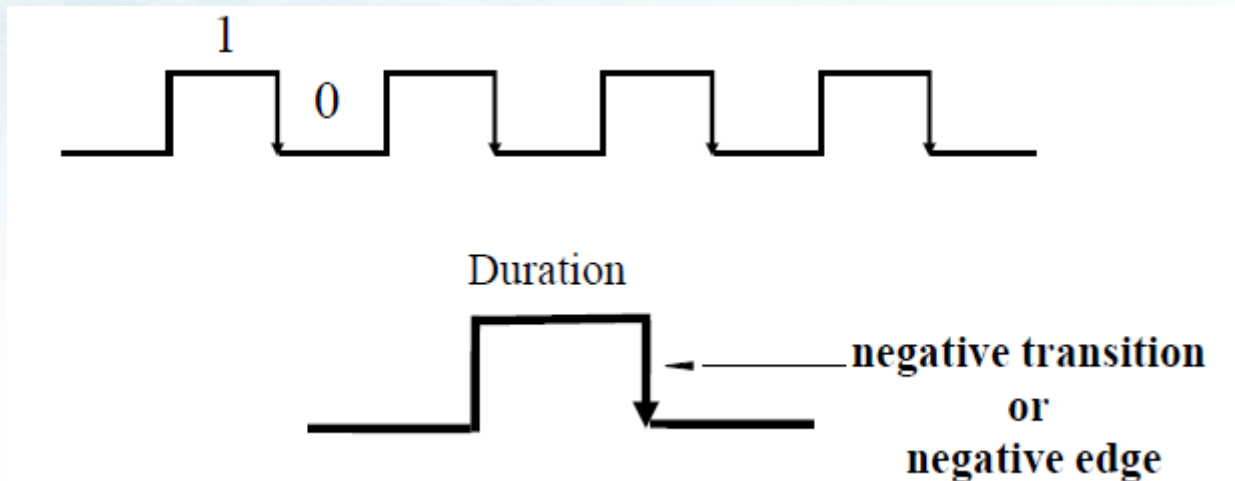- **During negative transition (or negative edge):**
 - The flip flop is triggered only during the signal transition from **1 to 0**; this transition is defined as **negative edge**




Memory Element: Latch


- A **flip-flop** can maintain a binary state indefinitely until directed by input signals to switch states
- The most **basic types of flip-flops** operate **without clock signal** are referred to as **Latches**
- **Latches** are **basic circuits** from which **all flip-flops** are constructed

Memory Element: Latch (cont'd)

- A stable value can be stored at inverter outputs

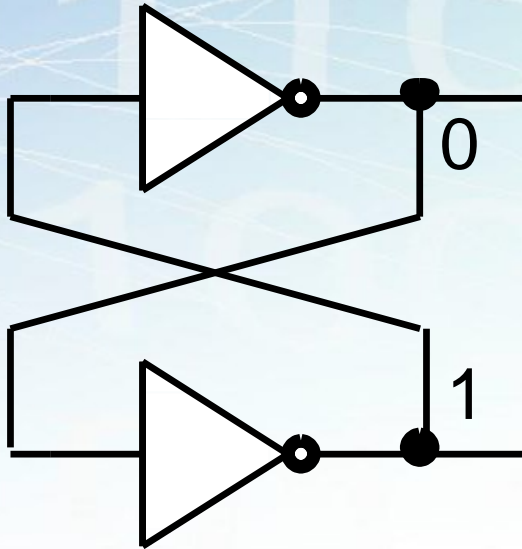

State 1

 

State 2


SEQUENTIAL CIRCUITS

The output of sequential circuits is logic function of the present state of external inputs, but also on the state of these inputs in past. Therefore, they are also referred to as circuits with memory.


The sequential circuits are formed by additional feedback signals, looped backward from the output to the input of the circuit (referred to as signals of internal state of the circuit). By this backward loop, the dependence on previous values of inputs is implemented as dependence on the current internal state of the machine.

The sequential switching circuits are classified in:

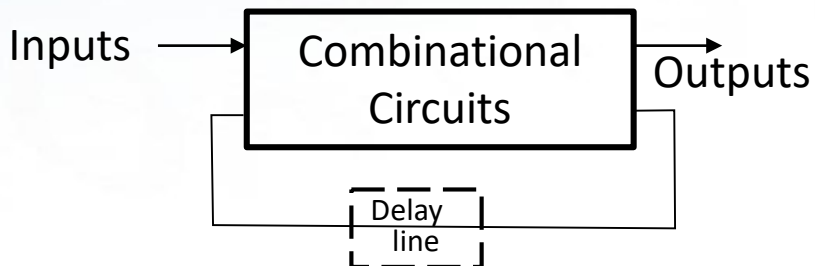- **Asynchronous** sequential circuits = any (asynchronously) change of an input may trigger an output change



 - **Synchronous** sequential circuits = outputs may change at time events defined by a periodical control signal (pulse) called **clock**.



Memory Element: SR Latch


- SR latch has **two input variables** that are defined as **S** and **R**
 - **S** for **SET**
 - **R** for **RESET**
- It also has **two outputs Q (normal state)** and **Q' (complement state)**



Symbol

Memory Element: SR Latch (cont'd)

- NOR implementation:

 

$$Q = (R+P)' = R'P'$$

$$P = (S+Q)' = S'Q'$$

Memory Element: SR Latch (cont'd)

		Present State		New State		
S	R	Q	Q	Q'	(or P)	
0	0	0	0	1		Unchanged
0	0	1	1	0		
0	1	0	0	1		Reset or Set to "0"
0	1	1	0	0		
1	0	0	0	0		Set to "1"
1	0	1	1	0		
1	1	0	0	0		Not allowed or forbidden
1	1	1	0	0		

 = Inconsistent

Memory Element: SR Latch (cont'd)

		Present State	New State		
S	R	Q	Q	Q' (or P)	
0	0	0	0	1	Unchanged
0	0	1	1	0	
0	1	0	0	1	Reset or Set to "0"
0	1	1	0	1	
1	0	0	1	0	Set to "1"
1	0	1	1	0	
1	1	0	X	X	Not allowed or forbidden
1	1	1	X	X	



At steady state

Memory Element: SR Latch (cont'd)

- Function table for SR latch with NOR gates:


S	R	Q	Q'	
1	0	1	0	Set to "1"
0	1	0	1	Set to "0"
0	0	1	0	unchanged (after SR = 10)
0	0	0	1	unchanged (after SR = 01)
1	1	?	?	Not allowed (0 0)

The Set-Reset Latch

 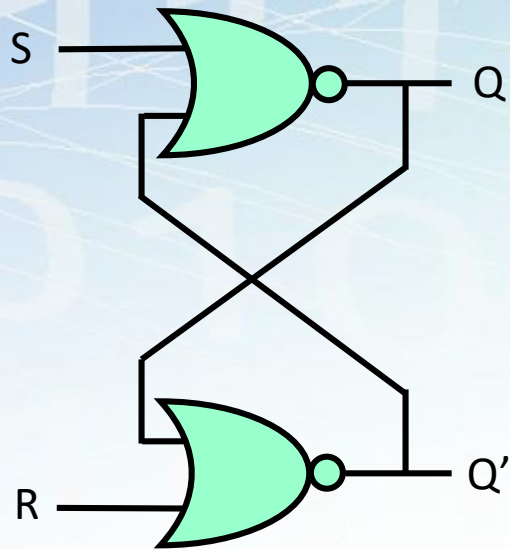


$S(t)$	$R(t)$	$Q(t)$	$Q(t+\epsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

The Set-Reset Latch

 


$S(t)$	$R(t)$	$Q(t)$	$Q(t+\varepsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

 

$$Q(t+\varepsilon) = S(t) + Q(t)R'(t)$$

Memory Element: SR Latch (cont'd)

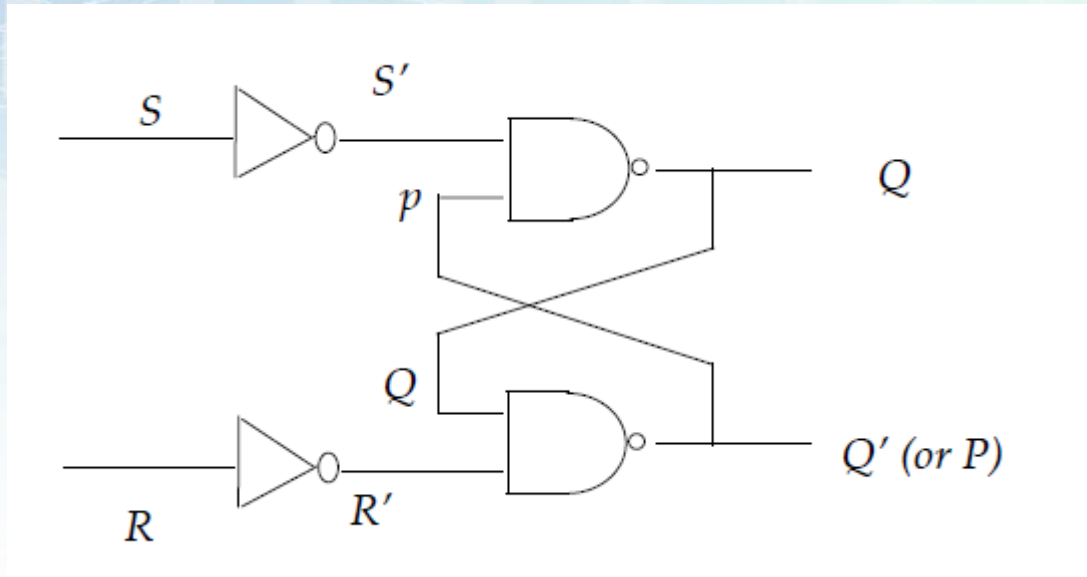- Inverter and NAND Implementation also called S'R' latch:



$$Q = (S'.P)' = S + P'$$

$$P = (R'.Q)' = R + Q'$$


Memory Element: SR Latch (cont'd)

- Function table for SR latch with Inverter and NAND gates:

S	R	Q	Q'	
1	0	1	0	Set to "1"
0	1	0	1	Set to "0"
0	0	1	0	unchanged (after SR = 10)
0	0	0	1	unchanged (after SR = 01)
1	1	?	?	Not allowed (0 0)

Memory Element: SR Latch (cont'd)

- **NAND Implementation:**

 

$$Q=(S.P)'=S'+P'$$

$$P=(Q.R)'=Q'+R'$$

Memory Element: SR Latch (cont'd)

Present State			New State		
S	R	Q	Q	Q' (or P)	
0	0	0	1	1	Not allowed or forbidden
0	0	1	1	1	
0	1	0	1	1	Set to "1"
0	1	1	1	0	Reset or Set to "0"
1	0	0	0	1	Unchanged
1	0	1	1	1	
1	1	0	0	1	
1	1	1	1	0	

= Inconsistent

Memory Element: SR Latch (cont'd)

		Present State	New State		
S	R	Q	Q	Q' (or P)	
0	0	0	X	X	Not allowed or forbidden
0	0	1	X	X	
0	1	0	1	0	Set to "1"
0	1	1	1	0	
1	0	0	0	1	Reset or Set to "0"
1	0	1	0	1	
1	1	0	0	1	Unchanged
1	1	1	1	0	

At steady state


Memory Element: SR Latch (cont'd)

- Function table for SR latch with NAND gates:

S	R	Q	Q'	
1	0	0	1	set to « 0 »
1	1	0	1	unchanged (after SR = 10)
0	1	1	0	set to « 1 »
1	1	1	0	unchanged (after SR = 01)
0	0	?	?	Not allowed! (1 1)

SR Latch with Control Input

 - Occasionally, desirable to avoid latch changes
- Change of state is regulated by a control signal, C**
- C = 0 disables all latch state changes**
- Control signal enables data change when C = 1**
- Right side of circuit same as ordinary SR latch**



(a) Logic diagram


C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; set state
1	1	1	Indeterminate

(b) Function table

SR latch with inverter and NAND implementation


SR Latch with Control Input (cont'd)

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

 

Latches with Control Input: D Latch

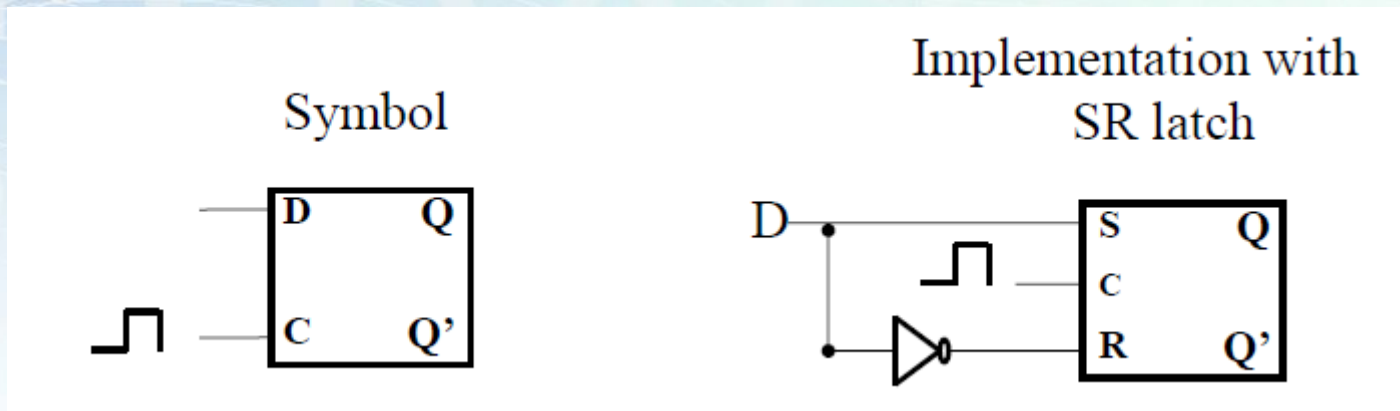- **D** for **Data**. Data is transferred to the Latch
- When **C** is **high**, **D** passes from **input** to **output (Q)**
- **D latch** ensures that inputs **S** and **R** are **never equal 1 at the same time**




Function table

D	C	Q	Q'
0	1	0	1
1	1	1	0
X	0	Q_n	Q_n'

Note: Q_n indicates the previous state (the previously stored value)

Latches with Control Input: D Latch (cont'd)

D	c	Q	Q'
0	1	0	1
1	1	1	0
X	0	Q_n	Q_n'

 

Synchronous Sequential Circuits


- If we **add to the memory element a synchronization signal** (i.e., clock impulse or control input), we would obtain **a synchronous SR latch** (i.e., a **flip-flop**)
- We will examine the following **synchronous flip-flops**:
 - SR
 - D
 - T
 - JK

Edge Sensitive Flip-Flop


- **Latches respond to trigger levels on control inputs**
 - Example: If $C = 1$, input is reflected at output
- **Flip-flops store data on a positive or negative edge of the control inputs**
 - Example: control input transitions from 0 to 1, data input available at output
- **Data remains stable in the flip-flop until next positive/ negative edge**
- **Different types of flip-flops are used for specific functions**

Edge Sensitive Flip-Flop (cont'd)

 - **Flip-flop is a latch with a clock input**
- **The sequential circuit output changes when its CLOCK input detects an edge. Edge-sensitive instead of level-sensitive**
- Symbol is a triangle on the CLK (clock) input of a flip-flop
- Flip flop can be triggered on positive or negative edge
- Bubble before Clock (CLK) input indicates negative edge trigger





Symbol with positive edge

 

Symbol with negative edge

Edge Sensitive SR Flip-Flop

  

S	R	Q_{n+1}	Function
0	0	Q_n	No change
0	1	0	RESET
1	0	1	SET
1	1	?	Forbidden


• Q_n = state *before* positive edge

• Q_{n+1} = state *after* positive edge

Characteristic Equation: $Q^{t+\Delta t} = S^t + Q^t \cdot \overline{R^t}$
 condition: $S^t \cdot R^t = 0$


D Flip-Flop

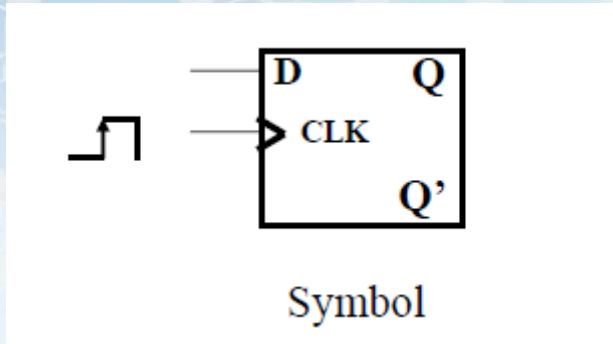- **Output changes only on the clock transition**
- **Input changes at other times have no effect on output**





D	CLK	Q	Q'
0	↑	0	1
1	↑	1	0
X	0	Q ₀	Q ₀ '

$$Q^{n+1} = D^n$$

 

D Flip-Flop (cont'd)

  


JK Flip-Flop

- Same as SR **except for** **K=J=1** the JK flip-flop will **output the opposite state** of Q_n
 - If $Q_n = 1$ then $Q_{n+1} = 0$
 - If $Q_n = 0$ then $Q_{n+1} = 1$

J	K	Q_{n+1}	Function
0	0	Q_n	No change
0	1	0	RESET
1	0	1	SET
1	1	Q'_n	complement (also Toggle)

 
• Q_n = state *before* positive edge
 • Q_{n+1} = state *after* positive edge



 (a) Circuit diagram


CHARACTERISTIC EQUATION:

$$Q^{n+1} = \overline{Q}^n \cdot J^n + Q^n \cdot \overline{K}^n$$




(b) Graphic symbol

JK Flip-Flop (cont'd)

 


J	K	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	Q_0 (toggles)

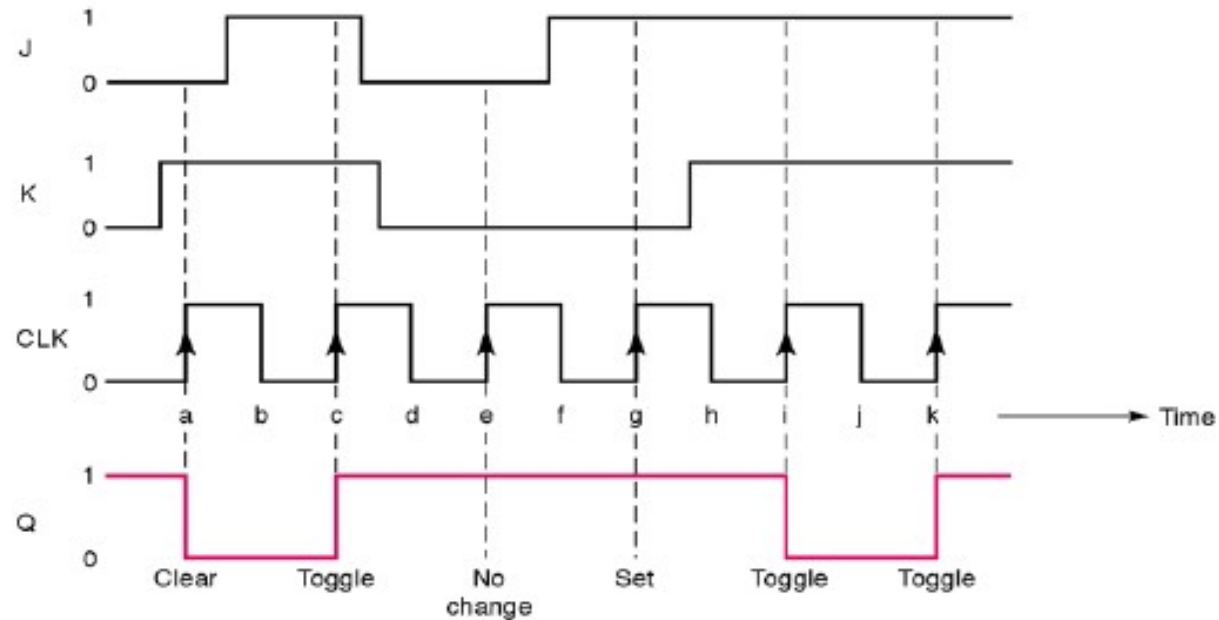


T Flip-Flop

 
- **T** stands for **toggle**
- Can be **created** from **JK** or **D** flip-flop



(a) From JK flip-flop

 

(b) From D flip-flop

 


(c) Graphic symbol

T	Q	Q_{next}	Q_{next}'
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

$$Q^{n+1} = \overline{Q}^n \cdot T + Q^n \cdot \overline{T}$$

Asynchronous Inputs

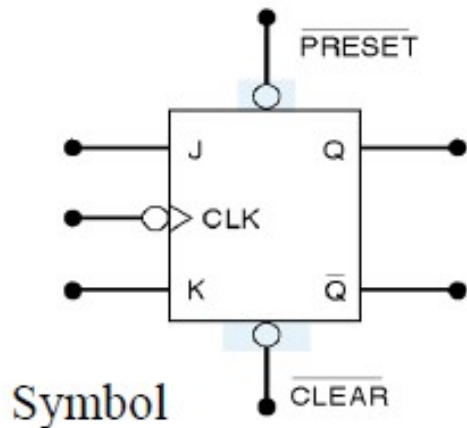- So far, we have only considered **synchronous inputs** (e.g. D, S, R, J, K, T)
 - Their **effects** on the **output** are **synchronized** with the **clock** or **control signal**
- Flip-flops have **asynchronous inputs**. They **operate independently of the synchronous inputs and clock**
 - Used to **set the Flip-Flop to 1 or 0 state at any time**



PRESET	CLEAR	FF response
1	1	Clocked operation*
0	1	Q = 1 (regardless of CLK)
1	0	Q = 0 (regardless of CLK)
0	0	Not used

*Q will respond to J, K, and CLK