

ITI1100 Section Z

Digital Systems I


Chapter 4: Combinational Logic (3)

Prof. Mohammad Alja'afreh
Winter 2017

Enable Decoder Inputs

- Many devices have an **additional enable input**, which is used to “activate” or “deactivate” the device
- For a **decoder**,
 - **EN=1** “activates” the decoder, so it behaves as specified earlier. **Exactly one of the outputs will be 1**
 - **EN=0** “deactivates” the decoder. By convention, that means **all of the decoder’s outputs are 0**
- We can include this **additional input in the decoder’s truth table**

| EN | S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

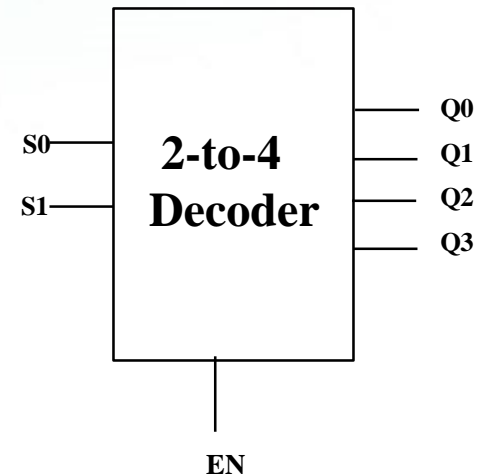

Enable Decoder Inputs (cont'd)

- In this table, whenever **EN=0**, the outputs are always 0, regardless of inputs S1 and S0


| EN | S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

- We can abbreviate the table by writing **x's** in the input columns for S1 and S0

| EN | S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|----|
| 0 | x | x | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |


Active-high and Active-low Decoders

 - The decoders studied so far are **active-high decoders** and they are implemented with **AND gates**




| EN | S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|----|
| 0 | x | x | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

 - Active-low decoders** are implemented using **NAND gates** (i.e. with an inverted EN input and inverted outputs)



| EN | S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | x | x | 1 | 1 | 1 | 1 |

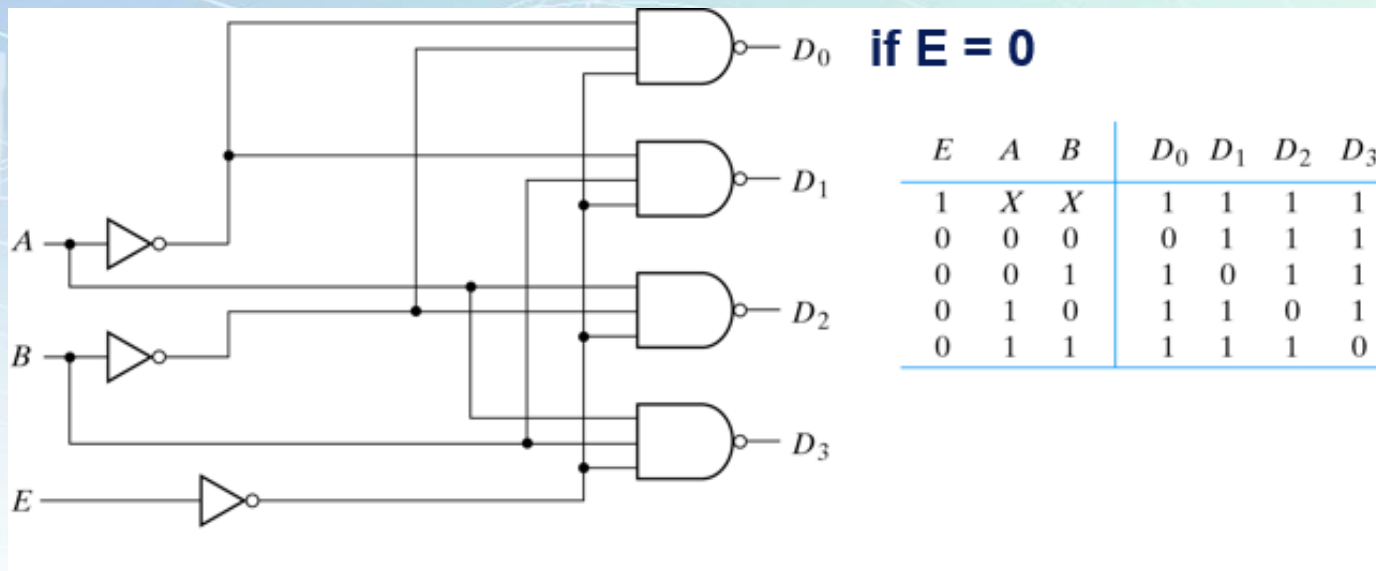Active-high and Active-low Decoders (cont'd)




Active-low 2-to-4 decoder implemented using NAND gates

Active-high and Active-low Decoders (cont'd)


- **Active-low decoders with AND gates** can be used to implement **product of maxterms (POS) functions**
- **Example:** $f(x,y,z) = \prod M(4,5,7)$

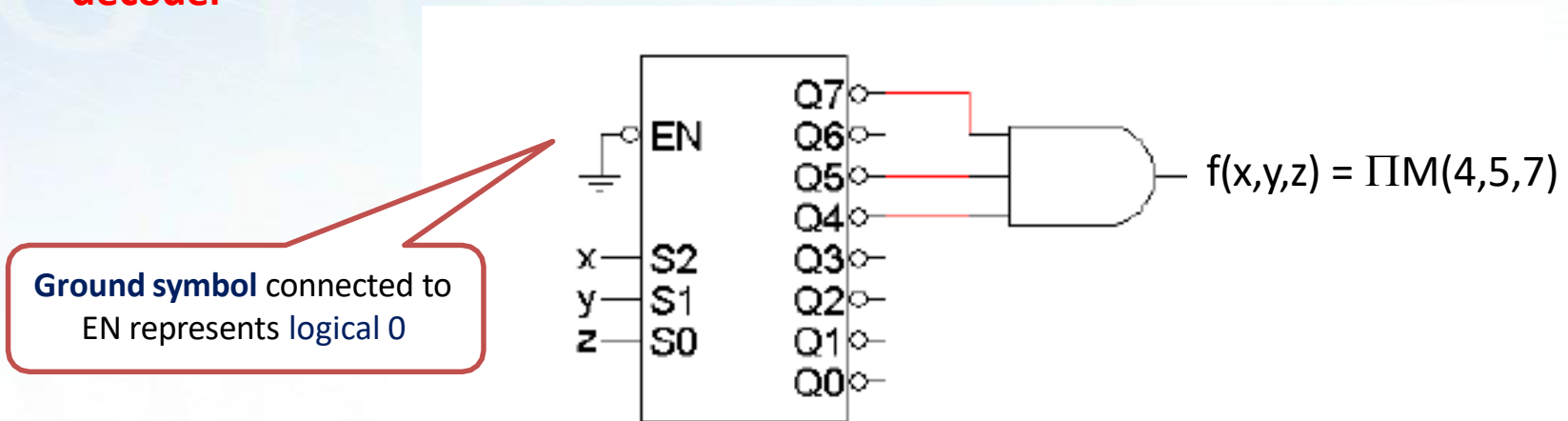Since there are 3 inputs and a total of 8 maxterms, we need a 3-to-8 active-low decoder



Decoder Expansions

 
- Larger decoders can be constructed using a number of smaller ones
- Enable inputs are used to string decoders together
- 3-to-8 decoder constructed from two 2-to-4 decoders
- Only one decoder can be active at a time



| S2 | S1 | S0 | Q0 | Q1 | Q2 | Q3 | Q4 | Q5 | Q6 | Q7 |
|----|----|----|----|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |


Decoder Expansions (cont'd)

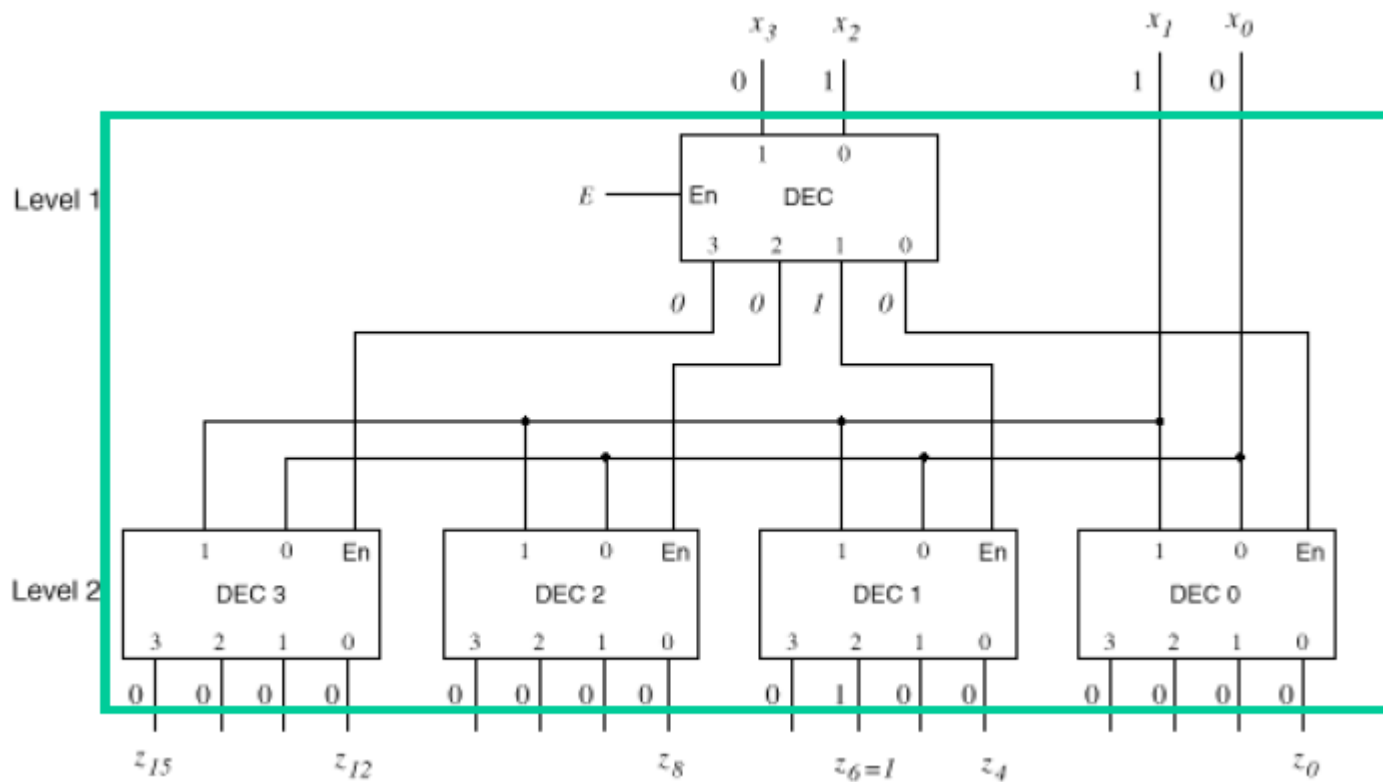- A 4-to-16 decoder can be designed using five 2-to-4 decoders and one of the 2-to-4 decoders is used to generate the enable signals to the four 2-to-4 decoders




Encoder

 - The opposite of the decoding process
- An "n-bit" binary encoder has 2^n (or fewer) input lines and **n-bit output lines**
- Only one of the input lines is activated at a given time
- The output lines generate the binary code corresponding to the input value




4-to-2 Encoder

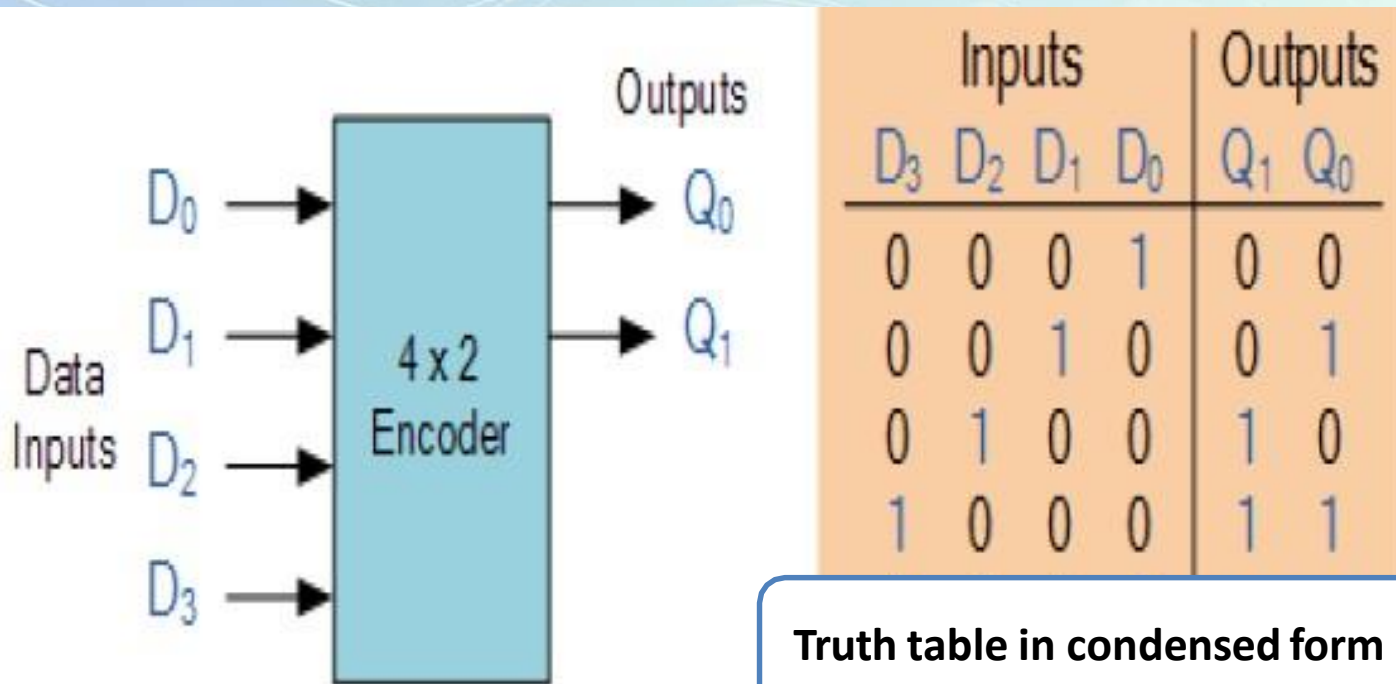- At any one time, only one input line has a value of 1




Truth table in condensed form

8-to-3 Encoder

 

| Inputs | | | | | | | | Outputs | | |
|--------|-------|-------|-------|-------|-------|-------|-------|---------|-------|-------|
| I_0 | I_1 | I_2 | I_3 | I_4 | I_5 | I_6 | I_7 | y_2 | y_1 | y_0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

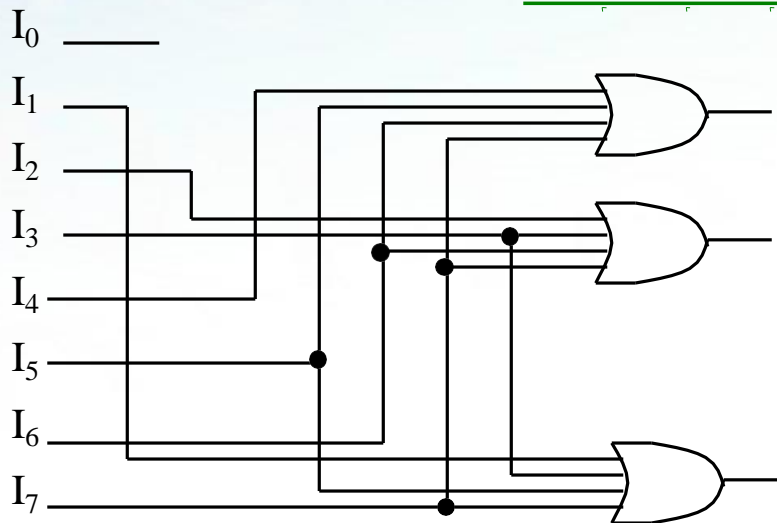

$$y_2 = I_4 + I_5 + I_6 + I_7$$

$$y_1 = I_2 + I_3 + I_6 + I_7$$

$$y_0 = I_1 + I_3 + I_5 + I_7$$

Simple Encoder Design Issues

- There are **two ambiguities associated with the design of a simple encoder**:
 - Only one input can be active at any given time. If two inputs are active simultaneously, the output produces an undefined combination (for example, in 8-to-3 encoder **if I_3 and I_4 are 1 simultaneously, the output of the encoder will be 111 (011 and 100)**)
 - An output with all 0's can be generated when **all the inputs are 0's, or when I_0 is equal to 1**

Priority Encoder

- Solves the ambiguities multiple assigned inputs are allowed; one has priority over all others
- **Separate output that indicates no input is a 1**

Priority 4-to-2 Encoder



| Inputs | | | | Outputs | | |
|--------|-------|-------|-------|---------|-------|-----|
| D_3 | D_2 | D_1 | D_0 | A_1 | A_0 | V |
| 0 | 0 | 0 | 0 | X | X | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | X | 0 | 1 | 1 |
| 0 | 1 | X | X | 1 | 0 | 1 |
| 1 | X | X | X | 1 | 1 | 1 |

Truth table in condensed form


Priority 4-to-2 Encoder (cont'd)

- The operation of the priority encoder is such that:
 - If two or more inputs are equal to 1 at the same time, the input in the **highest-numbered position will take precedence**. D_3 has the highest priority
 - **A valid output indicator, designated by V , is set to 1 only when one or more inputs are equal to 1. $V = D_3 + D_2 + D_1 + D_0$ by inspection**

Priority 4-to-2 Encoder (cont'd)

  


Priority 4-to-2 Encoder (cont'd)

 

(De)Multiplexers and Magnitude Comparators


Multiplexer

 - A multiplexer (MUX) selects one of several input signals and passes it on to the output
- Routing of selected data input to the output is controlled by SELECT inputs



Multiplexer (cont'd)

 
- **A real-life example:** in the old days before networking, **several computers could share one printer** through the use of a manual switch or **MUX**



Multiplexer (cont'd)

- A combinational circuit with **2^n data inputs**, **1 data output** and **a number of bit (n) control input** that select one of the data inputs

 C takes the value of A or B depending on the value of S




2-to-1 Multiplexer

| S | A | B | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

2-to-1 Multiplexer

 - When $S = 0 \Rightarrow C = A$
- When $S = 1 \Rightarrow C = B$




Function table

| S | C |
|---|---|
| 0 | A |
| 1 | B |

| Inputs | | | Output |
|--------|---|---|--------|
| S | A | B | C |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |


Two level implementation

 

$$C = S'AB' + S'AB + SA'B + SAB = S'A + SB$$

4-to-1 Multiplexer

| s_1 | s_0 | Y |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

 

if $(S_1S_0)_2 = 0$ Then $Y = I_0$

$$Q = \overline{S_0} \cdot \overline{S_1} \cdot I_0$$


if $(S_1S_0)_2 = 1$ Then $Y = I_1$

$$Q = S_0 \cdot \overline{S_1} \cdot I_1$$

and so on, thus we have

$$Y = \overline{S_1} \cdot \overline{S_0} \cdot I_0 + \overline{S_1} \cdot S_0 \cdot I_1 + S_1 \cdot \overline{S_0} \cdot I_2 + S_1 \cdot S_0 \cdot I_3$$

4-to-1 Multiplexer (cont'd)

 

$$Y = \overline{S_1} \cdot \overline{S_0} \cdot I_0 + \overline{S_1} \cdot S_0 \cdot I_1 + S_1 \cdot \overline{S_0} \cdot I_2 + S_1 \cdot S_0 \cdot I_3$$

Implementing Functions with Multiplexers

- **Multiplexers** can be used to **implement Boolean functions**. **One way** to implement **a function of n variables** is to use an **2^n -to-1 MUX**:
 - For **each minterm** of the function, **logic 1 is connected to data input D_i** . Each data input corresponds to one row of the truth table
 - **Connect the function's input variables to select inputs**. **These are used to indicate a particular input combination**
- **Example:** $f(x,y,z) = \sum m(1,2,6,7)$

| x | y | z | f |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

8x1 MUX

