

ITI1100 Section Z


Digital Systems I

Chapter 4: Combinational Logic (2)

Prof. Mohammad Alja'afreh
Winter 2019

Full Adder (cont'd)

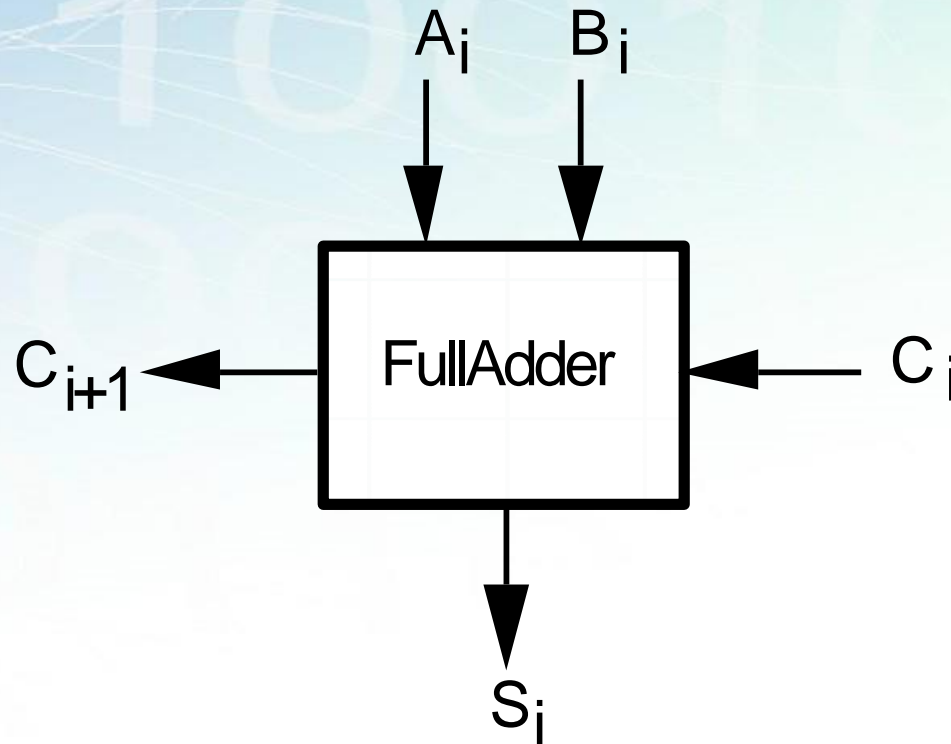
- Putting it all together
 - Single-bit full adder
 - **Common piece of computer hardware**



Block Diagram

Full Adder (cont'd)

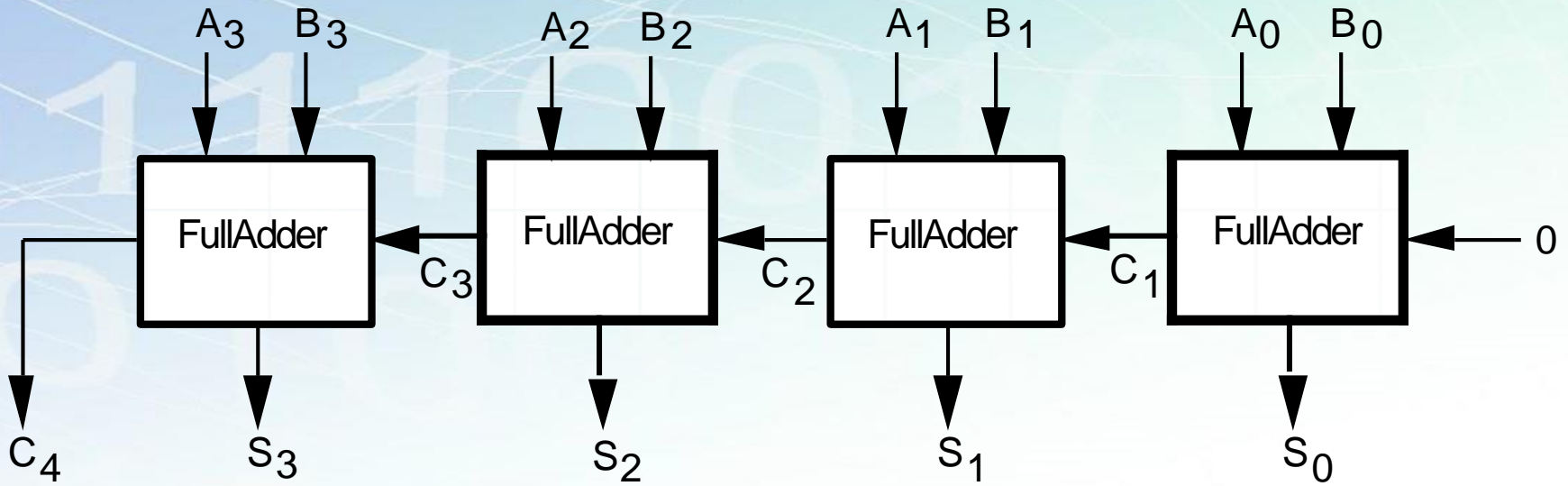
- 4-bit adder: Chain single-bit adders together



C	1	1	1	0
A	0	1	0	1
B	0	1	1	1
S	1	1	0	0


Parallel Adder

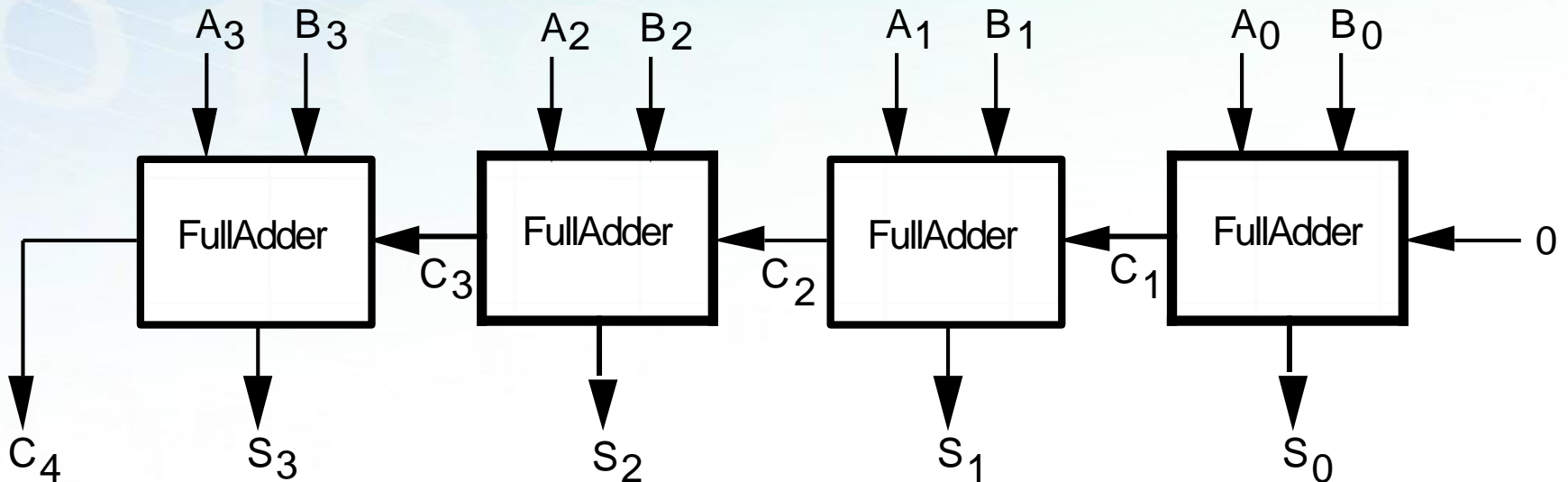- Add two n -bit numbers together, n full adders should be cascaded
- Each full-adder represents a **column** in the long addition.
- The **carry signals 'ripple'** through the adders from **right to left**




Parallel Adder (cont'd)

 - All logic gates take a **non-zero time delay** to **respond** to a **change in input**
- This is the propagation delay of the gate, typically measured in **tens of nanoseconds**



Parallel Adder (cont'd)

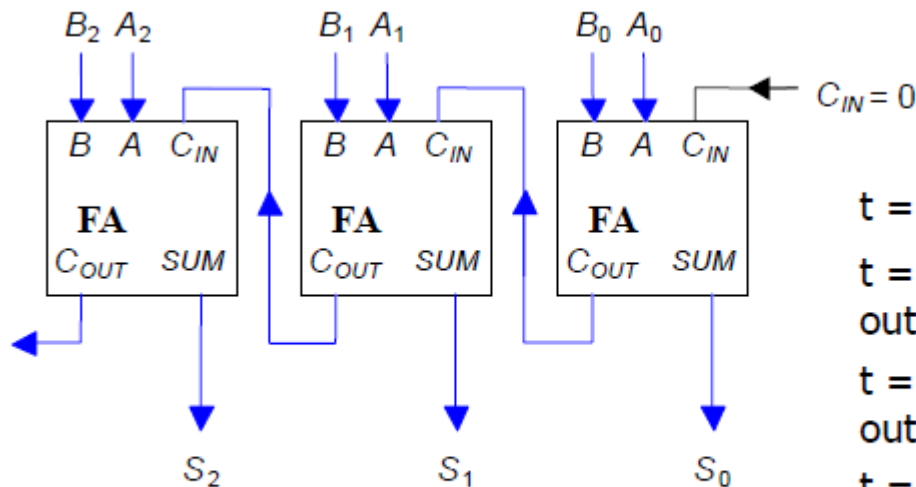- A and B inputs change, corresponding changes to C_{IN} inputs 'ripple' through the circuit




$t = 0$, A & B change
 $t = 30 \text{ ns}$, Adder 0 outputs respond
 $t = 60 \text{ ns}$, Adder 1 outputs respond
 $t = 90 \text{ ns}$, Adder 2 outputs respond

Parallel Adder (cont'd)

- The accumulated delay in large parallel adders can be very large
- **Example:** 64 bits using 30 ns full-adders:
 - $64 \times 30 \text{ ns} = 1.920 \mu\text{s}$
- **Solution:** Generate the carry-input signals directly from the A and B inputs rather than using the ripple arrangement

Parallel Adder (cont'd)

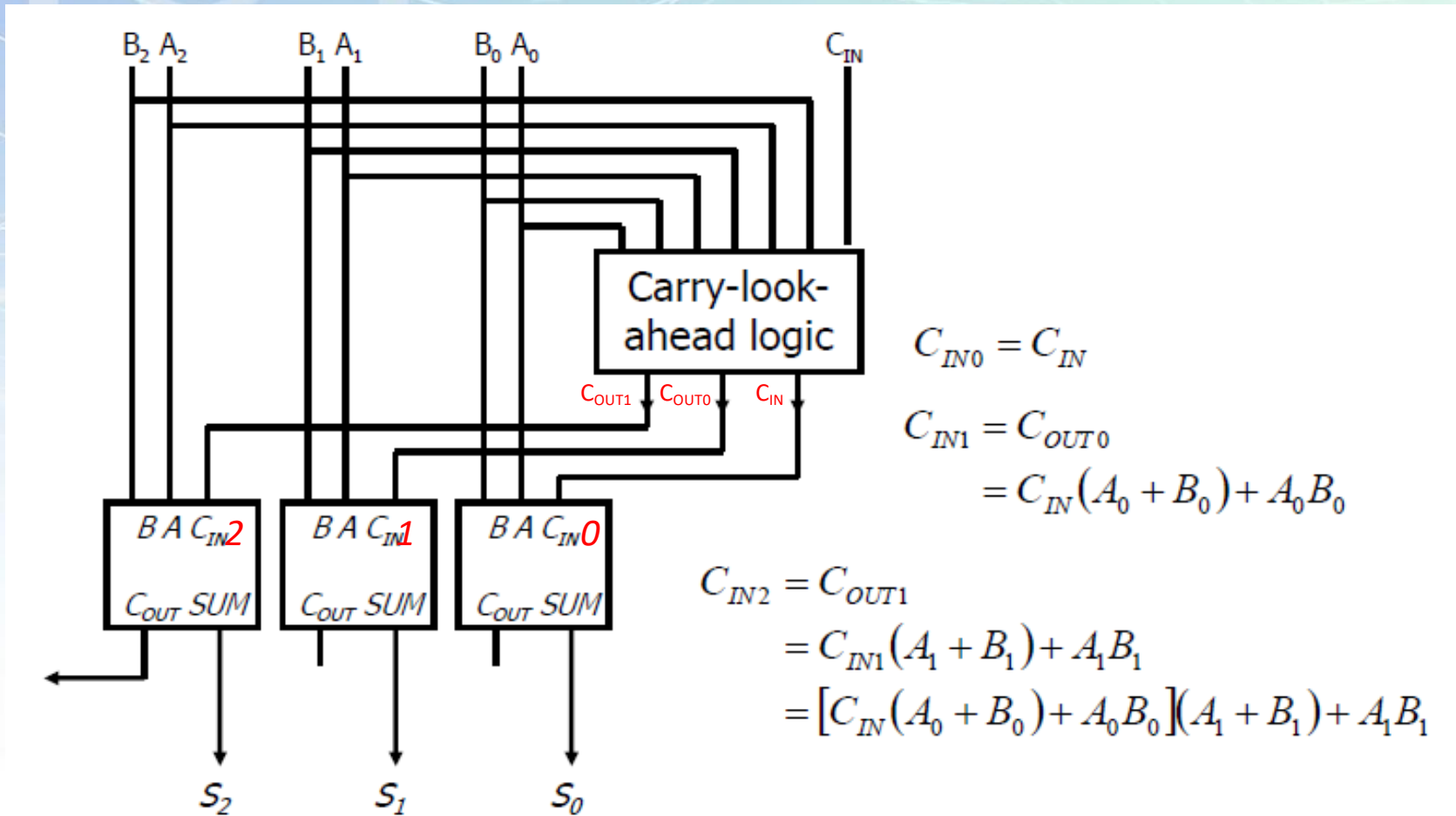- Designing a **carry-look-ahead logic circuit** for **3-bit parallel adder**




Subtractor

- **Subtracting a number is the same as:**
 - Perform 2's complement (2's complement = 1's complement +1)
 - **Perform addition**
- **We can augment adder with second's complement hardware**

Subtractor (cont'd)

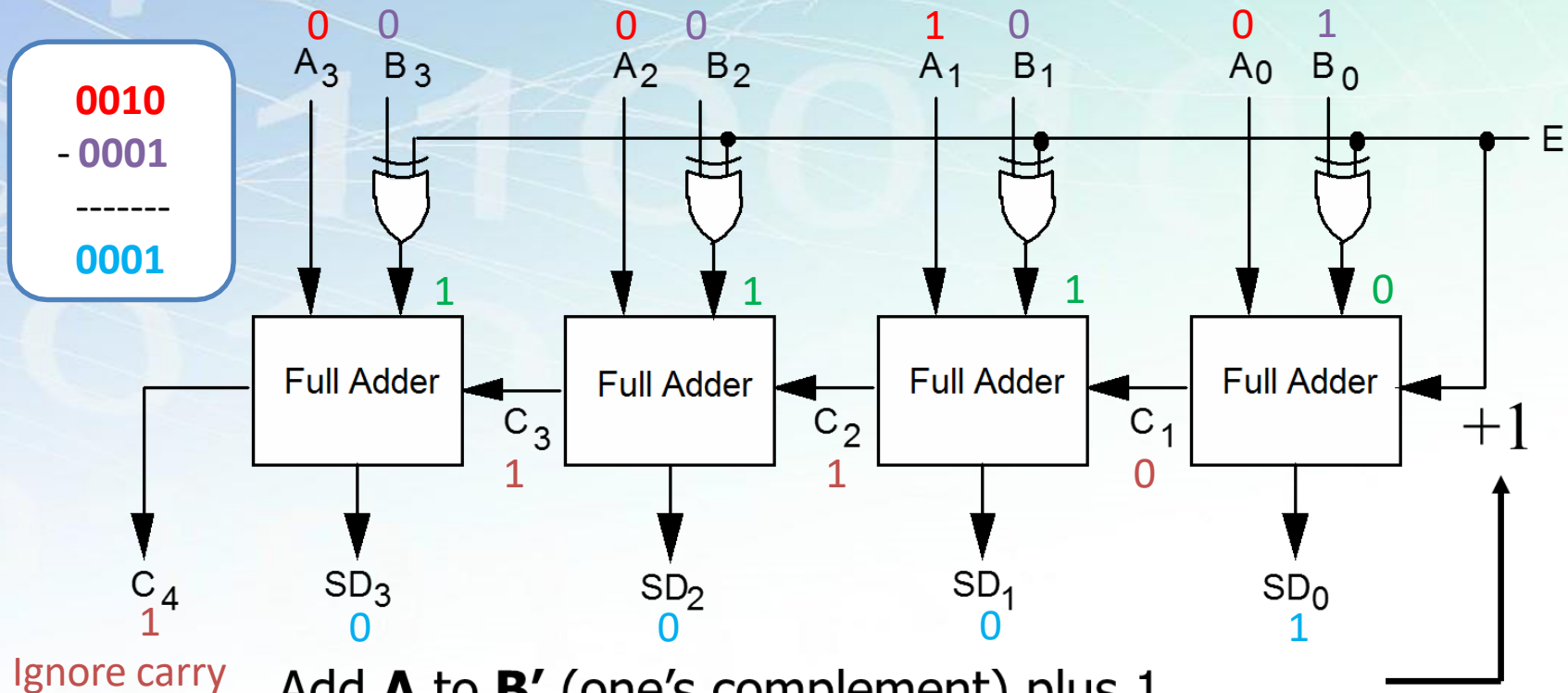- 4-bit subtractor: 4 Full adders plus 4 XORs



Add **A** to **B'** (one's complement) plus 1

That is, add **A** to two's complement of **B**

$$\mathbf{D} = \mathbf{A} - \mathbf{B}$$

Overflow


- **Overflow (OFL)** is an important issue for computers
 - Processors often have hardware to detect OFL
- **OFL occurs** when two values of the **same signs** are added:
 - Result won't fit in the number of bits provided
 - Result has the opposite sign

00	01	11	10	00	11
<u>00</u> 10	<u>00</u> 11	<u>11</u> 10	<u>11</u> 01	<u>00</u> 10	<u>11</u> 10
<u>00</u> 11	<u>01</u> 10	<u>11</u> 01	<u>10</u> 10	<u>11</u> 00	<u>01</u> 00

<u>01</u> 01	<u>10</u> 01	<u>10</u> 11	<u>01</u> 11	<u>11</u> 10	<u>00</u> 10
2	3	-2	-3	2	-2
3	6	-3	-6	-4	4
5	-7	-5	7	-2	2
	OFL		OFL		

X: sign bit


Overflow (cont'd)

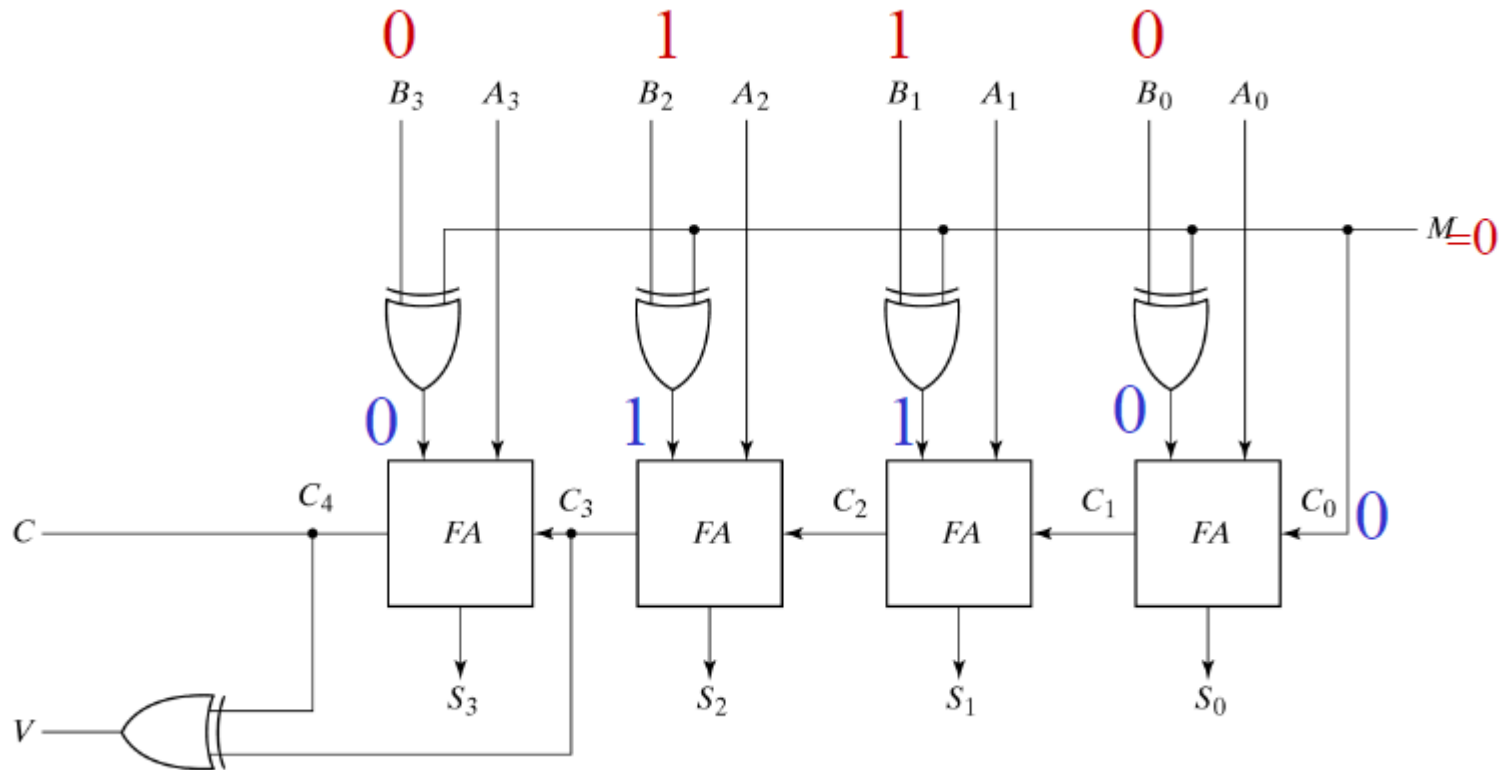


Overflow detector:
V=1 means there is
OFL

M=0 means 4-bit parallel adder

Overflow (cont'd)

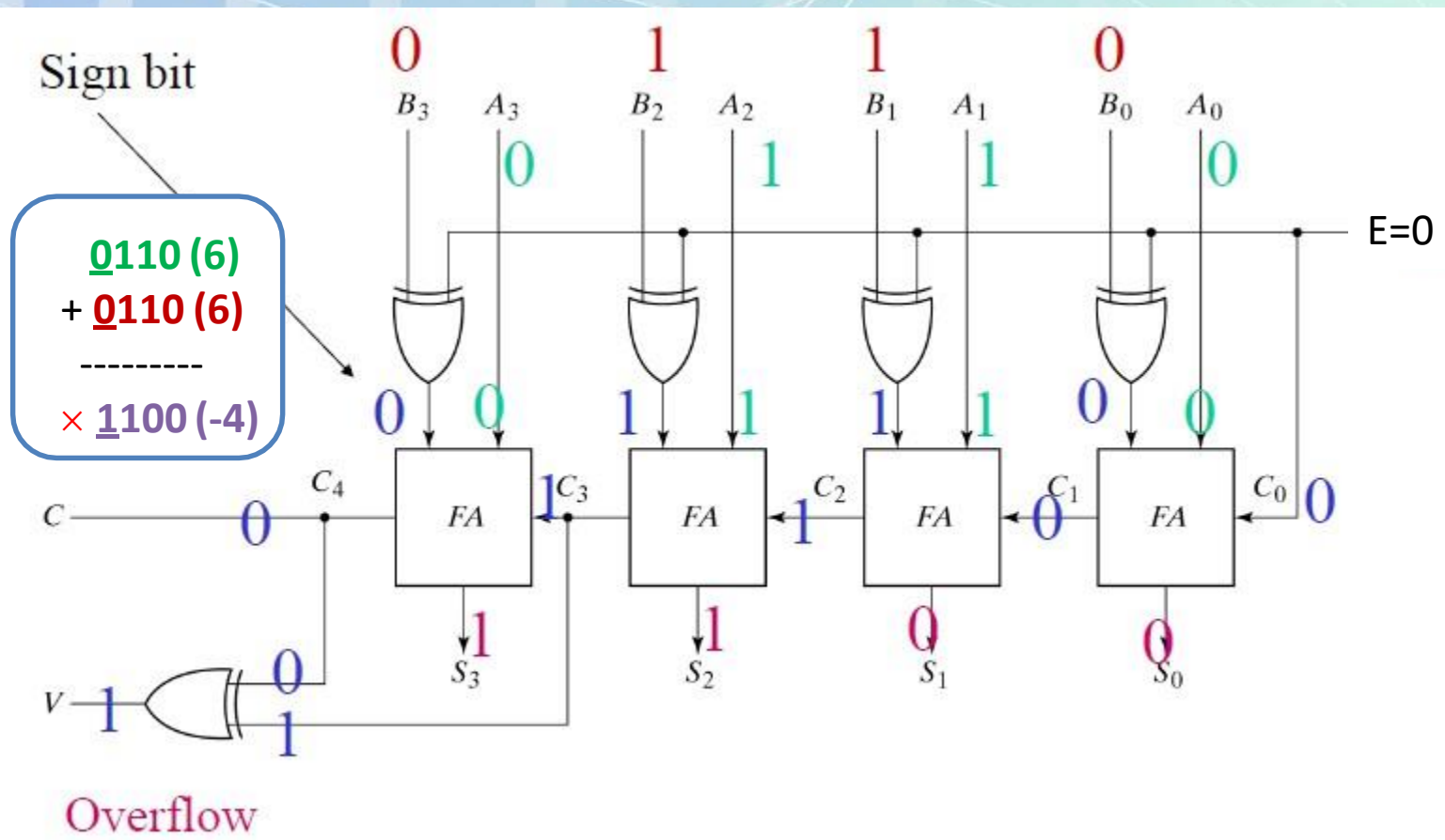

Overflow (cont'd)

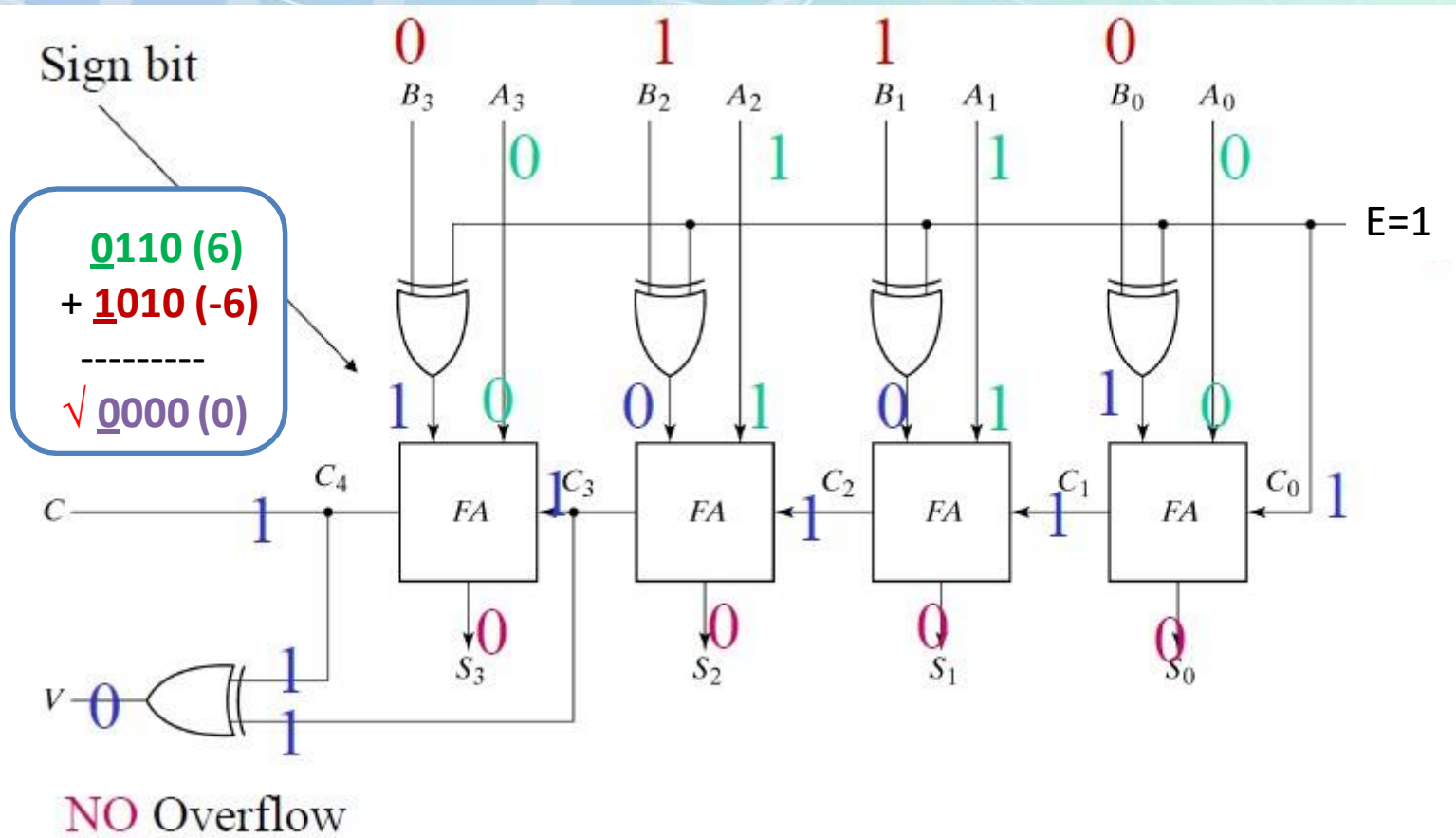

The background features a light blue-to-green gradient. Overlaid on this are several rows of binary code (0s and 1s) in a light, semi-transparent font. A white, wireframe-style globe is positioned in the upper right quadrant, partially overlapping the binary code.

Encoders and Decoders

Overview

- **Binary decoders**

- Converts an n -bit code to a single active output (one of the 2^n unique output lines)
- Can be developed using AND/OR gates
- Can be used to implement logic circuits


- **Binary encoders**

- Converts one of 2^n inputs to an n -bit output
- Can be developed using AND/OR gates


- **Both encoders and decoders are extensively used in digital systems**

Decoder

 - A combinational circuit with **n input lines** and **2^n output lines**
- **Only one output is a 1** for any given inputs
- BCD-to-7-segment decoder (**n=4** and **m=7**) is the case when the **n-bit coded information has unused combinations** \Rightarrow **less than 2^n outputs**




Implementation of 2-to-4 Decoder

 

Truth Table:


X	Y	F ₀	F ₁	F ₂	F ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- Circuit for 2x4 decoder is:

 


- From truth table, each output is a 2-variable minterm ($X'Y'$, $X'Y$, XY' , or XY)

Implementation of 3-to-8 Decoder

 

Truth Table:

x	y	z	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

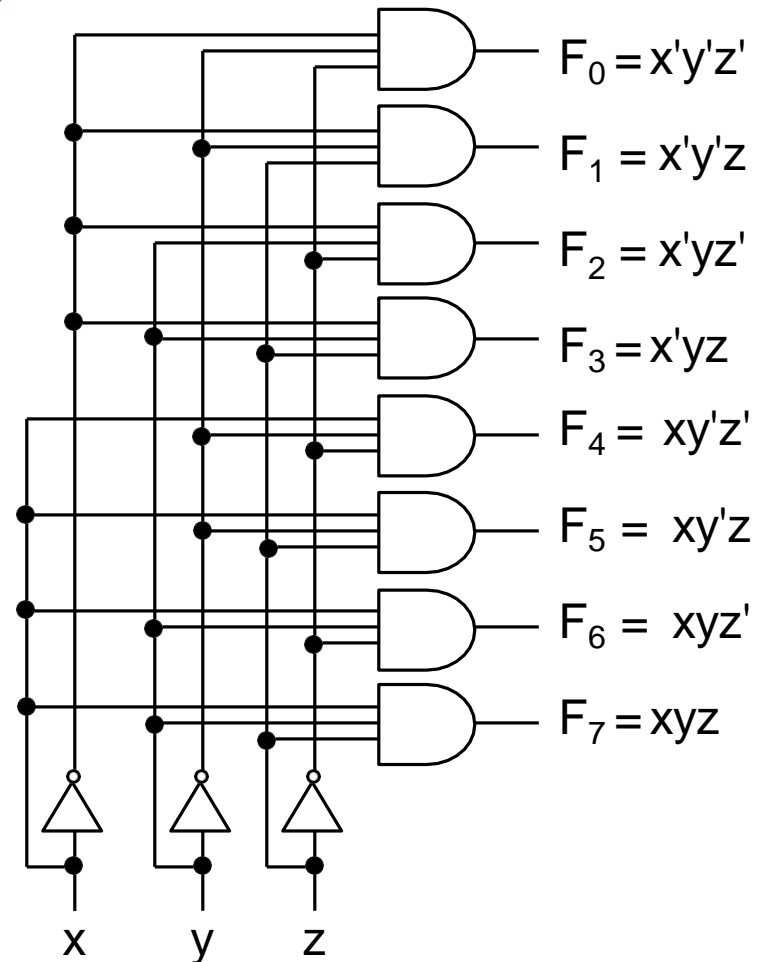

Implementing Boolean Functions Using Decoders

- **Any combinational circuit** can be **implemented with decoders and OR gates**
- A **single n-to- 2^n decoder** generates **2^n minterms**.
Decoders are sometimes called **minterm generators**
- **OR gate** forms the **sum**
- The **output lines of the decoder** corresponding to the **minterms** of the function are **used as inputs** to the **OR gate** to form **SOP expression**

Implementing Boolean Functions Using Decoders (cont'd)

■ Example: Full adder

$$S(x, y, z) = \Sigma(1,2,4,7)$$

$$C(x, y, z) = \Sigma(3,5,6,7)$$

Since there are 3 inputs and a total of 8 minterms, we need a 3-to-8 decoder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

