

ITI1100 Section z

Digital Systems I

Chapter 3:

Gate-Level minimization (2)

Prof. Mohammad Alja'afreh
Summer 2019

K-map: 4-variable Examples (cont'd)

	AB		A		
CD	0	0	0	0	
	1	0	0	0	D
	1	1	0	1	
C	1	1	0	0	
	B				

K-map for G

	AB		A		
CD	1	0	0	0	
	0	1	0	0	D
	0	0	1	0	
C	0	0	0	1	
	B				

K-map for Z

	AB		A		
CD	0	1	1	1	
	0	0	1	1	D
	0	0	0	0	
C	0	0	1	0	
	B				

K-map for Y

$$G = A' B' D + A' C + B' C D$$

$$Z = A' B' C' D' + A' B C' D + A B C D + A B' C D' \text{ (can not be simplified)}$$

$$Y = B C' D' + A C' + A B D'$$

Prime Implicants

Any single 1 or group of 1s in the Karnaugh map of a function F is an *implicant* of F .

A product term is called a *prime implicant* of F if it cannot be combined with another term to eliminate a variable.

A product term is an *essential prime implicant* of F if there is a minterm that is only covered by that prime implicant.

The minimal sum-of-products form of F must include all the essential prime implicants of F .

Simplifying logic functions using Karnaugh maps ...

looping

★ The logic function can be simplified by replacing canonical terms with a minimum cover of prime implicants, obtained by properly combining squares (looping) of the Karnaugh maps which contain 1s.

★ Looping a pair of adjacent 1s eliminates the variable that appears in both direct and complemented form.




PI: $AC, BC, A'B$

EPI: $AC, A'B$

Redundant Implicant: BC

	A	B	C	F
(0)	0	0	0	0
(1)	0	0	1	0
(2)	0	1	0	1
(3)	0	1	1	1
(4)	1	0	0	0
(5)	1	0	1	1
(6)	1	1	0	0
(7)	1	1	1	1

$$F = \sum(2,3,5,7) = AC + \bar{A}B$$

   

Simplifying logic functions using Karnaugh maps ... more


looping

$$F = \sum(0,2,5,6,7,8,10,13,14,15) =$$

$$= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + AB\bar{C}\bar{D} + ABC\bar{D} + ABCD$$

	A	B	C	D	F
(0)	0	0	0	0	1
(1)	0	0	0	1	0
(2)	0	0	1	0	1
(3)	0	0	1	1	0
(4)	0	1	0	0	0
(5)	0	1	0	1	1
(6)	0	1	1	0	1
(7)	0	1	1	1	1
(8)	1	0	0	0	1
(9)	1	0	0	1	0
(10)	1	0	1	0	1
(11)	1	0	1	1	0
(12)	1	1	0	0	0
(13)	1	1	0	1	1
(14)	1	1	1	0	1
(15)	1	1	1	1	1

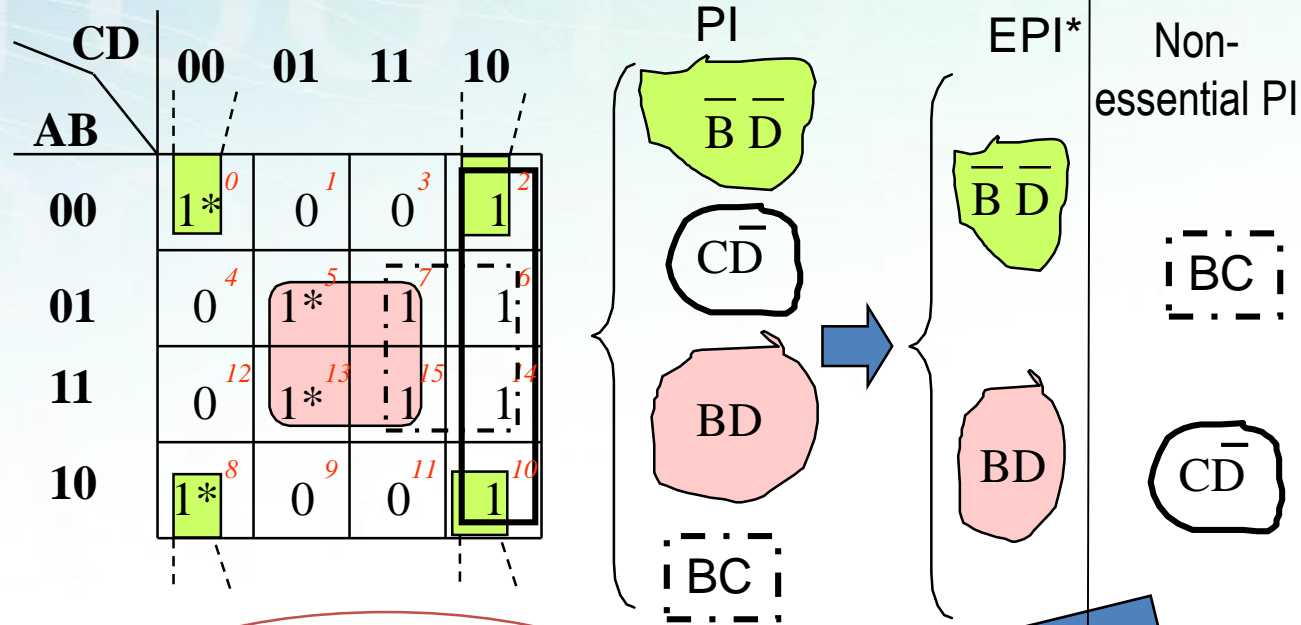★ Looping a *quad* of adjacent 1s eliminates the two variables that appears in both direct and complemented form.



$$F = \bar{B}\bar{D} + BD + \begin{cases} CD\bar{ } \\ \text{or} \\ BC \end{cases}$$

Product-of-Sums Simplification

- The best way to show this is by the following example:


$$F(A,B,C,D) = \sum m(0,1,2,3,5,7,8,10,14,15)$$

$$F(A,B,C,D) = \prod m(4,6,9,11,12,13)$$

		AB			
		00	01	11	10
CD	00	1	0	0	1
	01	1	1	0	0
	11	1	1	1	*0
	10	1	0*	1	1

$$F(A,B,C,D) = (A+B'+D) (A'+B+D') (A'+B'+C)$$

Incompletely Specified Functions

 

Assumption: it never produces the combinations
 $ABC = 001$ and $ABC = 110$.

Question: What value should F produce for the
combinations $ABC = 001$ and $ABC = 110$?

We don't care!!!

Incompletely Specified Functions (Cont.)

How can we use the fact that we don't care about the value produced by F when $ABC = 001$ or $ABC = 110$ to simplify the circuit N_2 ?

Given that N_2 gives TRUE at m_0, m_2, m_3 and m_7

A	B	C	F
0	0	0	1
0	0	1	X 0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X 0
1	1	1	1

If we assume that $F(0,0,1) = 0$ and $F(1,1,0) = 0$, we obtain the following equation

$$\begin{aligned}F(A,B,C) &= A'B'C' + A'BC' + A'BC + ABC \\ &= A'C'(B' + B) + (A' + A)BC \\ &= A'C' \cdot 1 + 1 \cdot BC \\ &= A'C' + BC\end{aligned}$$

Incompletely Specified Functions (Cont.)

However, if we assume that $F(0,0,1) = 1$ and $F(1,1,0) = 1$, we obtain instead the equation:

$$F(A,B,C) = A'B'C' + A'B'C + A'BC' + A'BC + ABC' + ABC$$

A	B	C	F
0	0	0	1
0	0	1	X 1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X 1
1	1	1	1

$$= A'B'(C' + C) + A'B(C' + C) + AB(C' + C)$$

$$= A'B' \cdot 1 + A'B \cdot 1 + AB \cdot 1$$

$$= A'B' + A'B + AB$$

$$= A'B' + A'B + A'B + AB$$

$$= A'(B' + B) + (A' + A)B$$

$$= A' \cdot 1 + 1 \cdot B$$

$$= A' + B$$


Compare this with the other solution: $F(A,B,C) = A'C' + BC$.

Which one is cheaper to implement?

Incompletely Specified Functions

Don't care values are easily used to simplify incompletely specified functions.

A	B	C	F
0	0	0	1
0	0	1	X
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	1

 

$$F = A' + B$$

Incompletely Specified Logic Functions


$$F = \sum(0,1,3,7,8,12) + dc(5,10,13,14) \quad \star dc \rightarrow x = \text{don't care terms}$$

Don't care terms can be treated as 1's or 0's, depending on which one is more advantageous.


So, if including a *don't care* in a group makes

1. the group bigger, or
 2. makes it possible to reduce the number of groups,
- the *don't care* should be included in the group, but not otherwise!

	A	B	C	D	F
(0)	0	0	0	0	1
(1)	0	0	0	1	1
(2)	0	0	1	0	0
(3)	0	0	1	1	1
(4)	0	1	0	0	0
(5)	0	1	0	1	x
(6)	0	1	1	0	0
(7)	0	1	1	1	1
(8)	1	0	0	0	1
(9)	1	0	0	1	0
(10)	1	0	1	0	x
(11)	1	0	1	1	0
(12)	1	1	0	0	1
(13)	1	1	0	1	x
(14)	1	1	1	0	x
(15)	1	1	1	1	0

 
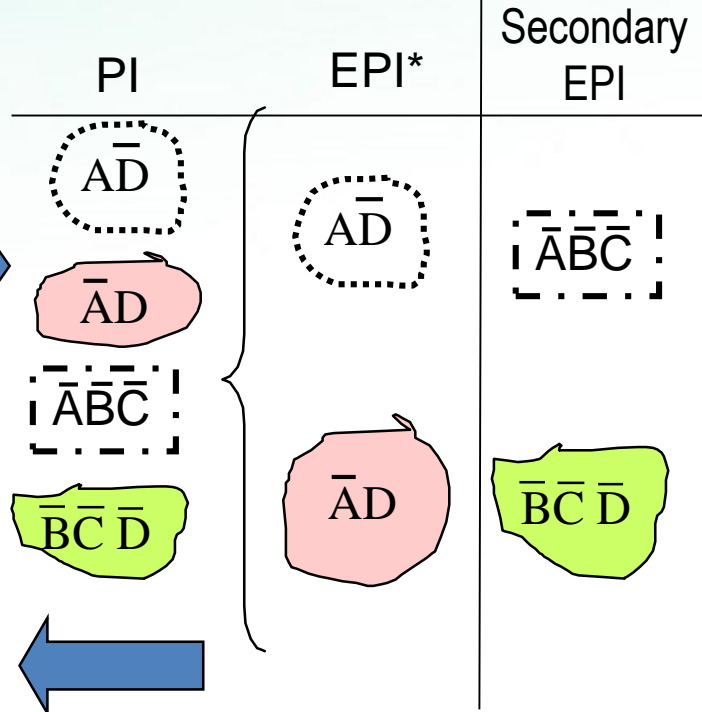
$$F_{\min} = \bar{A}\bar{D} + A\bar{D} + \begin{cases} \bar{A}\bar{B}\bar{C} \\ \text{or} \\ \bar{B}\bar{C}\bar{D} \end{cases}$$



Don't Cares Examples

$$F(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$$

$$F(A,B,C,D) = A'D + B'C'D \text{ without don't cares}$$

$$F(A,B,C,D) = C'D + A'D \text{ with don't cares}$$

		AB		A	
		00	01	11	10
C	CD	00	01	11	10
	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0
				B	

A	B	C	D	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	X
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	X
1	1	0	1	X
1	1	1	0	0
1	1	1	1	0

Example: BCD to Braille Conversion

A	B	C	D	W Z	X Y
0	0	0	0	•	•
0	0	0	1	•	•
0	0	1	0	•	•
0	0	1	1	•	•
0	1	0	0	•	•
0	1	0	1	•	•
0	1	1	0	•	•
0	1	1	1	•	•
1	0	0	0	•	•
1	0	0	1	•	•

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1
1	0	1	0	?	?	?	?
1	0	1	1	?	?	?	?
•	•	•	•	•	•	•	•
1	1	1	1	?	?	?	?


Example: BCD to Braille Conversion

A	B	C	D	W Z	X Y
0	0	0	0	.	.
0	0	0	1	.	.
0	0	1	0	.	.
0	0	1	1	.	.
0	1	0	0	.	.
0	1	0	1	.	.
0	1	1	0	.	.
0	1	1	1	.	.
1	0	0	0	.	.
1	0	0	1	.	.

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
.
1	1	1	1	X	X	X	X

Example: BCD to Braille Conversion

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1

 


AB \ CD	00	01	11	10
00	m ₀	m ₄	m ₁₂	m ₈
01	m ₁	m ₅	m ₁₃	m ₉
11	m ₃	m ₇	m ₁₅	m ₁₁
10	m ₂	m ₆	m ₁₄	m ₁₀

W = ?

Example: BCD to Braille Conversion

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1

 


CD	AB			
	00	01	11	10
00	m ₀	m ₄	m ₁₂	m ₈
01	m ₁	m ₅	m ₁₃	m ₉
11	m ₃	m ₇	m ₁₅	m ₁₁
10	m ₂	m ₆	m ₁₄	m ₁₀

W = ?

Example: BCD to Braille Conversion

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1

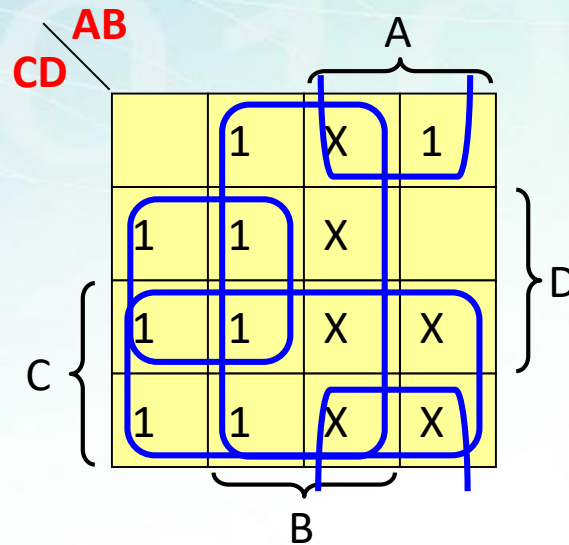


$$W = B + C + A'D + AD'$$

Example:

BCD to Braille Conversion

$$W = B + C + A'D + AD'$$

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1

 


X = ?

Example:

BCD to Braille Conversion

$$W = B + C + A'D + AD'$$

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1

 


X = ?

Example: BCD to Braille Conversion

$$W = B + C + A'D + AD'$$

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1

 

$$X = A'C'D' + CD + AD + BC$$


Example:

BCD to Braille Conversion

$$W = B + C + A'D + AD'$$

$$X = A'C'D' + CD + AD + BC$$

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1

 


Y = ?

Example: BCD to Braille Conversion

$$W = B + C + A'D + AD'$$

$$X = A'C'D' + CD + AD + BC$$

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1

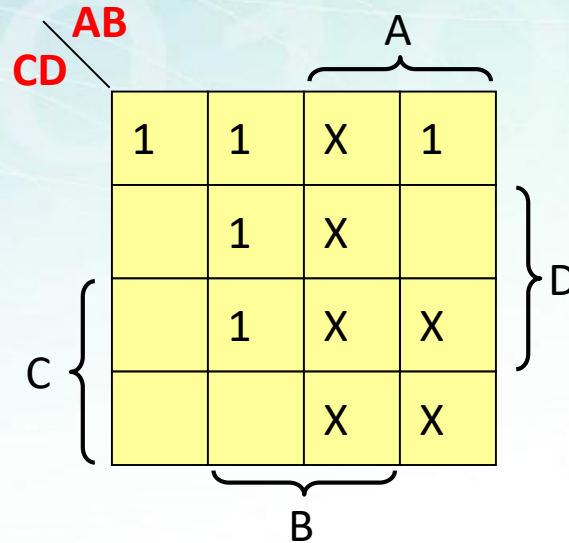


Y = ?

Example: BCD to Braille Conversion

$$W = B + C + A'D + AD'$$

$$X = C'D' + CD + AD + BC$$

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1

 

$$Y = A'C'D' + AD' + BD$$


Example: BCD to Braille Conversion

$$W = B + C + A'D + AD'$$

$$X = A'C'D' + CD + AD + BC$$

$$Y = A'C'D' + AD' + BD$$

A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	1
0	0	0	1	1	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1
1	0	0	1	0	1	0	1

 

$$Z = AD + BC + B'D'$$

Example:

BCD to Braille Conversion

$$W = B + C + A'D + AD'$$

$$X = A'C'D' + CD + AD + BC$$

$$Y = A'C'D' + AD' + BD$$

$$Z = AD + BC + B'D'$$

How can we use these standard sum-of-product equations to implement a multiple-output NAND network?

We use the DeMorgan Law:

$$X = AB + CD = ((AB + CD)')' = ((AB)'(CD)')'$$

Hardware Implementation

Truth table

K-map

minimized sum-of-products (SOP)/ product-of-sums (POS)

Physical implementation with fundamental gates: AND-OR/ OR-AND logic circuits

Design could be implemented using NANDs/ NORs