

Carleton University
 Department of Electronics
 ELEC 3605 Test 1
 October 16, 2019

Instructors, C. Plett, T, Forzley

Duration: 60 mins

Instructions: Attempt all questions. Solutions may be continued on the back of the page if required.

Authorized memoranda : Hambley Text book, Course Pack with annotations but no additional sheets of paper allowed. Scientific calculator.

Cell phones are not allowed

Name:	Student No.
-------	-------------

PA Section: Circle one

L1	L2	L3	L4	L5	L6	L7	L8	L9	L10
----	----	----	----	----	----	----	----	----	-----

PA Sections:

Day Time Room Sec

Mon 10:00 TB 446 L6

Mon 2:30 PA 115 L3

Mon 4:00 SA 311 L8

Tue 8:30 CO 214 L9

Tue 11:30 ME 3174 L2

Tue 4:00 UC 182 L10

Thu 8:30 SA 402 L5

Thu 10:00 PA 201 L7


Thu 2:30 ME 4236 L1

Fri 8:30 CO 210 L4 For faculty use only:

Q1 (10)	Q2 (10)	Q3 (10)	Total (30)
Graded by:			

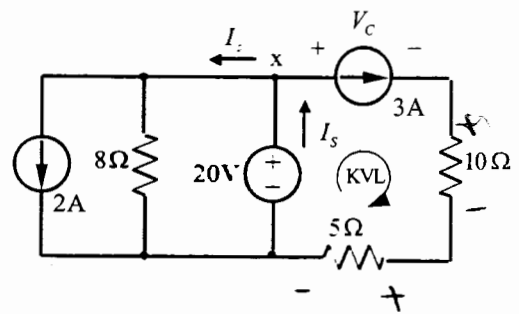1) Circuit analysis and power calculations

- Calculate the power absorbed by the 8 ohm resistor. [2]
- Calculate I_o . [2]
- Apply KCL at node x to solve for I_s . [1]
- Apply KVL to determine the voltage V_c across the 3 A current source. [2]
- Calculate the power of the 2A and 20V sources, Indicated if they are supplying or absorbing power. [3]



$$a) P = \frac{V^2}{R} = \frac{20^2}{8} = 50 \text{ W [2]}$$

$$b) I_o = 3 + \frac{20}{8} = 5.5 \text{ A [2]}$$

$$c) I_s = I_o + 3 = 5.5 + 3 = 8.5 \text{ A}$$

$$d) -20 + V_c + 3 \cdot 10 + 3 \cdot 5 = 0$$


$$V_c = 20 - 30 - 15 = -25 \text{ V [2]}$$

$$e) P_{2A} = VI = 20 \cdot 2 = +40 \text{ W absorb [1.5]}$$



$$P_{20V} = VI = 20(-8.5) = -170 \text{ W supplied [1.5]}$$

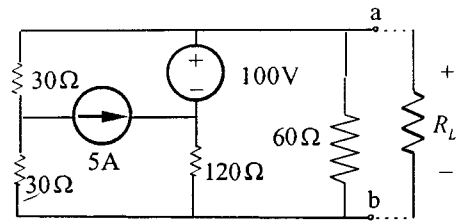2) Norton circuit analysis

- With R_L removed, determine R_t [2]
- With R_L removed, solve for the Norton current I_n using superposition. [6] **6.5**
- Draw the Norton circuit and specify the value for R_L for maximum power transfer [2]




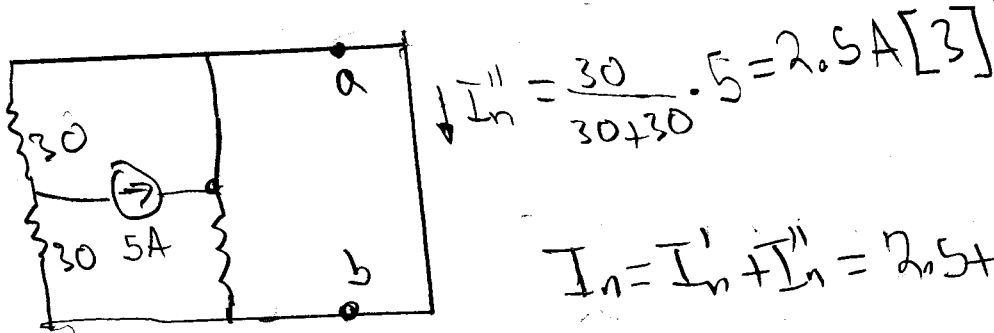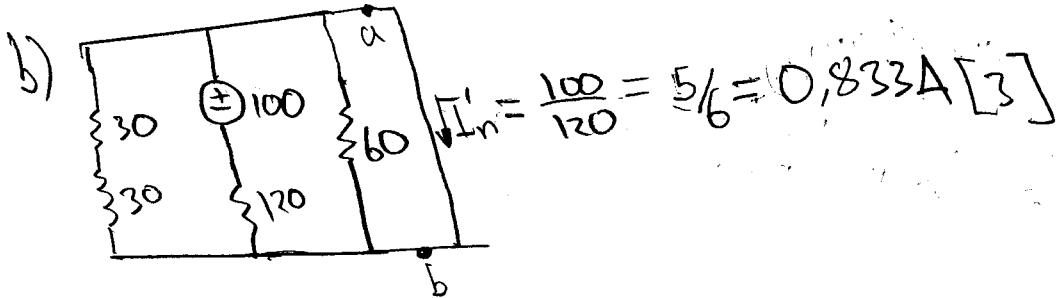a) $R_t = 60 \parallel 120 \parallel (30 + 30) = 24 \Omega$ [2]




$$I_n = I_n' + I_n'' = 2,5 + \frac{5}{6} = \frac{20}{6} = \frac{10}{3} \text{ A}$$

[2]

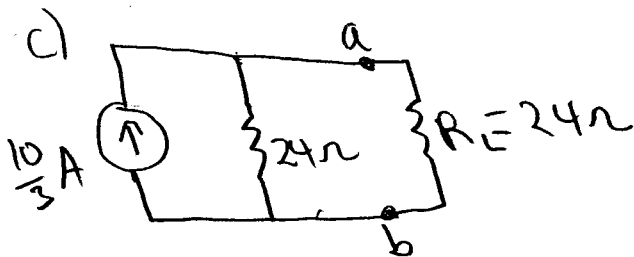

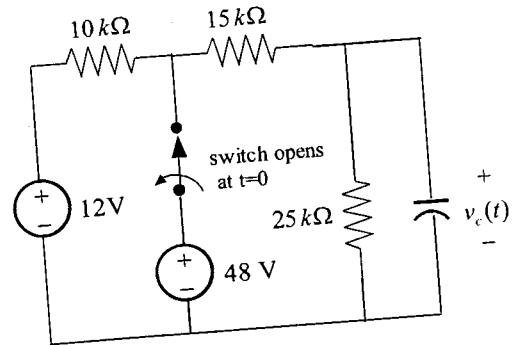3) Transient analysis

The switch is closed for a very long time such that the circuit has reached steady state. At $t=0$ the switch is open. The capacitor value is $2 \mu\text{F}$.



- Determine the time constant τ . [2]
- What is the initial capacitor voltage $v_c(0^+)$? [2]
- What is the final capacitor voltage $v_c(\infty)$? [2]
- Find an expression for $v_c(t)$ for $t > 0$ [4]

$$a) \tau = R \cdot C = [(10+15) \parallel 25] 2\mu = (12.5k)(2\mu) = 25\text{ms} [2]$$

$$b) v_c(0^-) = \frac{25}{25+15} \cdot 48 = 30\text{V} \quad v_c(0^+) = v_c(0^-) = 30\text{V} [2]$$

$$c) v_c(\infty) = \frac{25}{25+(10+15)} \cdot 12 = 6\text{V} [2]$$

$$d) v_c(t) = k_1 + k_2 e^{-t/\tau} + 70$$

$$v_c(0) = k_1 + k_2 = 30$$

$$v_c(\infty) = k_1 = 6 \rightarrow \therefore k_2 = 24$$

$$v_c(t) = 6 + 24 e^{-t/0.025} + 70 [4]$$

$$1a) P = \frac{V^2}{R} = \frac{20^2}{8} = 50 \text{ W}$$

$$b) I_0 = 4 + \frac{20}{8} = 6.5 \text{ A}$$

$$c) I_c = I_0 + 3 = 6.5 + 3 = 9.5 \text{ A}$$


$$d) V_c = -25 \text{ V}$$

$$e) P_{4A} = VI = 20(4) = 80 \text{ W} \quad \text{absorb} \quad P_{20V} = VI = (20)(-9.5) = -190 \text{ W} \quad \text{supplied}$$

$$2a) R_T = 24 \Omega$$

$$b) I_n' = \frac{90}{120} = \frac{3}{4} \text{ A} \quad I_n'' = 2.5 \text{ A}$$
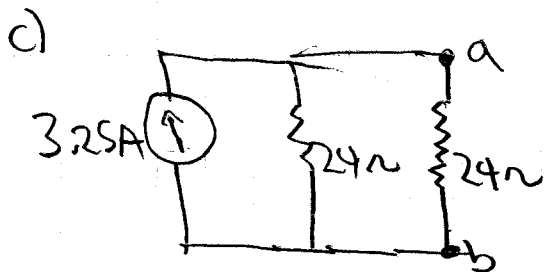
$$I_n = I_n' + I_n'' = 0.75 + 2.5 = 3.25 \text{ A}$$



$$3) a) T = R_T C = (12.5 \text{ k}) (5 \mu) = 62.5 \text{ ms}$$

$$b) V_c(0^+) = 30 \text{ V}$$

$$c) V_c(\infty) = 6 \text{ V}$$

$$d) V_c(t) = 6 + 24 \exp(-t/62.5 \text{ ms}) \quad t > 0$$