
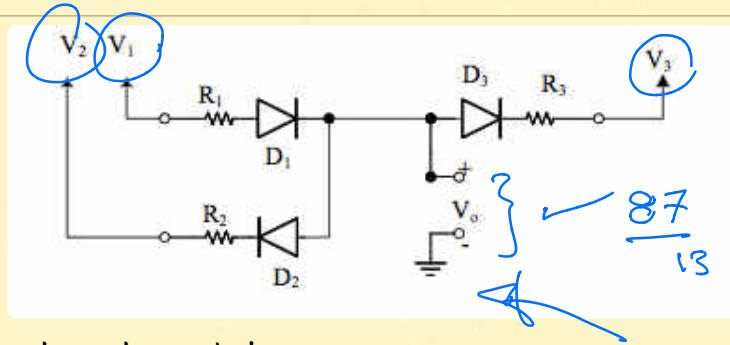


Solution
by Ecad
Cad

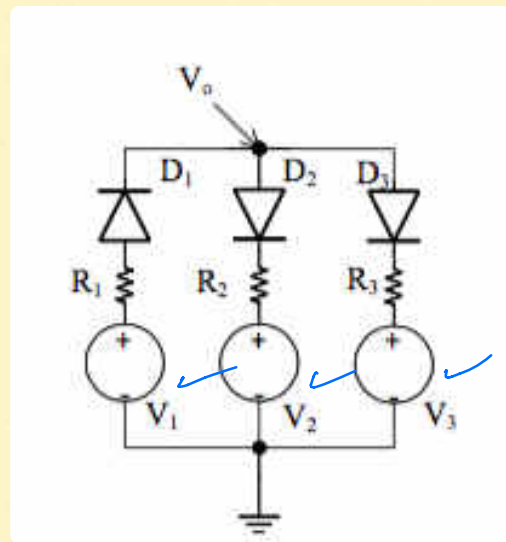

The circuit can be represented as shown below.



Assume all diodes to be ON

D_1, D_2, D_3 ON


KCL @ node V_0

$$I_1 = I_2 + I_3$$

$$\frac{7 - V_0}{R_1} = \frac{V_0 - 6}{R_2} + \frac{V_0 - 5}{R_3}$$

$$V_0 = \frac{87}{13} \text{ V} \approx 6.7 \text{ V}$$


1 - V.

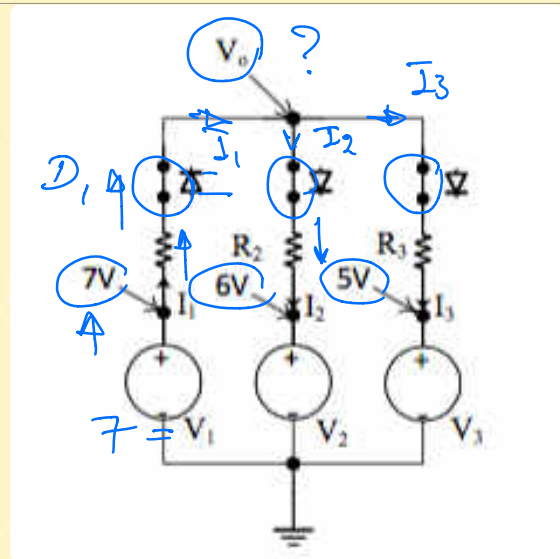

$$I_1 = \frac{V_1 - V_b}{R_1} = \frac{0.3}{R_1} > 0 \quad \text{ON is correct for } D_1$$



$$I_2 = \frac{V_2 - V_b}{R_2} > 0 \quad \text{ON is correct for } D_2$$

$I_3 > 0 \quad D_3 \text{ is correct}$

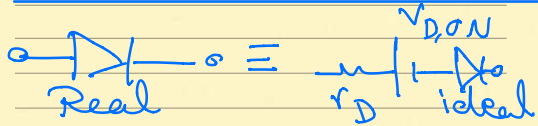

Part II

D_1, D_2, D_3
ON

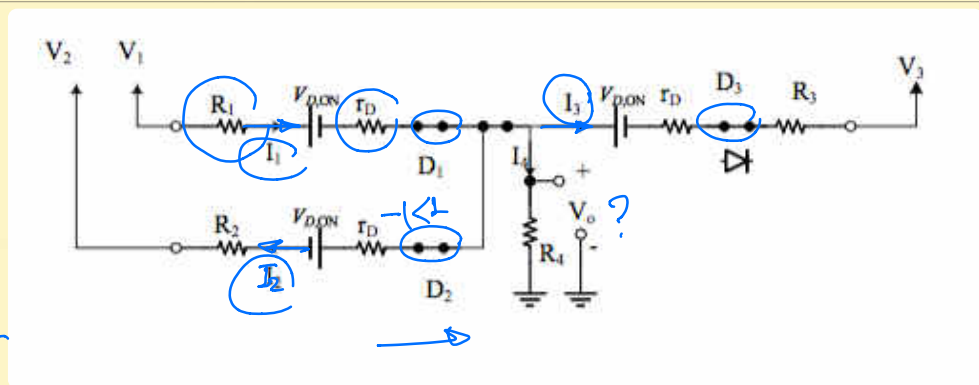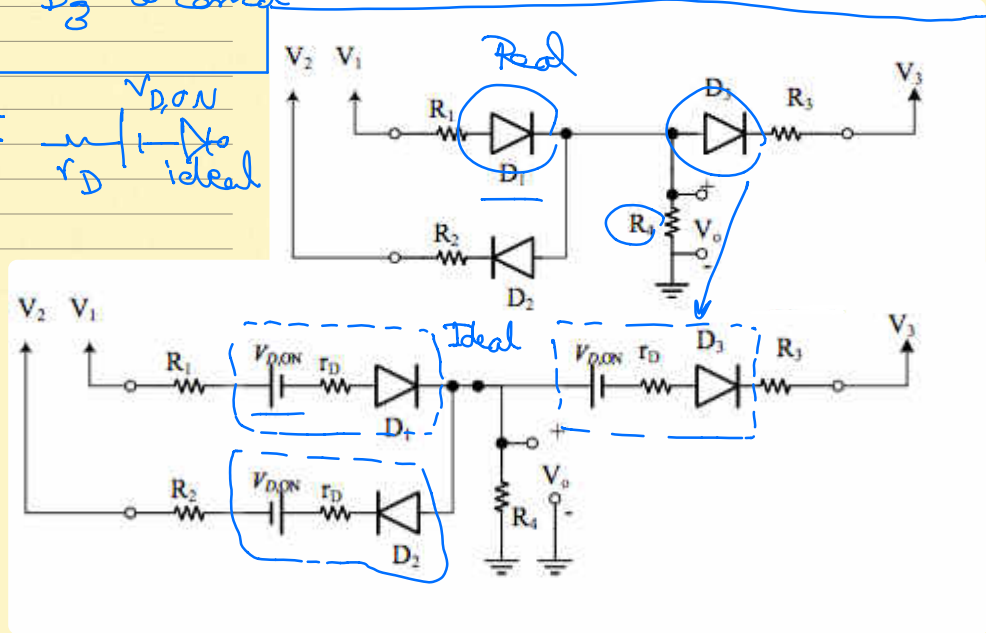


KCL @ Supernode $I_1 = I_2 + I_3 + I_4$

$$\frac{V_1 - (0.7 + V_b)}{R_1 + r_D} = \frac{V_b - 0.7 - V_2}{R_2 + r_D} + \frac{V_b - 0.7 - V_3}{R_3 + r_D}$$

$r_D = 0.1 \text{ k}\Omega$

$+ V_b$

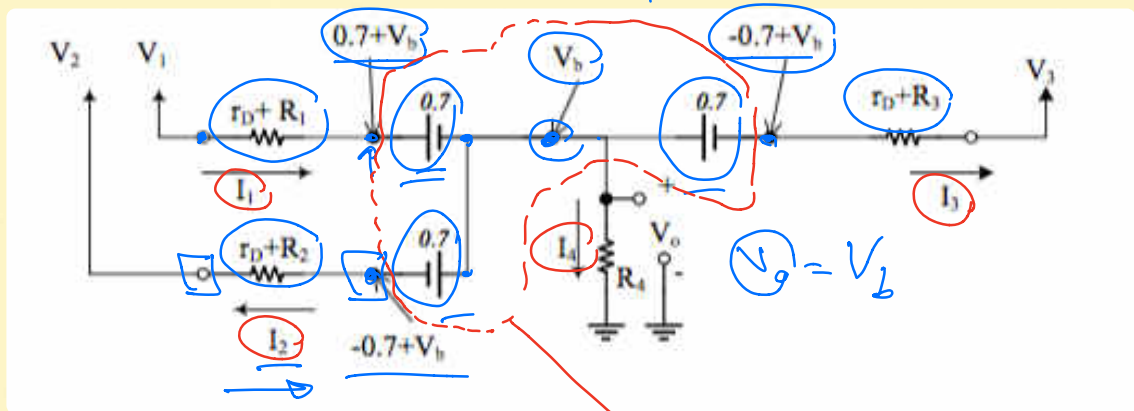$\checkmark \checkmark \quad D \quad R_1, R_2, R_3, V_1, V_2, V_3, R_4 \quad R_4$



$$V_b = 5.416 \text{ V}$$

Supernode

Validate I_1, I_2, I_3

$$I_1 = \frac{V_1 - (0.7 + V_b)}{R_1 + r_D} = 0.8 \text{ mA} \checkmark \text{ ON for } D \text{ of } R_1$$

$$I_2 = -0.25 \text{ mA} \quad \text{ON is Not ok}$$

$$I_3 = \frac{V_b - 0.7 - V_3}{R_3 + r_D} = -0.02 \text{ mA} \quad \text{ON is Not ok}$$

$$V_o = V_b = 5.416 \text{ V}$$

make another assumption

D_1 ON, (D_2 and D_3) OFF



$V_{D3} < 0$ $D3$ is OFF