

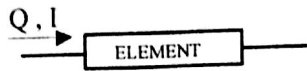


ELEC273 Winter 20115-16 BASIC CIRCUIT ANALYSIS
Tutorial Quiz 1 Week of Jan. 25

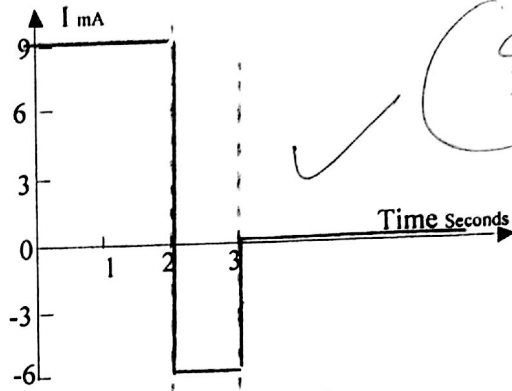Q #1: The charge Q entering an element varies as shown in Figure 1. Draw, in Figure 2, the corresponding curve for the current I entering the element, showing relevant values.




$$I = \frac{dQ}{dt}$$

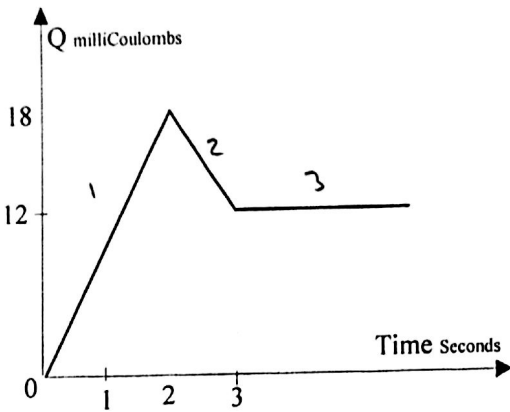

$m_1 = \frac{18-0}{2-0} = 9$
 $m_2 = \frac{12-18}{3-2} = -6$
 $m_3 = 0$

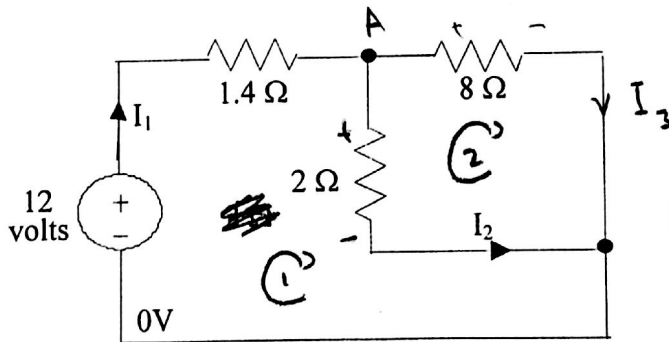Q #2: In the circuit shown, find the currents I_1 & I_2 , using KCL, KVL and/or Ohm's Law.



Solution:

KVL to loop 1 CW;
 $-12 + 1.4 I_1 + 2 I_2 = 0$

KVL to loop 2 CW
 $-2 I_2 + 8 I_3 = 0$

KCL at node A
 $I_1 = I_2 + I_3$



S
S

We obtain the system of equations

$$\begin{cases} 1.4 I_1 + 2 I_2 = 12 \\ -2 I_2 + 8 I_3 = 0 \\ I_1 = I_2 + I_3 \end{cases} \rightarrow \begin{cases} 1.4 I_1 + 2 I_2 = 12 \\ -2 I_2 + 8(I_1 - I_2) = 0 \\ I_3 = I_1 - I_2 \end{cases}$$

$$\rightarrow \begin{cases} 1.4 I_1 + 2 I_2 = 12 \\ 8 I_1 - 10 I_2 = 0 \end{cases} \rightarrow \begin{cases} I_2 = 6 - 0.7 I_1 \\ 8 I_1 - 10(6 - 0.7 I_1) = 0 \end{cases}$$

$$\rightarrow \begin{aligned} 3.8 I_1 &= -36 \\ I_1 &= \underline{9.474} \end{aligned}$$

$$\rightarrow 15 I_1 = 60 \rightarrow I_1 = \underline{4A}$$

$$I_2 = 6 - 0.7 I_1 = 6 - 0.7(4) = \underline{3.2A}$$

$$I_3 = I_1 - I_2 = 0.8A$$