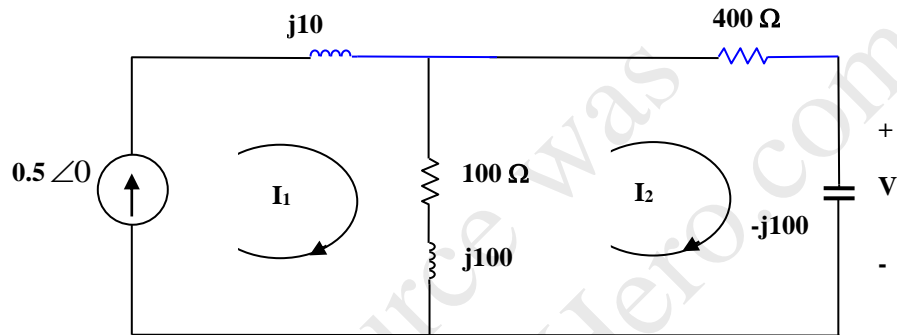


Elec-275: Winter 2013 Final Exam Solution

1. (a) For the time-domain circuit of Fig. 1, draw its phasor domain circuit. [Designate I_1 , I_2 , and V as the phasors of $i_1(t)$, $i_2(t)$, and $v(t)$ respectively]. Draw this phasor circuit.
- (b) Using **mesh analysis** on this phasor circuit, determine I_2 and V . Use the meshes shown.
- (c) Then write the time domain expressions of $i_2(t)$ and $v(t)$.

Solution:

(a) Phasor circuit:




(b) $I_1 = 0.5 \angle 0$

KVL: $500 I_2 - (100 + j100) I_1 = 0$; or $500 I_2 = (100 + j100) \times 0.5 \angle 0 = 50 + j50$.
 or $I_2 = 0.1 + j0.1 = 0.1414 \angle 45$; $V_2 = -j100 I_2 = 14.14 \angle -45$.

(c) $i_2(t) = 0.1414 \cos(10000t + 45)$ amps; $v_2(t) = 14.14 \cos(10000t - 45)$ volts.

2. Using **nodal analysis** in the phasor circuit of Fig.2,

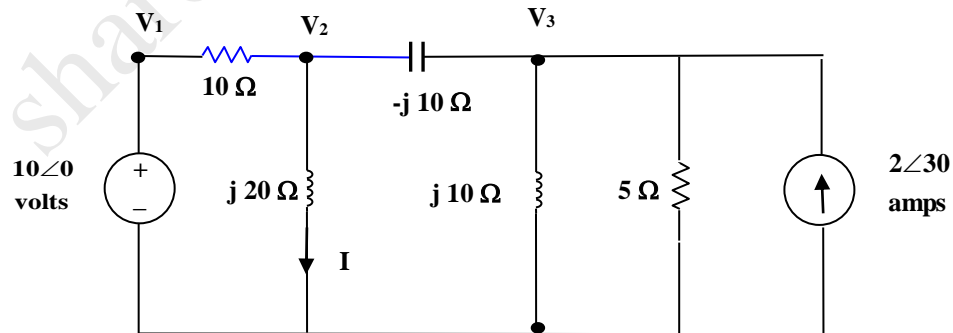- (a) determine the voltages V_2 , V_3 , and the current I ;
- (b) draw the phasor diagrams (plot of phasors in the complex plane) of V_1 , V_2 , V_3 , and I .



Ref = 0 V

Solution:

(a) KCL @ V_2 : $\frac{V_2 - 10\angle 0}{10} + \frac{V_2}{j20} + \frac{V_2 - V_3}{-j10} = 0$; or $(-1+j2)V_2 + 2V_3 = j20$... (1)


KCL @ V_3 : $\frac{V_3}{j10} + \frac{V_3}{5} + \frac{V_3 - V_2}{-j10} - 2\angle 30 = 0$; or $V_2 + j2V_3 = -10 + j17.32$... (2)

From (1) and (2): $V_2 = 6.33 \angle 41.6$; $V_3 = 5.3 \angle 24.2$; $I = V_2/(j20) = 0.3165 \angle -48.4$


(b) Phasor diagrams may now be drawn.

3. (a) Replace the circuit to the left of $a - b$ of Fig. 3 by its **Thevenin** equivalent. Draw this equivalent circuit.

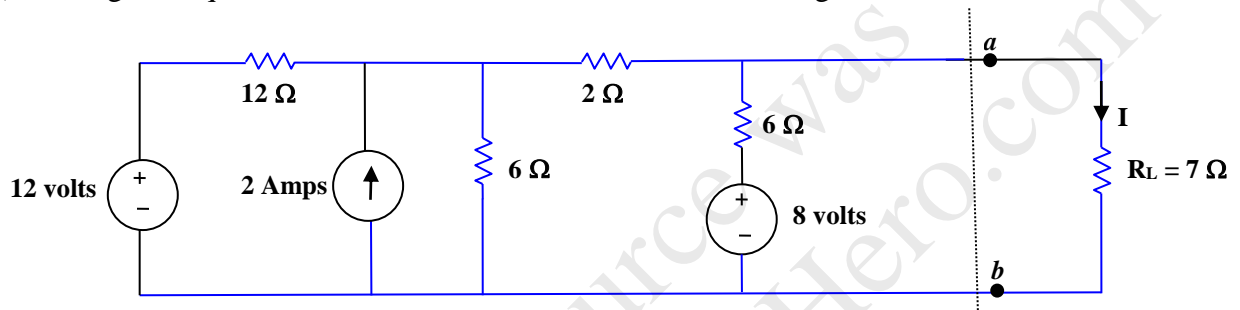(b) Using this equivalent circuits, determine the current I through the load resistor R_L .



Solution:

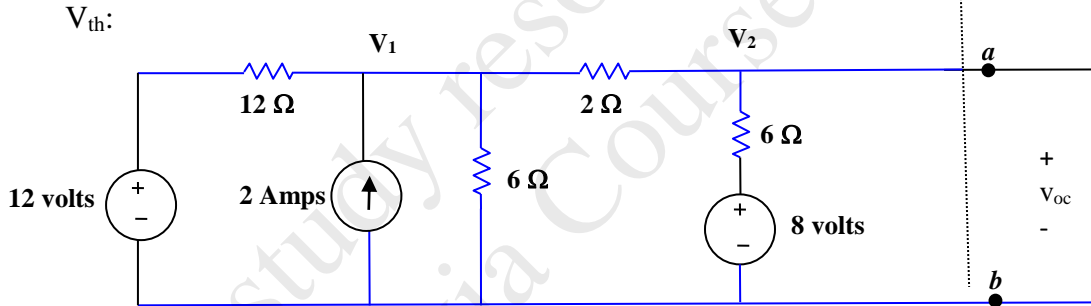


KCL @ V_1 : $\frac{V_1 - 12}{12} - 2 + \frac{V_1}{6} + \frac{V_1 - V_2}{2} = 0$; or $9V_1 - 6V_2 = 36$... (1)

KCL @ V_2 : $\frac{V_2 - V_1}{2} + \frac{V_2 - 8}{6} = 0$; or $-3V_1 + 4V_2 = 8$... (2).

From (1) and (2), $V_2 = V_{th} = 10$ volts.

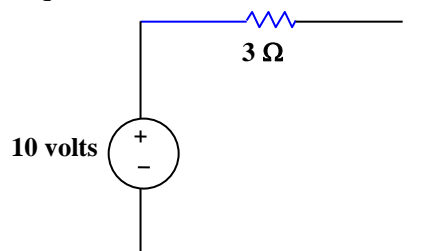
$R_{th} = 3 \Omega$. Thevenin equivalent:




(b) $I = 1 \text{ A}$.

4. An ideal transformer with a turns ratio of N in Fig. 4 is used to match the load Z_L for maximum power transfer. For that purpose, determine:

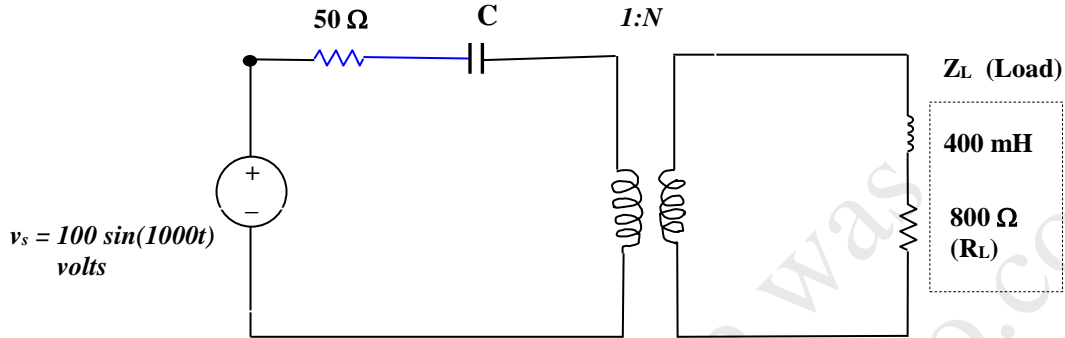- (a) the transformer turns ratio;
- (b) the value of the capacitor C ;
- (c) the power absorbed by the load.



Solution:

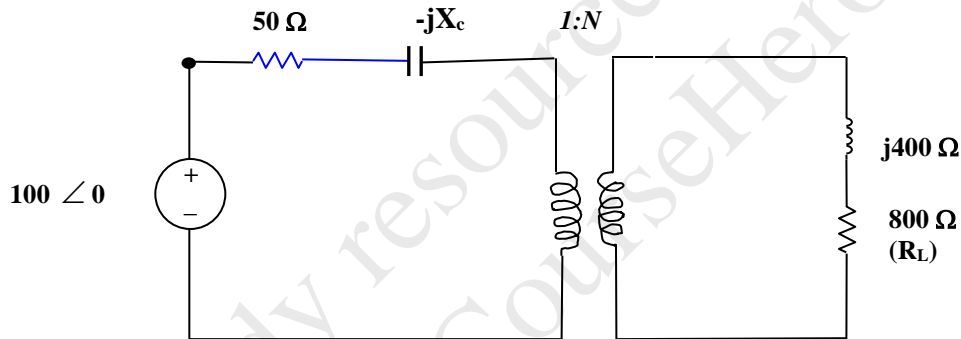


(a): $N^2 = \frac{800}{50} = 16$; $N = 4$.

(b) $X_c = \frac{400}{16} = 25 = \frac{1}{1000 \times C}$; $C = 40 \mu\text{F}$.

(c) $P = \frac{\left(\frac{50}{\sqrt{2}}\right)^2}{50} = 25 \text{ watts}$.

5. A three-phase 60 Hz power supply is connected to a three-phase motor as shown in Fig. 5. Find:

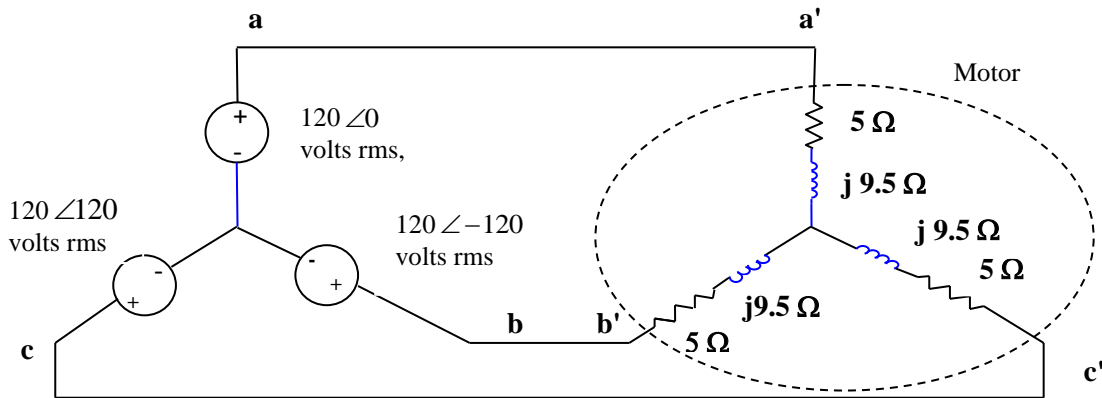- (a) the power factor
- (b) the apparent power of the motor
- (c) the real power of the motor
- (d) the reactive power of the motor.



Solution:

Using single phase circuit: $Z_L = 5 + j9.5 = 10.735 \angle 62.24$

(a) **P.F.** = $\cos 62.24 = 0.4657$.

(b)
$$S = \frac{V_{rms}^2}{Z^*} = \frac{120^2}{10.735 \angle -62.24} = 1341.4 \angle 62.24 = 624.7 + j 1187$$
 Total power = $3 S = 4024.2 \angle 62.24$
Apparent power = 4024.2 VA

(c) **Real power** = 1874.34 W

(d) **Reactive power** = 3561 VAR.

6. For the magnetic circuit of Fig.6:

- Air gap cross sectional area = 2 cm × 2 cm (for both gaps)
- Air gap lengths:
 - $l_{g1} = 2$ mm
 - $l_{g2} = 4$ mm
- Neglect the reluctance of the magnetic metallic structure (compared to those of the air gaps), as well as the fringing effect.
- The magnetizing coil has 100 turns and carries a current of 0.5 amps.

(a) Determine, for each air gap:

- (i) the reluctance **R**;
- (ii) the flux ϕ .

(b) Find

- (i) the flux density **B** for air gap-1 only;
- (ii) the field intensity **H** for air gap-1 only.

(c) Find the equivalent reluctance seen by the magnetomotive force **NI**.

Solution:

$$A = 4 \times 10^{-4} \text{ m}^2.$$

(a) Air gap 1: (i) $\mathbf{R}_1 = \frac{2 \times 10^{-3}}{4\pi \times 10^{-7} \times 4 \times 10^{-4}} = 3.98 \times 10^6 \text{ A-turns/Wb};$

(ii) $\phi_1 = \frac{NI}{R_1} = \frac{50}{3.98 \times 10^6} = 12.566 \times 10^{-6} \text{ Wb}.$

Air gap 2: (i) $\mathbf{R}_2 = 7.98 \times 10^6 \text{ A-turns/Wb};$

(ii) $\phi_2 = 6.283 \times 10^{-6} \text{ Wb}.$

(b) (i) $\mathbf{B} = \frac{\phi_1}{A} = \frac{12.566 \times 10^{-6}}{4 \times 10^{-4}} = 0.0314 \text{ Wb/m}^2$

(ii) $\mathbf{H} = \frac{B}{\mu_0} = \frac{0.0314}{4\pi \times 10^{-7}} = 25 \times 10^3 \text{ A-turn/m}.$

(c) $\mathbf{R}_{eq} = R_1 \parallel R_2 = 2.65 \text{ A-turn/Wb}.$

7. (a) $I_f = 240/120 = 2 \text{ A}.$

At no-load: $I_a = 6 - 2 = 4 \text{ A}.$ $E_b = 240 - 0.4 \times 4 = 238.4 = (K_a \phi) \omega_m$
 $= K_a \phi \times \frac{2000}{60} \times 2\pi$; or $K_a \phi = \frac{238.4}{2000 \times 2\pi} \times 60 = 1.138.$

(b) At full-load: $I_a = 50 - 2 = 48 \text{ amps};$ $E_b = 240 - 48 \times 0.4 = 220.8 \text{ volts}.$

(c) $\text{Speed} = \omega_m = \frac{220.8}{1.138} \times \frac{60}{2\pi} = 1852.35 \text{ rpm}.$

(d) $\text{Torque} = (K_a \phi) I_a = 1.138 \times 48 = 54.637 \text{ N-m}$

(e) $\text{Power} = \text{Torque} \times \text{speed} = 54.637 \times \frac{1852.35}{60} \times 2\pi = 10,598.4 \text{ W} = 14.2 \text{ HP}.$