

| | | |
|--|---|---|
| ELEC275 /2-T and V | Principles of Electrical Engineering | Fall 2017 October 21st (5-7 pm) |
| MIDTERM EXAM | | |
| This is a <u>closed</u> book, <u>closed</u> note exam No extra pages are allowed. Only ENCS-approved calculators carrying the ENCS sticker will be allowed. | | |
| Special notes: | | |
| <i>Use the back of the pages of this question booklet for your rough work. The work done on these pages will not be marked.</i> | | |
| <u>This question booklet should be returned with the answer booklet.</u> | | |
| <i>A <u>formula sheet</u> is given at the end of the exam booklet. <u>You can detach</u> this page from the rest of the booklet.</i> | | |
| Name: | | |
| ID Number: | | |
| Section: | | |
| Time: Two hours! | | |

| Question | Grade |
|-----------------|--------------|
| #1 | /10 |
| #2 | /10 |
| #3 | /10 |
| #4 | /10 |

Final exam grade: /40

Problem 1. In the circuit shown in Fig.1, $R_1=1\text{ k}\Omega$, $R_2=4\text{ k}\Omega$, $R_3=200\ \Omega$, $R_4=100\ \Omega$, and $R_5=1.2\text{ k}\Omega$.

(a) Calculate the equivalent resistance observed between nodes **a** and **b**, when switch S_1 is closed but S_2 is open. **(4 marks)**

(b) Calculate the equivalent resistance observed between nodes **c** and **d**, when S_1 is open but S_2 is closed. **(4 marks)**

(c) When both switches are closed, what is the total resistance observed between terminals **a** and **c**? **(2 marks)**

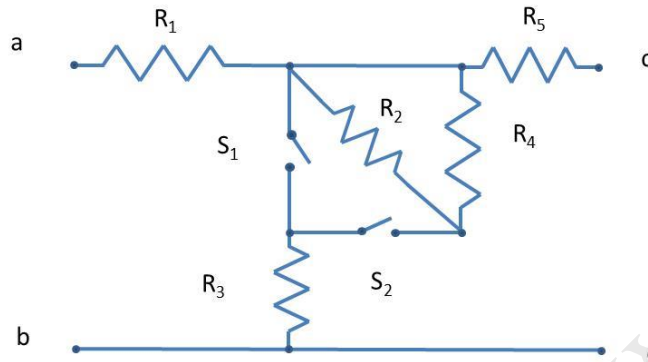


Fig. 1

(a) $R_{ab}=R_1+R_3=1200\ \Omega$

(b) $R_{cd}=R_5+R_3+R_2R_4=1497.6\ \Omega$

(c) $R_{ac}=R_1+R_5=2200\ \Omega$

This study resource was shared via CourseHero.com

Problem 2. Using **mesh analysis technique**, calculate the current through resistance R_3 in the resistive network shown in Fig.2 and identify the direction of its flow. You are expected to clearly write down the mesh equations. **(10 marks)**

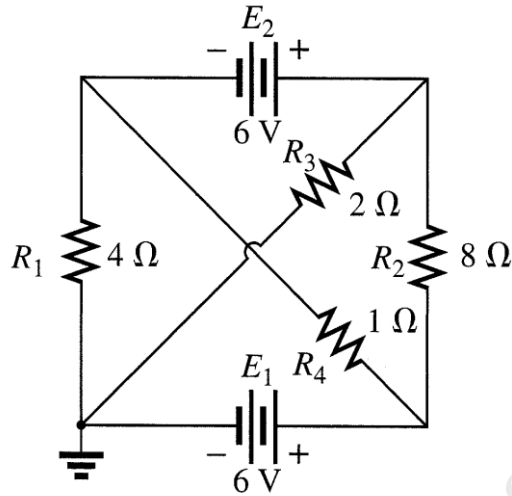


Fig.2.

R_3 , R_1 , and E_2 form an outer mesh (mesh#1).
 R_4 , R_1 , and E_1 form another mesh (mesh#2).
 R_4 , R_2 , and E_2 form another mesh (mesh#3).
 The mesh current among all three is assumed to be clock-wise.

KVL in mesh#1: $R_3 I_1 + E_2 + R_1 (I_1 - I_2) = 0$: $2I_1 + 6 + 4(I_1 - I_2) = 0$
 KVL in mesh#2: $R_4 (I_2 - I_3) + E_1 + R_1 (I_2 - I_1) = 0$: $(I_2 - I_3) + 6 + 4(I_2 - I_1) = 0$:
 KVL in mesh#3: $R_2 I_3 - E_2 + R_4 (I_3 - I_2) = 0$: $8I_3 - 6 + (I_3 - I_2) = 0$

Resulting in:
 $6I_1 - 4I_2 = -6$
 $-4I_1 + 5I_2 - I_3 = -6$
 $-I_2 + 9I_3 = 6$

I_1 is the current through R_3 .
 According to the above set, $-4(-1 + 0.66I_2) + 5I_2 - 0.11I_2 - 0.67 = -6$
 Hence, I_2 is approximately -4.14 A resulting in -3.76 A for I_1 and the direction is towards ground.

Problem 3. Consider the circuit diagram in Fig. 3. Answer the following.

(a) What will be the value of R_L for maximum power transfer? Show your derivations.

(4 marks)

(b) If we put $R_L = 3$ ohms, what will be power delivered to R_L ?

(6 marks)

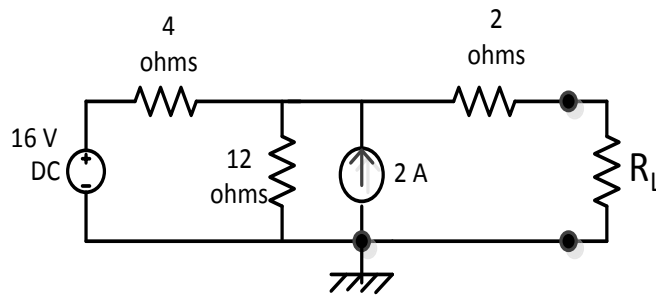


Fig. 3

(a) $R_L = R_{th} = 4 + 12 + 2 = 18 \Omega$

(b) $V_{th} = ?$

Write a KCL at the joint terminal of the three resistors:

$$(V-16)/4 + V/12 - 2 = 0$$

$$V = V_{th} = 18 \text{ V}$$

$$\text{Power delivered to the load: } (18^2/18) = 18 \text{ W}$$

This study resource was shared via CourseHero.com

Problem 4. Fig. 4 gives a RLC-network excited by a current source.

- (a) Obtain an equivalent network containing one resistance R_{eq} , one inductance L_{eq} , and one capacitance C_{eq} , excited by the current source. Give all the values of R_{eq} , C_{eq} , and L_{eq} . (6 marks)

$$L_1 = 5 \text{ mH}, L_2 = 10 \text{ mH}, L_3 = 4 \text{ mH}, L_4 = 8 \text{ mH}, \text{ and } L_5 = 12 \text{ mH}$$

$$C_1 = 5 \text{ } \mu\text{F}, C_2 = 10 \text{ } \mu\text{F}, C_3 = 4 \text{ } \mu\text{F}, C_4 = 8 \text{ } \mu\text{F}, \text{ and } C_5 = 12 \text{ } \mu\text{F}$$

$$R_1 = 12 \text{ k}\Omega, R_2 = 8 \text{ k}\Omega$$

- (b) If $i_s(t) = 10 \cos[(2\pi)(60)t]$, obtain the equivalent network in the sinusoidal frequency domain giving all the resistance and reactance values. (4 marks)

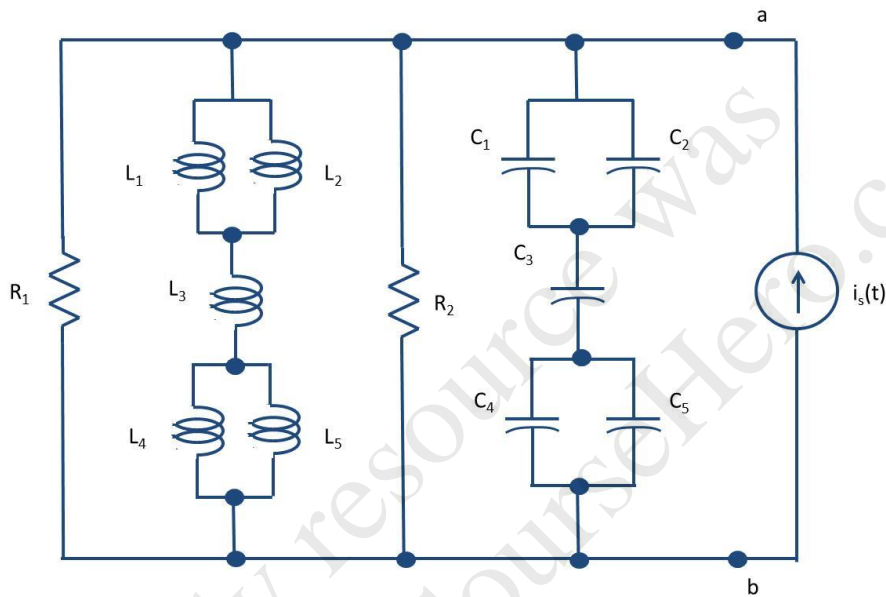


Fig. 4

- (a) Three elements in parallel:

$$R_{eq} = R_1 \parallel R_2 = 4.8 \text{ k}\Omega$$

$$L_{eq} = L_1 \parallel L_2 + L_3 + L_4 \parallel L_5 = 3.33 \text{ mH} + 4 \text{ mH} + 4.8 \text{ mH} = 12.13 \text{ mH}$$

$$C_{eq} = C_1 \parallel C_2 \parallel C_3 \parallel C_4 \parallel C_5 = 15 \text{ } \mu\text{F} \parallel 4 \text{ } \mu\text{F} \parallel 20 \text{ } \mu\text{F} = 2.73 \text{ } \mu\text{F}$$

- (b) $I_s = 10 \text{ A}$, $Z_R = 4.8 \text{ k}\Omega$; $Z_L = j12.13 \times 10^{-3} \times 60 \times 2 \times 3.14 = 4.57j \text{ } \Omega$;
 $Z_C = -j / (2.73 \times 10^{-6} \times 60 \times 2 \times 3.14) = -j 971.6 \text{ } \Omega$