

Name: Q. J. Zhang

Student #: _____

Section: _____

1

CARLETON UNIVERSITY

| | | |
|----------|-----------|-------|
| Question | Max Marks | Score |
| 1 | 10 | |
| 2 | 20 | |
| 3 | 20 | |
| 4 | 25 | |
| 5 | 20 | |
| Total | 95 | |

| | | |
|----------|-----------|-------|
| Question | Max Marks | Score |
| 1 | 10 | |
| 2 | 20 | |
| 3 | 20 | |
| 4 | 25 | |
| 5 | 20 | |
| Total | 95 | |

Duration: 3 hours

Department name and course number: Electronics ELEC-2507

Course Instructor(s): Q-J Zhang Number of students: 64

AUTHORIZED MEMORANDA:

NON-PROGRAMMABLE CALCULATOR

Students MUST count the number of pages in this examination paper before beginning to write, and report any discrepancies immediately to a proctor. **This question paper has 18 pages.**

This examination question paper MAY NOT be taken from the examination room.

This exam consists of 5 questions, which should be answered on this exam paper in the space provided. Attempt all questions. Marks allocated to each question are indicated (total marks = 95).

Note: The solution must be clearly indicated. Multiple solutions or solutions that are not clearly identified, will be marked incorrect. Using approximate relations (unless they are given below or specified in a question) is not accepted. Clearly state all assumptions made. **Clearly mark the units for all final answers. Clearly indicate axis/units for any graphs. SHOW YOUR WORK!**

Diode:Forward current: $I_D = I_S (\exp(V_D/V_T) - 1)$ Small signal resistance: $r_d = V_T/I_D$ $V_T = \frac{kT}{q} = 25mV$ at room temperatureBipolar Transistor:Active mode operation: $V_{BE} = 0.7V$ Saturation mode operation: $V_{CEsat} = 0.2V$ $i_C = \beta i_B$ $i_C = \alpha i_E$ $i_E = i_B + i_C$ $g_m = \frac{I_C}{V_T}$ $r_\pi = \frac{\beta}{g_m}$ $r_o = \frac{V_A}{I_C}$ $r_e = \frac{\alpha}{g_m} = \frac{r_\pi}{\beta + 1}$ $\alpha = \frac{\beta}{\beta + 1}$ Operational Amplifier: $V_o = A(V_+ - V_-)$; $R_i = \infty$; $R_o = 0$ MOSFET: $\epsilon_{ox} = 3.45 \times 10^{-11}$ F/m, $g_m = 2 I_D / V_{ov}$ $I_{DS} = k' \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right]$; $I_{DS,sat} = k' \frac{W}{L} \frac{(V_{GS} - V_t)^2}{2} (1 + \lambda V_{DS})$; $k' = \mu C_{ox}$; $K = k' \frac{W}{L}$ $V_{OV} = V_{GS} - V_t$ $g_m = k' \frac{W}{L} (V_{GS} - V_t) = \sqrt{2k' \frac{W}{L} I_{DS}}$ $r_{DS,triode} = \left[k' \frac{W}{L} (V_{GS} - V_t) \right]^{-1}$; $r_o = \frac{V_A}{I_D}$

Q1: Answer the following by filling in the corresponding circles with your selection *a, b, c* or *d* (10 marks)

i) What is the gain, V_o/V_{in} , for the circuit in Fig. 1.i, assuming the operational amplifier is ideal?

(C)

- (a) 3
- (b) -3
- (c) 4
- (d) -4

 


Fig. 1.i

ii) For a center-tapped full wave rectifier using ideal diodes, the peak-to-peak input voltage is $\pm 12V$. Which one of the following diodes you will be the optimum picks for your circuit taking into consideration of proper circuit functioning ?

(d)

- (a) diodes with a PIV (peak inverse voltage) of 6V.
- (b) diodes with a PIV of 12V.
- (c) diodes with a PIV of 18V.
- (d) diodes with a PIV of 24V.

iii) Using a piecewise-linear model for the diode in the circuit in Fig. 1.iii., what is the voltage V_D in that circuit (given the linear-piecewise diode data of $V_{D0} = 0.65V$ and $r_D = 20\Omega$)?

(b)

- (a) 1.4V
- (b) 1V
- (c) 0.65V
- (d) 0.4V

 


Fig. 1.iii

iv) In the circuit in Fig. 1.iv, each diode has a forward constant voltage drop of 0.7V. What is the value of V_{out} if V_{in} is -4V?

(a)

- (a) -4V
- (b) 0.7V
- (c) -2.1V
- (d) 2.1V

 


Fig 1.iv

v) Given the characteristic curves for a MOSFET in Fig. 1.v, what are the regions I and II known as?

(a)

- (a) I – triode, II – saturation
- (b) I – cut-off, II – saturation.
- (c) I - saturation, II - active.
- (d) I – triode, II – active


 


Fig. 1.v

vi) What is the correct small signal model equivalent circuit for a MOSFET with *channel length modulation*?

(b)

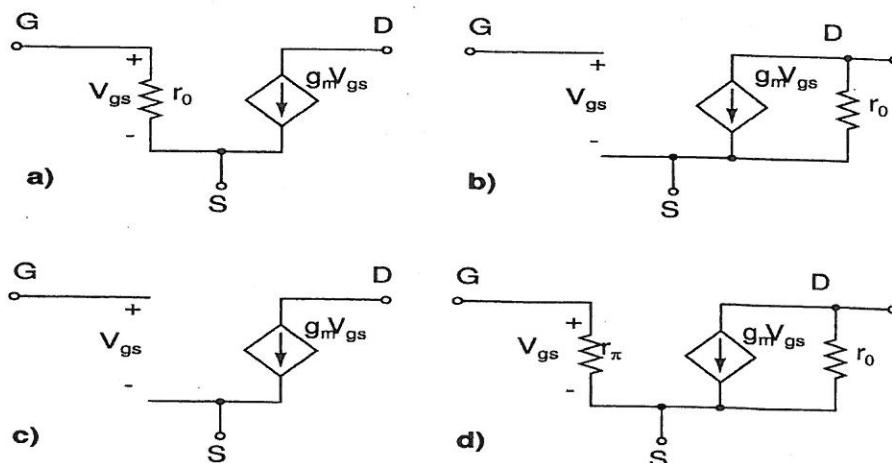

vii) Which of the following statements is **incorrect** for an ideal operational amplifier?

(C)

- (a) It has an infinite open loop gain.
- (b) It has an infinite common-mode rejection.
- (c) It has a zero input impedance.
- (d) It has a zero output impedance.

viii) Which of the following statements is **incorrect** about a well designed common emitter amplifier?

(C)

- (a) The transistor should be biased in the active mode.
- (b) The input can be coupled through a coupling capacitor.
- (c) The input resistance should be very small.
- (d) The gain depends upon the resistance in the collector branch of the circuit.

ix) What is V_c for the DC circuit shown in Fig.1.ix, given the transistor has a β of 100 and assuming V_{BE} is 0.7V.

(b)

- (a) 8V
- (b) 7.8V
- (c) 4.8V
- (d) 4V

 


Fig.1.ix


x) The bipolar junction transistor can be placed in the cut-off mode of operation when the

(d)

- (a) emitter-base junction is forward biased and the collector-base junction is reverse biased,
- (b) emitter-base junction is forward biased and the collector-base junction is forward biased,
- (c) emitter-base junction is reverse biased and the collector-base junction is forward biased,
- (d) emitter-base junction is reverse biased and the collector-base junction is reverse biased.

Q2. Operational Amplifier

 - a) For the circuit below, write an **Time-Domain** expression of the output voltage $v_o(t)$ in terms of the 3 input voltages $v_1(t)$, $v_2(t)$, and $v_3(t)$. Assume that the op-amp is ideal. (5 marks)



$$v_o = -(10\mu\text{F} \times 30\text{k}\Omega) \frac{dv_3}{dt} - \frac{30\text{k}\Omega}{15\text{k}\Omega} \left(-\frac{20}{5} v_1 - \frac{20}{10} v_2 \right)$$


answer:

$$v_o = 8v_1 + 4v_2 - 0.3 \frac{dv_3}{dt}$$

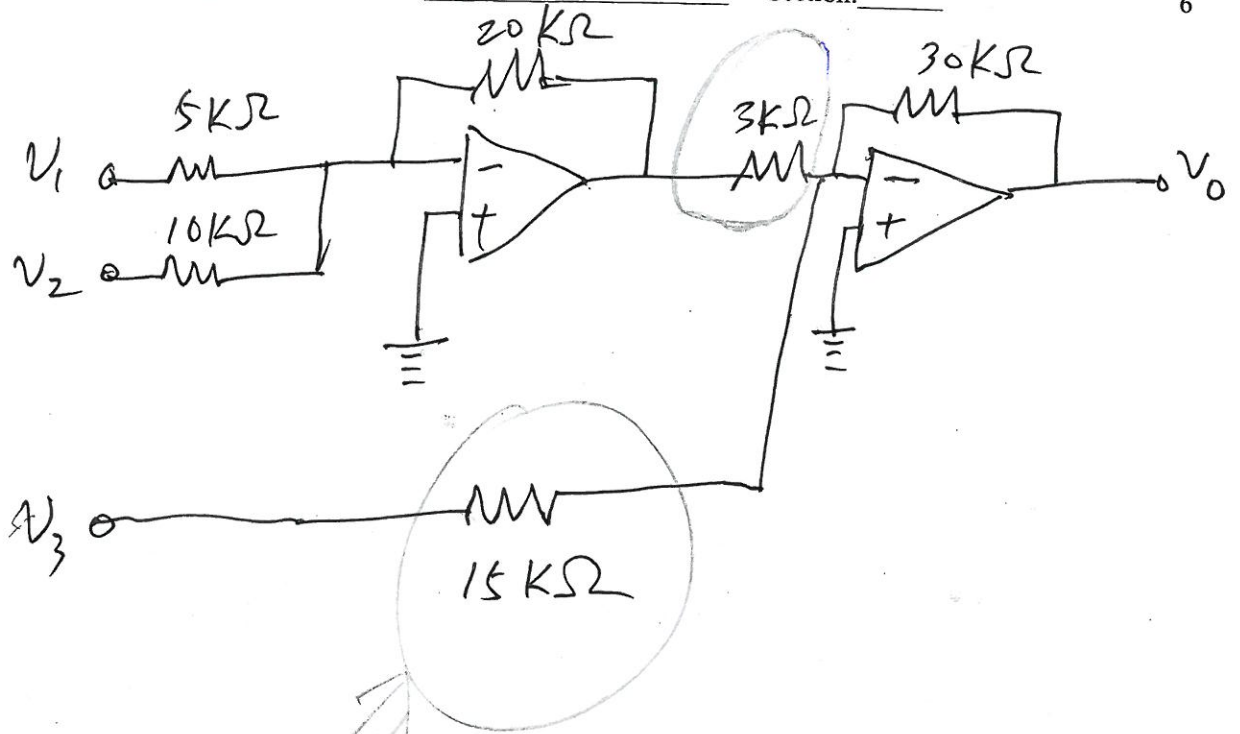- b) Modify the circuit in a) by changing at most two components such that the response will become


$$v_o = 40v_1 + 20v_2 - 2v_3$$

Re-draw the circuit clearly labeling the values of all components (4 marks)



(Remark: The solution is not unique.)

 c) Consider the op-amp circuit below. Assume that all the op-amps are ideal. Write the expression for the response v_o (using phasor notations) in terms of v_1 and v_2 . (2 marks)




$$v_o = -40k\Omega \cdot 8\mu F j\omega V_1 - \frac{40}{5} V_2$$

answer:

$$v_o = -0.32 j\omega V_1 - 8 V_2$$

$j\omega$ ← Greek omega

 d) Consider the circuit below, where the op-amp is ideal.



i) Derive the gain $H(j\omega) = v_o(j\omega)/v_i(j\omega)$. Show the steps (6 marks)

$$H = \frac{R_2 \parallel \frac{1}{j\omega C_2}}{R_1 \parallel \frac{1}{j\omega C_1}}$$

$V_x = 0$


$$= - \frac{R_2}{j\omega C_2} \frac{1}{R_2 + \frac{1}{j\omega C_2}} \cdot \frac{(R_1 + \frac{1}{j\omega C_1}) j\omega C_1}{R_1}$$

$$H = - \frac{R_2}{R_1} \frac{j\omega R_1 C_1 + 1}{j\omega R_2 C_2 + 1}$$

$\leftarrow j\omega$ omega

 
ii) Suppose $R_1 = 500 \Omega$, $R_2 = 10K\Omega$, $R_3 = 45K\Omega$, and $C_1 = 20\mu F$, and $C_2 = 100\mu F$. Sketch the magnitude of the gain (in DB) with respect to angular frequency (3 marks)

$$H = - \frac{10K\Omega}{500\Omega} \frac{j\omega 500\Omega \cdot 20\mu F + 1}{j\omega 10K\Omega \cdot 100\mu F + 1} = - 20 \frac{j\omega 0.01 + 1}{j\omega + 1}$$



Q3: Diodes

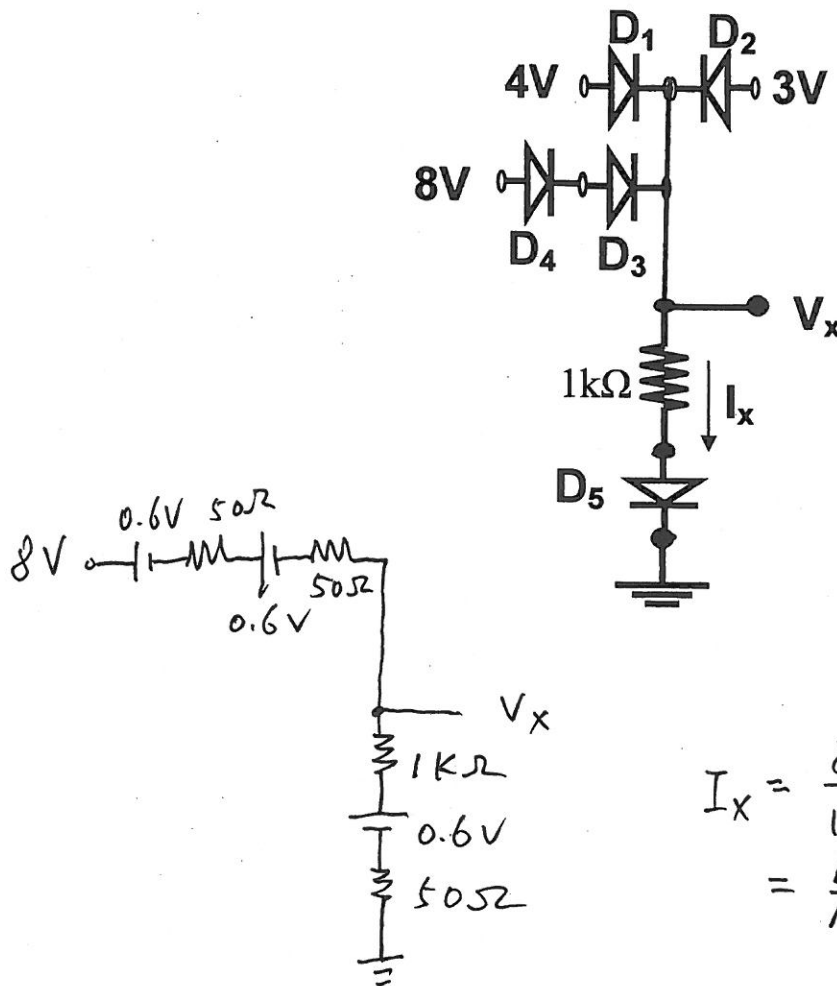- a) Consider the circuit below. Suppose the model for each of the diodes is a piece-wise linear model with $V_{D0}=0.6V$ and $r_D = 50\Omega$. For the given inputs, find the output voltage V_x and the current I_x ? (7 Marks)



$$I_x = \frac{8V - 0.6V - 0.6V - 0.6V}{1K\Omega + 50\Omega + 50\Omega + 50\Omega}$$

$$= \frac{6.2V}{1.15K} = 5.39mA$$

$$V_x = 0.6 + 5.39 \times (1K + 50\Omega)$$

$$= 6.26V$$


$$V_x = 6.26V$$

$$I_x = 5.39mA$$

- b) Design limiter circuits using only diodes and $5k\Omega$ resistors to provide an output signal limited to the specified ranges (given below). Assume a constant-voltage drop model for the diodes with $V_D = 0.7V$.


- i. Output specification: 1.4V and below.

(2 marks)

 


ii. Output specification: ± 2.1 V.

(2 marks)

 


iii. Output specification: -1.4 V and above.

(2marks)

 

c) For the circuit below, if the input were a pulse train of ± 15 V, what would be the minimum and maximum voltages at v_x and v_o ? Assume ideal diodes.

(3 Marks)

 


| | |
|---------------|------------|
| $v_{x\min} =$ | <u>-15</u> |
| $v_{x\max} =$ | <u>3</u> |
| $v_{o\min} =$ | <u>-18</u> |
| $v_{o\max} =$ | <u>0</u> |

- d) Using diodes and capacitors design clamper circuits for a -6V to 6V peak to peak square wave periodic input, v_i , to satisfy the following output specifications. Assume that the time constant of the circuit are much larger than the cycle time (period) of the input wave form. Assume ideal diode models.


- i. Output specification: $0\text{V} \leq v_o \leq 12\text{V}$

(2 marks)

 

- ii. Output specification: $-12\text{V} \leq v_o \leq 0\text{V}$

(2 marks)

 

Q4: BJT

For the amplifier in Fig. 4.1, $V_{CC} = 15V$. The values for the resistors are $R_1 = 12K\Omega$, $R_2 = 8.5K\Omega$, $R_3 = 1K\Omega$, $R_4 = 1K\Omega$, $R_s = 10\Omega$, and $R_L = 2K\Omega$. The values of the coupling capacitors C_1 , C_2 and C_3 are very large and can be considered to be infinity. The transistor parameter $\beta = 100$.


 



Fig. 4.1

 - a) Draw the DC equivalent circuit that can be used for calculating DC voltages and currents
(3 marks)



- b) Assuming room temperature, determine values for V_B , V_C , I_B , and I_C (Where V_B and V_C represent the voltages at the base and collector, respectively; and I_B , and I_C represent the currents through the base and the collector terminals, respectively.)

(7 marks)

 

$$I_B = \frac{6.22 - 0.7}{4.97 + 101 \times 1} = 0.05208 \text{ mA}$$

$$I_C = 5.2 \text{ mA}$$

$$V_C = 15 - 1 \times 5.2 = 9.8 \text{ V}, \quad V_B = 1 \times 5.2 + 0.7 = 5.9 \text{ V}$$

$$V_C = 9.8 \text{ V}$$

$$V_B = 5.9 \text{ V}$$

$$I_B = 0.052 \text{ mA}$$

$$I_C = 5.2 \text{ mA}$$

- c) The BJT in Fig. 4.1 had an early voltage of 150V. Compute parameters r_e , g_m , and r_o .

$$g_m = \frac{I_C}{V_T} \approx \frac{5.2 \text{ mA}}{25 \text{ mV}} = 0.208 \text{ A/V} \quad (3 \text{ marks})$$

$$r_e = \frac{\alpha}{g_m} = \frac{\beta}{1 + \beta} \frac{1}{g_m} = \frac{0.99}{0.208} = 4.8 \Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{150}{5.2} = 28.84 \text{ k}\Omega$$


$$g_m = 0.208 \text{ A/V}$$

$$r_o = 28.84 \text{ k}\Omega$$

$$r_e = 4.8 \Omega$$

- d) Draw the small signal AC equivalent circuit based on parameters calculated above in c)

(5 marks)

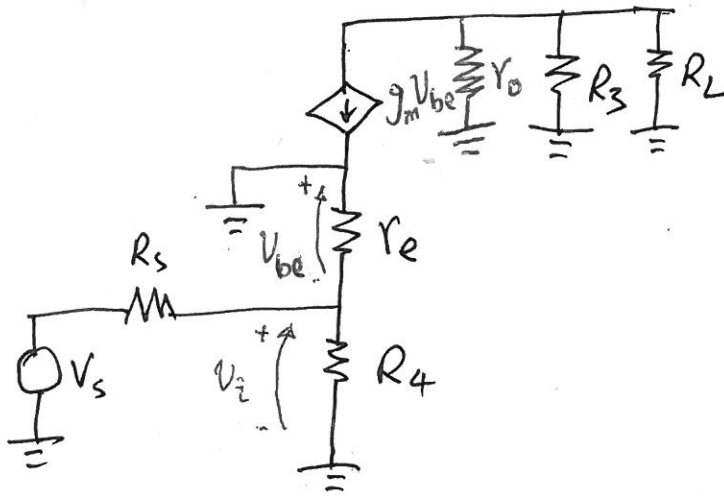

- e) Find the value of the input resistance R_i

(2 marks)

$$R_i = R_4 \parallel r_e = \frac{1000 \times 4.8}{1000 + 4.8} = 4.77$$

$$R_i = 4.77$$

- f) Find the value of the intermediate voltage gain, $A_{v1} = v_i/v_s$, where v_i is the small-signal voltage between the emitter and the ground.

(1 mark)

$$A_{v1} = \frac{v_i}{v_s} = \frac{R_4 \parallel r_e}{R_s + R_4 \parallel r_e} = \frac{R_i}{R_s + R_i}$$

$$= \frac{4.77}{10 + 4.77} = 0.324$$

$$A_{v1} = 0.324$$

- g) Find the value of the intermediate voltage gain $A_{v2} = v_o/v_i$.

(3 marks)

$$V_o = -g_m V_{be} (R_3 \parallel r_o \parallel R_L) = -g_m V_i (R_3 \parallel r_o \parallel R_L)$$

$$\begin{aligned} A_{v2} &= g_m (R_3 \parallel r_o \parallel R_L) \\ &= 0.208 \times (1\text{K} \parallel 2\text{K} \parallel 28.84\text{K}) \\ &= 0.208 \times (0.652 \text{ k}\Omega) \\ &= 135.56 \end{aligned}$$

| |
|-------------------|
| $A_{v2} = 135.56$ |
|-------------------|

- h) Find the overall voltage gain, $G_v = v_o/v_s$.

(1 mark)

$$A_v = A_{v1} \cdot A_{v2}$$


$$= 0.324 \times 135.56$$

$$= 43.923$$

| |
|---------------|
| $G_v = 43.92$ |
|---------------|

Q5: MOSFET

 a) In the figure below, the transistor has $V_t = 1V$, $k_n' = 200 \mu A/V^2$, $L = 1 \mu m$, and $W = 5 \mu m$.



i) Find the bias voltages V_G , V_S and current I_D (3 marks)

$$V_G = \frac{3}{2+3} * 15 = 9, \quad K_n = k_n' \cdot \frac{W}{L} = 1 \text{ mA}/V^2$$

$$I_D = \frac{1}{2} K_n V_{ov}^2 = \frac{1}{2} K_n (V_G - V_S - V_t)^2 = \frac{1}{2} (8 - V_S)^2$$

$$I_D = \frac{V_S}{R_4} = \frac{1}{4} V_S$$

$$\frac{1}{2} (8 - V_S)^2 = \frac{1}{4} V_S, \quad 2V_S^2 - 33V_S + 128 = 0$$

$$V_S = \frac{33 \pm \sqrt{33^2 - 4 \cdot 2 \cdot 128}}{2 \cdot 2} = \begin{cases} 10.2655 \\ 6.2344 \end{cases}$$

$$I_D = \frac{1}{4} V_S = \begin{cases} 2.566 \text{ mA} \\ 1.5586 \text{ mA} \leftarrow V \end{cases}$$

| | | |
|-----------------|--------------------|-----------------------|
| V_G <u>9V</u> | V_S <u>6.23V</u> | I_D <u>1.558 mA</u> |
|-----------------|--------------------|-----------------------|

ii) Verify the mode of operation of the transistor and state what mode the transistor is in (3 marks)

$$V_{GS} = V_G - V_S = 9 - 6.23 = 2.77 > V_t$$

$$V_{DS} = 15 - 2\text{k}\Omega \times 1.558\text{mA} - 6.23\text{V}$$


$$= 5.654$$

$$V_{OV} = V_{GS} - V_t = 2.77 - 1 = 1.77$$

$$V_{DS} > V_{OV}$$

Mode = Saturation

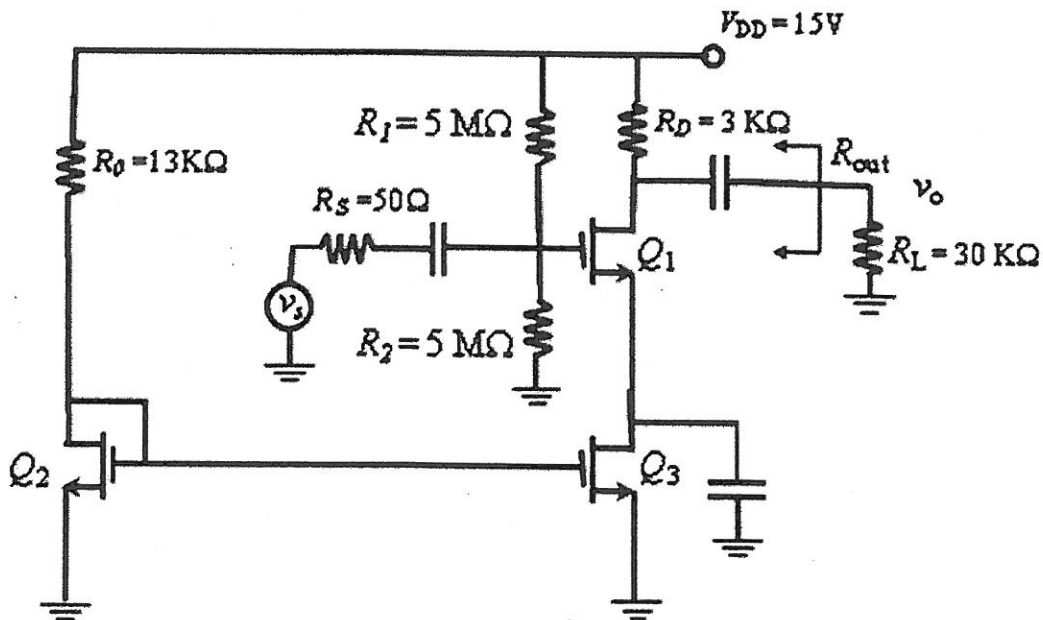b) Consider the amplifier in the figure below. Assume that for all the MOSFETs, $V_t = 1\text{V}$, $k_n' = 200 \mu\text{A}/\text{V}^2$. The channel length of the MOSFETs are $L_1 = L_2 = L_3 = 1 \mu\text{m}$. The channel width are $W_1 = 10 \mu\text{m}$, $W_2 = 10 \mu\text{m}$, and W_3 is unknown.



i). Assume that the current mirror by Q_2 and Q_3 will provide a constant current of 2mA to bias the transistor Q_1 . Determine channel width W_3 . (3 marks)

$$\frac{I_{D2}}{I_{D3}} = \frac{W_2/L_2}{W_3/L_3}, \quad I_{D3} = 2 \text{ mA}, \quad K_n = k_n' \frac{W}{L} =$$

$$I_{D2} = \frac{V_{DD} - V_{GS}}{R_0} = \frac{15 - V_{GS}}{13}$$

$$I_{D2} = \frac{1}{2} k_n' \frac{W_2}{L_2} (V_{GS} - V_t)^2 = (V_{GS} - 1)^2$$

$$\frac{15 - V_{GS}}{13} = (V_{GS} - 1)^2, \quad 13V_{GS}^2 - 25V_{GS} - 2 = 0$$

$$V_{GS} = \frac{25 \pm \sqrt{25^2 + 4 \times 13 \times 2}}{2 \times 13} = \frac{25 \pm 27}{26} = \begin{cases} 2 & \leftarrow V \\ -0.076 & \leftarrow X \end{cases}$$

$$V_{GS} = 2 \text{ V}$$

$$I_{D2} = 1 \text{ mA}$$

$$\frac{I_{D2}}{I_{D3}} = \frac{W_2/L_2}{W_3/L_3}, \Rightarrow \frac{1}{2} = \frac{10}{W_3} \Rightarrow W_3 = 20$$

$$W_3 = 20 \mu\text{m}$$

- ii). Compute the small-signal parameter g_m of transistor Q_1 , assuming the drain current for Q_1 is biased at 2mA. (2 marks)



$$g_m = \frac{2 I_{D1}}{V_{OV}}$$

$$I_{D1} = 2 \text{ mA}, \quad I_{D1} = \frac{1}{2} k_n' \frac{W_1}{L_1} V_{OV}^2 = V_{OV}^2, \quad V_{OV} = \sqrt{I_{D1}} = 1.414$$

$$g_m = \frac{2 I_{D1}}{V_{OV}} = \frac{2 \times 2}{1.414} = 2.828$$

$$g_m = 2.828 \text{ A/V}$$

  - iii). Assume that the current mirror by Q_2 and Q_3 makes an ideal current source. Assume all the capacitors are infinitely large. Suppose the channel length modulation for Q_1 is to be considered. Draw the small-signal equivalent circuit. (2 marks)



iv). Compute a value for the voltage gain $G_v = v_o/v_s$ assuming that $V_A = 100V$ for Q_1 . (5 marks)

$$r_o = \frac{V_A}{I_D} = \frac{100}{2\text{mA}} = 50\text{K}\Omega$$

$$v_o = -g_m v_{gs} (r_o \parallel R_D \parallel R_L)$$

$$v_{gs} = \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \cdot v_s$$

$$G_v = \frac{v_o}{v_s} = -g_m (r_o \parallel R_D \parallel R_L) \cdot \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2}$$

$$= -2.828 \times 2.5864 \cdot \frac{2.5}{2.5 + 50 \times 10^{-6}}$$

$$= -7.314$$

$G_v = -7.314$

v). Compute the value of the amplifier output resistance R_{out} . (2 marks)

$$R_{out} = R_D \parallel r_o$$

$$= 3\text{K}\Omega \parallel 50\text{K}\Omega$$

$$= \frac{3 \times 50}{3 + 50}$$

$$= 2.83\text{K}\Omega$$

$R_{out} = 2.83\text{K}\Omega$

END