

|  |                            |                       |
|--|----------------------------|-----------------------|
| Course:<br>Digital Signal Processing     | Course Number:<br>COEN 212 | Sections:<br>EC and W |
| Examination: Midterm                     | Date:<br>April 20, 2020    | Time:<br>3 hours      |
| Instructor:<br>Dr. M.R. Soleymani        |                            |                       |
| Books and Material: Open Book            |                            |                       |
| Special Instructions: Try all questions. |                            |                       |

- 1) Simplify and implement the circuit  $F(x, y, z) = [(x + y)(x' + z)]'$  with NOR gates only. Use the minimum number of gates. (10 Marks)
- 2) A combinational circuit has a has input bits  $w, x, y, z$  and an output  $F$ . The output is one when the number of one at the input is more than one. Design the circuit using a multiplexer (10 Marks)
- 3) Using a decoder and minimal external gates design a combinational circuit with inputs bits  $x, y, z$  and two outputs

$$F = x'y'z' + xz$$

and

$$G = (x + y)z$$

(10 Marks)

- 4) A sequential circuit has three D flip-flops with the following input equations:

$$D_A = (AC' + BC)x'$$

$$D_B = (B \oplus C)x'$$

$$D_C = A'C'x'$$

and the output equation  $y = AB'C'x'$ .

Draw the state transition table (4 Marks), and state diagram (4 Marks). What does the function do? (2 Marks)

- 5) Using minimum possible of JK flip-flops design a counter that counts: 0, 1, 6, 3, 5, 2, 4, 0, ... (repeat).