


LECTURE 10

THEVENIN'S AND NORTON'S THEOREMS

Often, we use ^{mis} use a relatively complex circuit to deliver power to a load.

Thevenin's theorem says that the entire circuit (exclusive of the load) can be replaced by an equivalent circuit containing only an independent voltage source in series with a resistor.

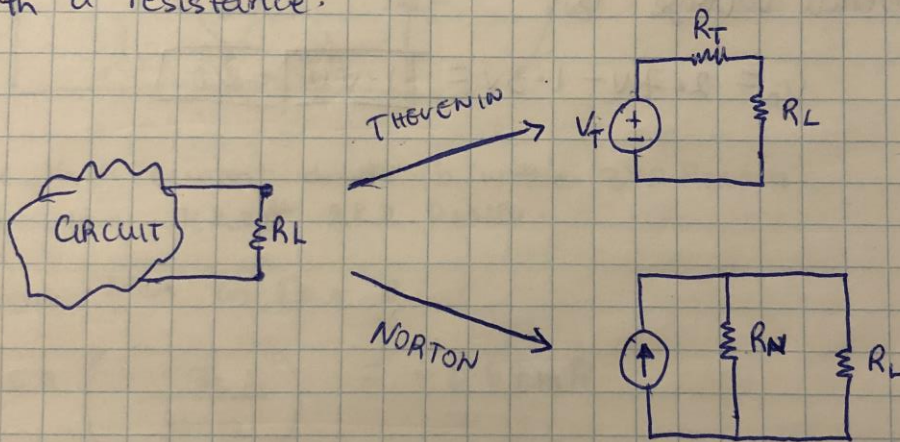
Norton's theorem says we can replace the driving circuit by an independent current source in parallel with a resistance.



In both cases the current-voltage relation at the load stays the same. We can change the load value and the equivalent will accurately model the actual circuit.

Consider the Thevenin equivalent first

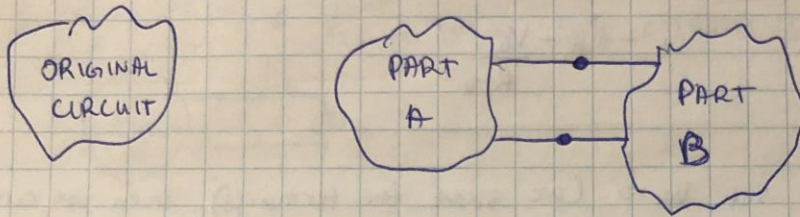Consider a complex circuit that can be split into two parts: A and B



There is a current i between the circuits and a voltage V_B at the terminals. We could replace part B with a voltage source V_B without changing the voltage or current at the terminals.



If we were to apply superposition to the circuit, we could find the current i_B due to the new source V_B , and the current with $V_B = 0$ (short circuit) due to other sources in circuit i_A , then the total will be

$$i = i_A + i_B$$

Setting all sources in A to zero we find!



$$i_B = \frac{-V_B}{R_{TH}}$$

$$i_B = \frac{-V_B}{R_{TH}}$$

Where R_{TH} would be the resistance between the terminals of circuit A with all independent sources $\rightarrow 0$

therefore:
$$i = i_A - \frac{V_B}{R_{TH}}$$

Now if we set $V_B = 0$ (we short the terminals) then we are left with:

$$i = i_{sc} = i_A \quad (i_{sc} = \text{short circuit current})$$

\Rightarrow
$$i = i_{sc} - \frac{V_B}{R_{TH}} \quad \text{--- (1)}$$
 $\frac{V_{oc}}{i_{sc}} =$

Now say we open terminals, then $V_B = V_{oc}$ and the current is equal to zero so:

$$i \Rightarrow 0 = i_{sc} - \frac{V_{oc}}{R_{TH}} \quad (V_{oc} = \text{open circuit voltage})$$

$$V_{oc} = R_{TH} \cdot i_{sc}$$

Thus the ratio of the open circuit voltage and the short current is related by the resistance of circuit A with all sources zeroed out! we can therefore rewrite (1) as

$$\frac{i R_{TH} + V_B}{R_{TH}} \quad i = V_{oc}/R_{TH} - V_B/R_{TH}$$

$$\frac{V_{oc}}{i_{sc}} = \frac{R_{TH} \cdot i_{sc}}{i + \frac{V_B}{R_{TH}}}$$


$$\frac{V_{oc}}{i_{sc}} = \frac{R_{TH} \cdot i_{sc}}{\frac{i R_{TH} + V_B}{R_{TH}}} = \frac{R_{TH}^2 \cdot i_{sc}}{i R_{TH} + V_B}$$

THEVENIN

R_{TH} = resistance looking into the terminals of driving circuit A
with all sources = 0 \rightarrow Thevenin resistance

V_{OC} = the voltage at the terminals of circuit A when the terminals
are open circuit.

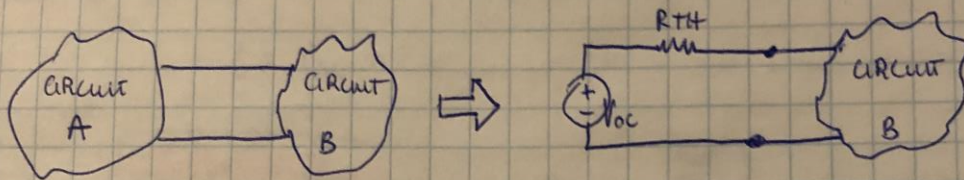
The circuit A can then be replaced by a source V_{OC} in series
with a resistor R_{TH} :



THEVENIN'S THEOREM

NORTON'S THEOREM

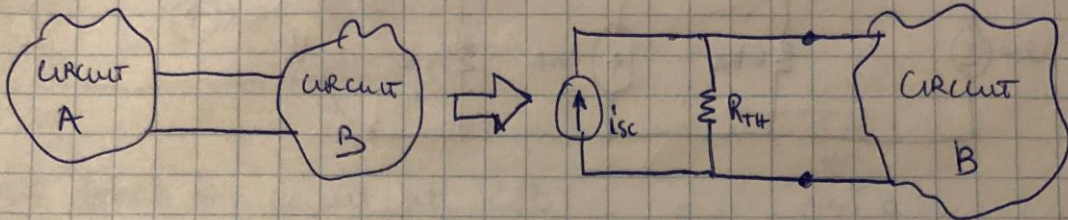
This indicates circuit A can also be replaced by a current source in parallel with a resistor R_{TH} .



Note: the two circuits ~~are~~ equivalents are different representations of the same equations. Note they are equivalent only in terminal characteristics \rightarrow Norton dissipates power 0ϵ .


EX

Use Thevenin to find V_o

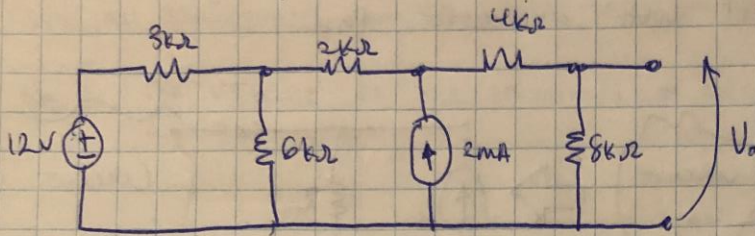

We can do this in stages.

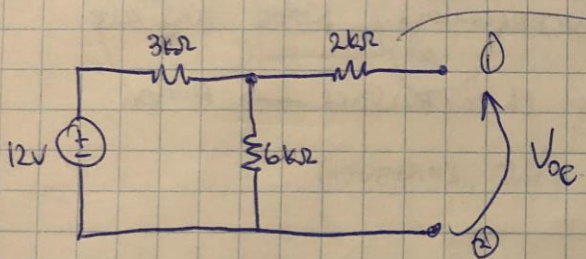Consider just the part left of the current source!




1st
No current, no voltage
If terminals ① & ② are open circuited then there is no current flow through the 2kΩ resistor

∴ using a voltage divider:


$$V_{Th} = V_{oc} = 12V \times \frac{6k}{(6+3)k} = 8V$$

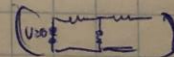$R_{Th} \rightarrow$ find R_{eq} with sources $= 0$



$$R_{Th} = 2k + 6k \parallel 3k = 4k\Omega$$

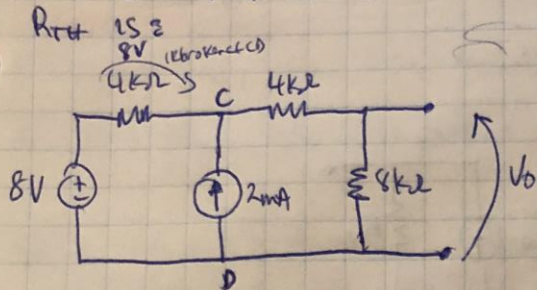
Our new circuit with the left side replaced with V_{th}




Now break the circuit at C/D:

The new $V_{th} = 8V + 2mA \times 4k = 16V$

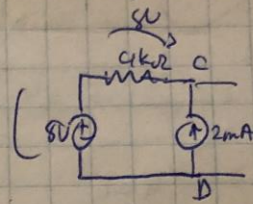New $R_{th} = 4k$ (Current source open)
 (Voltage source short)





Our equivalent is now:

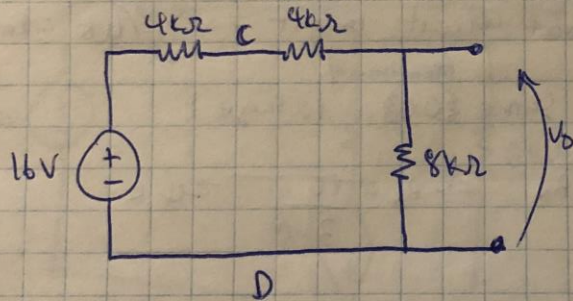

And $V_0 = 16V \times \frac{8k}{(8k+4k)} = 8V$

$R_{th} = 8k \parallel (4+4) = 4k$ (Voltage source again a short circuit)

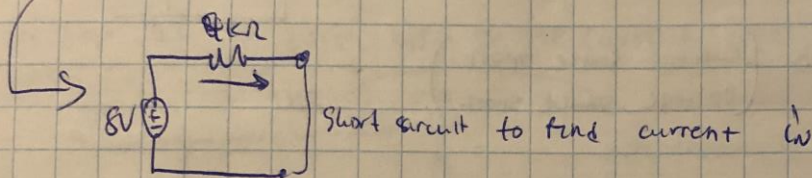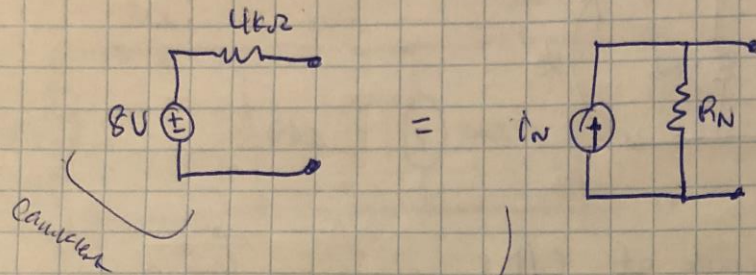
The equivalent could also be found using ~~equivalent~~ or
 Superposition of 2 sources.



i_N would be the short circuit current = $8V / 4k\Omega = 2mA$
 R_N would provide the same ^{open circuit} {OC} voltage!

$$8V = i_N \cdot R_N \Rightarrow R_N = \frac{8V}{2mA} = 4k\Omega$$

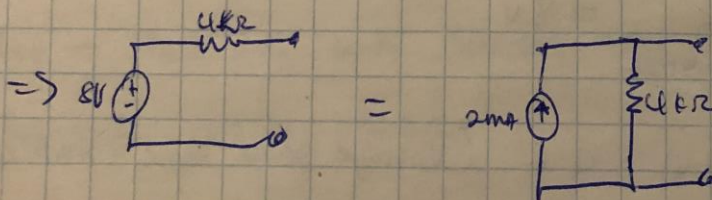i.e. $R_N = R_{TH} \rightarrow$ source transformation




Thevenin steps

- ① Remove load, find OC voltage
- ② Find R_{eq} b/w the output terminals with independent sources set to zero
- ③ If there are dependent sources present, R_{TH} may not be obvious so a 'test source' is connected to the output and R_{TH} is found from V_{test}/i_{test} (Ohm's law)
- ④ Re-attach the load & complete the analysis

Example with Dependent & Independent Sources

Find V_0 using Thevenin's Theorem:

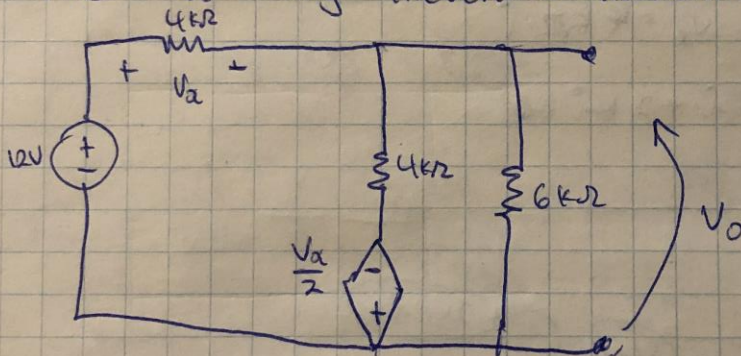


FIRST

Remove load = $6k\Omega$

First

Remove load = $6k\Omega$

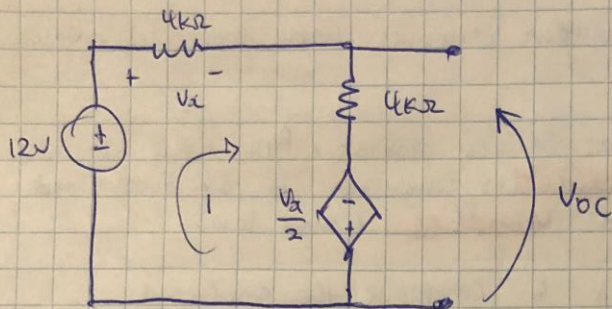

using KVL:

$$12V - v_x - 4k\Omega \cdot i + \frac{v_x}{2} = 0$$

we also note that $v_x = 4k\Omega \cdot i$

$$\Rightarrow 12V - 4k\Omega \cdot i - 4k\Omega \cdot i + 2k\Omega \cdot i = 0$$

$$\boxed{i = 2mA}$$


we know $i = 2mA$

$$V_{OC} = 4k\Omega \cdot i - \frac{v_x}{2}$$

$$V_{OC} = 2k\Omega \cdot i = 2k\Omega \cdot 2mA = \boxed{4V}$$


②

$$P_{eq} = R_{TH} =$$

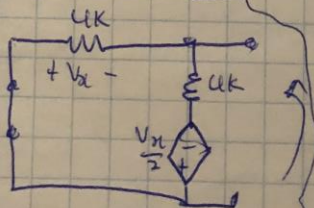

② Find $R_{eq} = R_{th}$

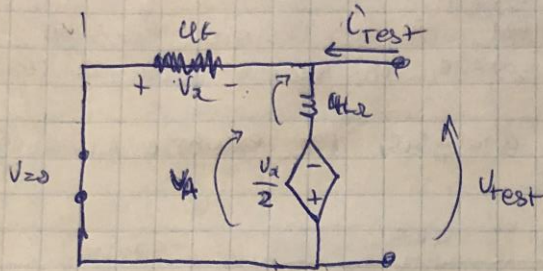We apply a test voltage to find a test current!
after zeroing all dependent sources



$$V_{test} + V_A = 0$$

$$\Rightarrow V_A = -V_{test}$$

$$\Rightarrow \frac{V_A}{2} = \frac{-V_{test}}{2}$$

$$V_A = \frac{-V_A}{2} = \frac{+V_{test}}{2}$$


$$I_{test} = I_1 + I_2 = \frac{V_{test}}{4k} + \frac{(V_{test}/2)}{4k}$$

$$\frac{V_{test}}{4k} + \frac{V_{test}}{8k} = \frac{2V_{test} + V_{test}}{8k} = \frac{3V_{test}}{8k}$$

$$I_{test} = \frac{3}{8} V_{test}$$

$$\frac{V_{test}}{I_{test}} = \left(\frac{8k}{3} \right) = \boxed{2.7k\Omega}$$

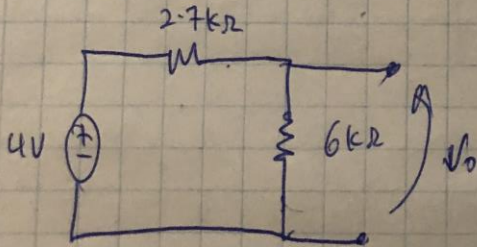Now we can replace the 6k resistor with our simple model to give



$$V_0 = 4V \times \frac{6k}{(2.7+6)k} = \boxed{2.75V}$$