

Assignment 3

Thomas Bayl
#: 300117763

P 7.5-22

$$V(t) = R \cdot 0.25 \cos(2t) \text{ A}$$

$$V_c = R i(t)$$

$$10 \cos(2t) = R \cdot 0.25 \cos(2t)$$

$$R = 40 \Omega$$

$$V(t) = \frac{1}{C} \int_0^t i(t) dt$$

$$V_c = \frac{1}{C} \int_0^t i(t) dt$$

$$10 \sin(2t) = \frac{1}{C} \cdot 0.125 \sin(2t)$$

$$C = \frac{1}{80} \text{ F}$$

$$i(t) = 0.25 \cos(2t) \text{ A}$$

$$V_a = -10 \sin(2t)$$

$$V_b = 10 \sin(2t)$$

$$V_c = 10 \cos(2t)$$

$$V_c(t) = L \frac{di}{dt} = -L \cdot 0.5 \sin(2t)$$

$$V_a = L \frac{di}{dt}$$

$$-10 \sin(2t) = -L \cdot 0.5 \sin(2t)$$

$$L = 20 \text{ H}$$

P 7.6-4

$$L = \frac{1}{4} \text{ H}$$

$$i(t) = \begin{cases} 0 & t \leq 0 \\ 4t e^{-t} & t \geq 0 \end{cases}$$

Partial Answer: $w = 2t^2 e^{-2t} \text{ J}$

$$V(t) = L \frac{di}{dt}$$

$$V(t) = \begin{cases} 0 \text{ V} & t \leq 0 \\ e^{-t}(1-t) \text{ V} & t \geq 0 \end{cases}$$

$$P(t) = i(t) V(t)$$

$$P(t) = \begin{cases} 0 & t \leq 0 \\ 4t e^{-2t}(1-t) \text{ W} & t \geq 0 \end{cases}$$

$$W(t) = \int_0^t P(t) dt$$


$$W(t) = \int_0^t 4t e^{-2t}(1-t) dt$$

$$= 4 \left(\left(\frac{e^{-2t}}{-2} \left(t - \frac{1}{2} \right) \right) \Big|_0^t - \left(\frac{e^{-2t}}{-2} \left(t^2 - \frac{2t}{-2} + \frac{2}{(-2)^2} \right) \right) \Big|_0^t \right)$$

$$= 2t^2 e^{-2t}$$

$$W(t) = \begin{cases} 0 & t \leq 0 \\ 2t^2 e^{-2t} & t \geq 0 \end{cases}$$

P. 7.7-5 $L_{eq} = 18H$

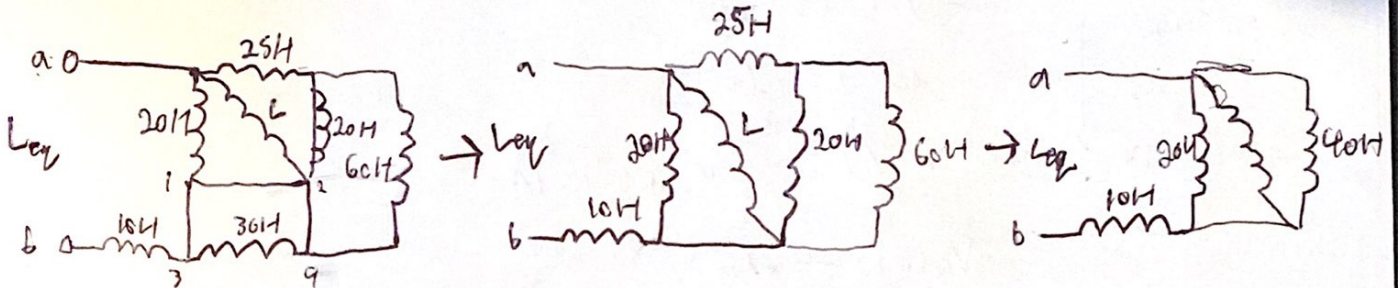

$$L_{12} = 0$$

$$L_{34} = 30$$

$$L_p = \frac{0 \times 30}{0 + 30} = 0$$

$$L_p = \frac{20 \times 60}{20 + 60} = 15H$$

$$L_s = 25 + 15 = 40H$$

$$\frac{1}{L_p} = \frac{1}{20} + \frac{1}{L} + \frac{1}{40}$$

$$\frac{1}{L_p} = \frac{40L + 800 + 20L}{800L}$$

$$L_p = \frac{800L}{80L + 800}$$


$$\therefore L_{eq} = 10 + \frac{800L}{60L + 800}$$

$$L_{eq} = \frac{8000 + 1400L}{800 + 60L}$$

$$18 = \frac{8000 + 1400L}{800 + 60L}$$

$$L = 20H$$

P. 7.8-11

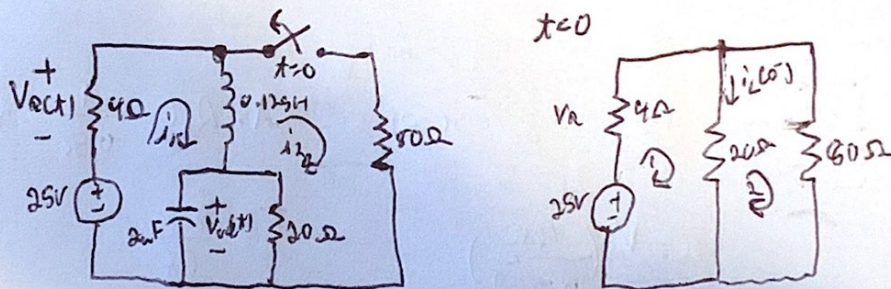

$$KVL_1 \quad -25 + 4i_1 + 20(i_1 - i_2) = 0$$

$$24i_1 - 20i_2 = 25 \quad (1)$$

$$KVL_2 \quad 20(i_2 - i_1) + 60i_2 = 0$$

$$-20i_1 + 100i_2 = 0$$

$$i_1 = 5i_2 \quad (2)$$

$$24(5i_2) - 20i_2 = 25 \quad (2) \text{ into } (1)$$

$$100i_2 = 25$$

$$i_2 = 0.25A \quad i_1 = 1.25A$$

$$i_L(0^-) = i_1 - i_2$$

$$= 1.25 - 0.25$$


$$= 1A$$

$$V_C(0^-) = 20 \times i_L(0^-) \quad V_R(0^-) = -4 \times i_1(0^-)$$

$$= 20V \quad = -5V$$

7.8-11

$t > 0$

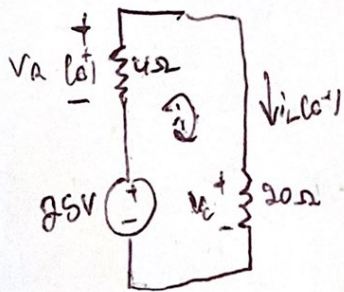

$$v_C(t^-) = v_C(t^+)$$


$$i_C(t^-) = i_C(t^+)$$

$$\therefore v_C(t^+) = 20V, i_C(t^+) = 1A$$


$$v_A(t^+) = -4 \times i_C(t^+) = -4V$$

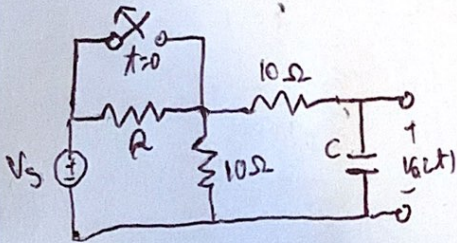8.3-8

$$v_O(t) = 2 + 8e^{-0.5t} V \text{ for } t > 0$$




for $t < 0$

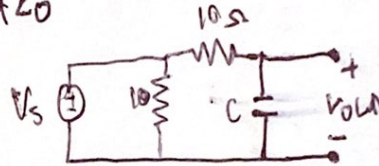

$$\therefore v_S = v_O = 2 + 8e^{-0.5t} V \text{ at } t=0$$

$$v_S = 2 + 8e^{-0.5(0)} V = 10V$$

for $t > 0$

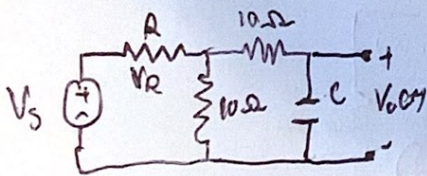

$$v_A = v_O = 2 + 8e^{-0.5t} V$$

$$v_A = 2 + 8e^{-0.5(2.0)} V = 2V$$

$$v_A = v_S \left(\frac{10\Omega}{R+10\Omega} \right)$$

$$2V = 10V \left(\frac{10\Omega}{R+10\Omega} \right)$$

$$R = 40\Omega$$

$$\tau = R_T C = \frac{1}{0.5s^{-1}} = 2.0s$$

$$C = \frac{2.0s}{R_T}$$



$$R_T = \frac{(40\Omega)(10\Omega)}{40\Omega + 10\Omega} + 10\Omega$$

$$= 18\Omega$$

$$C = \frac{2.0s}{18\Omega}$$

$$C = 0.111 F$$

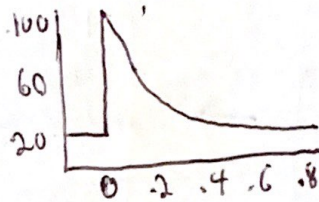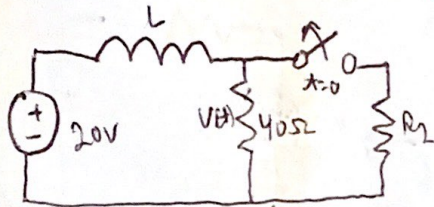8.3-25 $V(t) = \begin{cases} D & \text{for } t < 0 \\ E + F e^{-at} & \text{for } t > 0 \end{cases}$



for $t < 0$

$$V(t) = 20V = D$$

$$V(0) = 100V = E + F$$

$$V(\infty) = 20V = E$$

$$F = 100V - 20V = 80V$$

$$V(0.143) = 20V + 80V e^{-a(0.143)} = 60V$$

$$e^{-a(0.143)} = \frac{60V - 20V}{80V} = 0.5$$


$$-a(0.143) = \ln(0.5)$$

$$a = 4.95 s^{-1}$$

$$V(t) = \begin{cases} 20V & t < 0 \\ 20V + 80V e^{-(4.95 s^{-1})t} & t > 0 \end{cases}$$

for $t > 0$
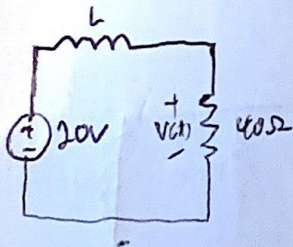
$$i_L = i_{40} + i_{R_2} = 20V \left(\frac{1}{40\Omega} + \frac{1}{R_2} \right)$$



$$i_L = i_{40} = \frac{V(t)}{40\Omega} = \frac{100V}{40\Omega} = 2.50A$$

$$\alpha = \frac{R_t}{L} = 4.95 s^{-1}$$

$$2.50A = 20V \left(\frac{1}{40\Omega} + \frac{1}{R_2} \right)$$

$$L = \frac{40\Omega}{4.95 s^{-1}}$$


$$R_2 = \frac{1}{0.100 \Omega^{-1}}$$

$$L = 8.08 H$$

$$R_2 = 10 \Omega$$

8.6-9


$$V_s(t) = 7 - 14u(t) \text{ V}$$

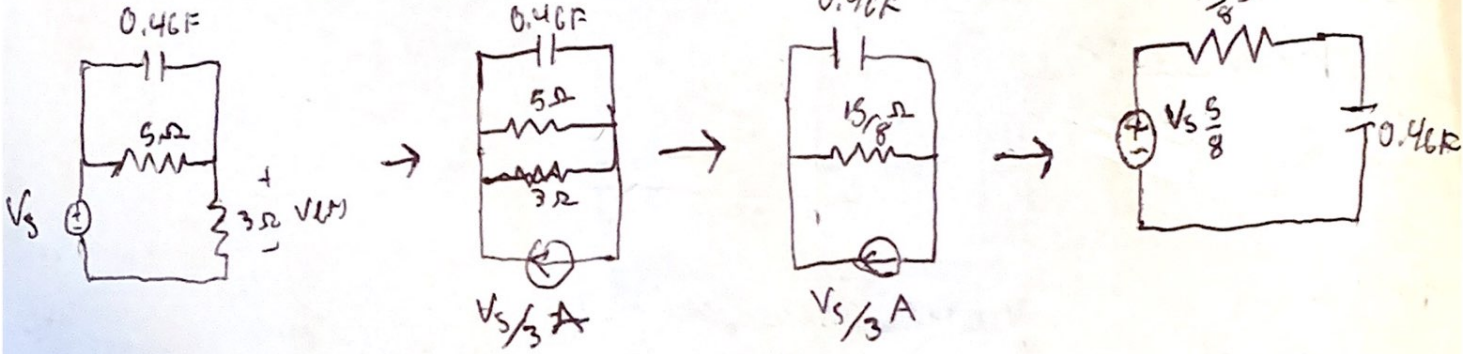

$$\frac{1}{R_{eff}} = \frac{1}{3} + \frac{1}{5} = \frac{8}{15}$$

8.6-2

$$V_s(t) = 30 - 24u(t) \text{ V}$$

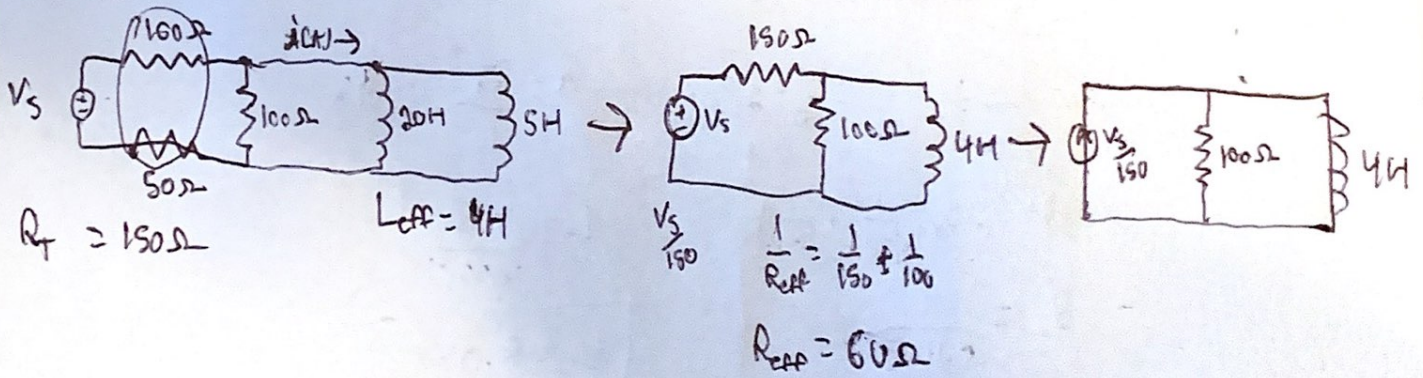


$$i(0) = \frac{(30 - 24u(0))}{150} = 0.2 \text{ A}$$

$$i(\infty) = \frac{(30 - 24u(\infty))}{150} = 0.04 \text{ A}$$

$$i(t) = i_{\infty} + (i(0) - i_{\infty})e^{-t/(R_{eff}L)}$$

$$i(t) = 0.04 \text{ A} + 0.16e^{-(25s^{-1})t} \text{ A}$$

8.7-3 $i_s = (2 \cos(2t)) \text{ mA}$

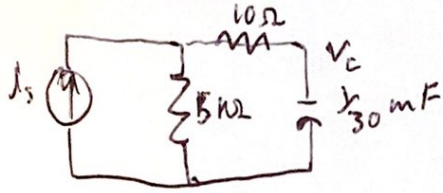

$$i_s = i_5 + i_{10} = \frac{V_5}{5k\Omega} + C \frac{dv_c}{dt}$$

$$V_5 - V_{10} - V_c = 0$$

$$V_5 = i_{10}(10k\Omega) + V_c$$

$$i_{10} = C \frac{dv_c}{dt}$$

$$i_s = \frac{C \frac{dv_c}{dt} (10k\Omega)}{5k\Omega} + C \frac{dv_c}{dt} + \frac{V_c}{5k\Omega}$$

$$5k\Omega i_s = (5k\Omega) C \frac{dv_c}{dt} + V_c$$

$$5k\Omega (2 \cos(2t)) = (15k\Omega) \left(\frac{1}{30} \text{ mF}\right) \frac{dv_c}{dt} + V_c$$

$$20 \cos 2t = \frac{dv_c}{dt} + 2V_c$$

$$V_c = A \sin(2t) + B \cos(2t)$$

$$\frac{dv_c}{dt} = 2A \cos 2t - 2B \sin 2t$$

$$20 \cos 2t = 2A \cos 2t - 2B \sin 2t + 2(A \sin 2t + B \cos 2t)$$

$$20 = 2A + 2B \quad \text{cos}$$

$$0 = 2A - 2B \quad \text{sin}$$

$$A = B$$

$$20 = A + B = 2B$$

$$A = B = 5$$

$$V_c = 5 \sin(2t) + 5 \cos(2t)$$

$$V_c = 5 \sin(2t) + 5 \cos(2t) + K e^{-t/5}$$

$$R_T = 5k\Omega + 10k\Omega = 15k\Omega$$

$$\tau = (15k\Omega) \left(\frac{1}{30} \text{ mF}\right) = \frac{1}{2} \text{ s}$$

$$i_s(t=0) = 2 \cos(0) \text{ mA} = 2 \text{ mA}$$

$$V_c(0) = 0 = 5 \sin(0) + 5 \cos(0) + K e^0 = 0 + 5 + K$$

$$K = -5$$

$$\therefore V_c(t) = 5 \sin(2t) + 5 \cos(2t) - 5 e^{-2t}$$