

Question A5/B1 (20 marks) A solid, insulating sphere of radius a has a uniform charge density ρ and a total charge Q . Concentric with this sphere is an uncharged, conducting hollow sphere whose inner and outer radii are b and c , as shown in Figure 1. Find the magnitude of the electric field in the regions:

- (a) (5 marks) $r < a$ (write your answer in terms of Q , not ρ)
- (b) (5 marks) $a < r < b$
- (c) (5 marks) $b < r < c$
- (d) (5 marks) $r > c$

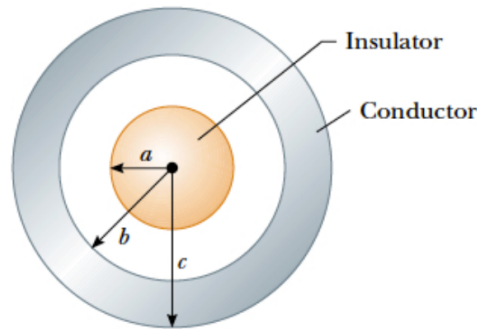


Figure 1: Concentric conducting shell and insulating sphere.

Gauss's Law $\int \vec{E} \cdot d\vec{A} = \frac{Q_{\text{encl}}}{\epsilon_0}$ gives

$$EA = \frac{Q_{\text{encl}}}{\epsilon_0}$$

$$E = \frac{1}{4\pi r^2} \frac{Q_{\text{encl}}}{\epsilon_0} \quad \text{For a spherical Gaussian surface}$$

From here, the solution requires figuring out what the enclosed charge, Q_{encl} , is for the given range of radii.

a) $Q_{\text{enc}} = \rho V_r = \frac{Q}{V_a} V_r$ V_r - volume enclosed by sphere at r

$$= \frac{Q}{\frac{4\pi a^3}{3}} \cdot \frac{4\pi r^3}{3}$$

$$= Q \frac{r^3}{a^3}$$

This gives $E = \frac{Qr}{4\pi a^3 \epsilon_0}$

b) $Q_{\text{enc}} = Q$, so $E = \frac{Q}{4\pi \epsilon_0 r^2}$

c) Electric field is zero inside a conductor, so $Q_{\text{enc}} = 0$ and $E = 0$.

d) At $r > c$, the charge enclosed is $Q_{\text{enc}} = Q$, so the answer is $E = \frac{Q}{4\pi \epsilon_0 r^2}$.

Question A4/B2 (20 Marks) An initially uncharged $4.50 \times 10^{-6} \text{ F}$ capacitor and a $6.00 \times 10^3 \Omega$ resistor are connected in series to a 2.50 V battery that has negligible internal resistance.

- (a) (5 marks) What is the initial current of the circuit?
- (b) (5 marks) Calculate the time constant for the circuit.
- (c) (10 marks) How much time must elapse from the closing of the circuit for the current to decrease to 15% of its initial value?

B2 | a) $I_0 = \frac{\mathcal{E}}{R} = \frac{2.50 \text{ V}}{6000 \Omega} = \underline{4.17 \times 10^{-4} \text{ A}}$

b) $\tau = RC = (6000 \Omega)(4.50 \times 10^{-6} \text{ F}) = \underline{0.0270 \text{ s}}$

c) $I = I_0 e^{-t/\tau}$

$$I/I_0 = 15\% = 0.15$$

Rearrange to get $t = -\tau \ln\left(\frac{I}{I_0}\right) = -(0.0270 \text{ s}) \ln(0.15) = \underline{0.0512 \text{ s}}$

A4 | The same except some of the variables were different. The solutions are:

a) $2.14 \times 10^{-4} \text{ A}$

b) 0.0245 s

c) 0.0734 s

Question A1/B3 (20 marks) Calculate the power delivered to the $1.00\ \Omega$ and $4.00\ \Omega$ resistors in the circuit shown in Figure 2.

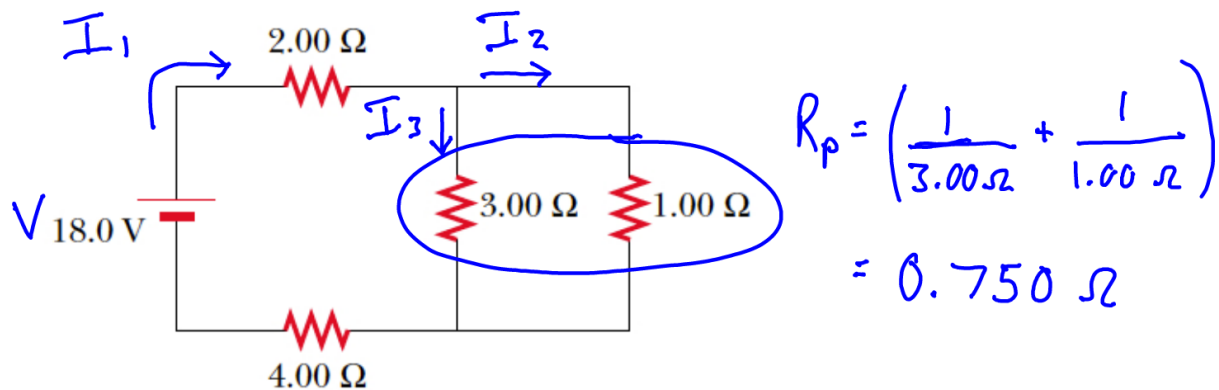


Figure 2: Circuit for Question 3.

With R_p , the total resistance for the circuit can be found:

$$R_{\text{TOT}} = (2.00\ \Omega + 0.750\ \Omega + 4.00\ \Omega) = 6.75\ \Omega$$

$$I_1 = \frac{V}{R_{\text{TOT}}} = \frac{18.0\ \text{V}}{6.75\ \Omega} = 2.67\ \text{A}$$

The power delivered to the $2.00\ \Omega$ resistor is:

$$P_2 = I_1^2 R = (2.67\ \text{A})^2 (2.00\ \Omega) = \underline{14.2\ \text{W}}$$

$$\text{Similarly, } P_4 = I_1^2 R = (2.67\ \text{A})^2 (4.00\ \Omega) = \underline{28.4\ \text{W}}$$

Now we need I_2 & I_3 to get P_1 and P_3 .

$$I_1 = I_2 + I_3 = 2.67\ \text{A}$$

$$I_2 = 2.67\ \text{A} - I_3$$

$$\text{Using } \sum V = 0 \text{ around a loop: } -1I_2 + 3I_3 = 0$$

$$-(2.67 - I_3) + 3I_3 = 0$$

$$I_3 = 0.668\ \text{A}$$

$$P_3 = I_3^2 R = (0.668 \text{ A})^2 (3.00 \Omega) = \underline{1.34 \text{ W}}$$

$$I_2 = 3I_3$$

$$I_2 = 2.00 \text{ A}$$

$$P_1 = I_2^2 R = (2.00 \text{ A})^2 (1.00 \Omega) = \underline{4.00 \text{ W}}$$

Question A2/B4 (20 marks) Two protons are released from rest when they are 0.550×10^{-9} m apart.

- (a) (10 marks) When do they reach their maximum speed? Calculate the maximum speed.
- (b) (10 marks) The force between the protons is given by

$$F = \frac{U}{r} \quad (1)$$

where U is the potential energy function and r is the distance between the protons. When do the protons achieve their maximum acceleration? Calculate the maximum acceleration.

For this problem, see solution to DGO 7, question 3.

Question A3/B5 (20 Marks) Figure 3 shows a system of five capacitors, where the potential difference across ab is 20.0 V. (Note: $1 \text{ nF} = 1 \times 10^{-9} \text{ F}$)

- (a) (10 marks) Find the equivalent capacitance of this system between a and b .
- (b) (10 marks) How much charge is stored by this combination of capacitors?

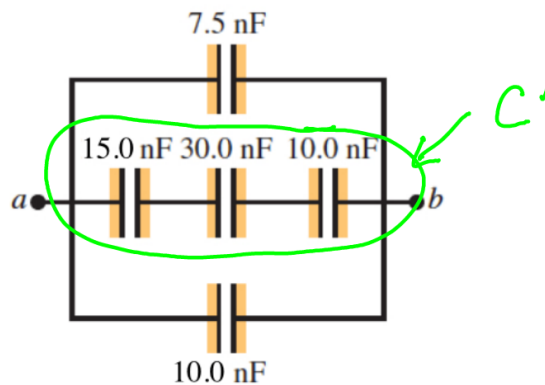


Figure 3: Five capacitor arrangement.

B5 | a) $\frac{1}{C'} = \left(\frac{1}{15.0} + \frac{1}{30.0} + \frac{1}{10.0} \right) \text{ nF}^{-1}$

$$C' = 5.0 \text{ nF}$$

C_{eq} for whole combination

$$C_{eq} = 7.5 \text{ nF} + 5.0 \text{ nF} + 10.0 \text{ nF} = \underline{22.5 \text{ nF}}$$

b) $Q = C_{eq} V_{ab} = (22.5 \times 10^{-9} \text{ F})(20.0 \text{ V}) = \underline{4.5 \times 10^{-7} \text{ C}}$

A3 | One of the capacitors and V_{ab} were different. The solutions are: a) $C' = \underline{5.0 \text{ nF}}$

b) $Q = (19.0 \times 10^{-9} \text{ F})(25.0 \text{ V}) = \underline{4.75 \times 10^{-7} \text{ C}}$