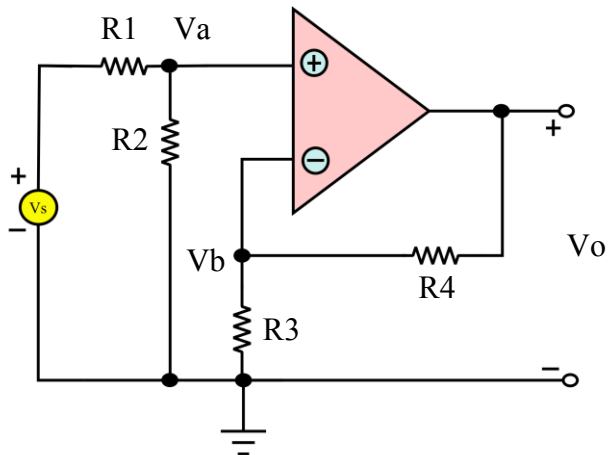


Name:		ID:	
Answer all Questions. Time 1.5 Hours			
Q1	Q2	Q3	Total

Question: 1: For the following circuit and stated conditions, find the output voltage, V_o .



The resistances are: $R_1 = 100$ Ohms, $R_2 = 200$ Ohms, $R_3 = 300$ Ohms, $R_4 = 400$ Ohms.
Also, V_s is 5 volts DC.

Solution for the question:

$V_1 = V_s * R_2 / (R_1 + R_2)$ (R1 and R2 are a voltage divider b/c of Golden Rule #2: no current into the opamp.)

$V_2 = V_o * R_3 / (R_3 + R_4)$ (R4 and R3 are also a voltage divider b/w V_o and ground)
(Can also be expressed as $V_o = V_2 * (1 + R_4 / R_3)$)


$V_1 = V_2$ because of Golden Rule #1 (output makes the inverting and non-inverting input voltages the same). Note that V_1 will be found to be equal to 3.33 volts.

Therefore, $V_s * R_2 / (R_1 + R_2) = V_o * R_3 / (R_3 + R_4)$.

So $V_o = V_s * (R_2 / (R_1 + R_2)) * (R_3 + R_4) / R_3$

And then $V_o = V_s * (200/300) * (700/300) = 5 * 14/9 = 7.78$ volts.

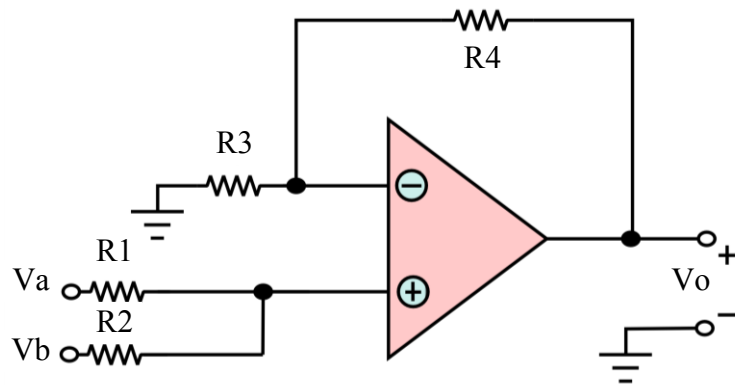Question: 2 For the following circuit, find the output voltage, V_o , given the stated conditions.



Resistances: $R_1=100$ Ohms, $R_2=200$ Ohms, $R_3=300$ Ohms and $R_4=400$ Ohms.
The voltage V_a is 1 Volt and the voltage V_b is 5 Volts.

Solution

At the non-inverting input node, we have a voltage V_2 :

$$(V_2 - V_a)/R_1 + (V_2 - V_b)/R_2 = 0,$$

yielding

$$V_2 = (V_a/R_1 + V_b/R_2)/(1/R_1 + 1/R_2)$$

At the inverting input node, we have a voltage V_1 :

$$(0 - V_1)/R_3 = (V_1 - V_o)/R_4$$

yielding

$$V_1 = V_o/(1 + R_4/R_3)$$

Because of Golden Rule #1 (Feedback makes the two opamp input voltages identical), $V_1 = V_2$. Therefore:

$$V_o/(1 + R_4/R_3) = (R_2 * V_a + R_1 * V_b)/(R_1 + R_2)$$

So


$$V_o = (R_2 * V_a + R_1 * V_b) * (R_3 + R_4) / (R_3 * (R_1 + R_2))$$

Substituting the values above:

$$V_o = (200 * 1 + 100 * 5) * (300 + 400) / (300 * (100 + 200)) = 700 * 700 / (300 * 300) = 5.4 \text{ volts.}$$

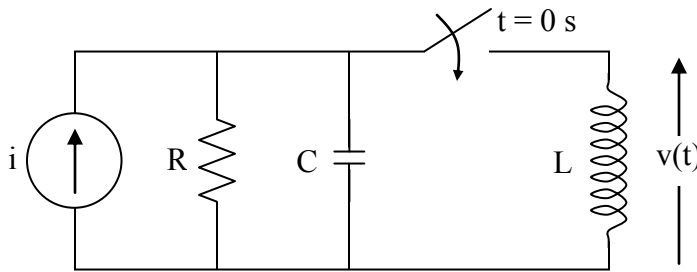Question: 3 RLC Circuits:

Consider the circuit shown below. $R = 1.0 \text{ k}\Omega$; $L = 1.6 \text{ H}$; $C = 10 \text{ }\mu\text{F}$; $i = 0.02 \text{ A}$



Answer the following:

$$\begin{aligned} \text{a)} \quad i(t) &= i_R(t) + i_L(t) + i_C(t) \\ &= \frac{v}{R} + i_0 + \frac{1}{L} \int v \cdot dt + C \cdot \frac{dv}{dt} \end{aligned}$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v(t) = \frac{1}{C} \frac{di}{dt} \quad (\text{ODE}) \quad (5)$$

b) Write a characteristic equation and its natural solution.

$$S^2 + \frac{1}{RC} S + \frac{1}{LC} = 0 \quad \rightarrow \quad S^2 + 2 \cdot (50) S + 250^2 = 0 \quad (2)$$

$$S_1, S_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -50 \pm j 244.95 \text{ rads / sec}$$

$$\text{natural solution: } v_n(t) = A \cdot e^{-50t} \cdot \cos(244.95 t + \phi) \text{ volts} \quad (3)$$

c) determine initial conditions for the circuit

$$\text{Voltage across the cap: } v_0 = i \cdot R = 20 \text{ volts;} \quad (2)$$

$$\text{Current through the ind: } i_0 = 0 \text{ amps} \quad (1)$$

$$i = v_0/R + C \cdot \frac{dv}{dt} + i_0; \quad \text{thus: } (i - v_0/R)/C = \frac{dv}{dt} = 0 \text{ v/s;} \quad (2)$$

d) find the forced solution and complete solution: $v(t)$, $t \geq 0$

$$v_f = 0 \text{ volts as the inductor will act as a short circuit.} \quad (1)$$

Hence: the total solution: $v = v_n + v_f$;

$$v = A \cdot e^{-50t} \cdot \cos(244.95 t + \phi) \text{ volts}$$

$$\text{From IC: } v(0) = 20 = A \cdot \cos(\phi); \quad \frac{dv}{dt} = 0 = -50 A \cos(\phi) - 244.95 \cdot A \sin(\phi).$$

$$\text{OR: } 0 = 50 \times 20 + 244.95 A \sin(\phi). \quad \text{OR: } -50 \times 20 / 244.95 = A \sin(\phi) = -4.0825$$

$$\text{Hence: } \phi = -0.2014 \text{ rads} = -11.5369 \text{ degrees; } A = 20 / \cos(\phi) = 20.4124.$$

$$\text{Hence: } v = 20.4124 \cdot e^{-50t} \cdot \cos(244.85 t - 0.2014) \text{ volts} \quad (4)$$

$$\text{Hence: } v = 20 \cdot e^{-50t} \cdot \cos(244.85 t) + 4.0824 \cdot e^{-50t} \cdot \sin(244.85 t) \text{ volts}$$